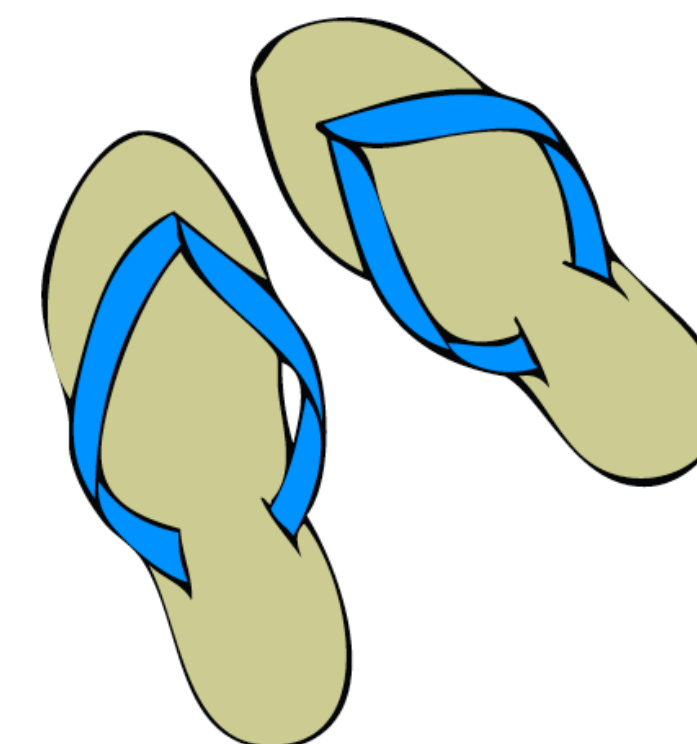




Sequential Logic and State


Latch: CC-BY Rberteig@flickr



Output depends on inputs *and stored values*.
(vs. combinational: output depends only on inputs)

Elements to store values: latches, flip-flops, registers,
memory

Motivation

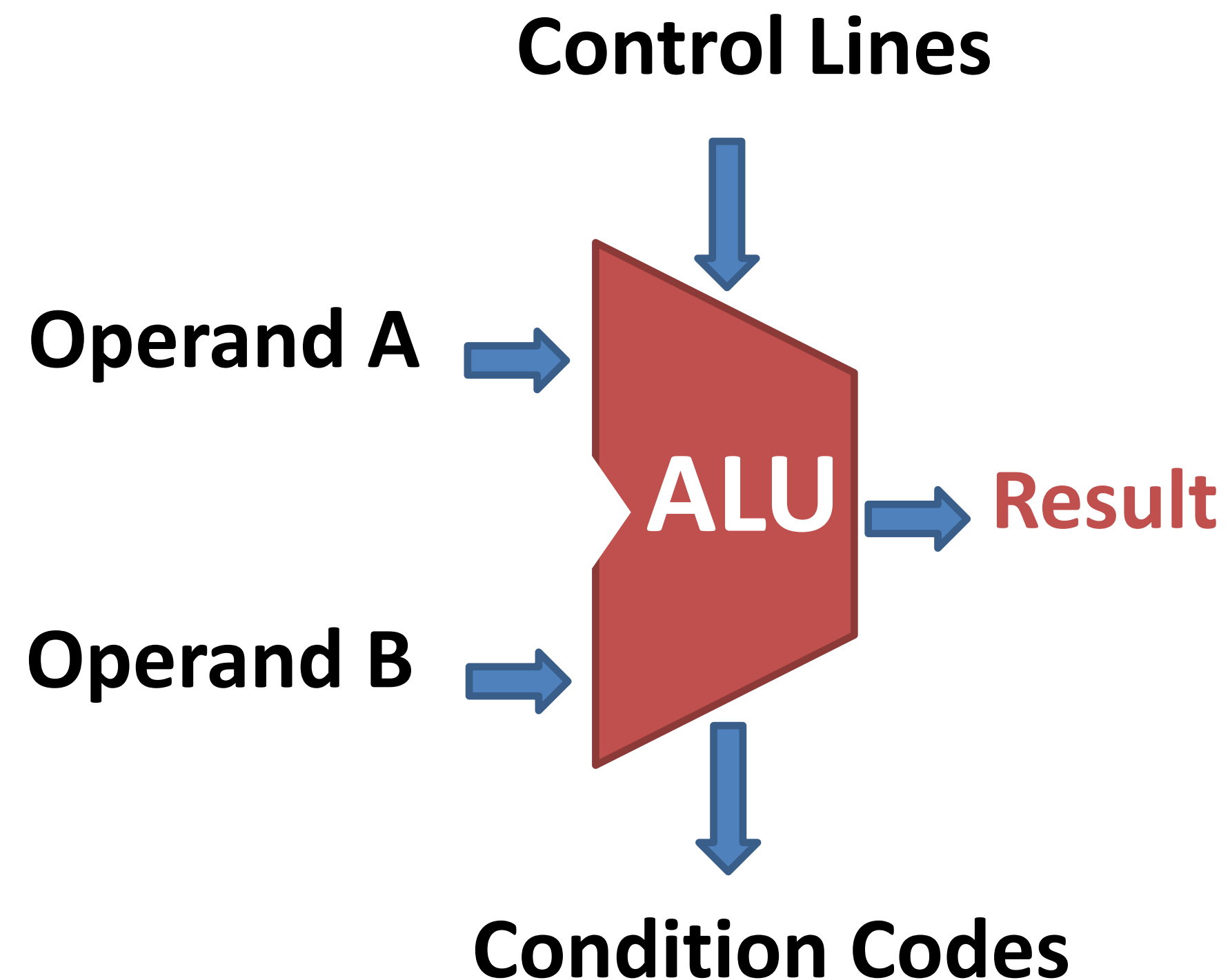

Now that we have ALUs to perform computations, how do we store the results?

How do we calculate different results over time?


Answer: we need circuits that depend not just on inputs, but also on *prior state*
= Sequential Logic

Can you think of an example from lab of a sequential circuit you used?
Hint: previous button pushes are past state.


Nobody has responded yet.

Hang tight! Responses are coming in.

Example from previous lab

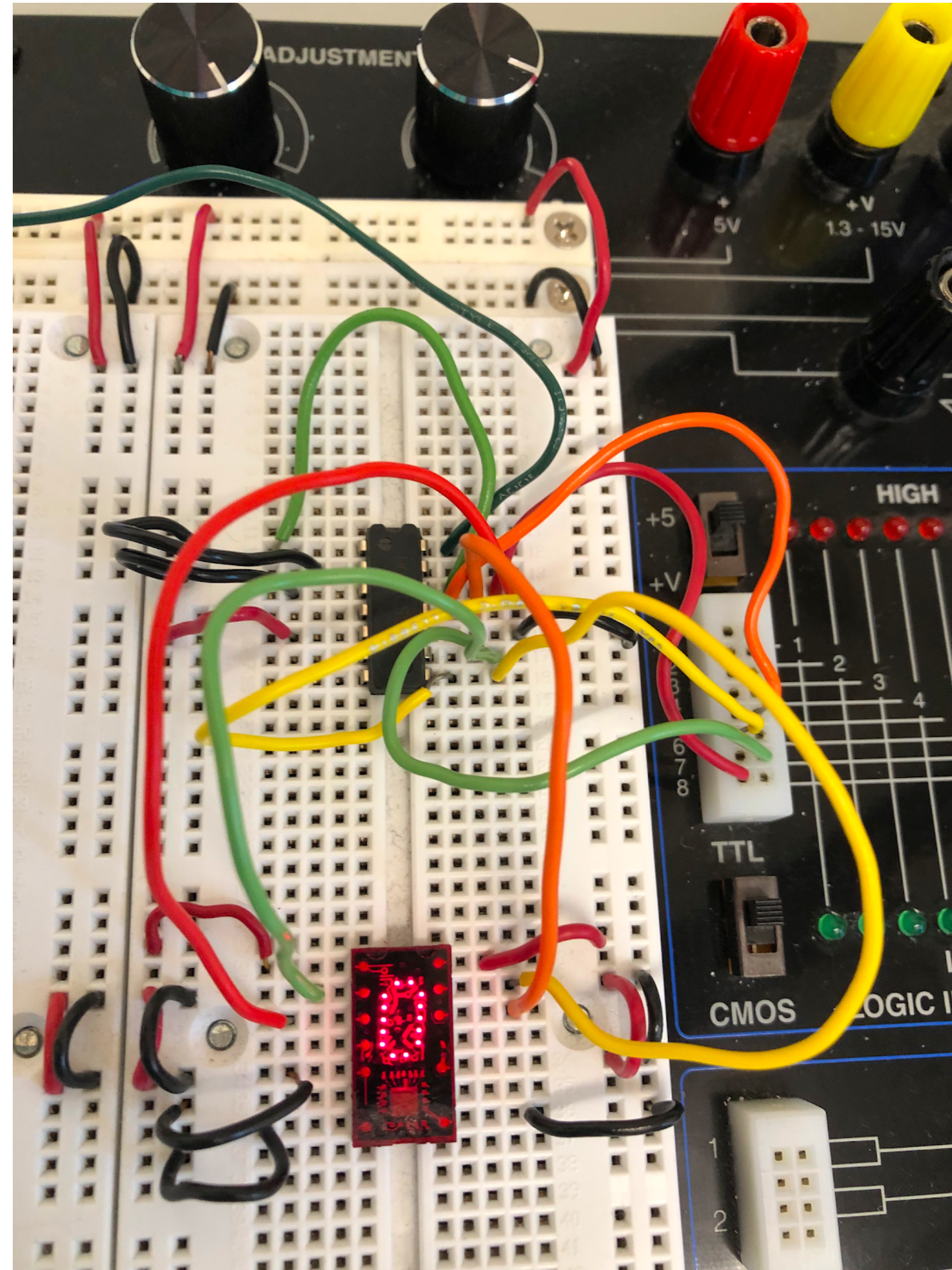

Processor: Data Path Components

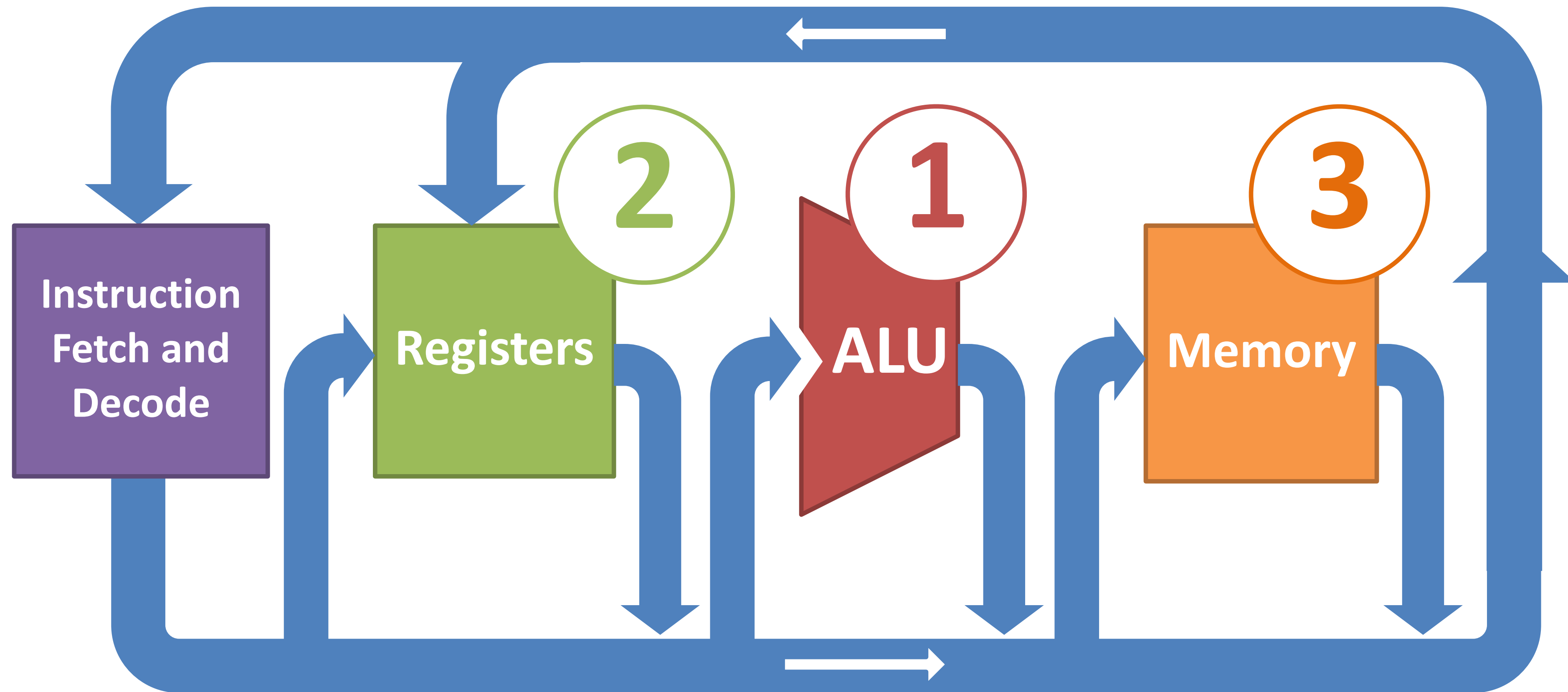


Goal for this section

Design a circuit state that **holds** a state over time

- We should be able to set the value to 0 or 1
- We should be able to read the value off the circuit

First attempt: Unstable circuit


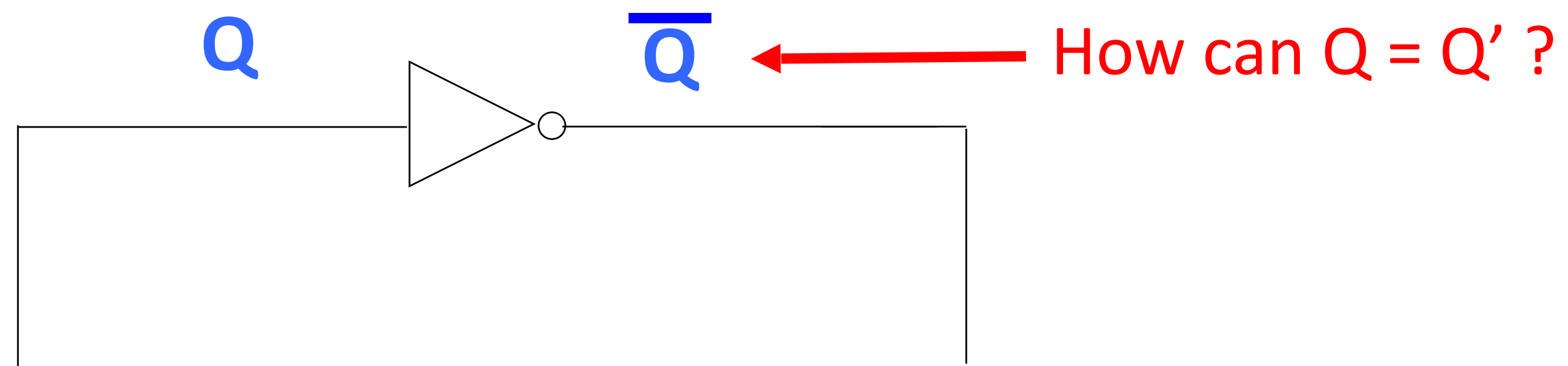


Have this issue with any **odd** number of inverters in a loop.


Second attempt: stable circuit?

Things are more sensible with an **even** number of inverters in a loop.

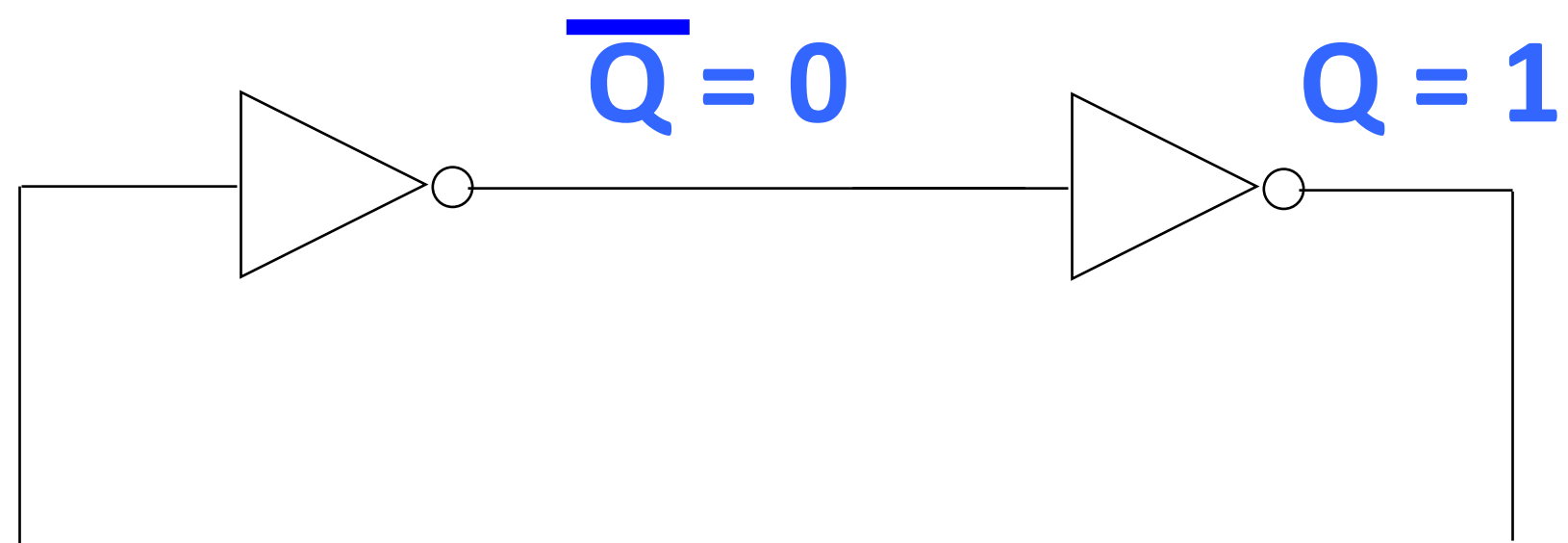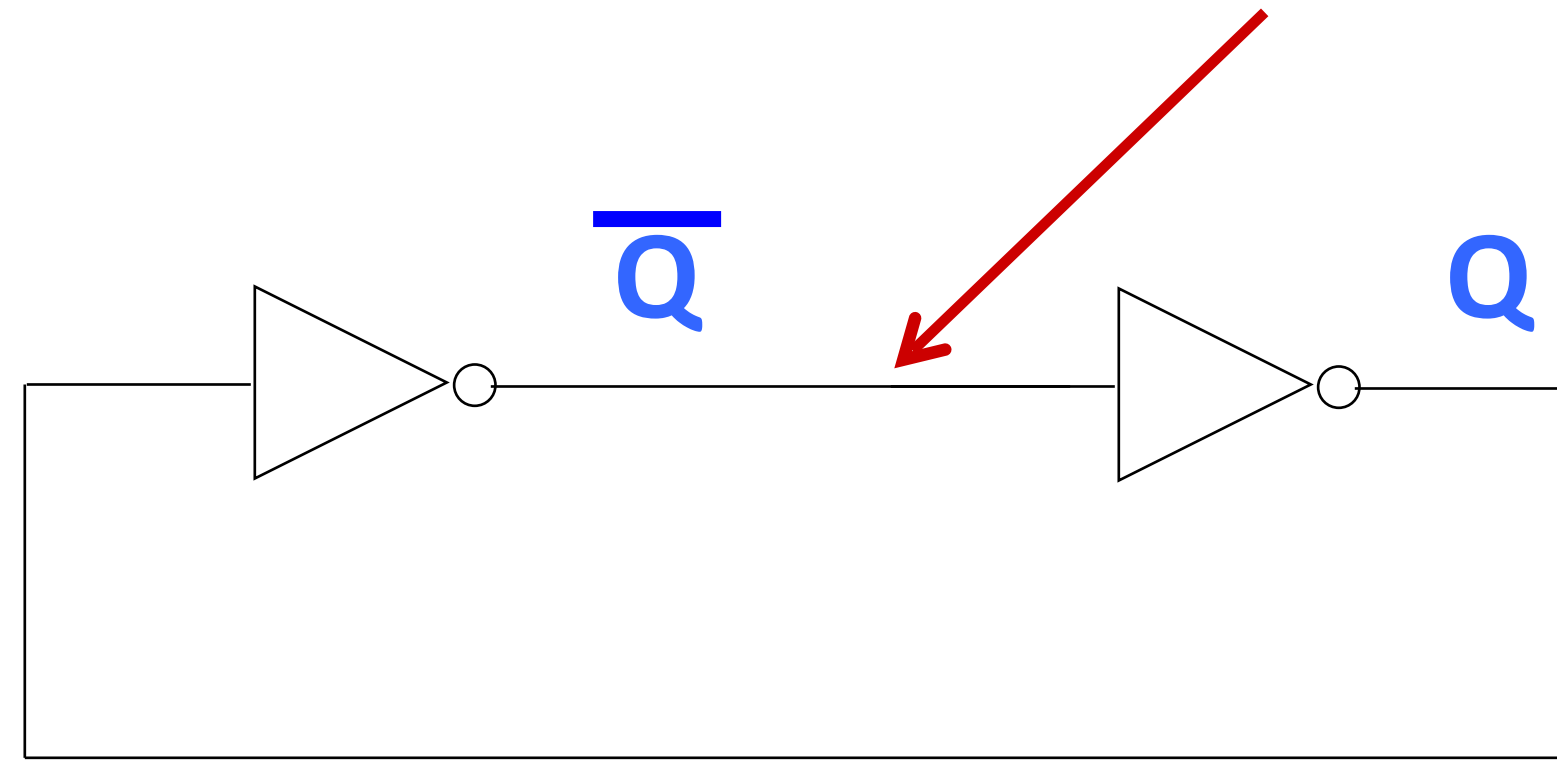Suppose we somehow get a 1 (or a 0?) on here.



or


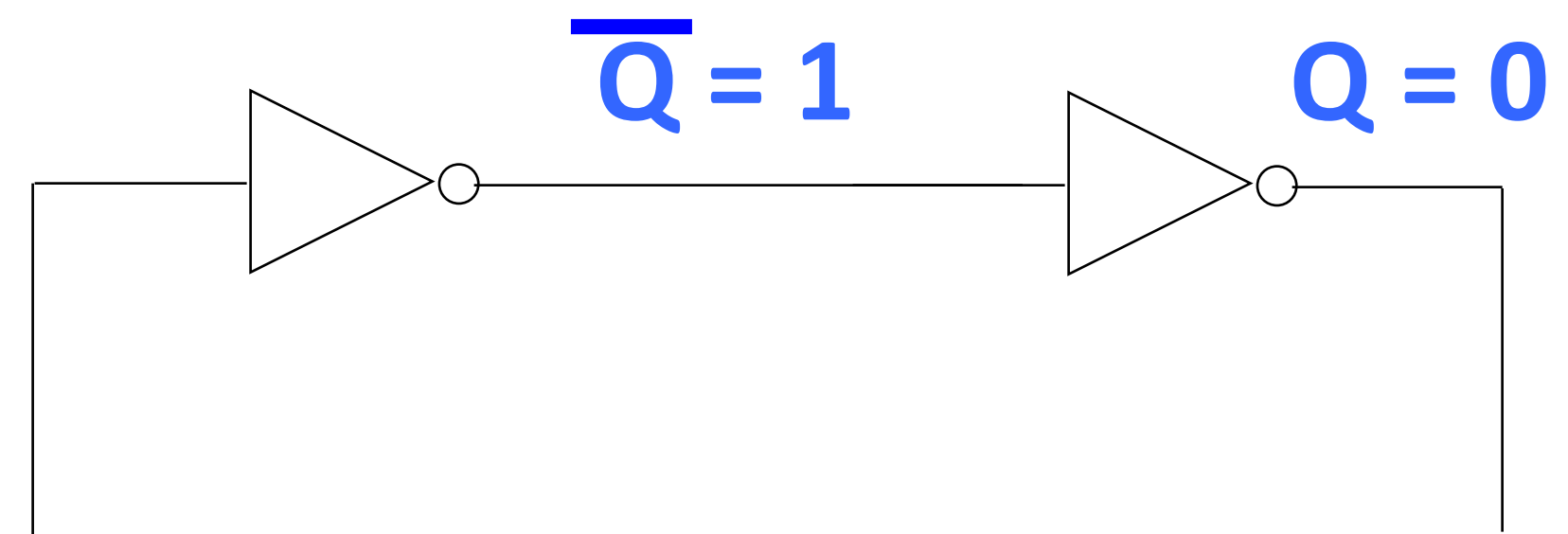


Now stable, but how do we set the value?


Bistable latches

Things are more sensible with an **even** number of inverters in a loop.

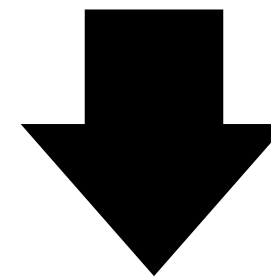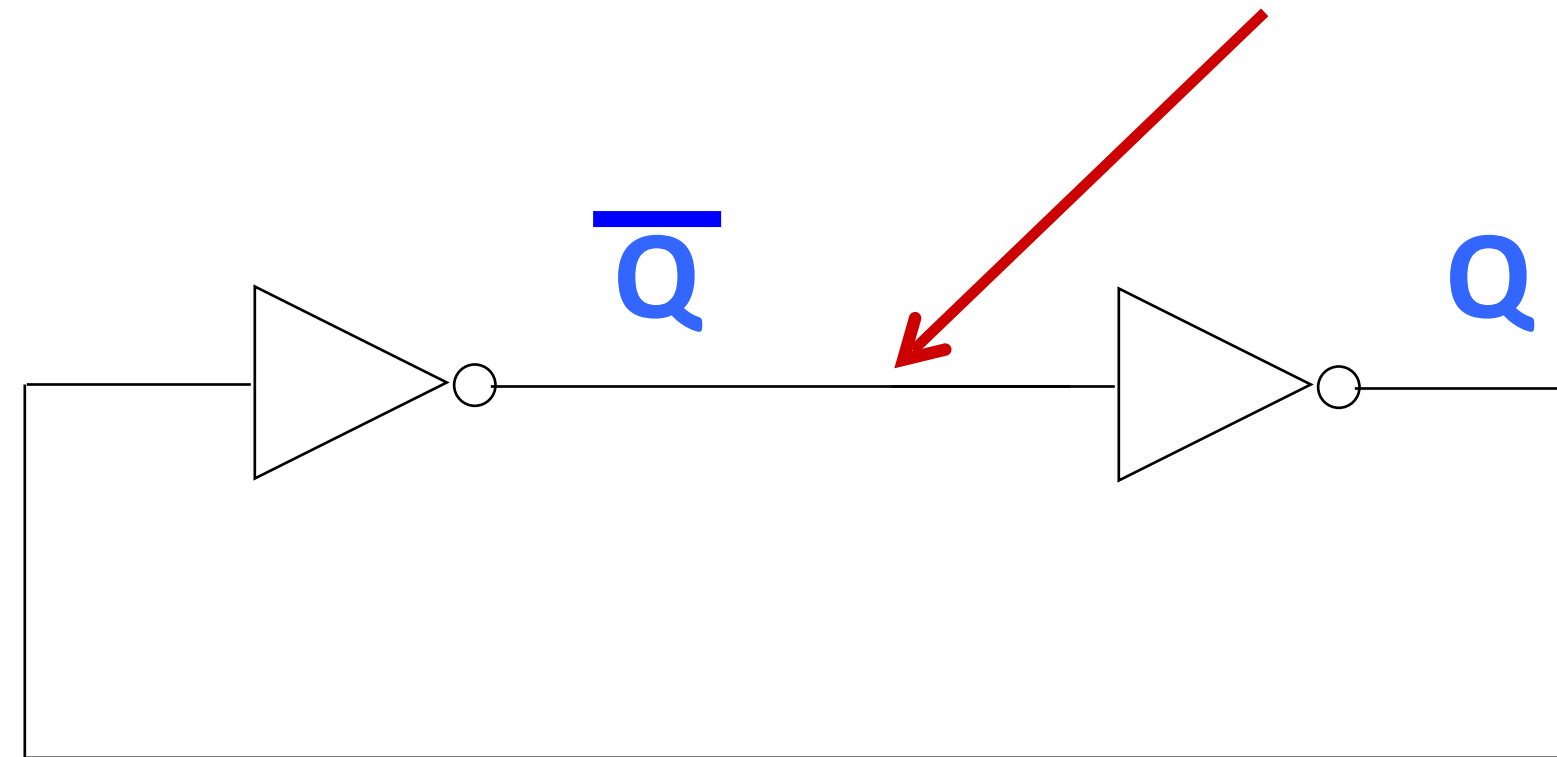
Suppose we somehow get a 1 (or a 0?) on here.



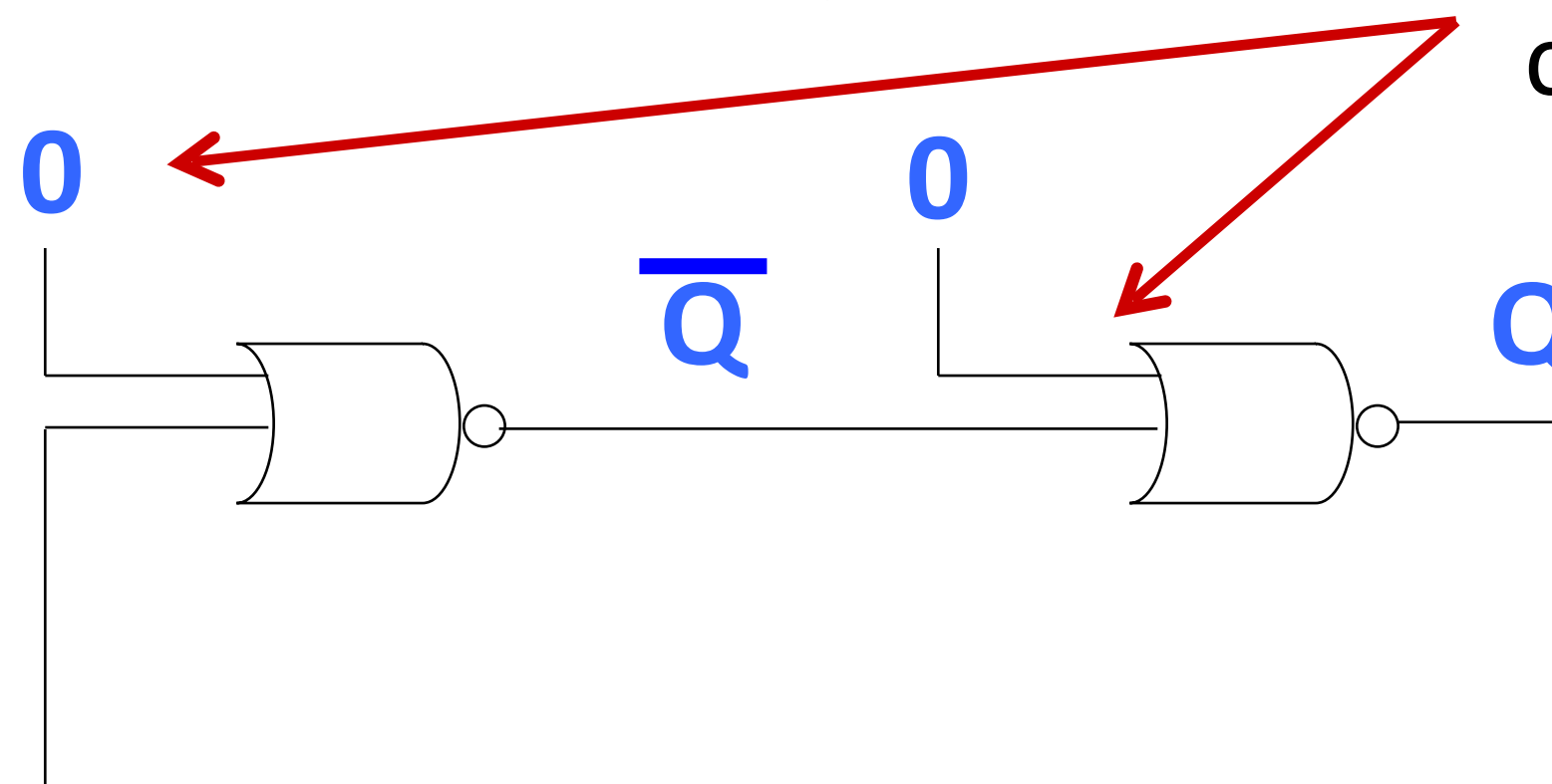Change to a 2-input gates so that we can **set** updated values to be stored



SR latch


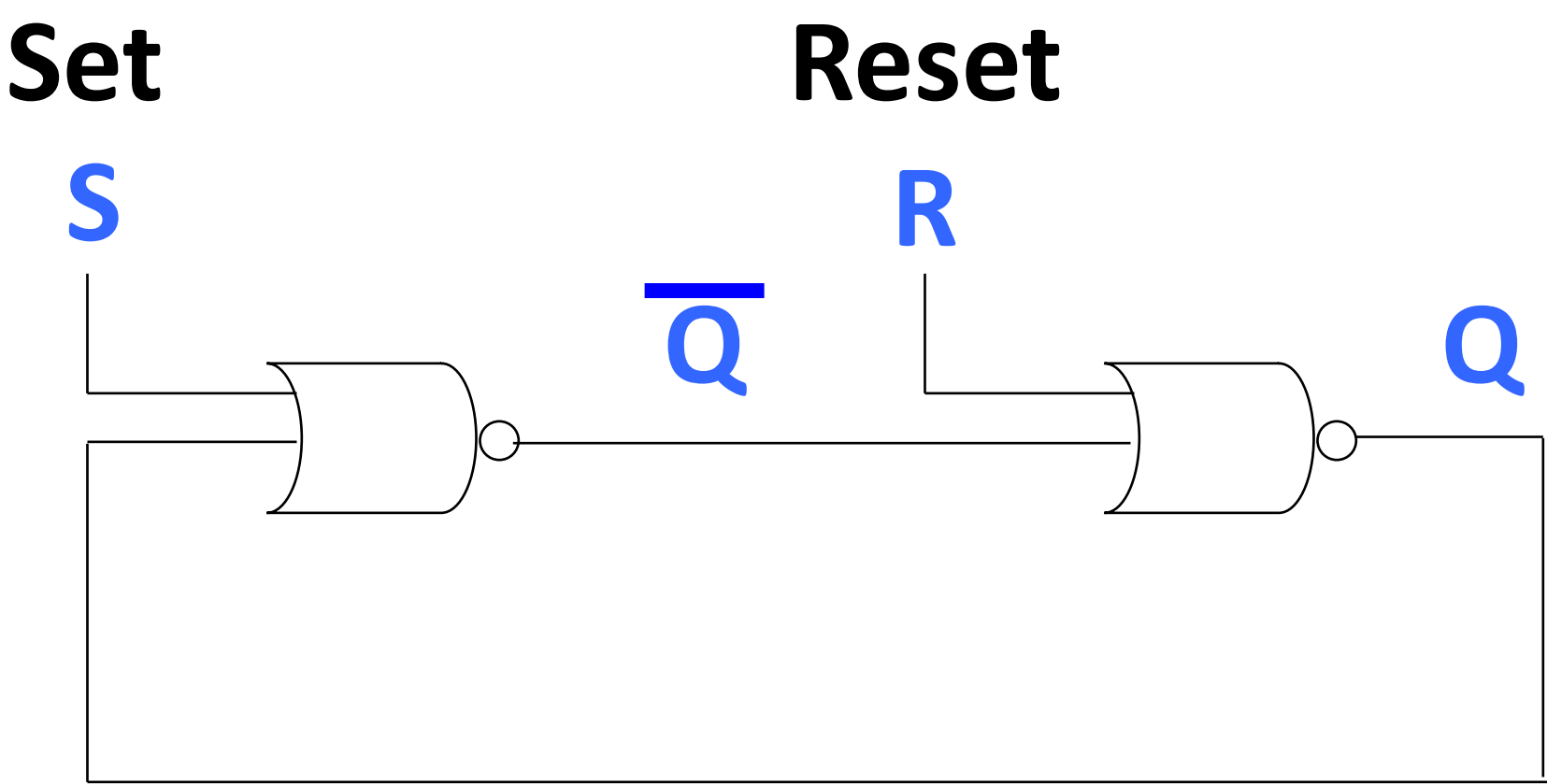


S	R	Q _{prev}	Q' _{prev}	Q _{next} (stable)	Q' _{next} (stable)
0	0	0	1	0	1
0	0	1	0	1	0
1	0	any	any	1	0
0	1	any	any	0	1
1	1	any	any	0	0

← Violates invariant that Q and Q' are inverses!

SR latch

 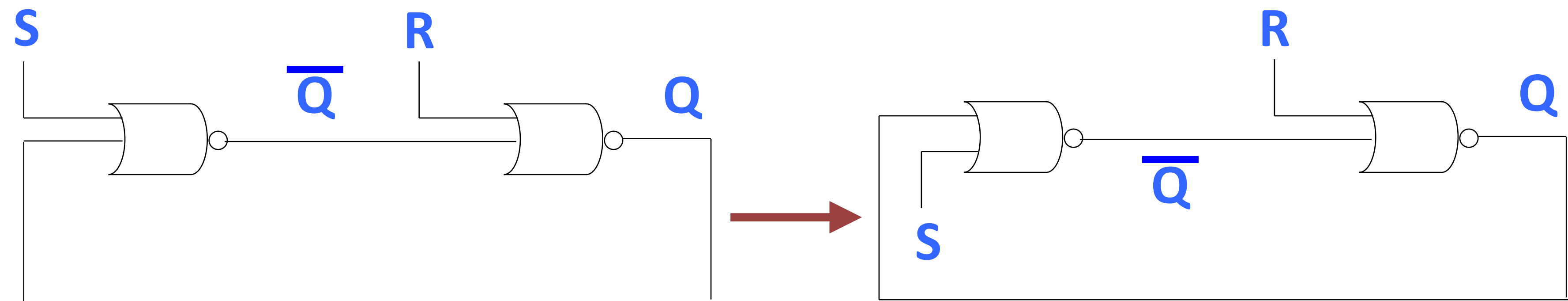Move from the circuit we built to the canonical form



SR latch

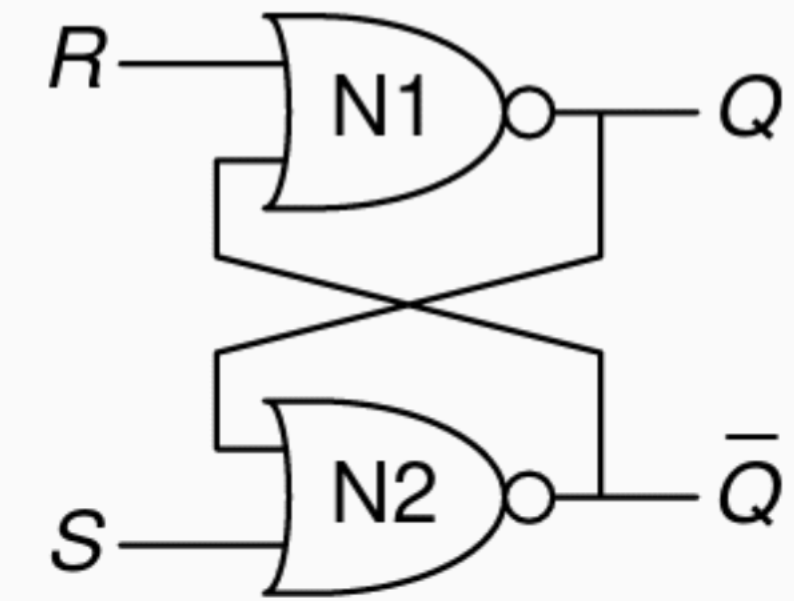
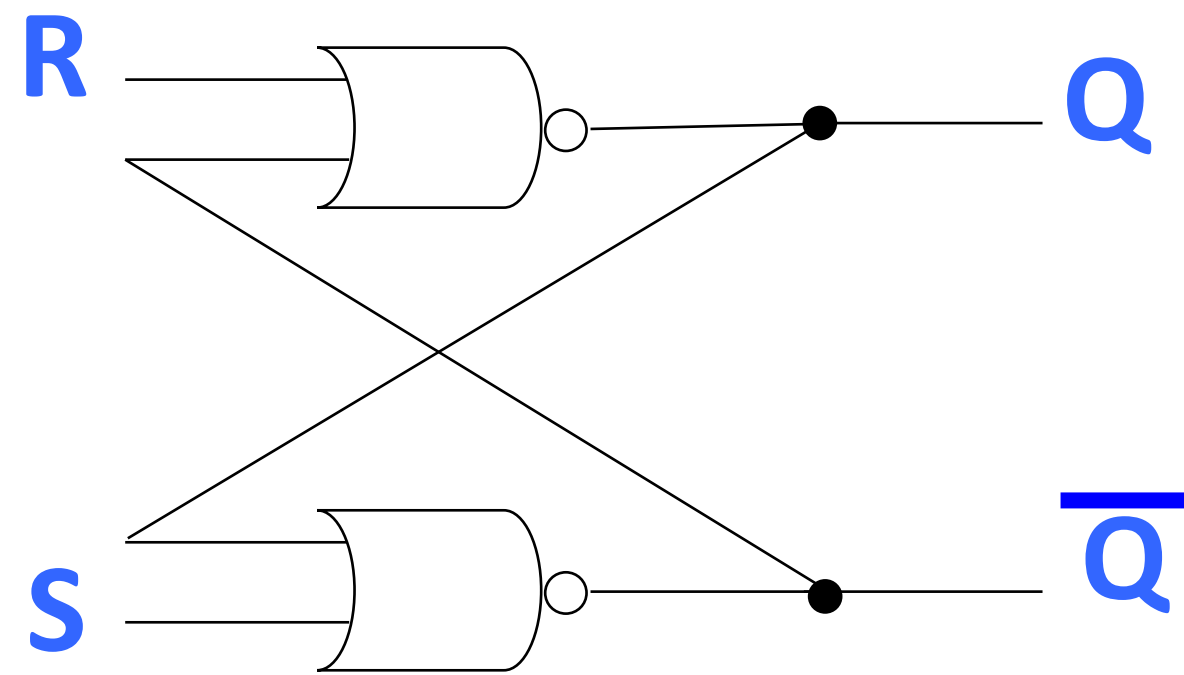


Figure 3.3 SR latch schematic

- Meets our goals:
- Able to set the value to 0 or 1
 - Able to read the value off the circuit

How do we set Q to 1?

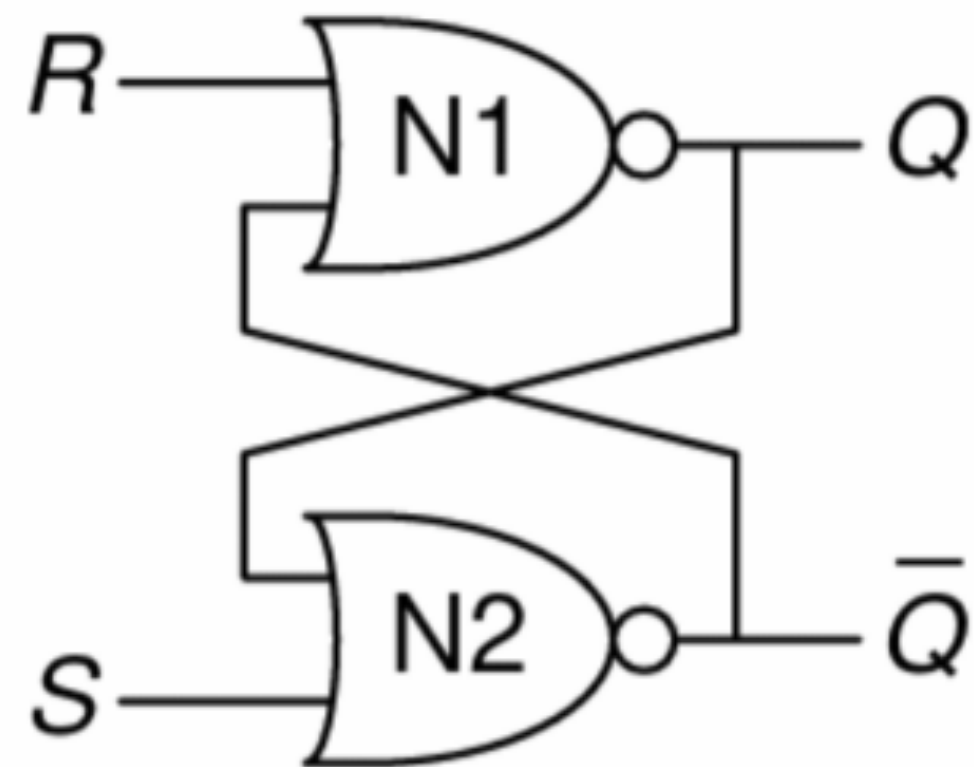


Figure 3.3 SR latch schematic

$S = 0; R = 0$

$S = 1; R = 0$

$S = 0; R = 1$

$S = 1; R = 1$

None of the above

How do we set Q to 1?

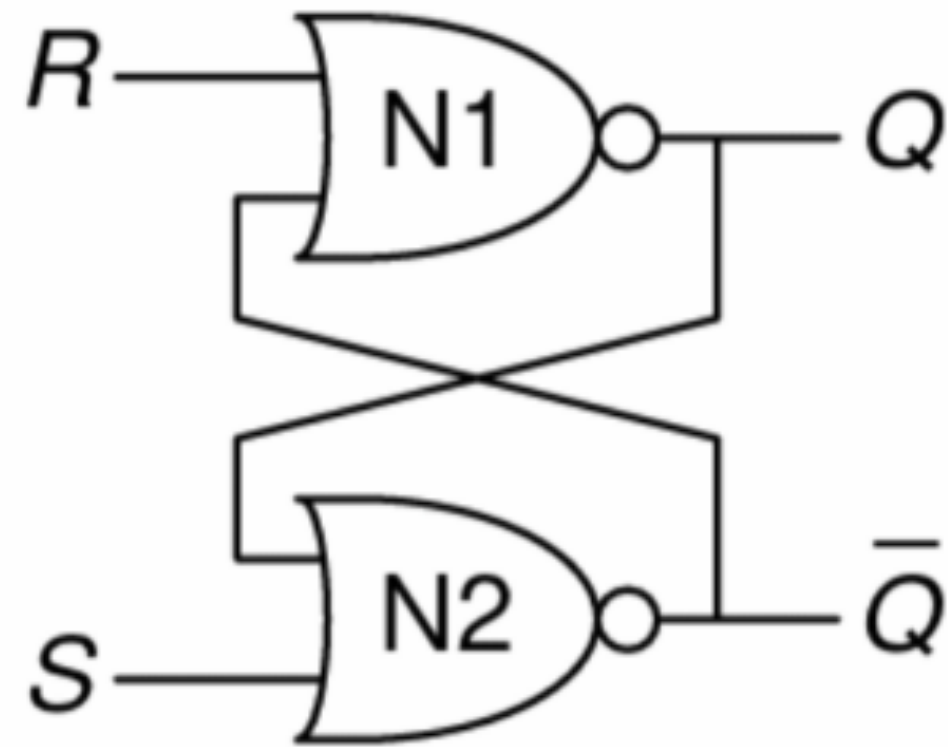


Figure 3.3 SR latch schematic

$S = 0; R = 0$

0%

$S = 1; R = 0$

0%

$S = 0; R = 1$

0%

$S = 1; R = 1$

0%

None of the above

0%

How do we set Q to 1?

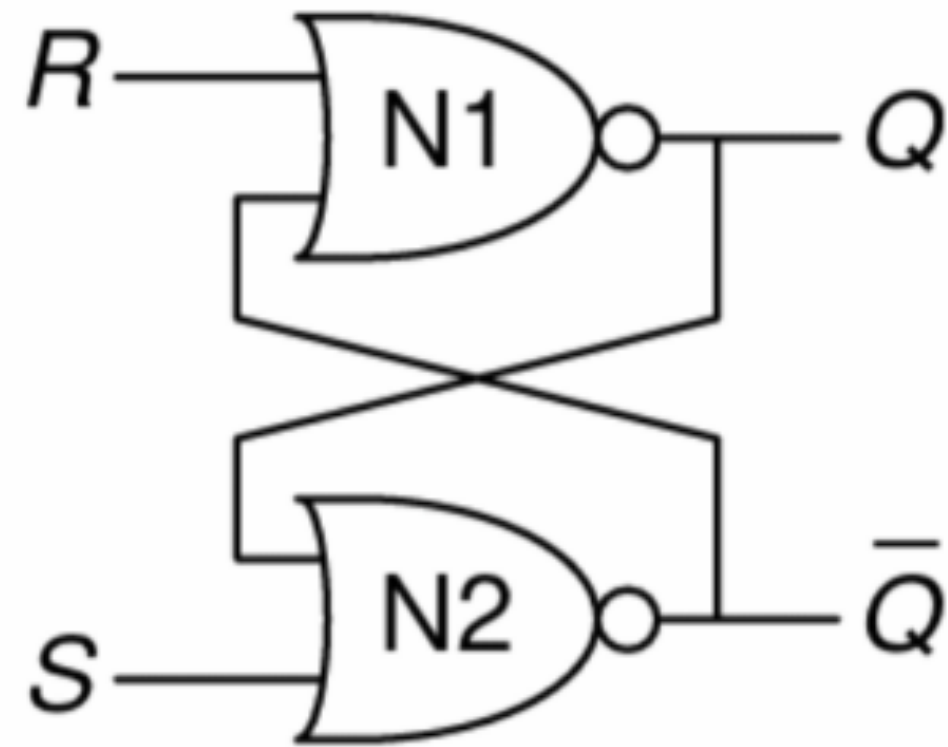


Figure 3.3 SR latch schematic

$S = 0; R = 0$

0%

$S = 1; R = 0$

0%

$S = 0; R = 1$

0%

$S = 1; R = 1$

0%

None of the above

0%

SR latch

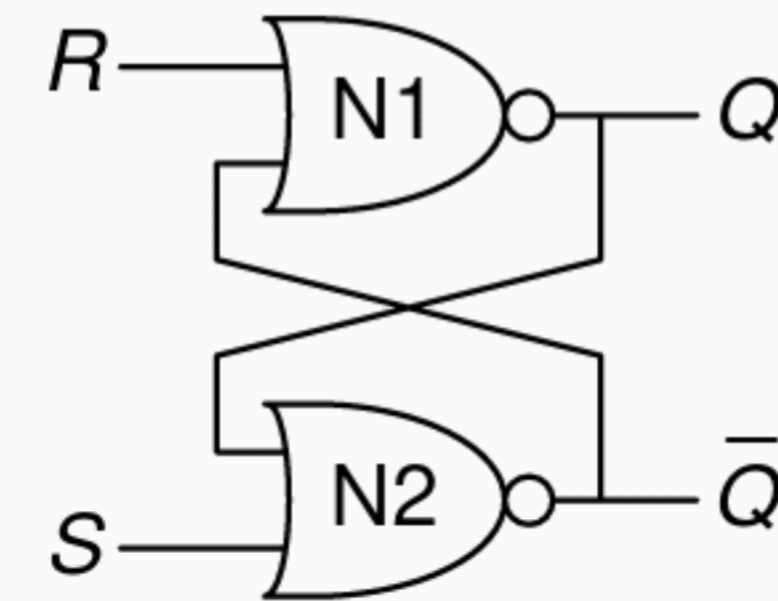
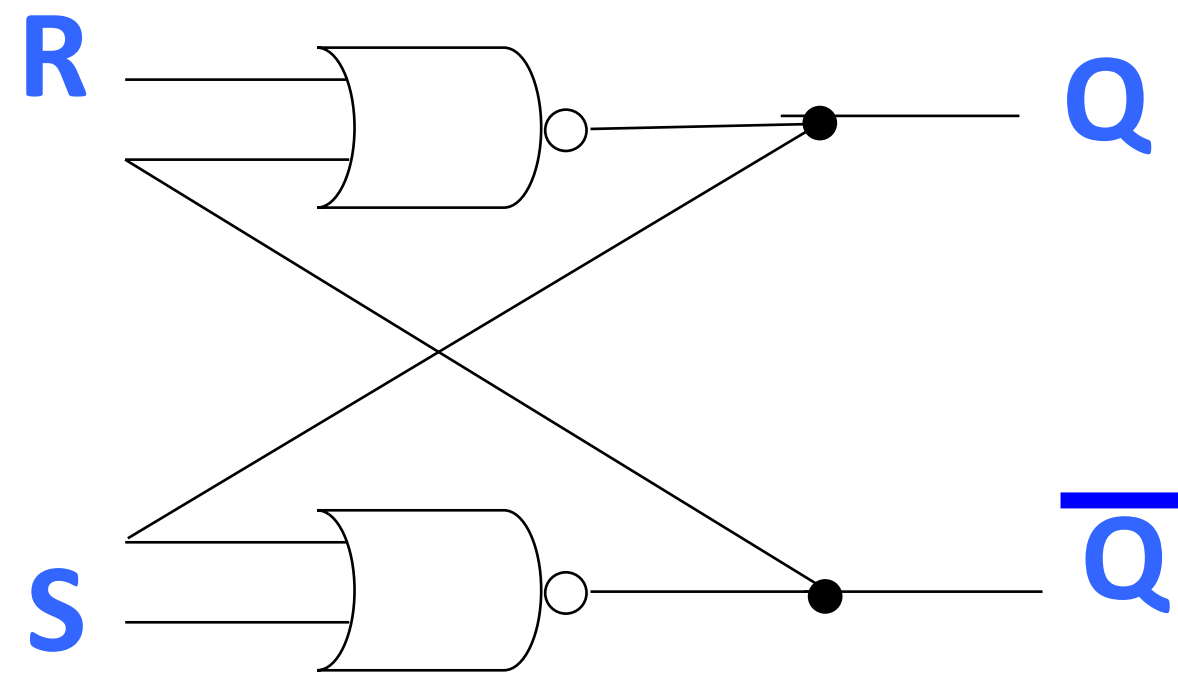


Figure 3.3 SR latch schematic

Meets our goals:

- Able to set the value to 0 or 1
- Able to read the value off the circuit


But:

- Ambiguous when $S = 1$ and $R = 1$
- No distinction between new value and timing

D latch

Goals:

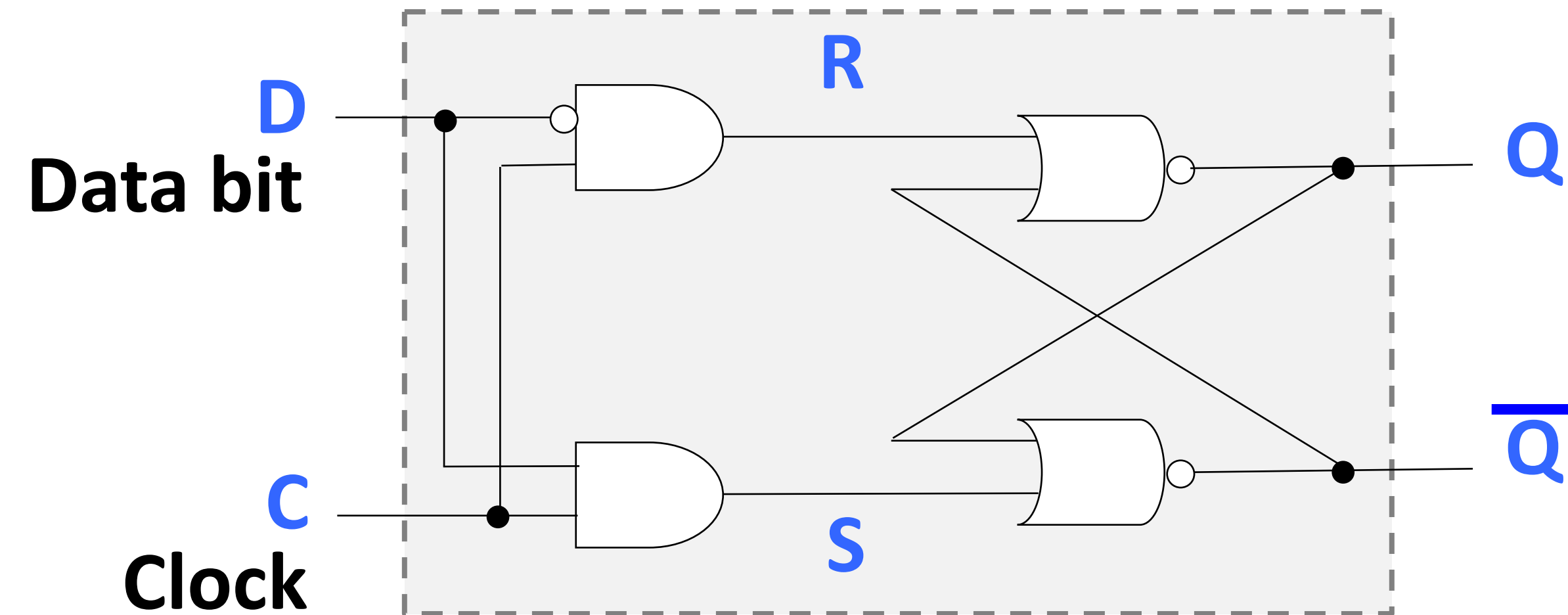- Only 1 bit for data
- Control over timing



if $C = 0$, then SR latch stores current value of Q .

if $C = 1$, then D flows to Q :


if $D = 0$, then $R = 1$ and $S = 0$, $Q = 0$

if $D = 1$, then $R = 0$ and $S = 1$, $Q = 1$


Notes:

- Data bit D replaces S & R : it's the bit value we want to store when $\text{Clock} = 1$
 - Internally, Data bit D prevents bad case of $S = R = 1$
- This logic is **level-triggered**; as long as $\text{Clock} = 1$, changes to D flow to outputs

Time matters!

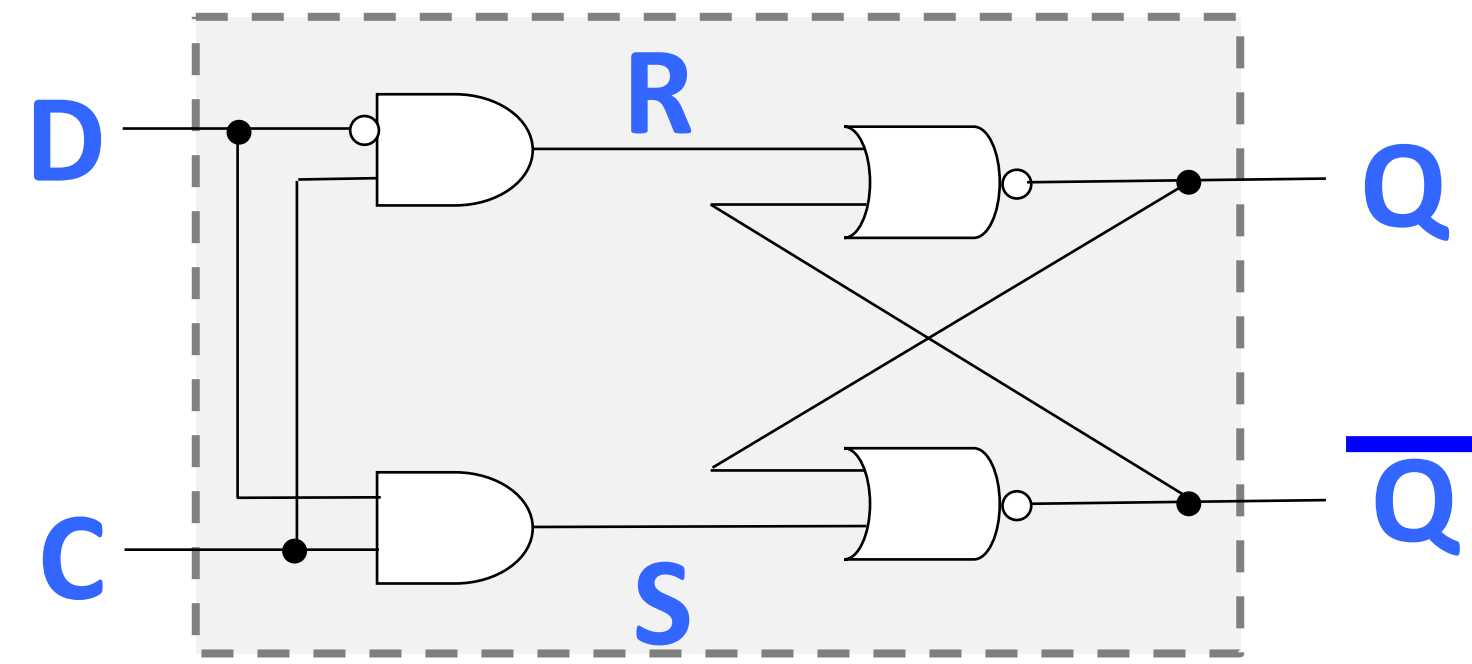

ex

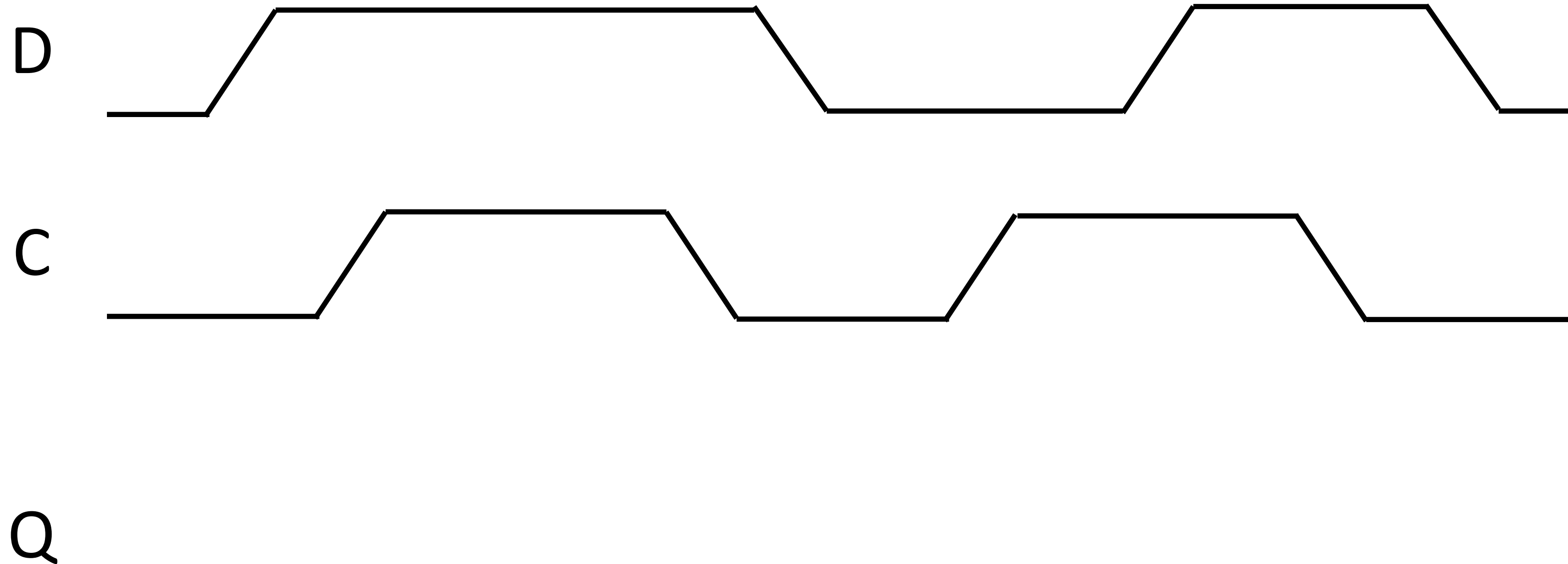


Assume Q has an initial state of 0

In general: clocks

Clock: free-running signal

with fixed **cycle** time = **clock period** = T .

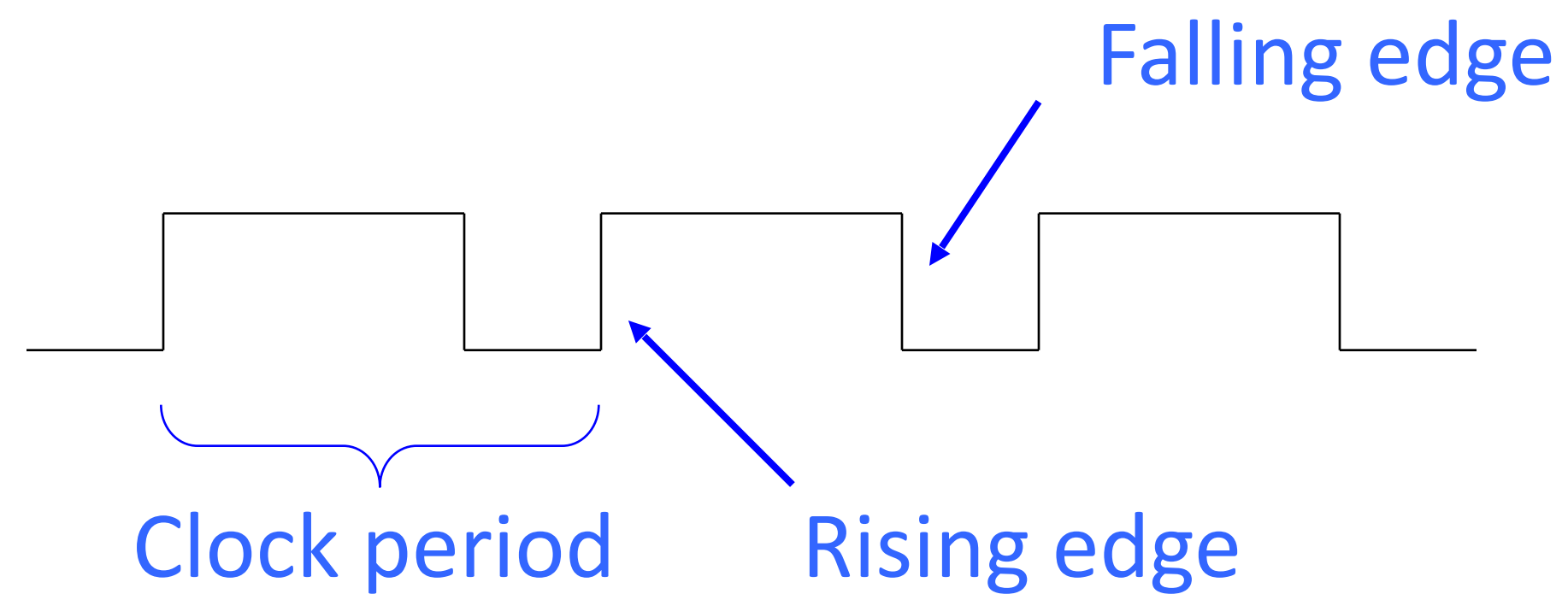Clock frequency = $1 / \text{clock period}$



A clock controls when to update a sequential logic element's state.




Aside: “Clock frequency”

Clock frequency


$$= 1 / \text{period} = 1 / \text{s} = \text{Hz}$$

Typical CPU: 3-4 GHz


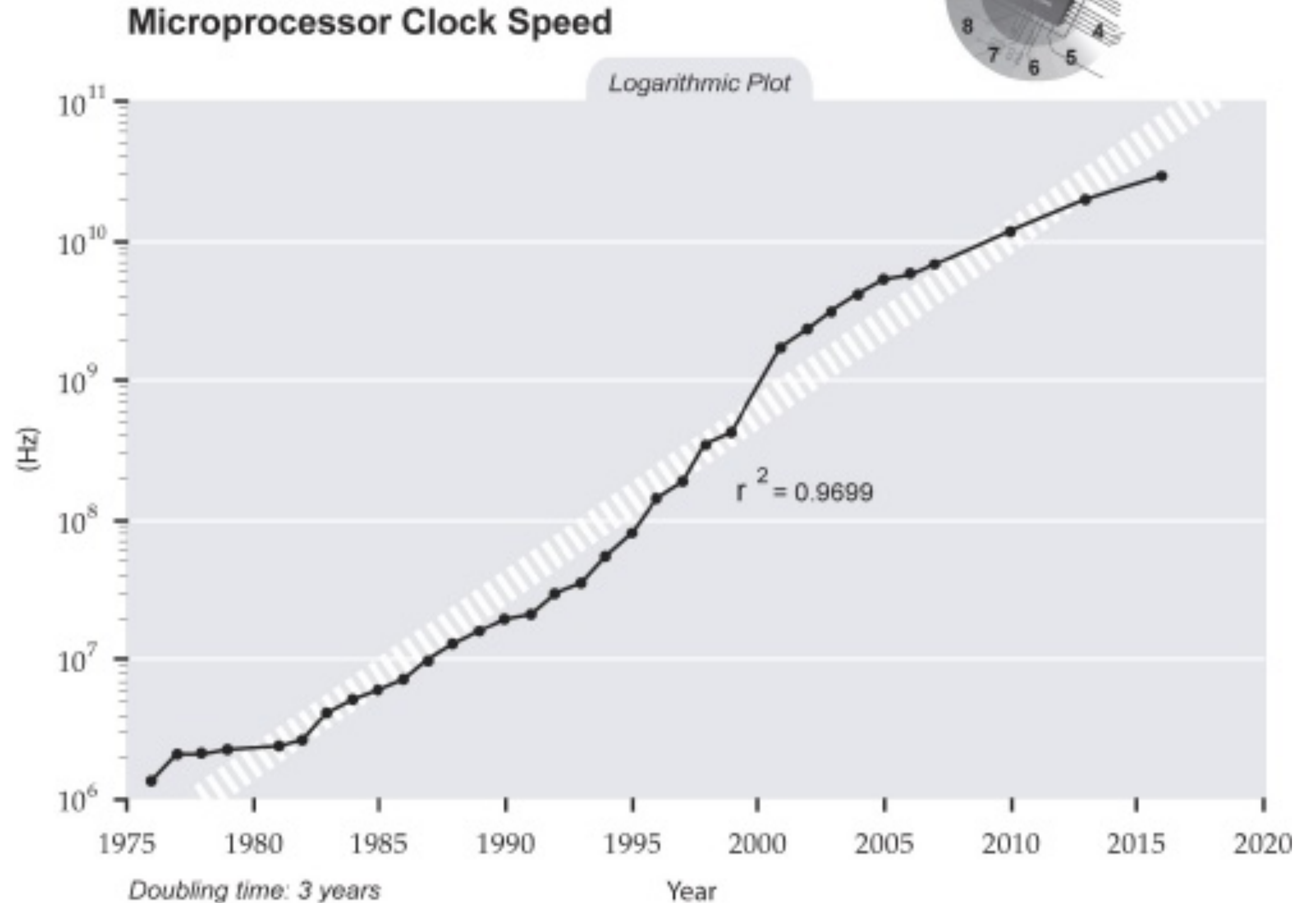


Synchronous systems

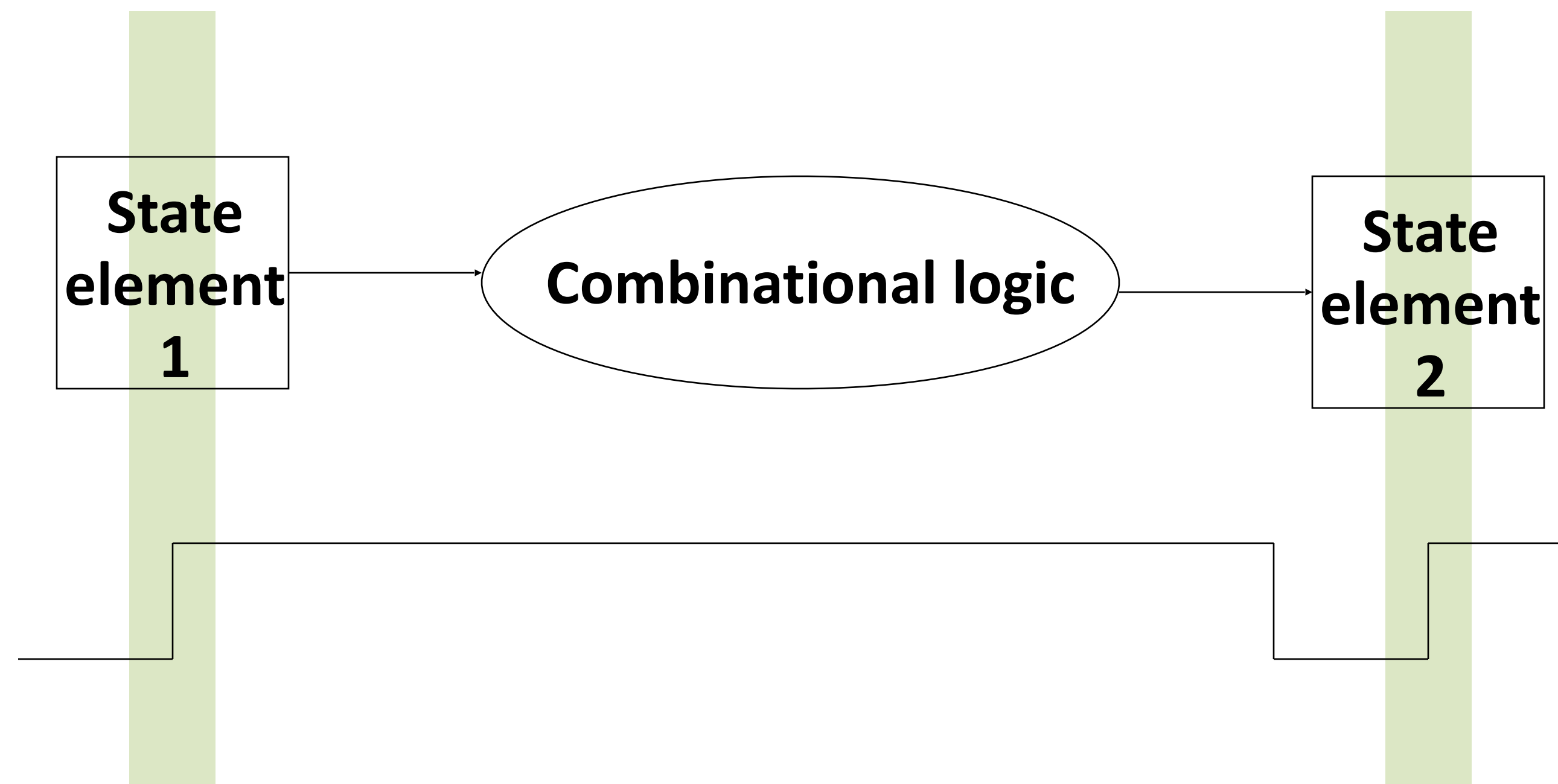Inputs to state elements must be **valid** on active clock edge.




D flip-flop with *falling*-edge trigger

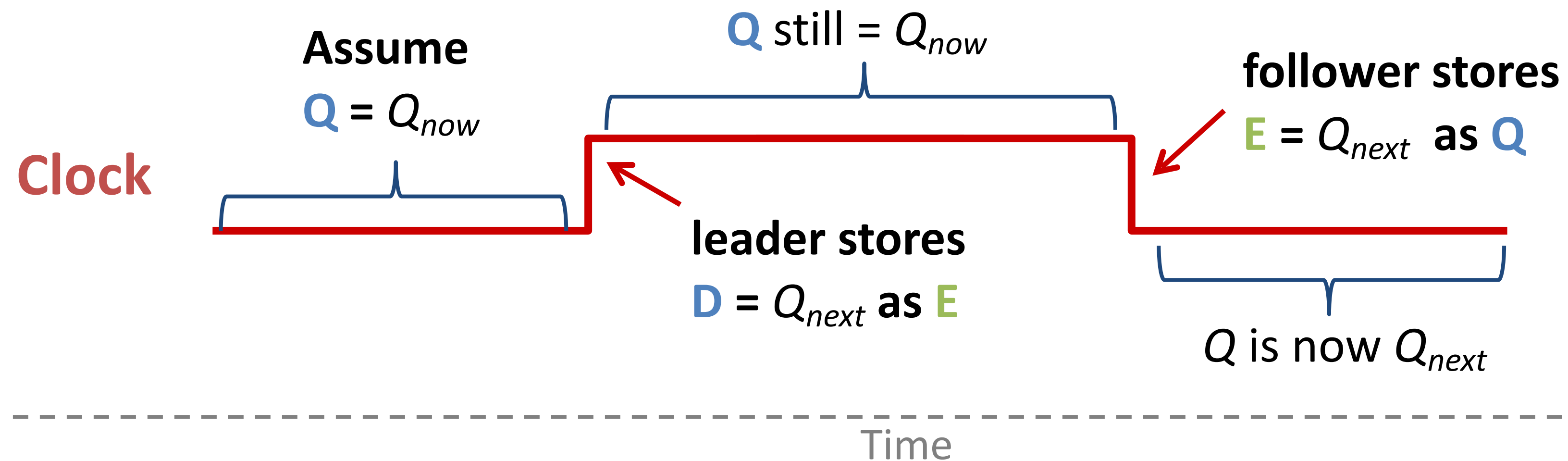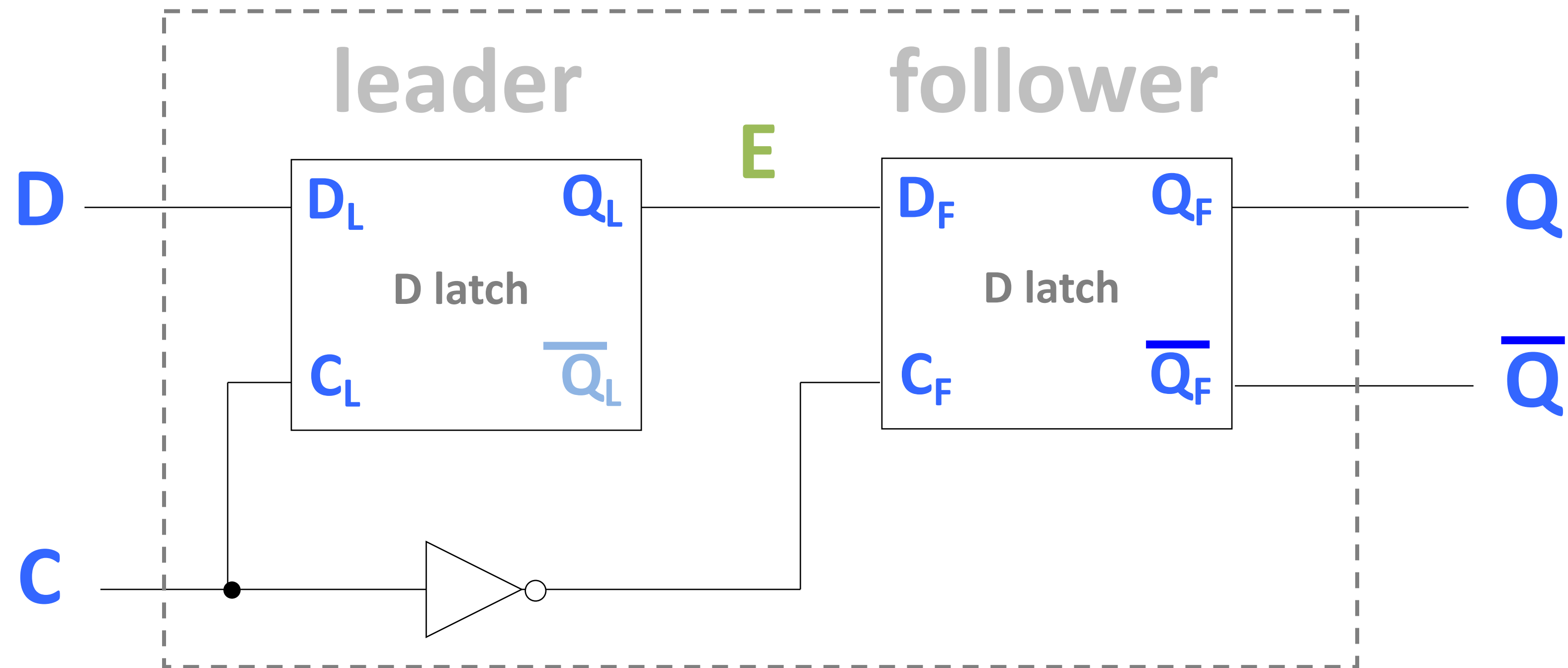


Time matters! D flip-flop with *falling*-edge trigger

ex

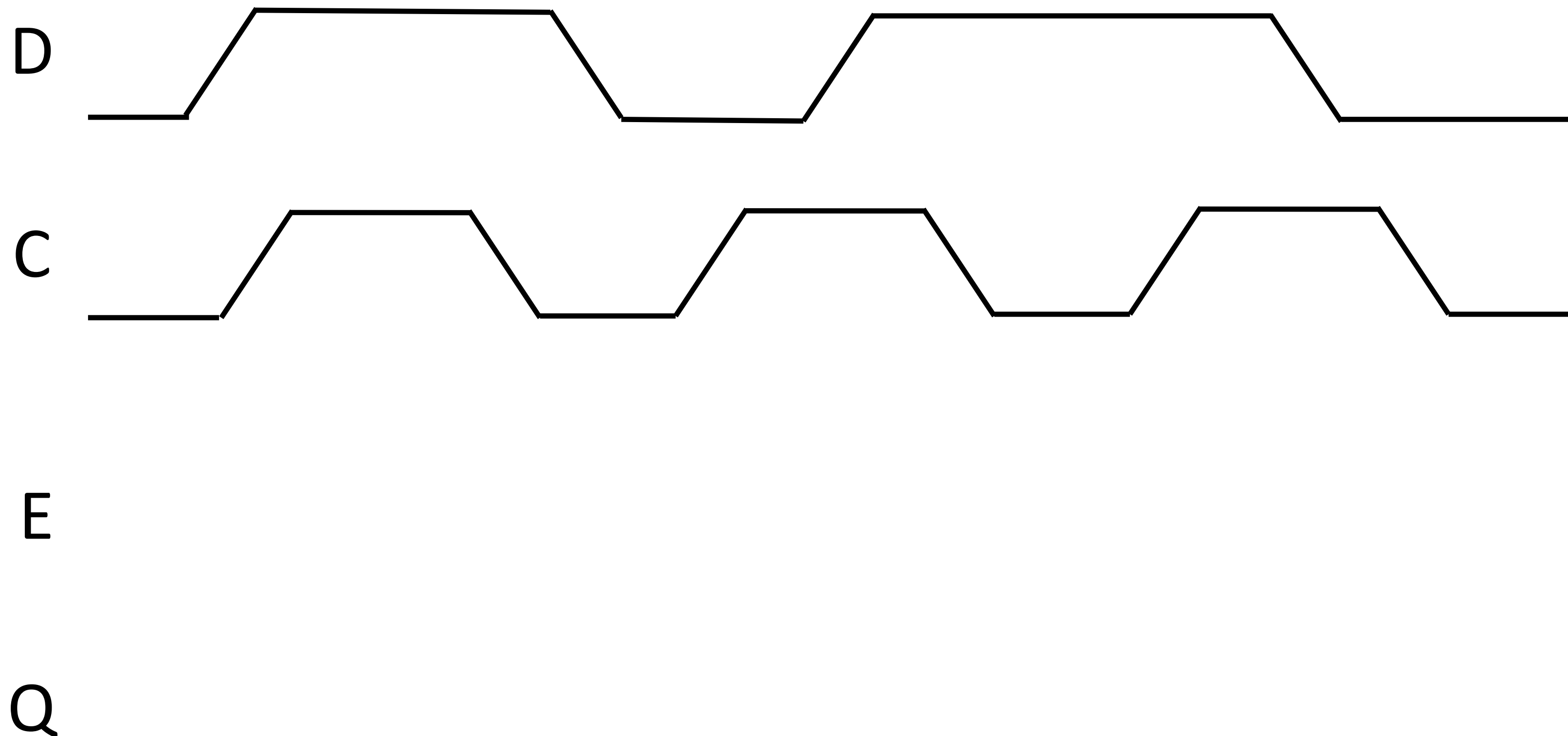

Assume Q and E have an initial state of 0

Reading and writing in the same cycle

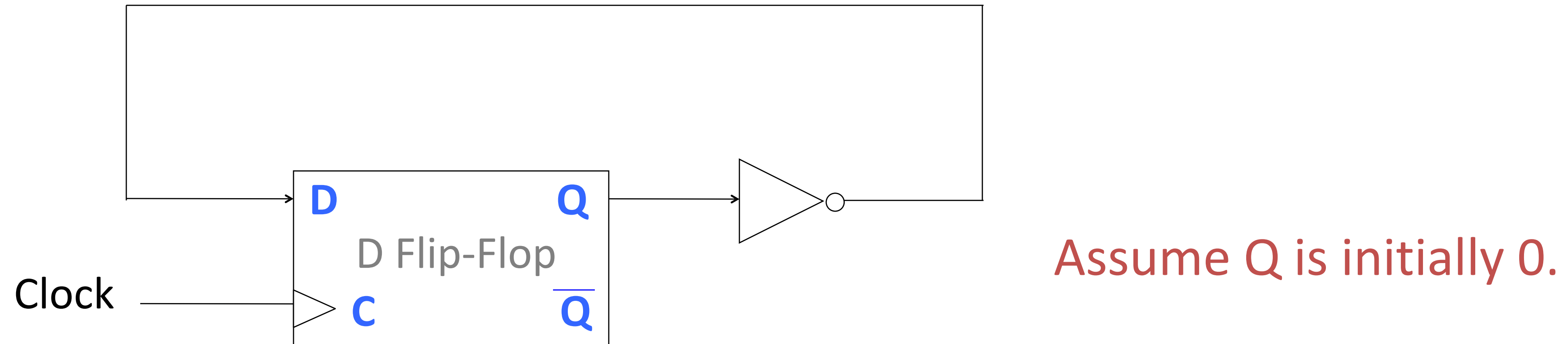


Moral: It's OK to use the current output Q of a flip-flop as part of the the next data input D to the same flip-flop.

D flip-flop = one bit of storage



The bit value of D when C has a falling edge is remembered at Q until the next falling edge of C.

Registers

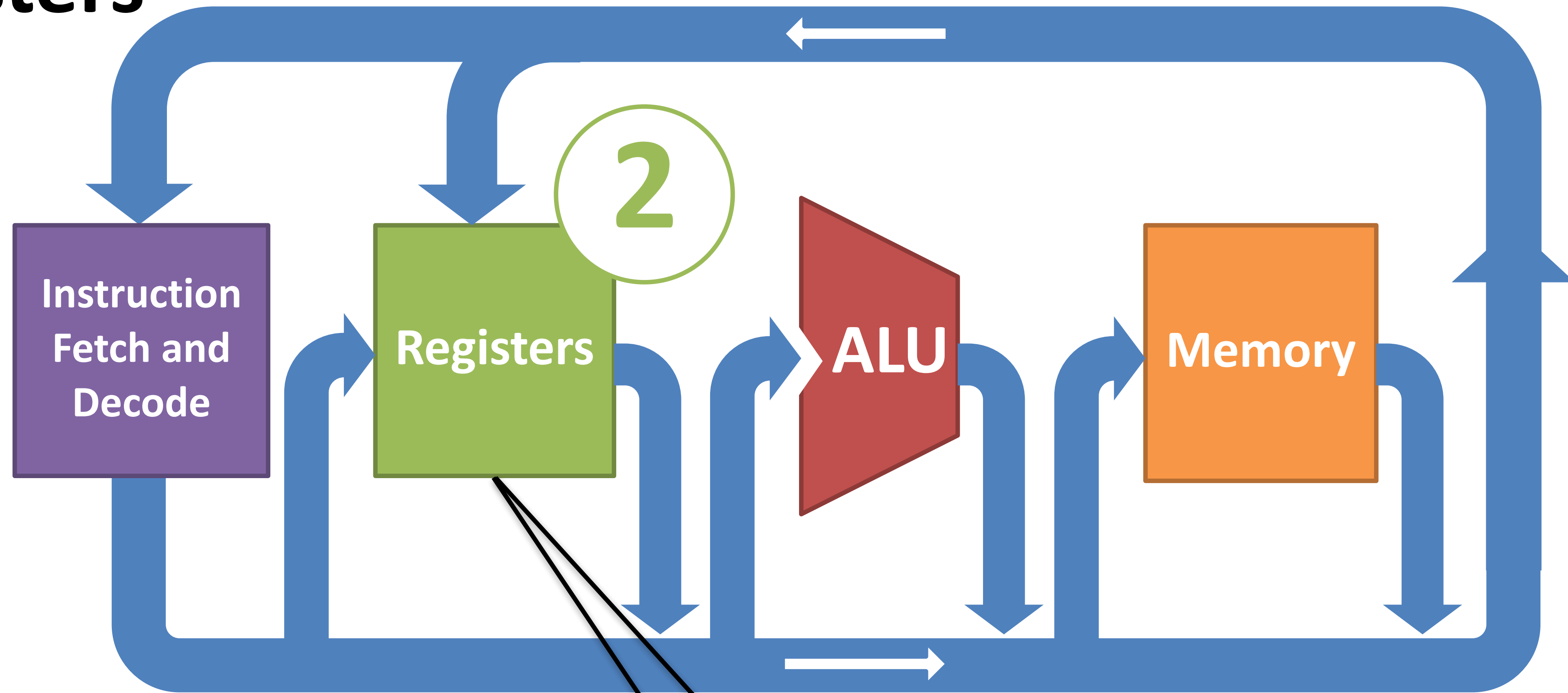

Assembly code (later this semester):


`addq %rdi, %rsi`

A 1-nybble* register

**Half a byte!*

(a 4-bit hardware storage cell)

Write value

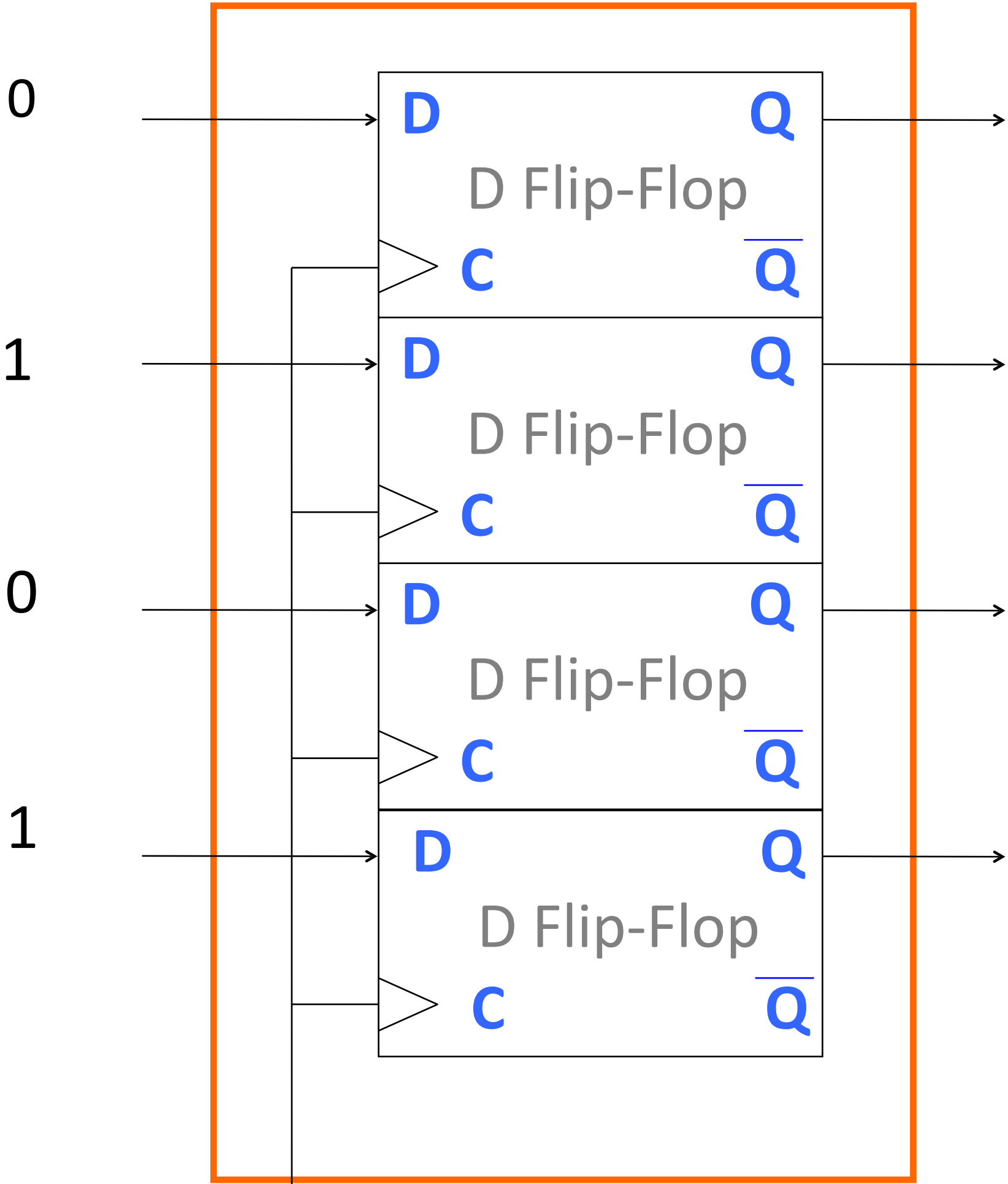


Shared clock

write control
Clock



Clock line may be indicated


Register file

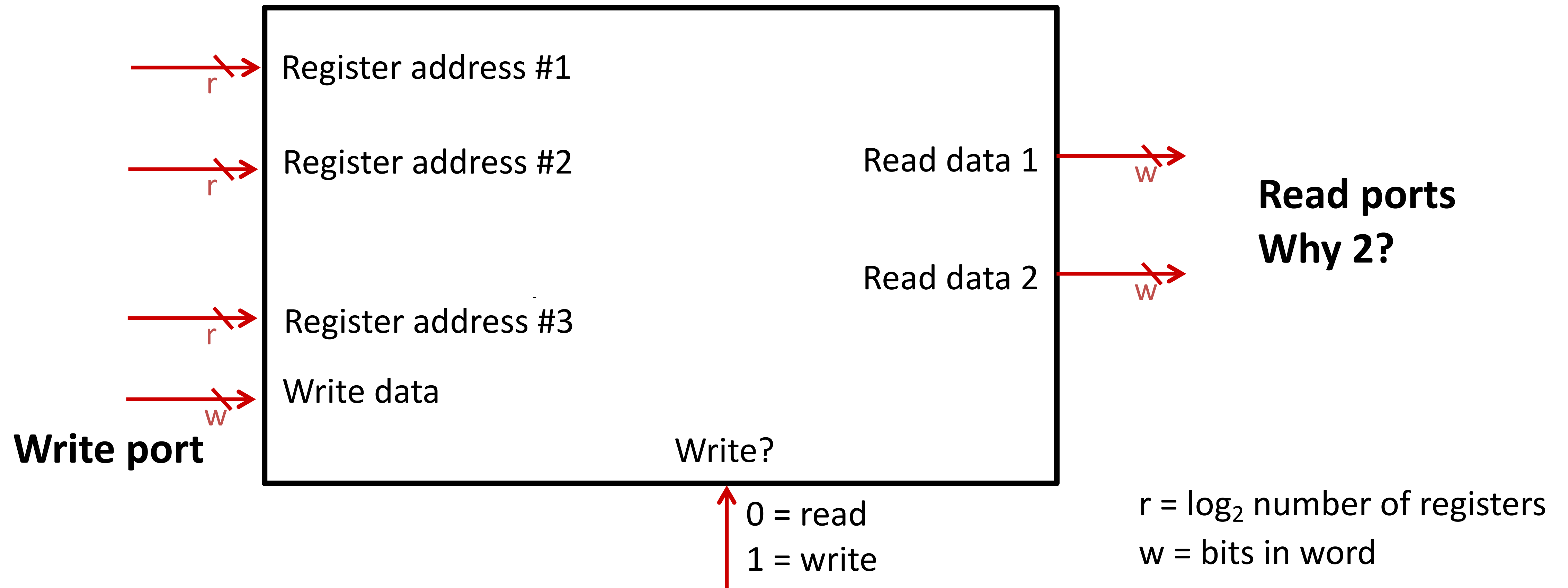

Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.

Read ports (data out)

Register address #1
($\log_2 k$ bits)

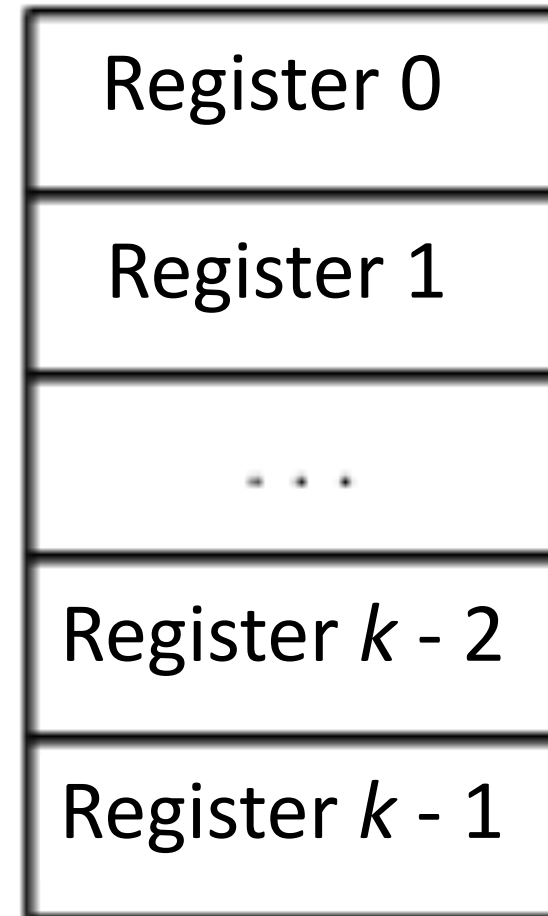


Register address #2
($\log_2 k$ bits)


n Data read from
register address #1
(n bits)

n Data read from
register address #2
(n bits)


Read ports (data out)

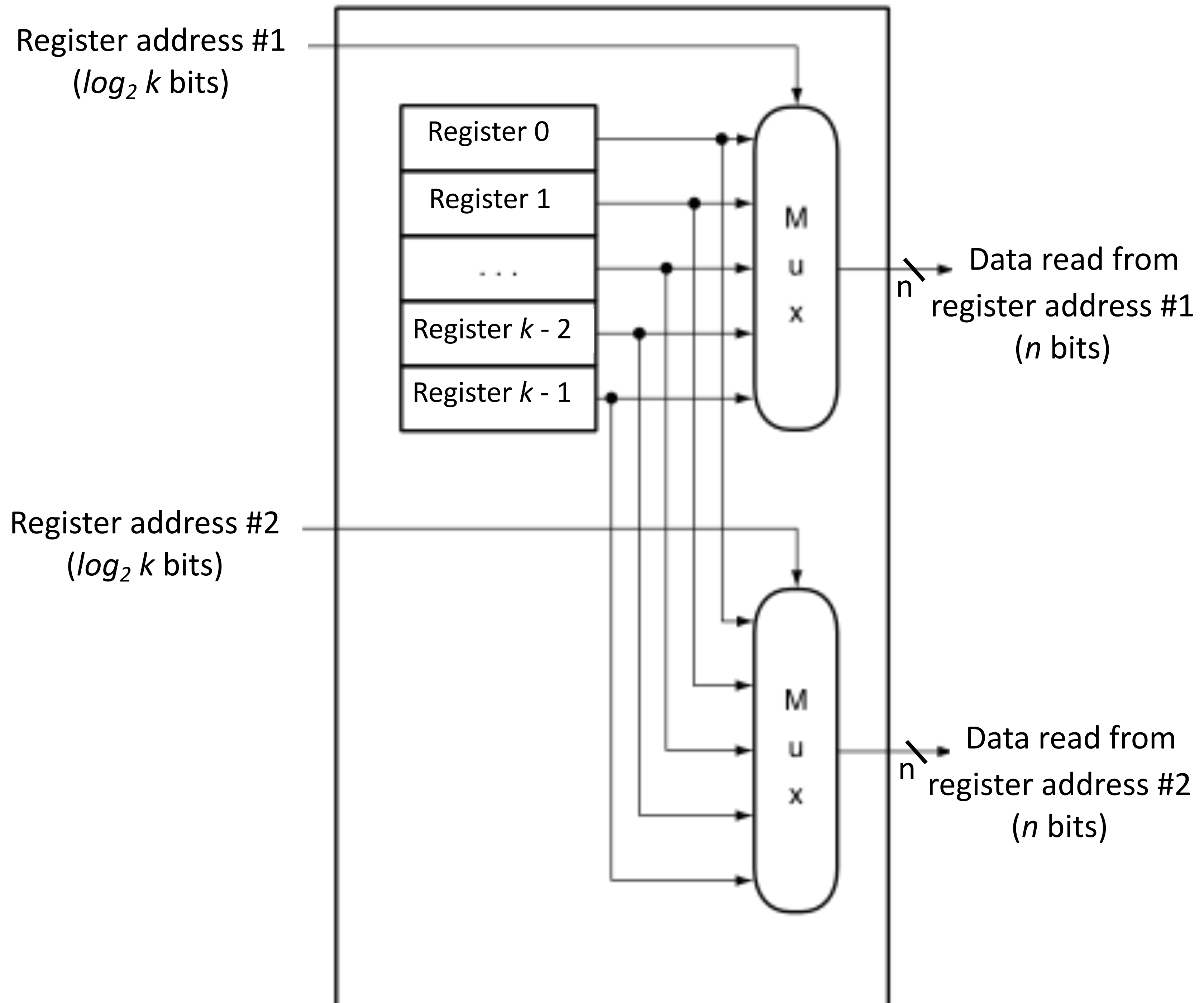


Write port (data in)

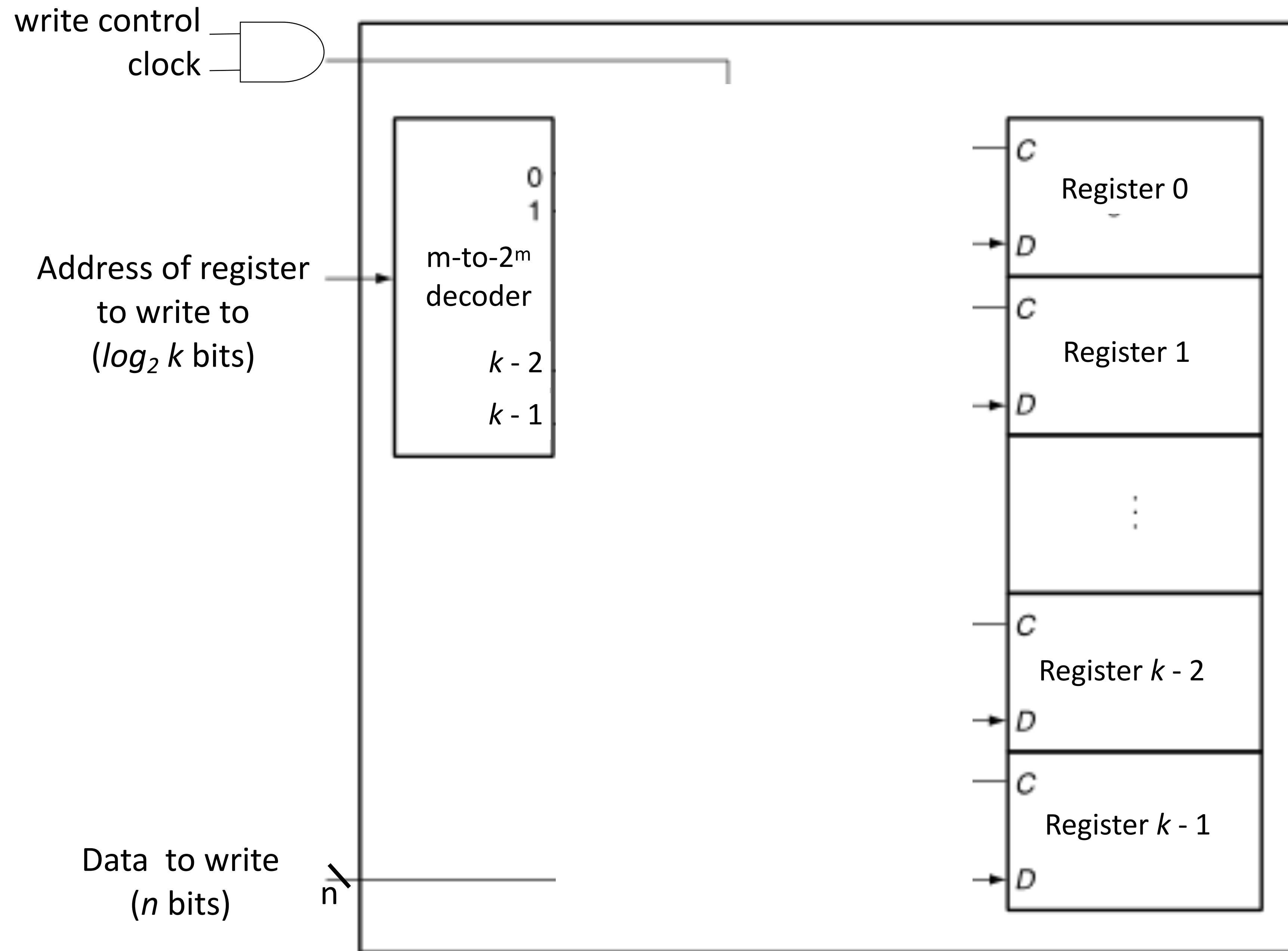

Write port (data in)

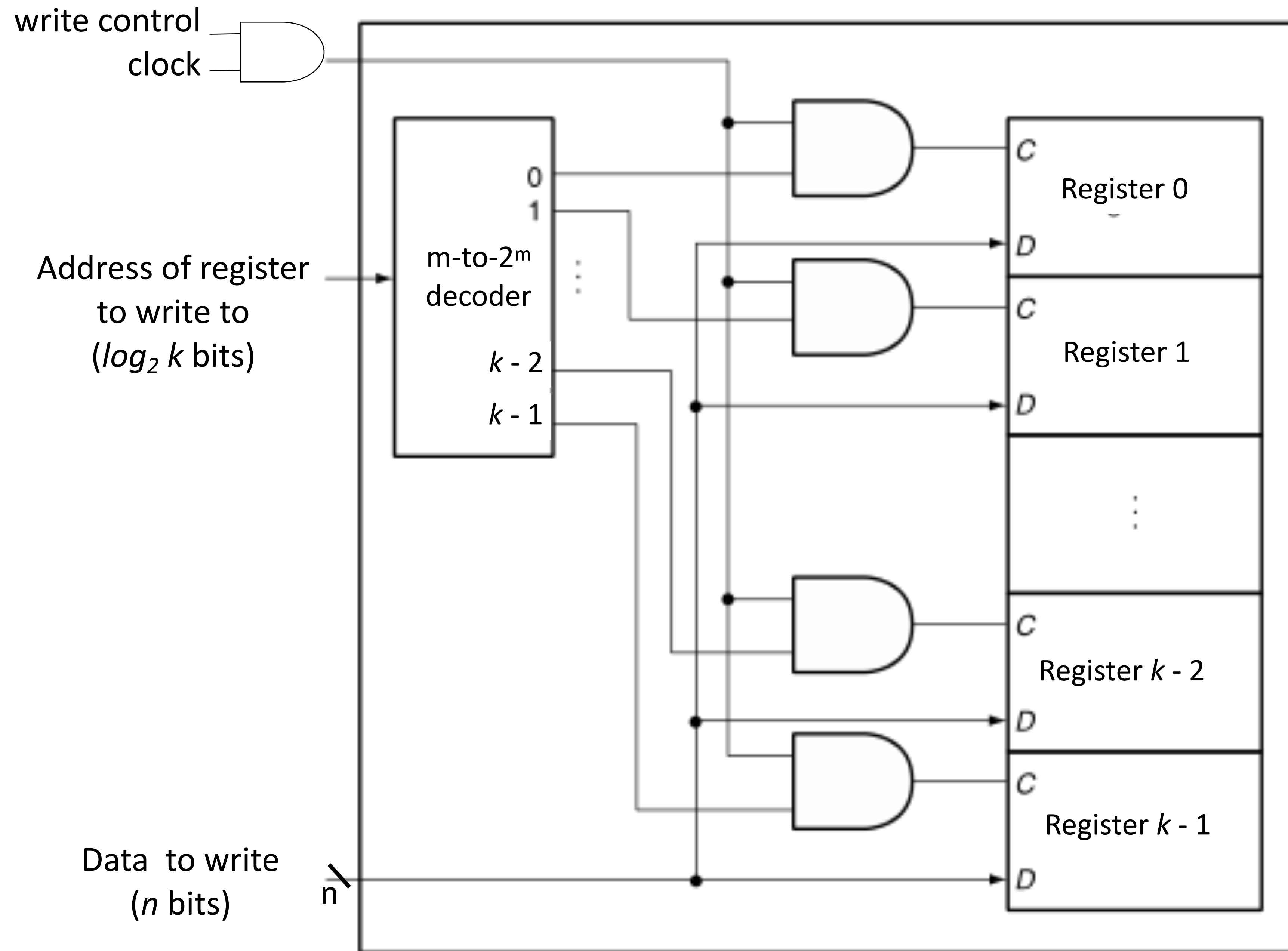


Registers summary

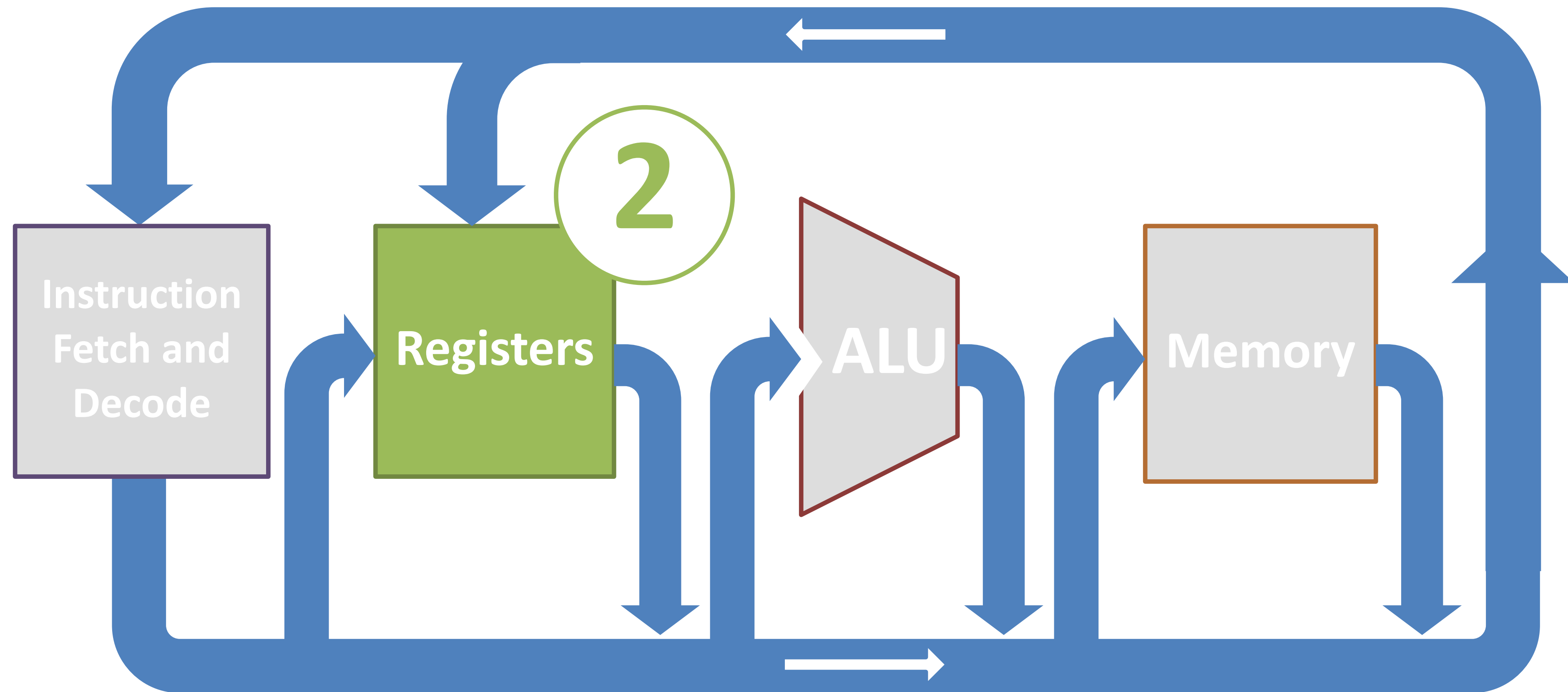


- For our purposes: implemented with flip-flops
- Very fast access
- Limited in size:
 - Need an m -to- 2^m decoder
 - CPUs typically have **~10s of words** of register storage

Registers summary

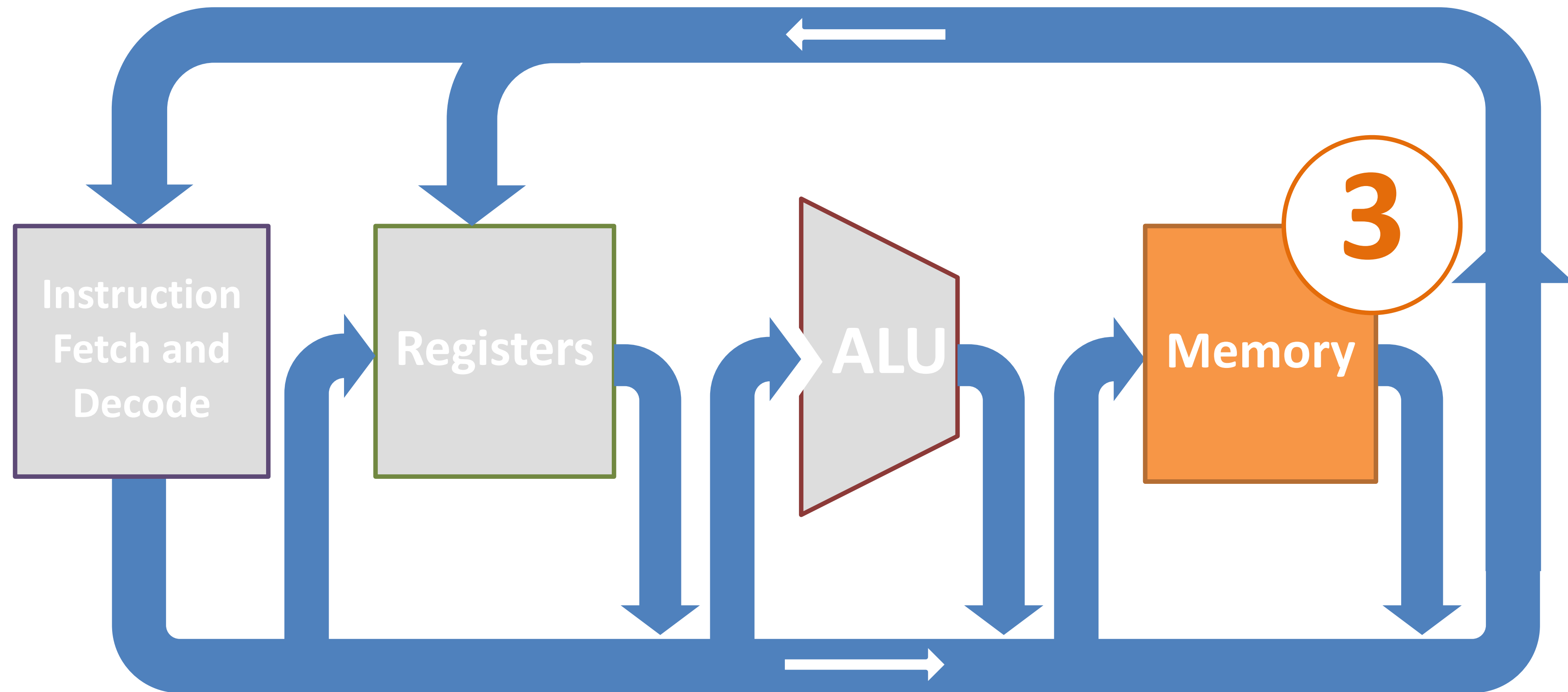

- We'll think about at a higher level of abstraction
- Designed to handle a much larger amount of data
 - CPUs can have **millions-billions of words** of memory storage

RAM (Random Access Memory)

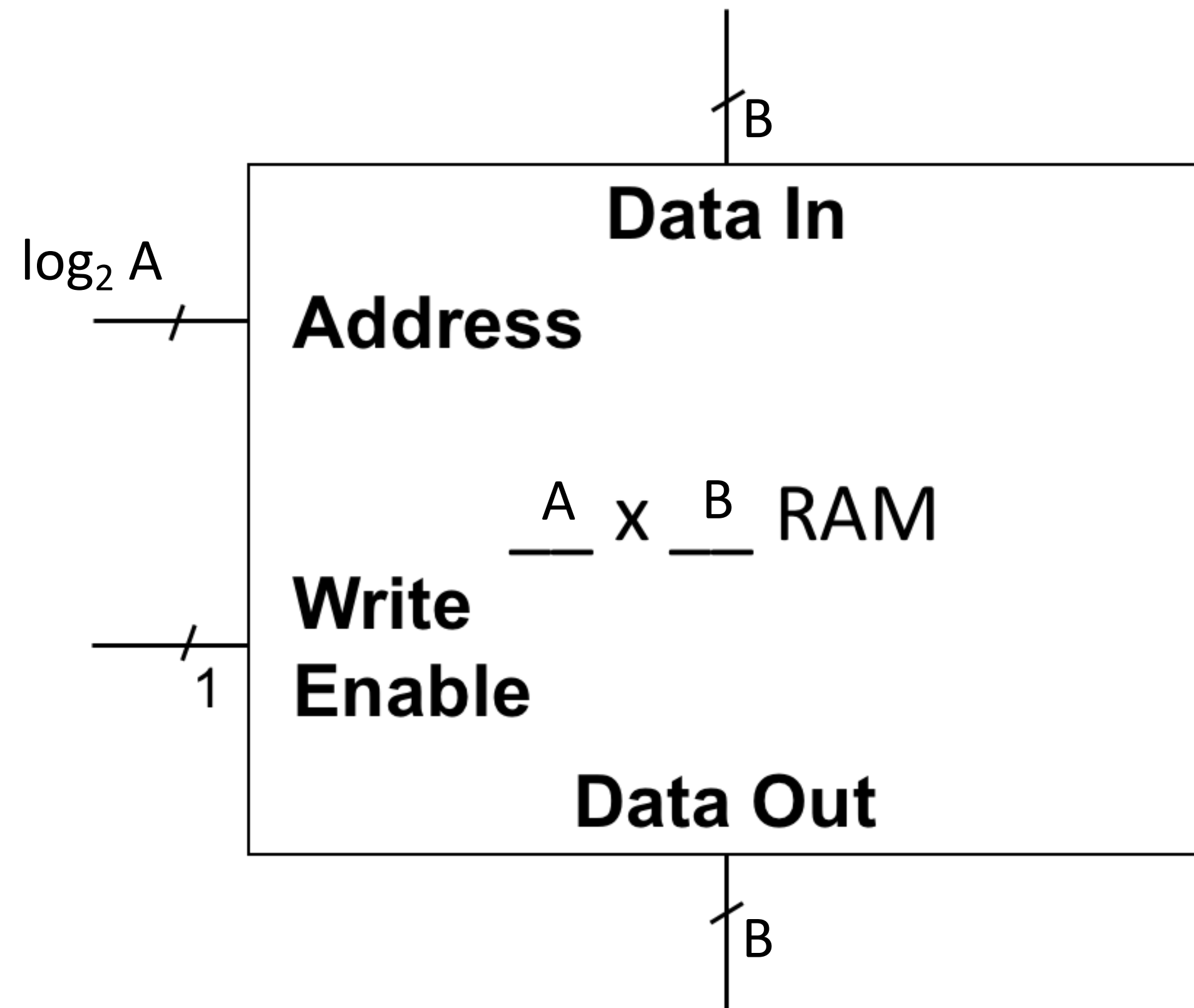

- A is number of words in RAM
- Specify the desired word by an address of size $\log_2 A$
- B is the width of each word (in bits)

16 x 4 RAM

