



# Memory Devices


Small: **Register file** (*group of numbered registers*)

Medium: **SRAM** (*Static Random Access Memory*)


Large: **DRAM** (*Dynamic Random Access Memory*)

Future?

# Processor: Data Path Components

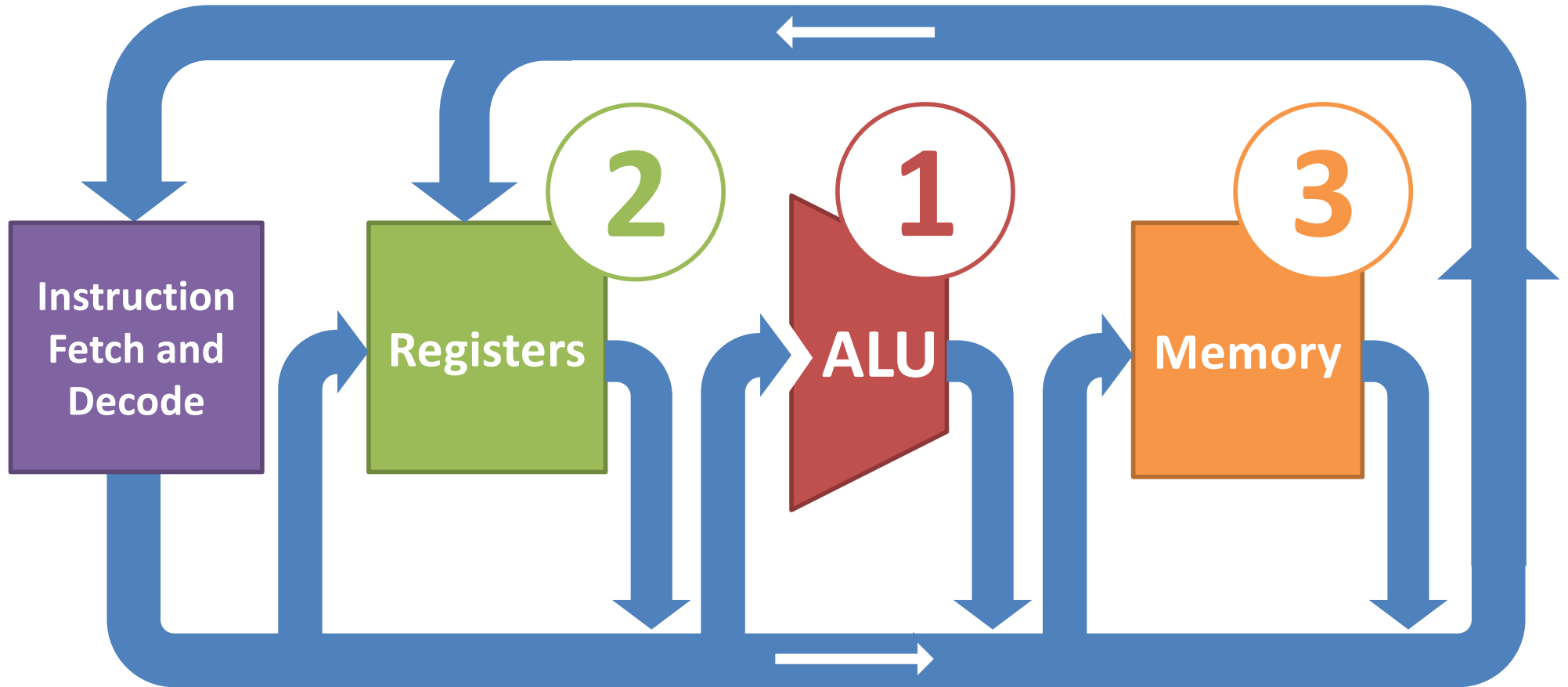

# SRAM: Static Random Access Memory

 


# SRAM read port: data out

Large register files are impractical.

Big MUX = *significant* gate delay.

Large memories use a shared output line.


No central gates/MUX to choose output!

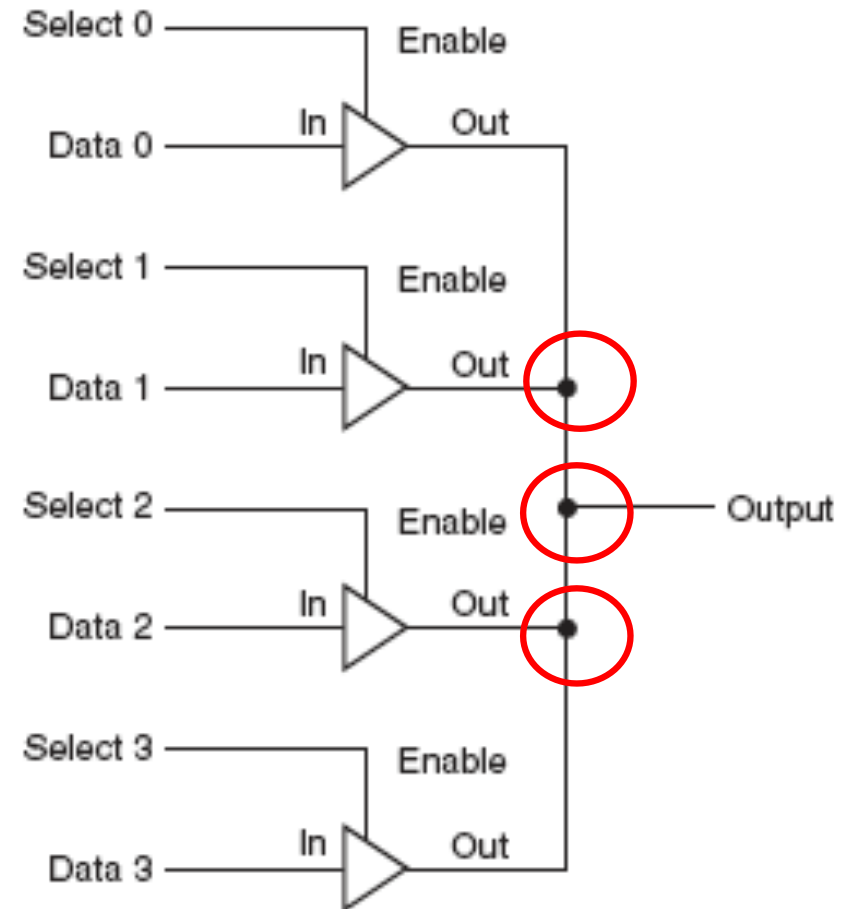

# Wired ORs


(don't try this at home/in the lab, kids)

Data signal 1

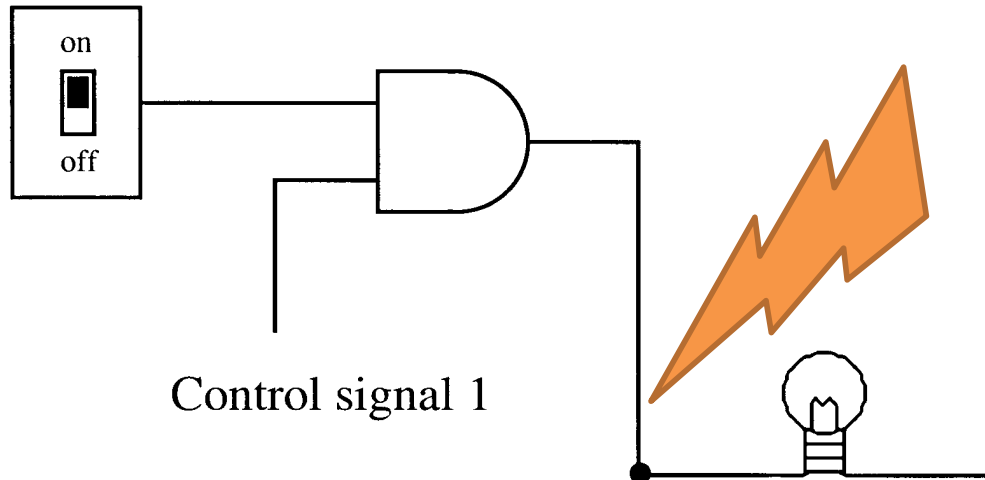

Control signal 1

Data signal 2

 

Control signal 2


Data signal out

[Danger, Will Robinson!](#)



# (noninverting) tristate buffers


Data signal 1

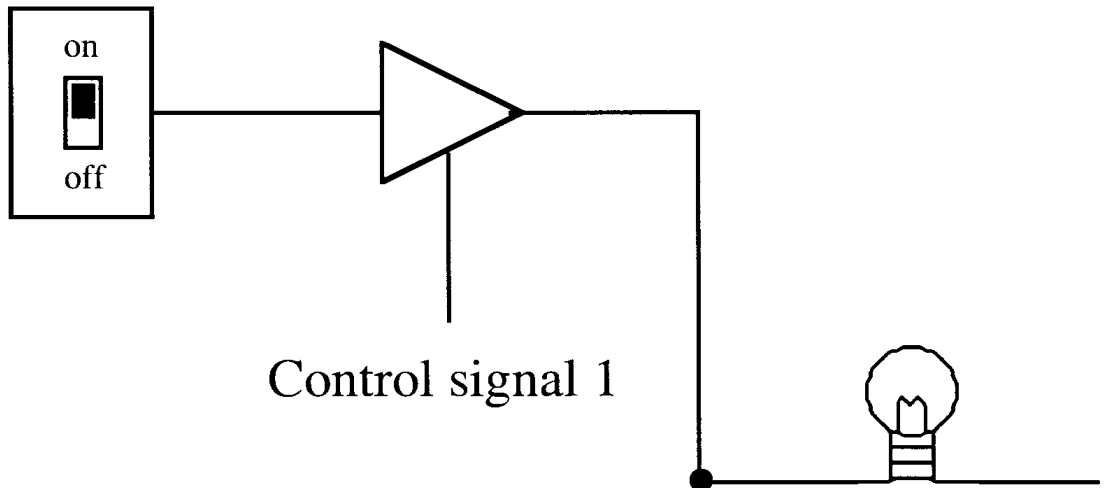


Control signal 1

Data signal out

Data signal 2

 


Control signal 2

 


In	Control	Out
0	0	Z
1	0	Z
0	1	0
1	1	1

(active high)

 


# SRAM cell

one option

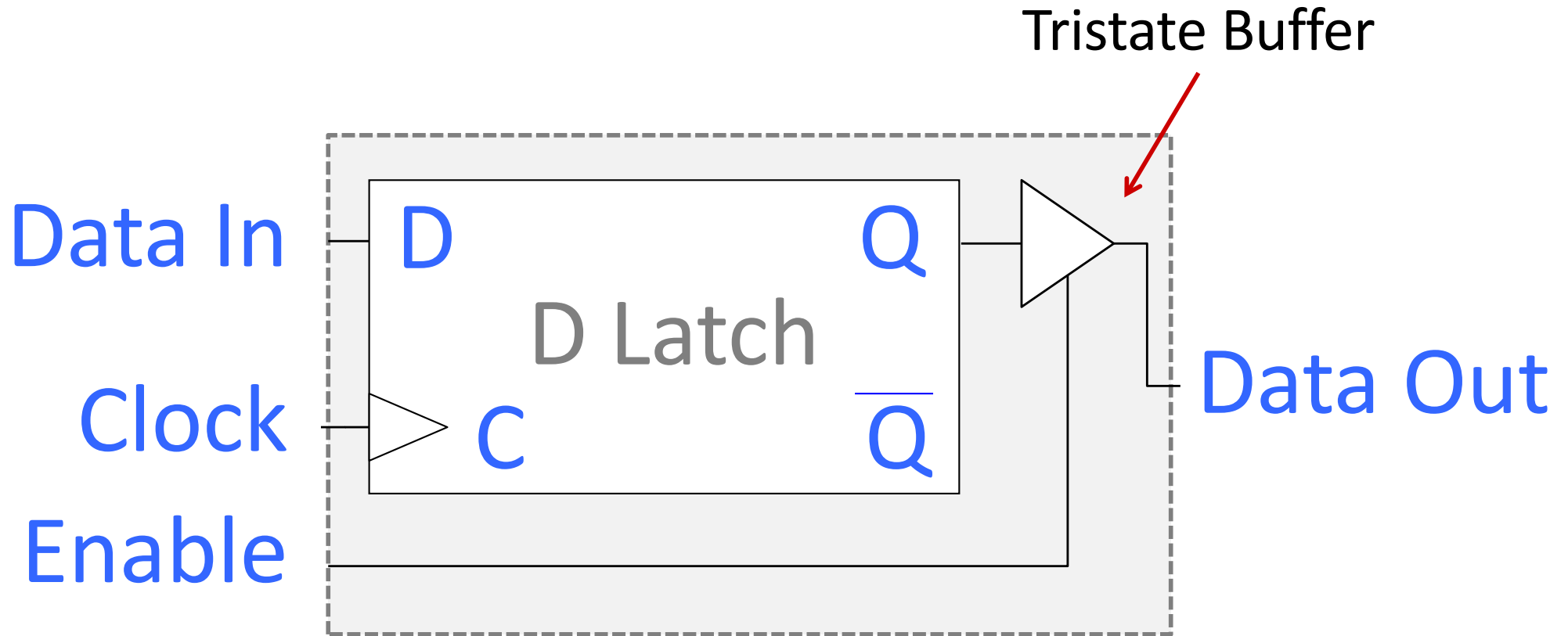

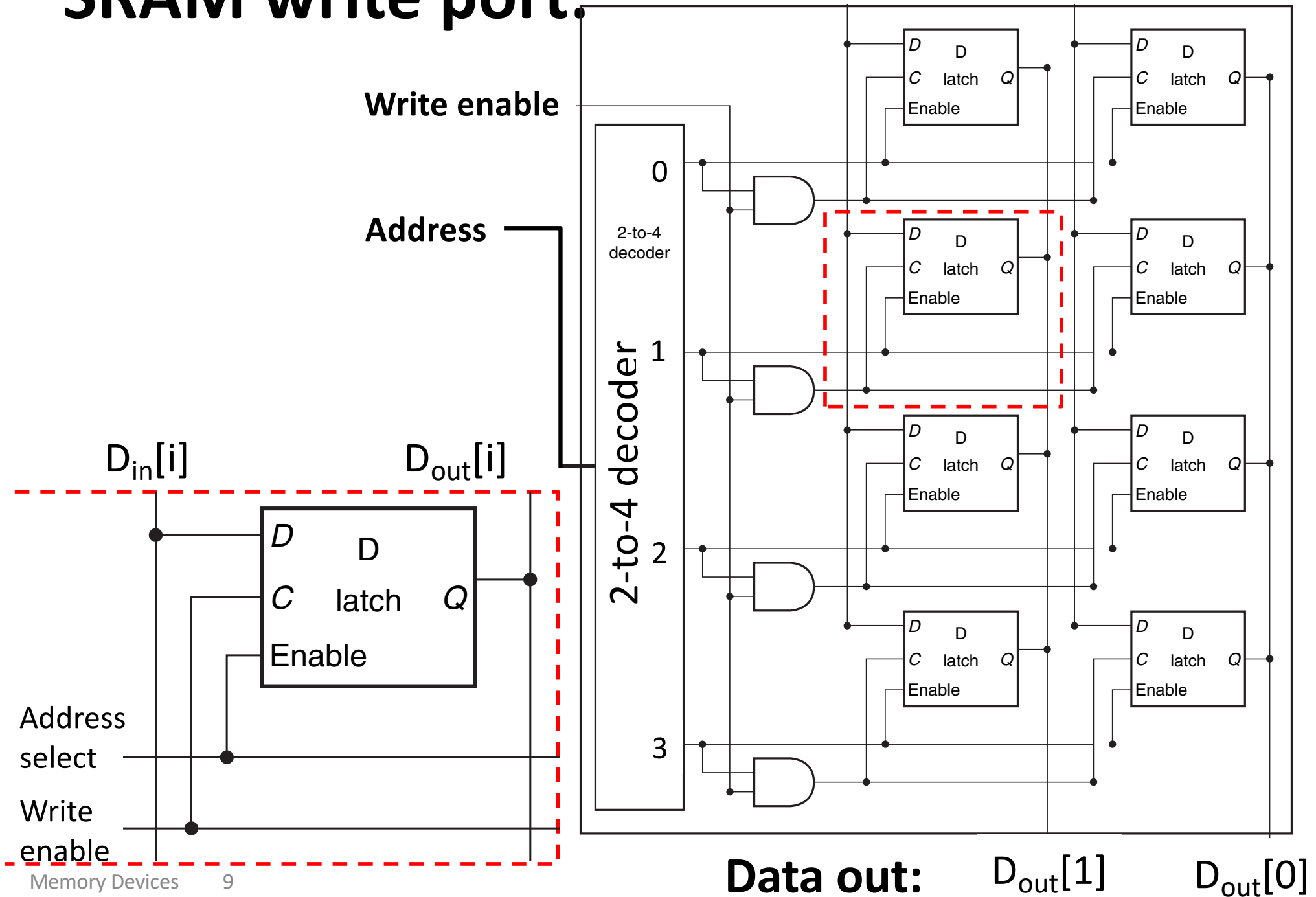
# SRAM write port: Data in: $D_{in}[1]$ $D_{in}[0]$






# Organization of a 16 x 4 SRAM

(one option)

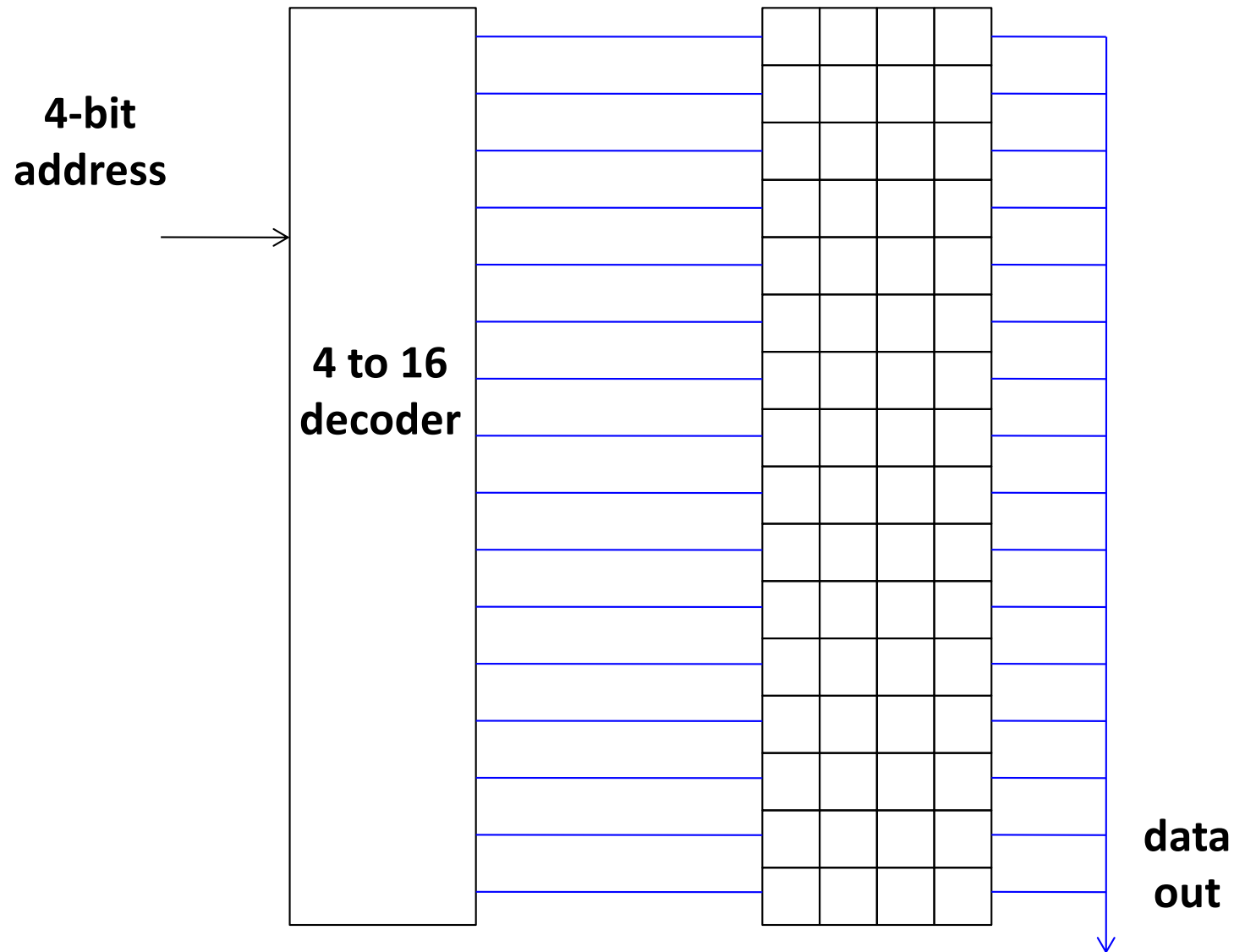


# Selecting location 1101

 
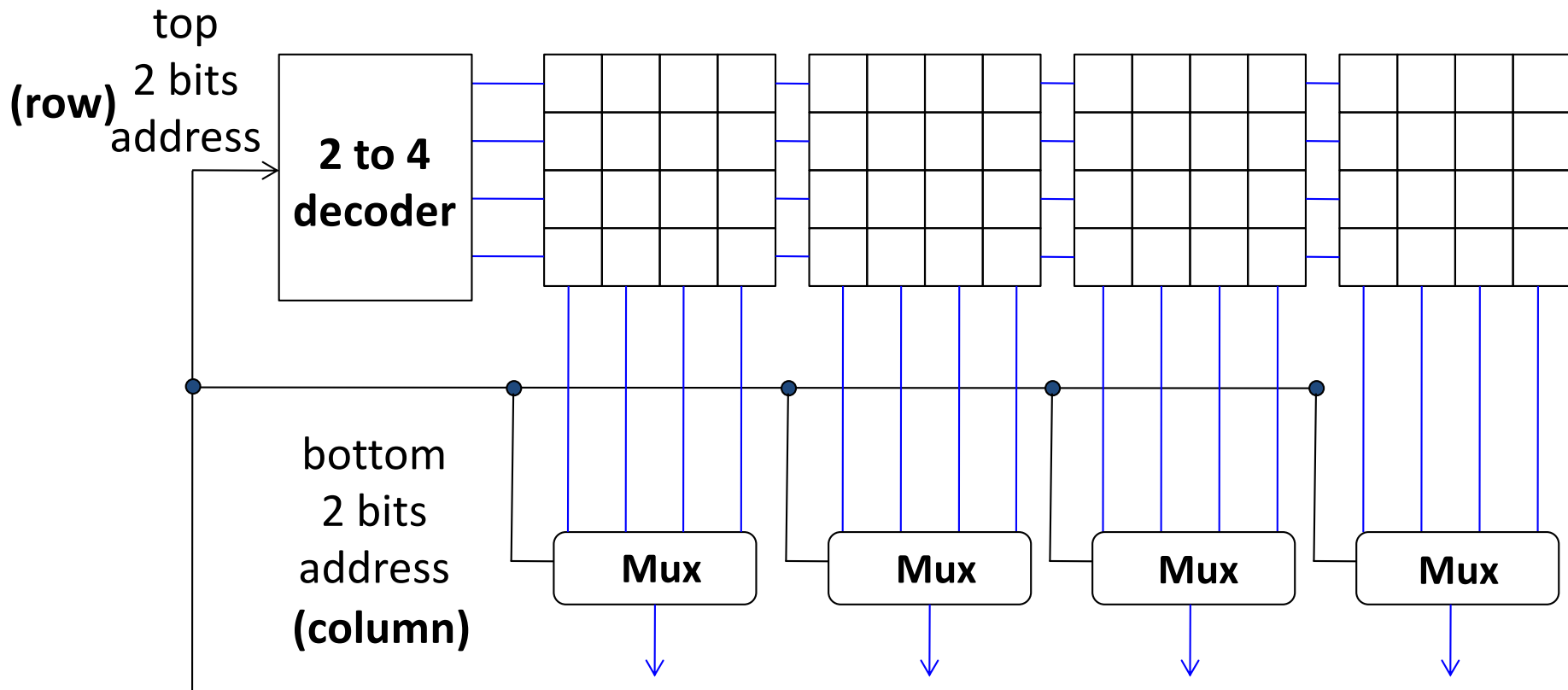
# Another organization of a 16 x 4 SRAM


Split-level row/column addressing = physical multidimensional array!



Notice the smaller decoder... how does this affect timing?

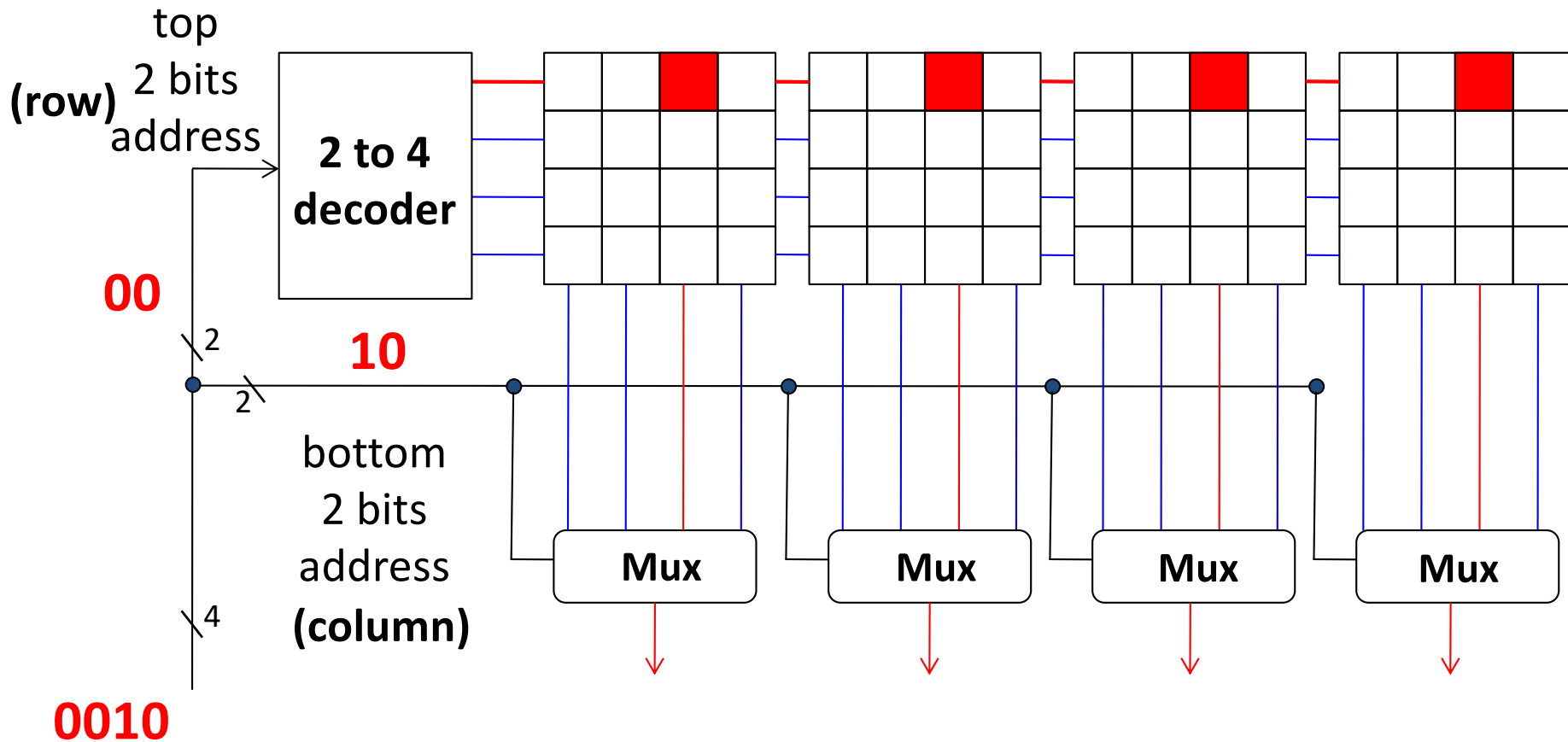
# Selecting location 0010

Nibbles "striped" across 4 smaller memories.



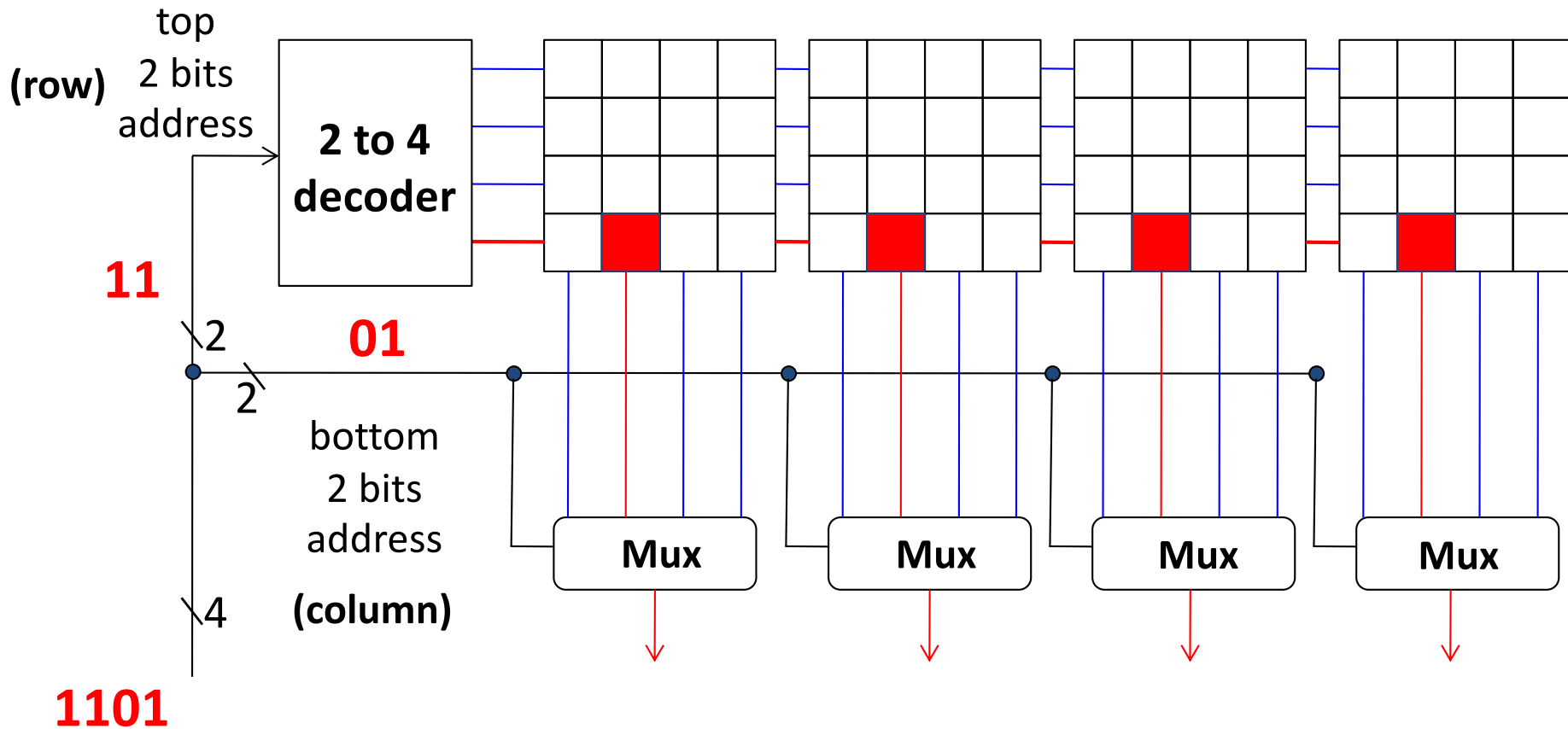
# Selecting location 1101

Nibbles "striped" across 4 smaller memories.




# What value does location 1010 hold?

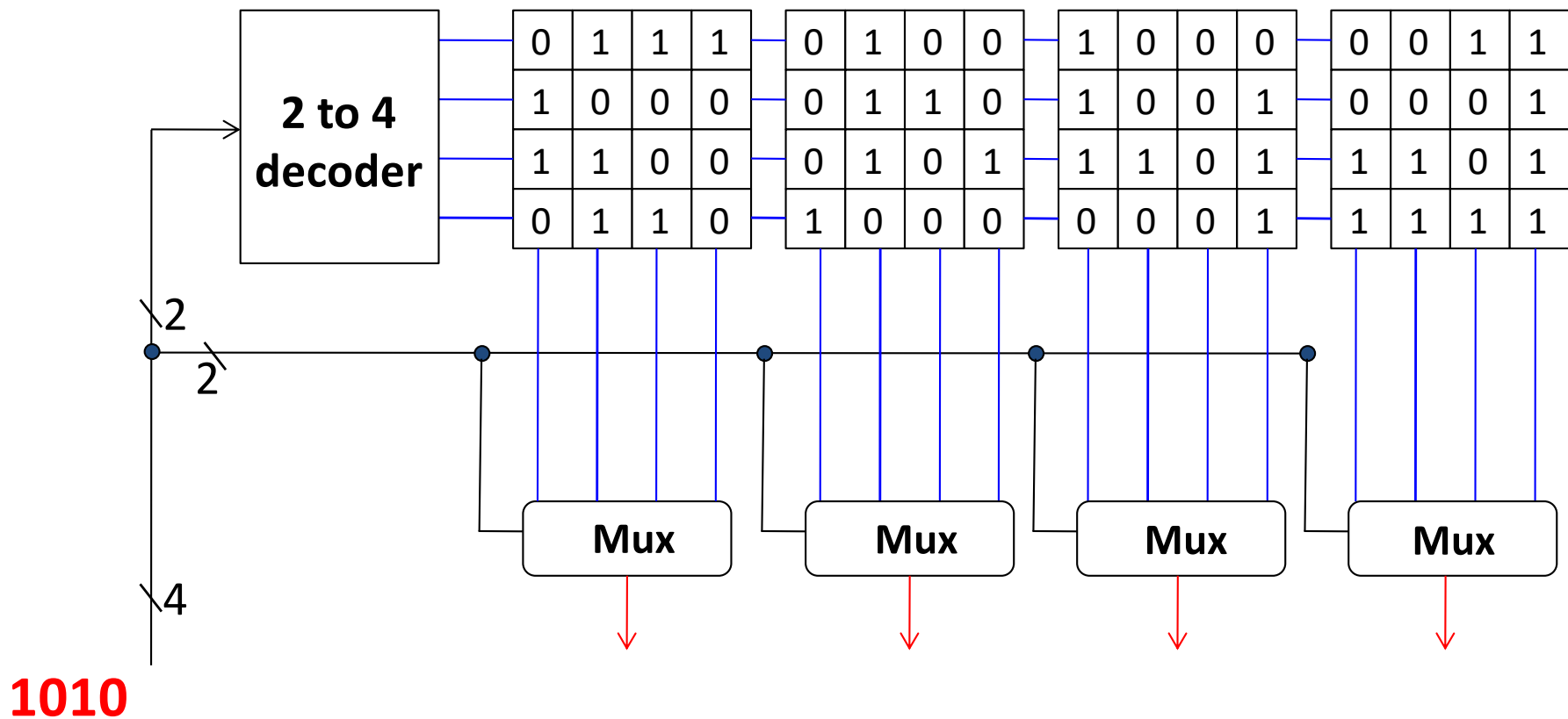

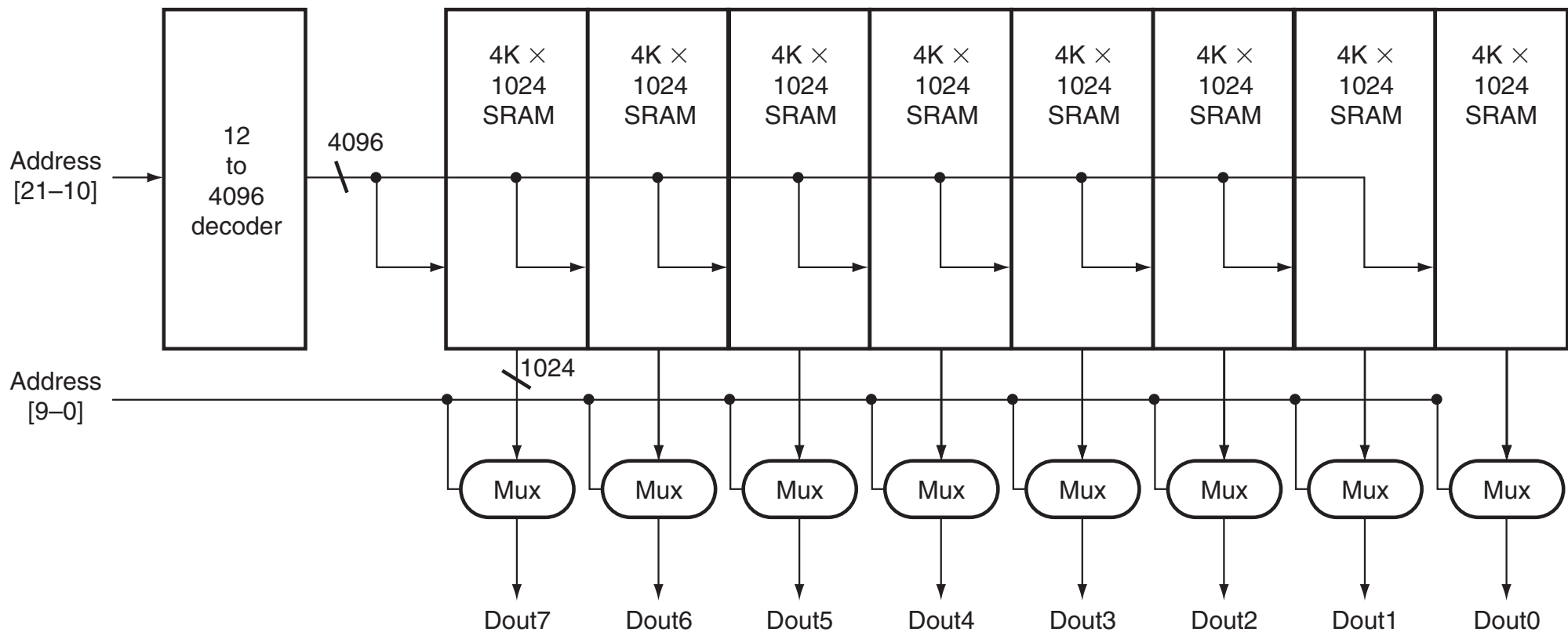
# Organization of a 4M x 8 SRAM

(one option)

= 4 MB memory, size of a large cache for modern laptop



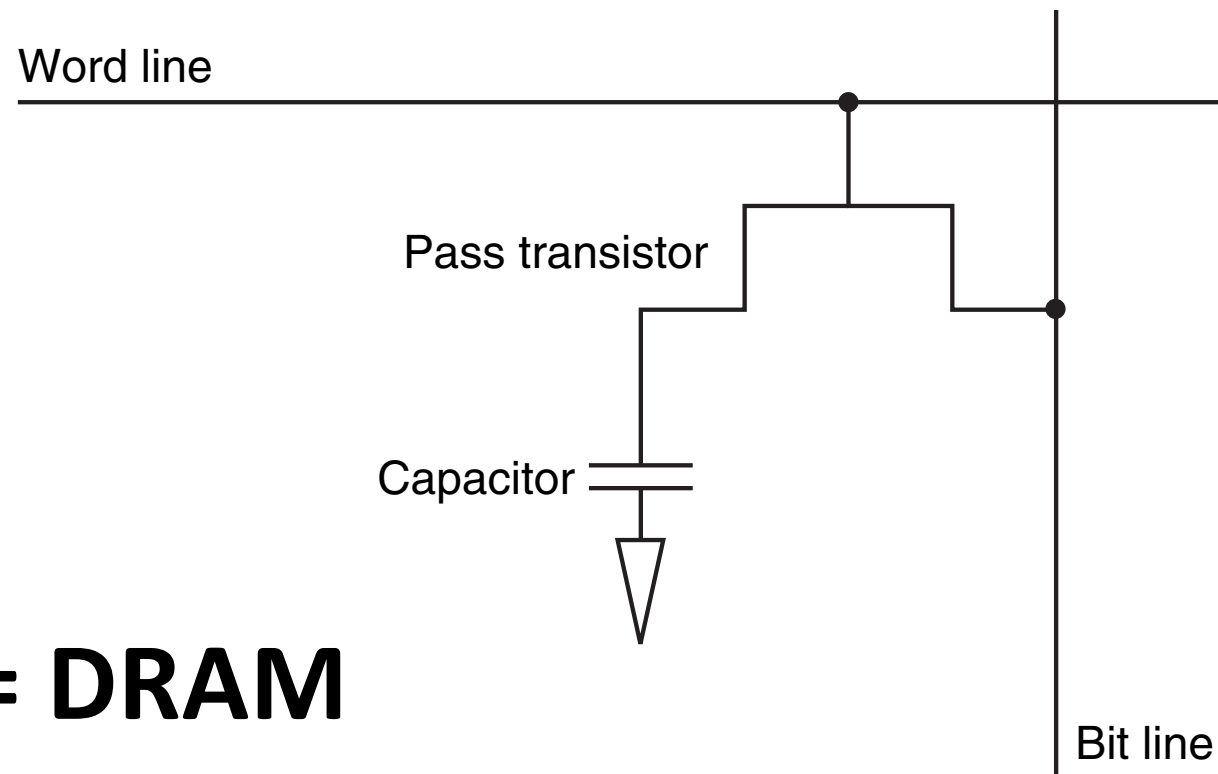In practice, single set of data lines often time-shared for read (out)/write (in).



## Dynamic RAM = DRAM

DRAM stores bit as charge on capacitor:


- 1 transistor accesses stored charge.
- requires periodic refresh = read-write (dynamic power)

SRAM stores bit on pair of inverting gates:

- several transistors
- requires continuous (static) power.




# 64-bit DRAM

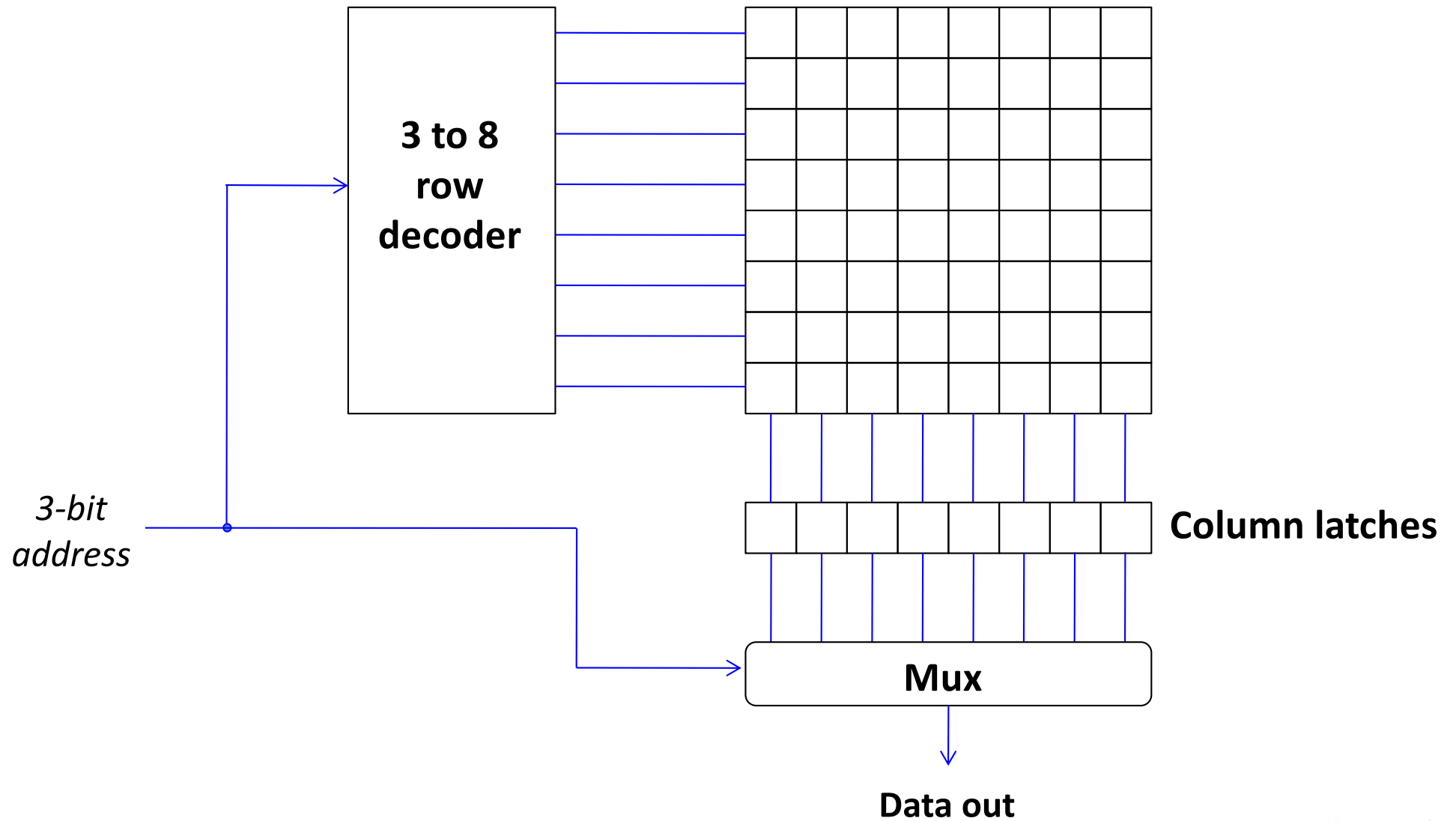


# Reading bit at address 101011

## 1. Select row

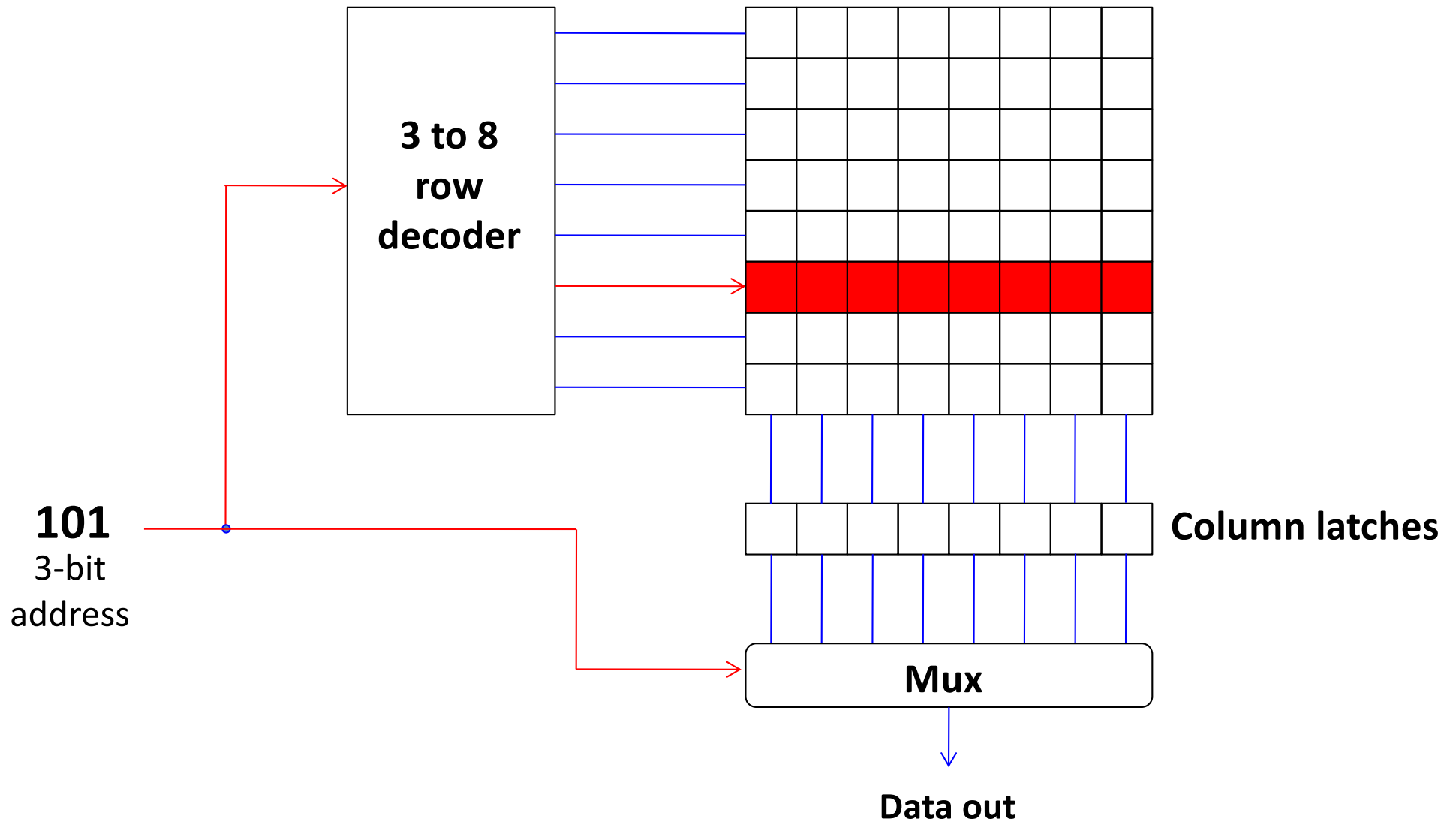


# Reading bit at address 101011

## 2. Copy row to latches

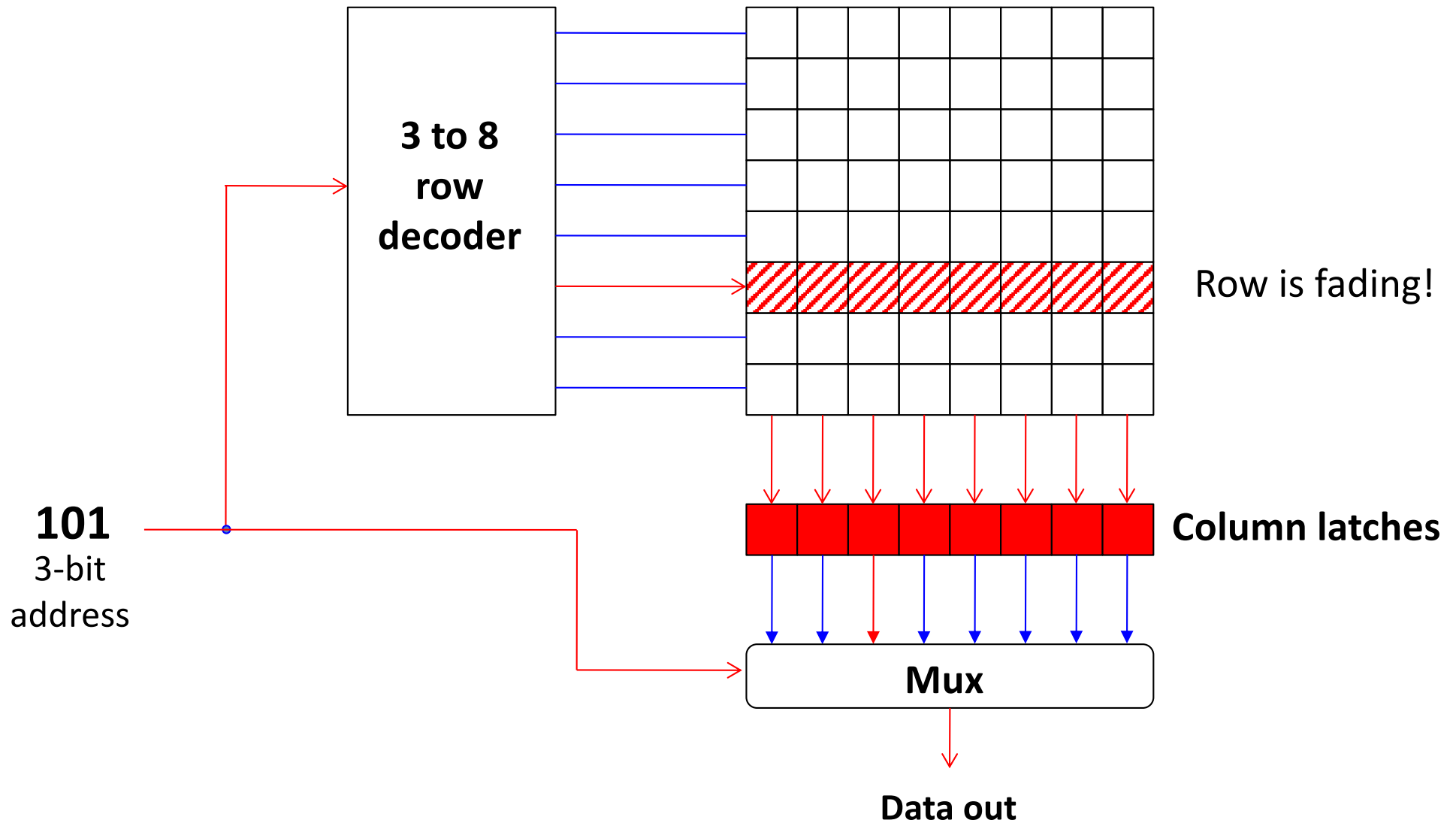

# Reading bit at address 101011

## 3. Refresh row from latches

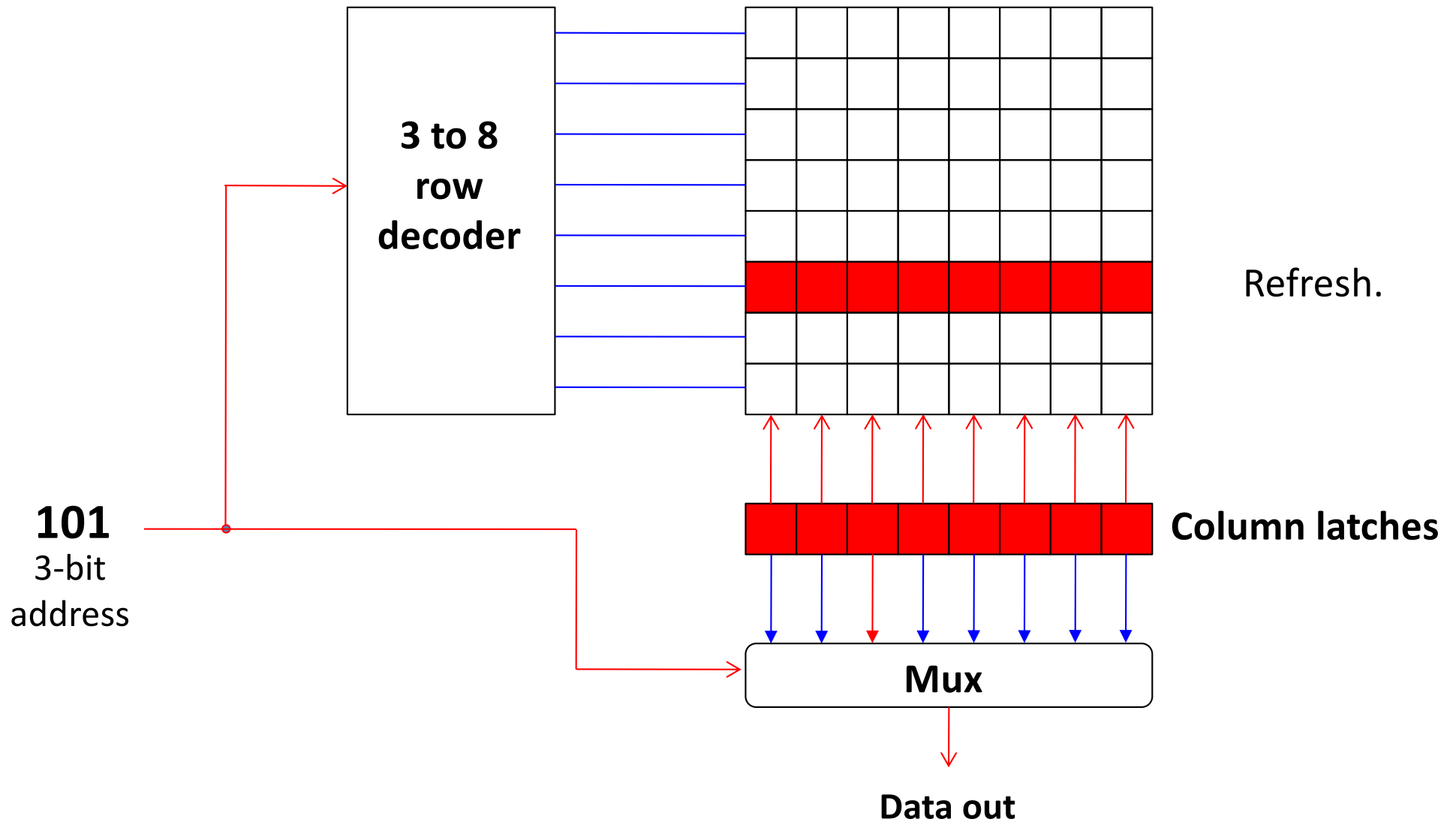

# Reading bit at address 101011

## 4. Select column from latches

