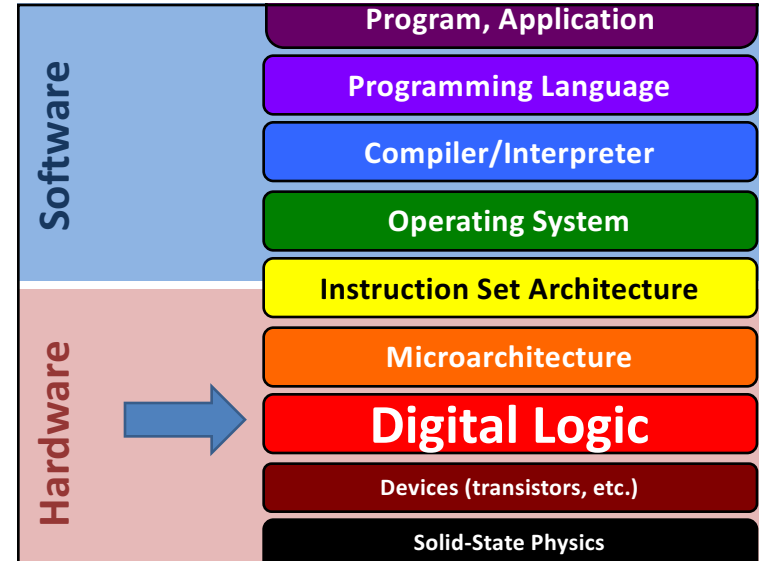


Digital Logic

Gateway to computer science



Digital data/computation = Boolean

Boolean value (*bit*): 0 or 1

Boolean functions (AND, OR, NOT, ...)

Electronically:

bit = high voltage vs. low voltage

Boolean functions = logic gates, built from transistors

Abstraction!

Transistors (more in lab)

If Base voltage is high:
Current may flow freely from *Collector* to *Emitter*.

If Base voltage is low:
Current may not flow from *Collector* to *Emitter*.

Truth table					
V_{in}	V_{out}	in	out	in	out
low	high	0	1	F	T
high	low	1	0	T	F


NOT gate

Abstraction!


Digital Logic Gates

Abstraction! ex


Tiny electronic devices that compute basic Boolean functions.

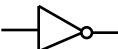NOT 


V _{in}	V _{out}
0	1
1	0

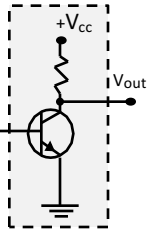



V ₂	
0	1
V ₁	0
1	1

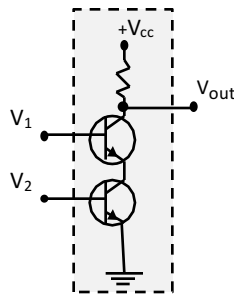


Integrated Circuits (1950s -)

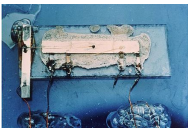Early (first?) transistor 

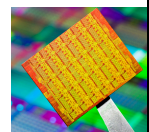Chip 

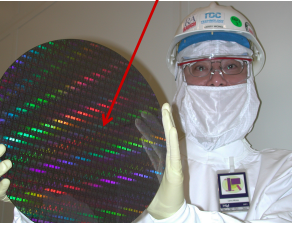
Wafer 

Small integrated circuit

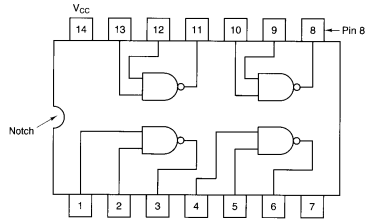


Five basic gates: define with truth tables


ex

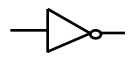


NOT	
0	1
1	0

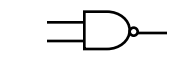


NAND	
0	1
0	1
1	1
1	0

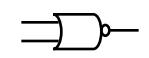

NOR	
0	1
0	1
1	1
1	0

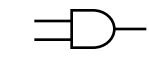

AND	
0	1
0	1
1	1
1	0

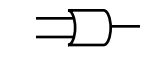


OR	
0	1
0	1
1	1
1	0

Boolean Algebra


for combinational logic

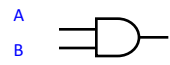inputs = variables
wires = expressions
gates = operators/functions
circuits = functions




AND = Boolean product

.	0	1
0	0	0
1	0	1

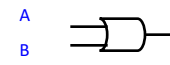


OR = Boolean sum

+	0	1
0	0	1
1	1	1

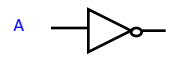

NOT = inverse or complement

	0	1
1	1	0

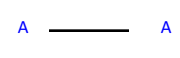

wire = identity

	0	1
1	0	1

ex

Circuits

Connect inputs and outputs of gates with wires.
Crossed wires touch **only if** there is a dot.

What is the output if A=1, B=0, C=1?
What is the truth table of this circuit?
What is an equivalent Boolean expression?

ex

Translation

Connect gates to implement these functions. Check with truth tables.
Use a direct translation -- it is straightforward and bidirectional.

$F = (A\bar{B} + C)D$

$Z = \bar{W} + (X + \bar{W}Y)$

Note on notation: bubble = inverse/complement

Identity law, inverse law

Commutativity, Associativity

Idempotent law, Null/Zero law

$A + A = A$

$0A = 0$

Note on notation: bubble = inverse/complement

$\overline{A+B} = \overline{A} \overline{B}$

DeMorgan's Law

(double bubble, toil and trouble, in Randy's words...)

$AB = \overline{\overline{A} \overline{B}}$

$A+B = \overline{\overline{A} \overline{B}}$

One law, Absorption law

Write truth tables. Do they correspond to simpler circuits? ex

$A + 1 = 1$

$A + AB = A$


NAND is universal.

ex

All Boolean functions can be implemented using only NANDs.
Build NOT, AND, OR, NOR, using only NAND gates.

ex

XOR: Exclusive OR

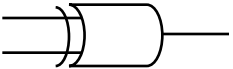


Output = 1 if exactly one input = 1.

Truth table: Build from earlier gates:

Often used as a one-bit comparator.

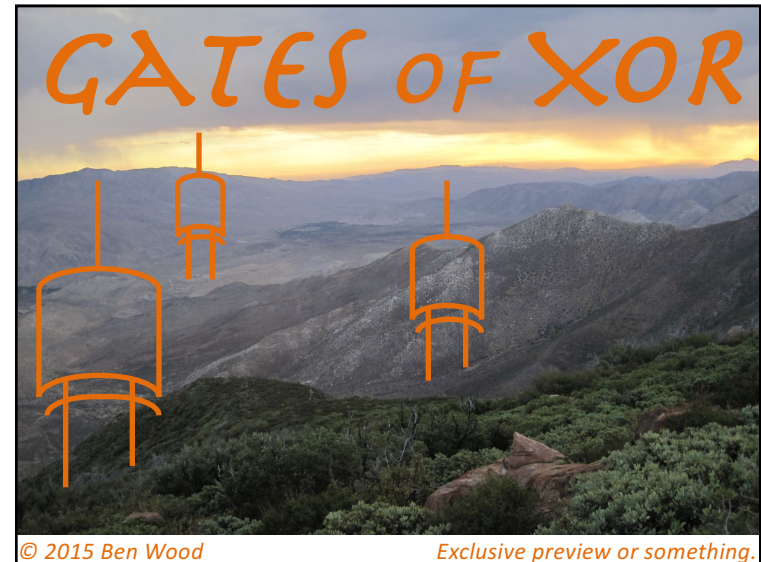
Video game designers, Halloween costumers extraordinaire, sci-fi/fantasy screenwriters, I have an idea...



ex

Larger gates

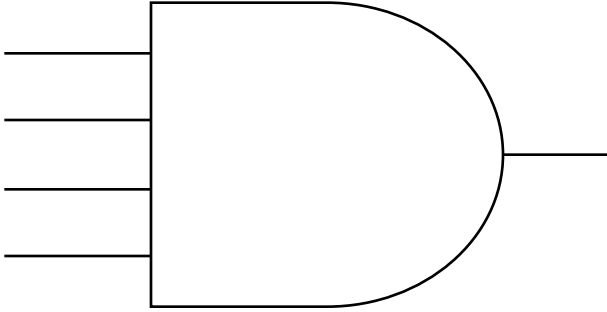
Build a 4-input AND gate using any number of 2-input gates.



Why simplify? **ex**

Circuit simplification

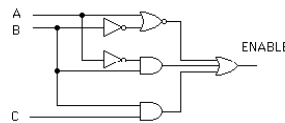Is there a simpler circuit that performs the same function?



Start with an equivalent Boolean expression, then simplify with algebra.


$F(A, B, C) =$

Check the answer with a truth table.

Circuit derivation: *code detectors*

ex

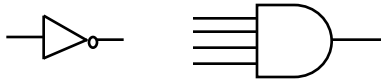AND gate + NOT gates = code detector, recognizes exactly one input code.



Design a 4-input code detector to output 1 if ABCD = 1001, and 0 otherwise.



Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others. (accept = 1, reject = 0)

Circuit derivation: *sum-of-products* form

ex

logical sum (OR)
of products (AND)
of inputs or their complements (NOT)

Draw the truth table and design a sum-of-products circuit for a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others.
How are the truth table and the sum-of-products circuit related?

Voting machines

ex

A **majority circuit** outputs 1 if and only if a majority of its inputs equal 1.
Design a majority circuit for three inputs. **Use a sum of products.**

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Triply redundant computers in spacecraft

- Space program also hastened Integrated Circuits.

Margaret Hamilton *(speaking of space and reliability)*

Led software team for **Apollo 11** Guidance Computer.
Developed software engineering techniques for correctness and reliability.
Coined "software engineering".

Software avoided mission abort on first moon landing!

Apollo 11 code print-out

