

Latch: CC-BY Rberteig@flickr




Latches, Flip-flops, and Registers

Sequential logic: fundamental elements to store values

Output depends on inputs *and stored values*.


(vs. combinational logic: output depends only on inputs)

Processor: Data Path Components

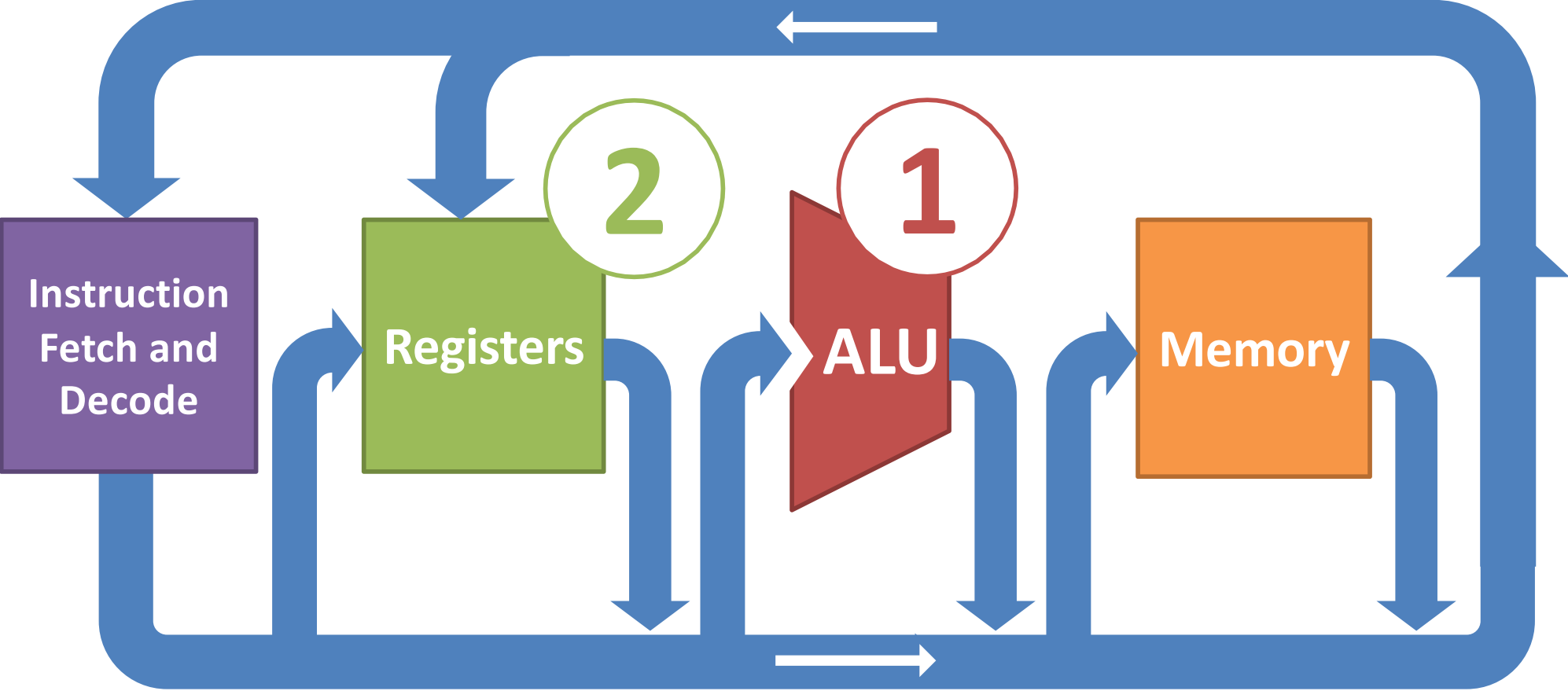


Bistable latches

 Suppose we somehow get a 1 (or a 0?) on here.




=




 


SR latch


S	R	Q	Q'	Q (stable)	Q' (stable)
0	0	0	0	?	?
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
1	0	?	?	1	0
0	1	?	?	0	1

 

SR latch

    

D latch

 

if **C = 0**, then SR latch stores current value of Q.

if **C = 1**, then D flows to Q:

if **D = 0**, then **R = 1** and **S = 0**, **Q = 0**

if **D = 1**, then **R = 0** and **S = 1**, **Q = 1**

Time matters!

D


C

Q

Clocks

Clock: free-running signal
with fixed **cycle** time = **clock period** = T .

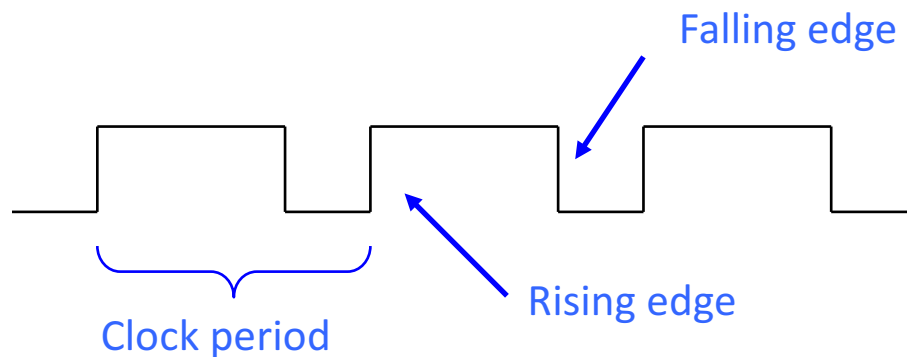Clock frequency = $1 / \text{clock period}$




A clock controls when to update
a sequential logic element's state.




Synchronous systems

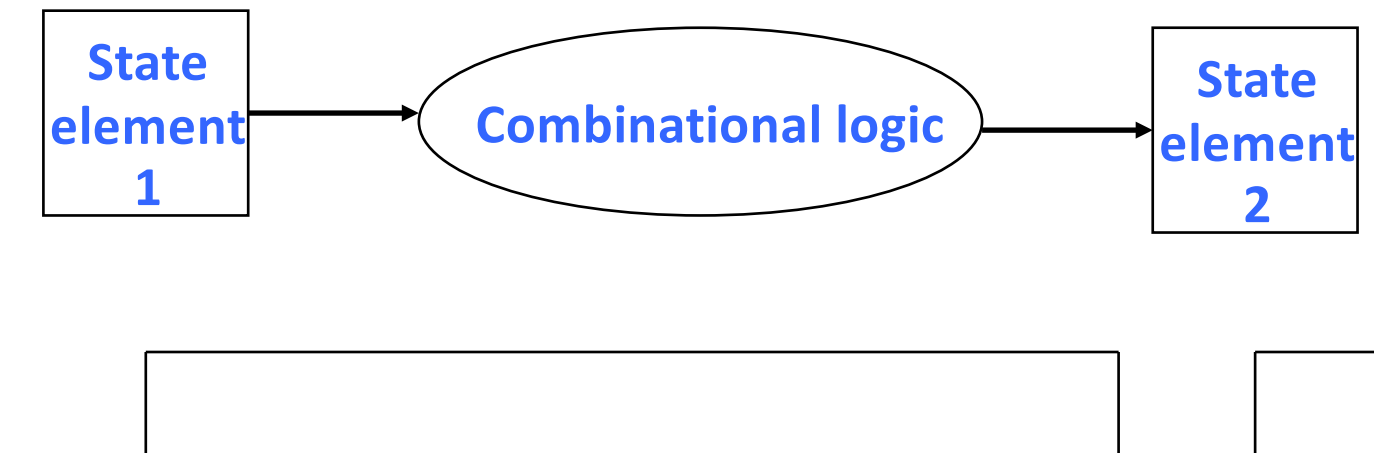Inputs to state elements must be **valid** on active clock edge.



D flip-flop with falling-edge trigger

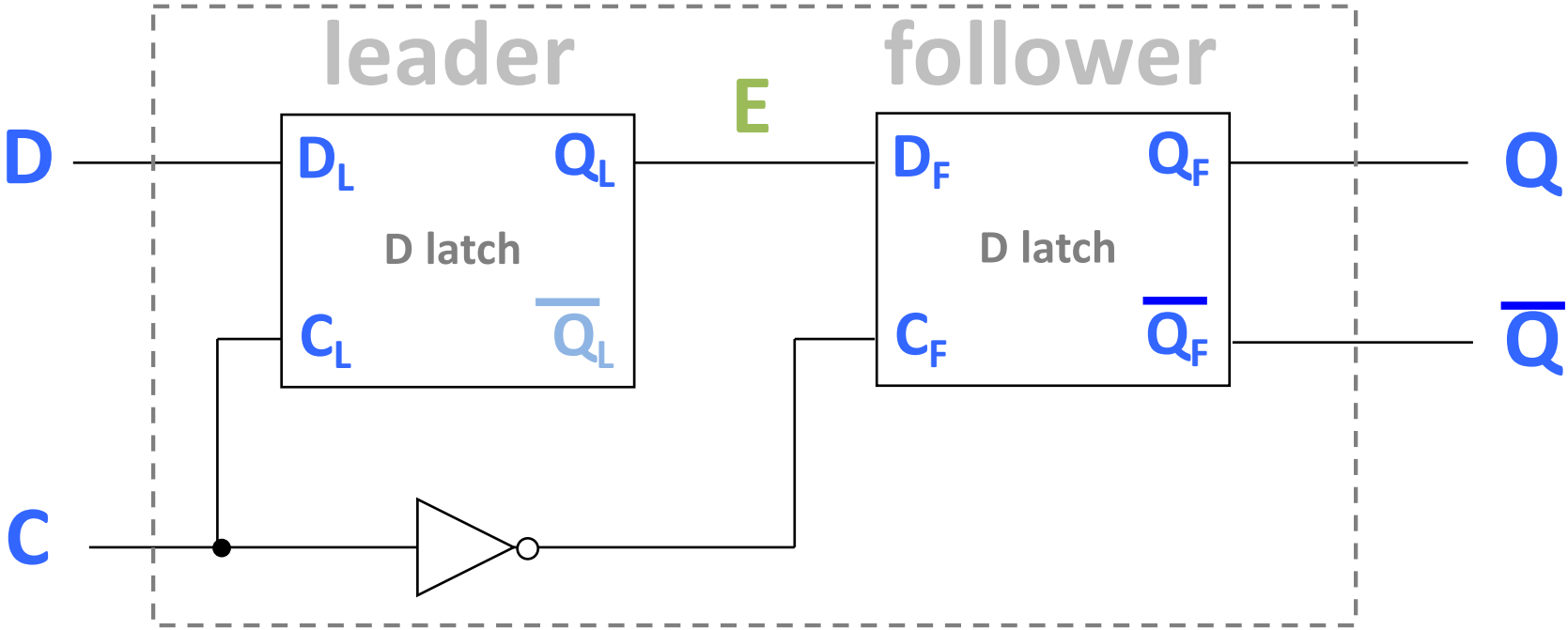

Time matters!


D

C

E


Q

Reading and writing in the same cycle

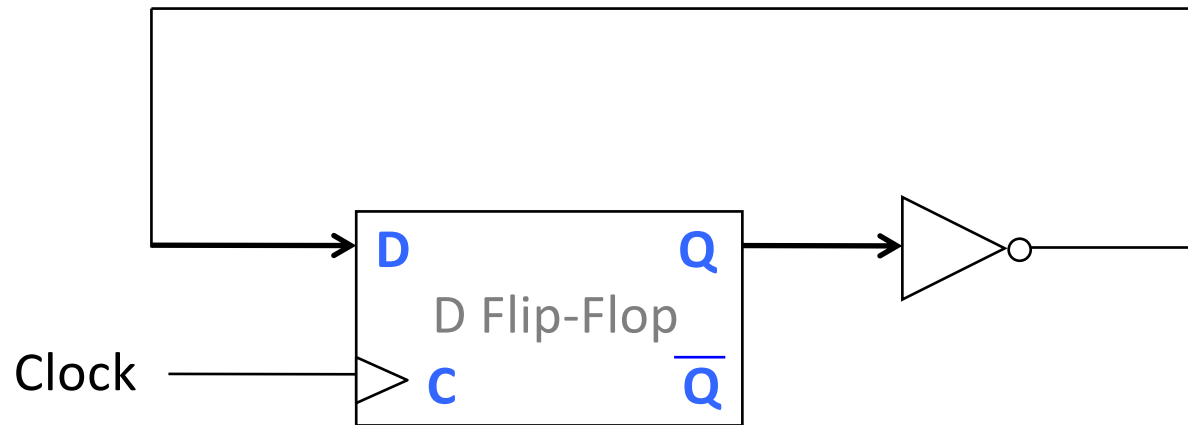


Assume Q is initially 0.

D flip-flop = one bit of storage

 


A 1-nybble* register

(a 4-bit hardware storage cell)

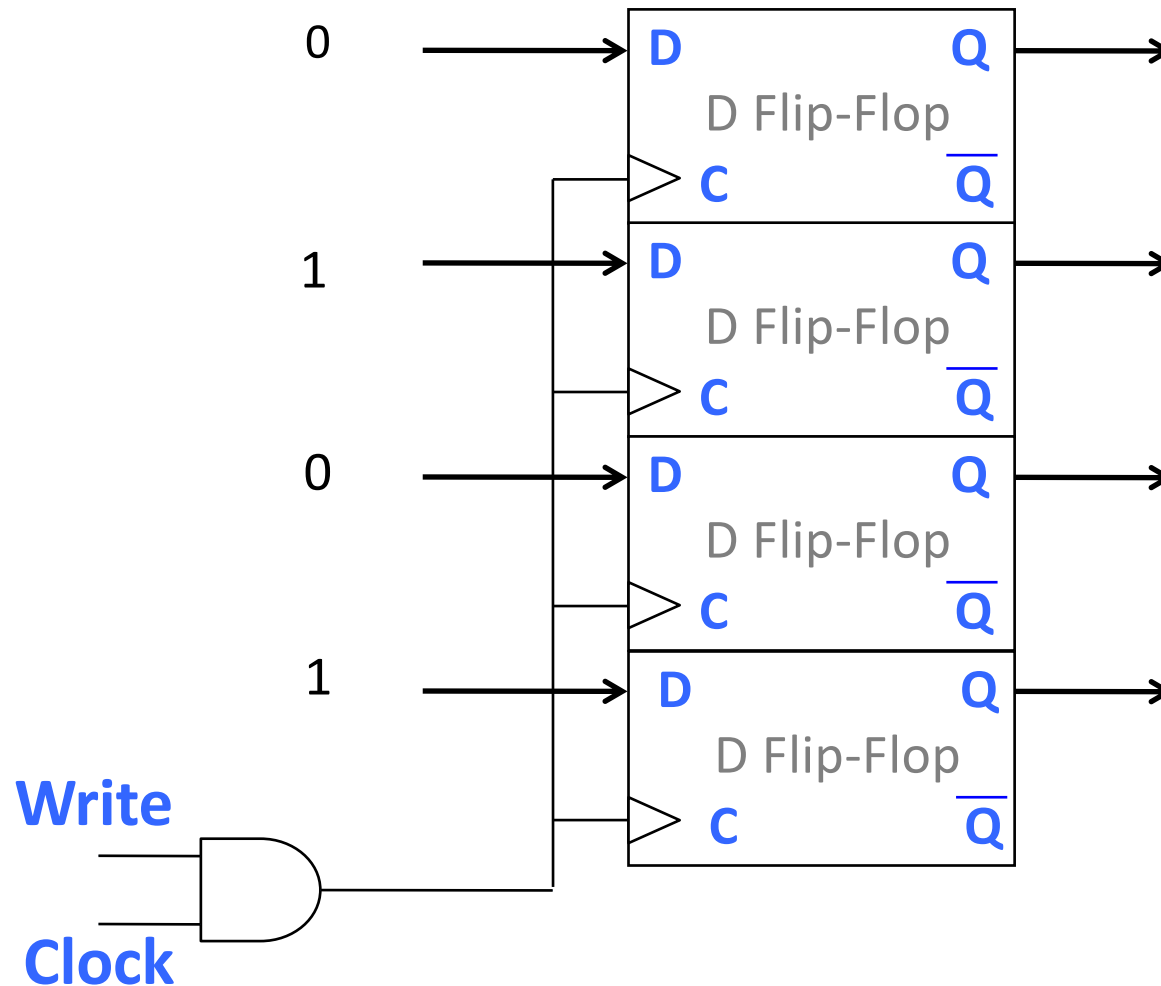

Register file

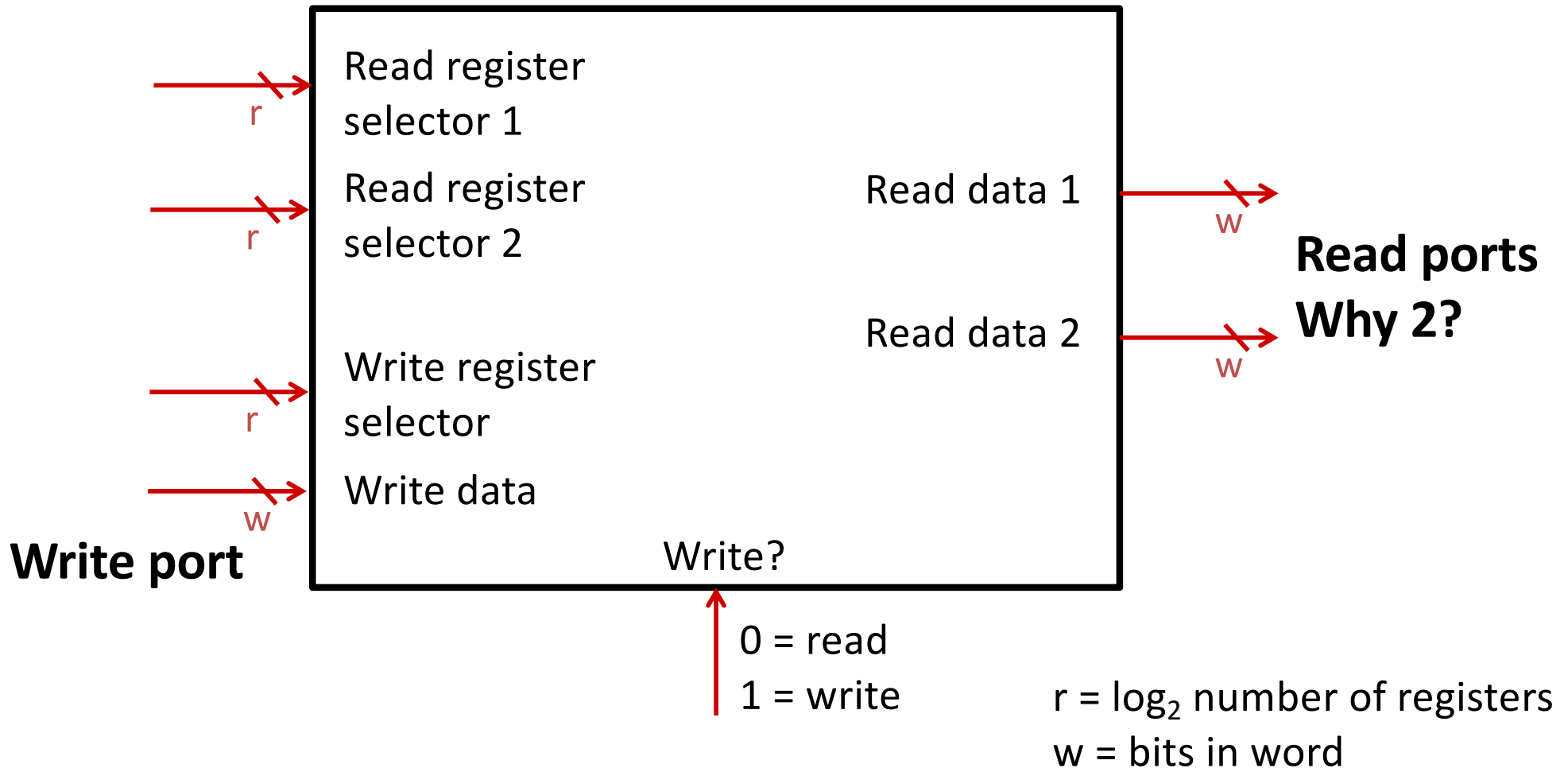

Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.

Read ports (data out)


Read register
number 1




Read register
number 2

Read data 1


Read data 2

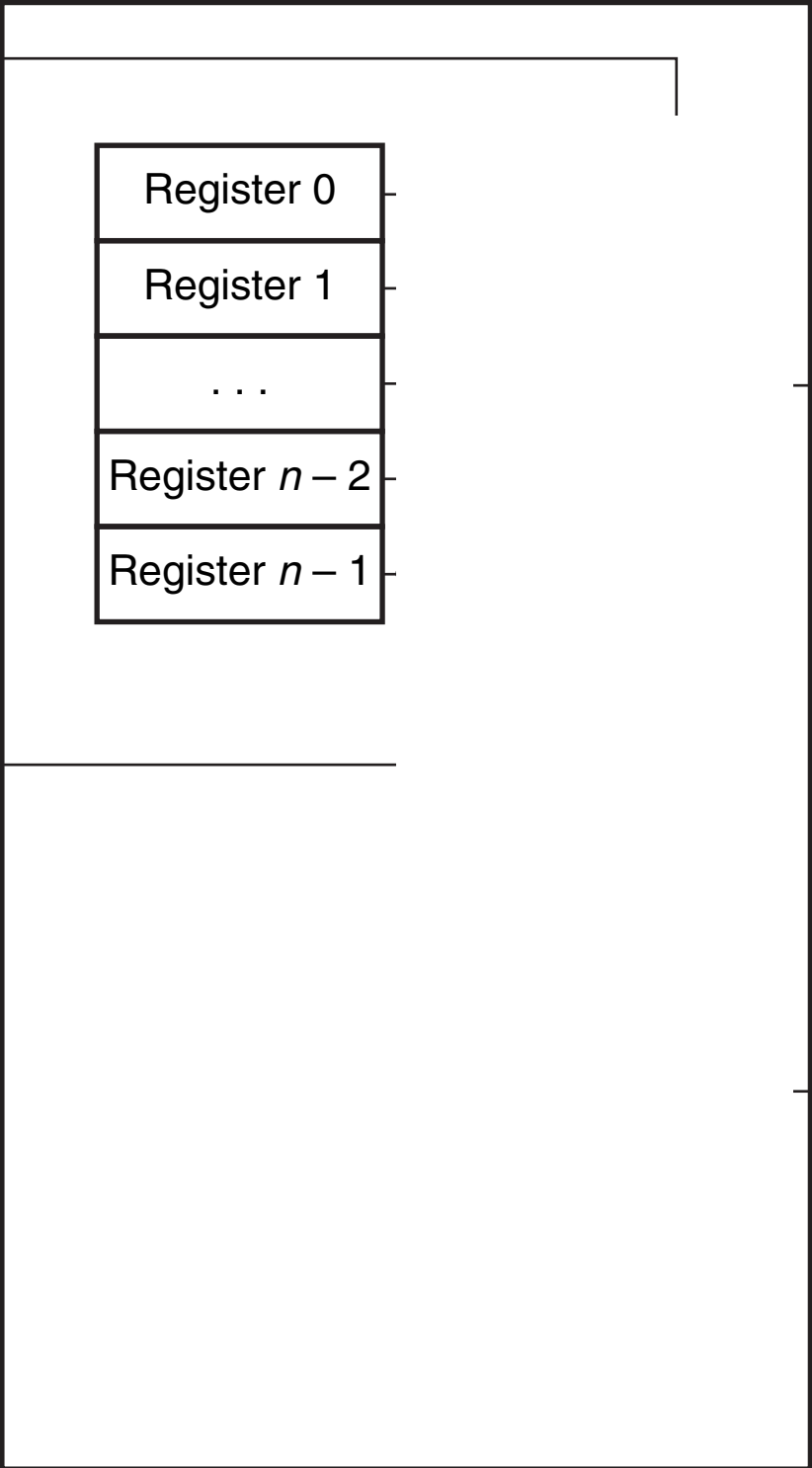

Write port (data in)

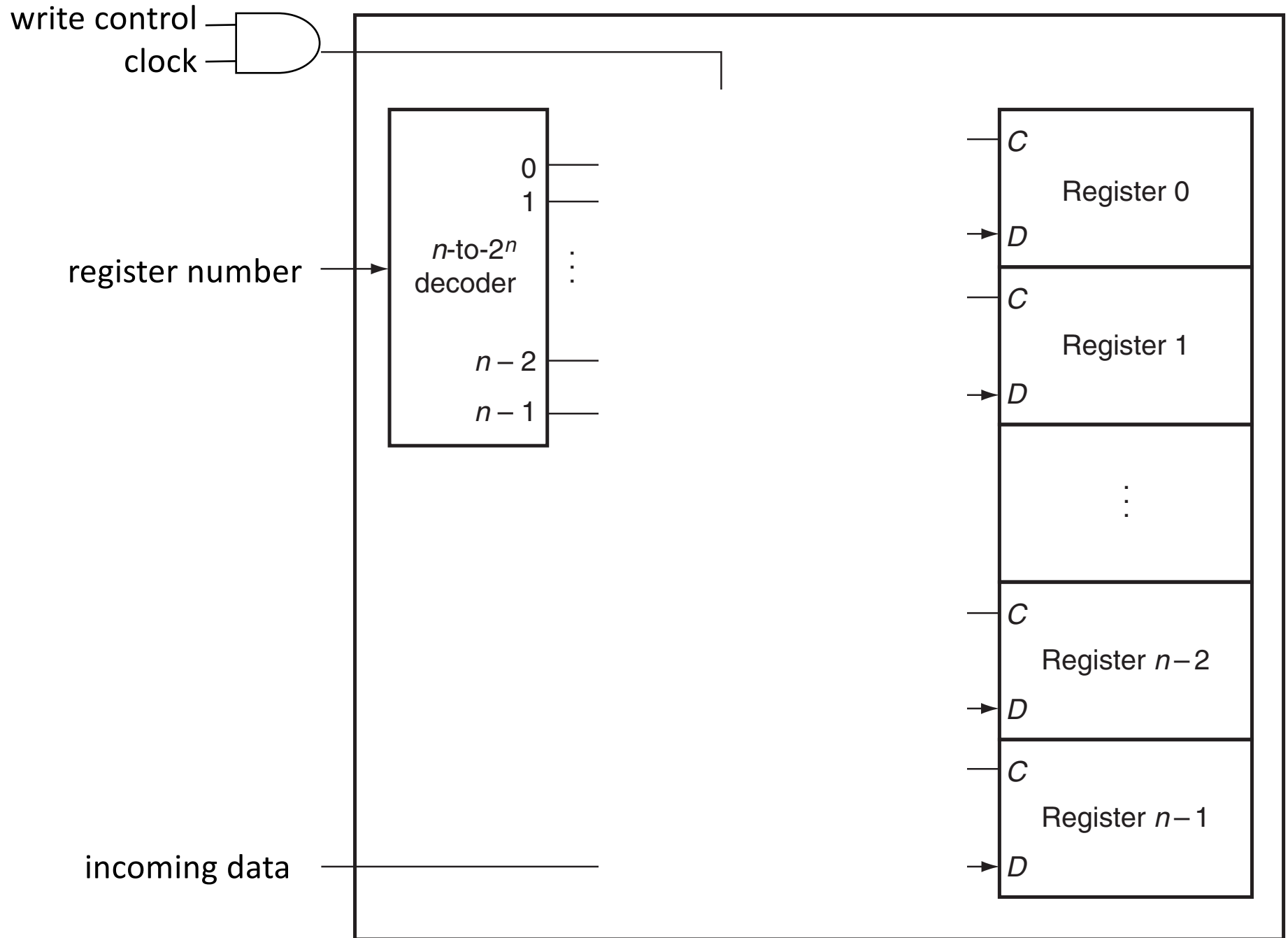

RAM (Random Access Memory)

 

Similar to register file, except...

16 x 4 RAM

