

Laboratory 6

Processor Datapath


Description of HW Instruction Set Architecture

- **16 bit data bus**
- **8 bit address bus**
- Starting address of every program = 0 (PC initialized to 0 by a reset to begin execution)
- PC incremented by 2 to move to the next instruction.
- **16 registers**
 - R0 = 0 (constant)
 - R1 = 1 (constant)
 - R2-R15 general purpose

Instruction Set


Instruction	Meaning	Op 4-bit	Rs 4-bit	Rt 4-bit	Rd 4-bit
LW Rs,Rt,offset	Rt loaded with word from Data Memory at address(Rs + offset)	0000	0-15	0-15	offset
SW Rs,Rt,offset	Data Memory address(Rs + offset) stored with word from Rt	0001	0-15	0-15	offset
ADD Rs,Rt,Rd	$Rd := Rs + Rt$	0010	0-15	0-15	0-15
SUB Rs,Rt,Rd	$Rd := Rs - Rt$	0011	0-15	0-15	0-15
AND Rs,Rt,Rd	$Rd := Rs \text{ AND } Rt$	0100	0-15	0-15	0-15
OR Rs,Rt,Rd	$Rd := Rs \text{ OR } Rt$	0101	0-15	0-15	0-15
BEQ Rs,Rt,offset	If $Rs=Rt$ then $pc:=pc+2+(offset*2)$ else $pc:=pc+2$	0111	0-15	0-15	offset
JMP offset	Jump to abs. addr = $offset*2$	1000	---12 bit offset-----		

Instruction Fetch

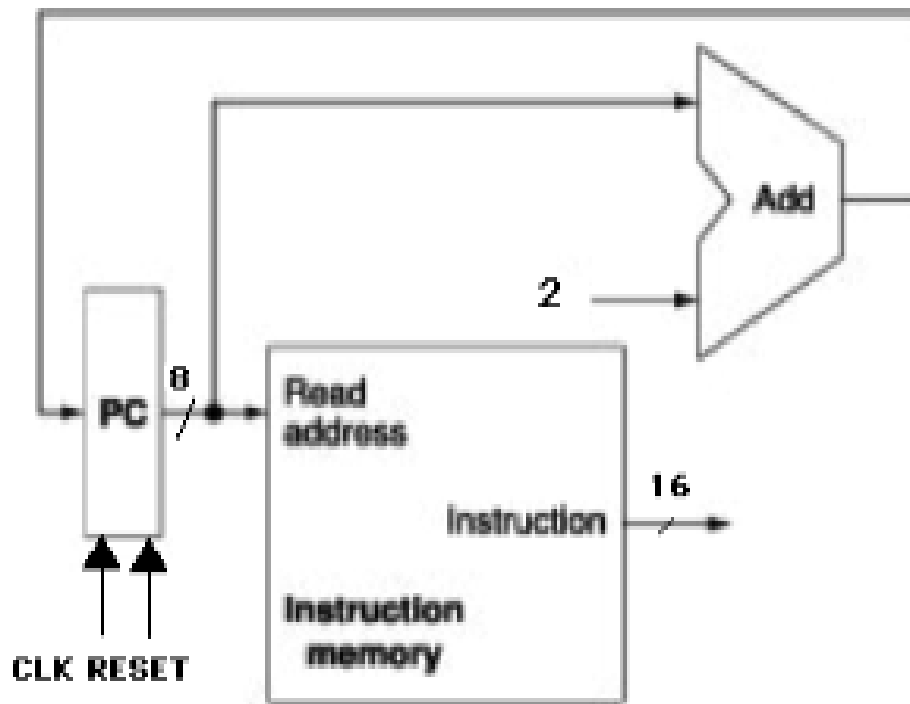

Branch Address

 Either $PC + 2$ or $PC + 2 + (2 * \text{offset})$ is the next value of the PC.




On a BEQ instruction, **BEQ Rs,Rt,offset**

- The **offset** = number of instructions away from the next value of the PC to branch to, so must be multiplied by 2.
- Since **offset** is 4 bits, it must be sign-extended to 8 bits to be added to the PC.

A **2x8 multiplexer** circuit to select the next value of the PC. The value of the **Branch** and **Zero** bits are used to determine which is used:

- The **Branch** control line = 1 if a BEQ instruction is being executed.
- The **Zero** bit from the ALU is used to check whether $R_s = R_t$: it is 1 if $R_s - R_t = 0$ (meaning they're equal). If **Branch** = 1 and **Zero** = 1, then the next value of the PC will be the branch address ; otherwise, it will simply be $PC + 2$:

Register File and ALU

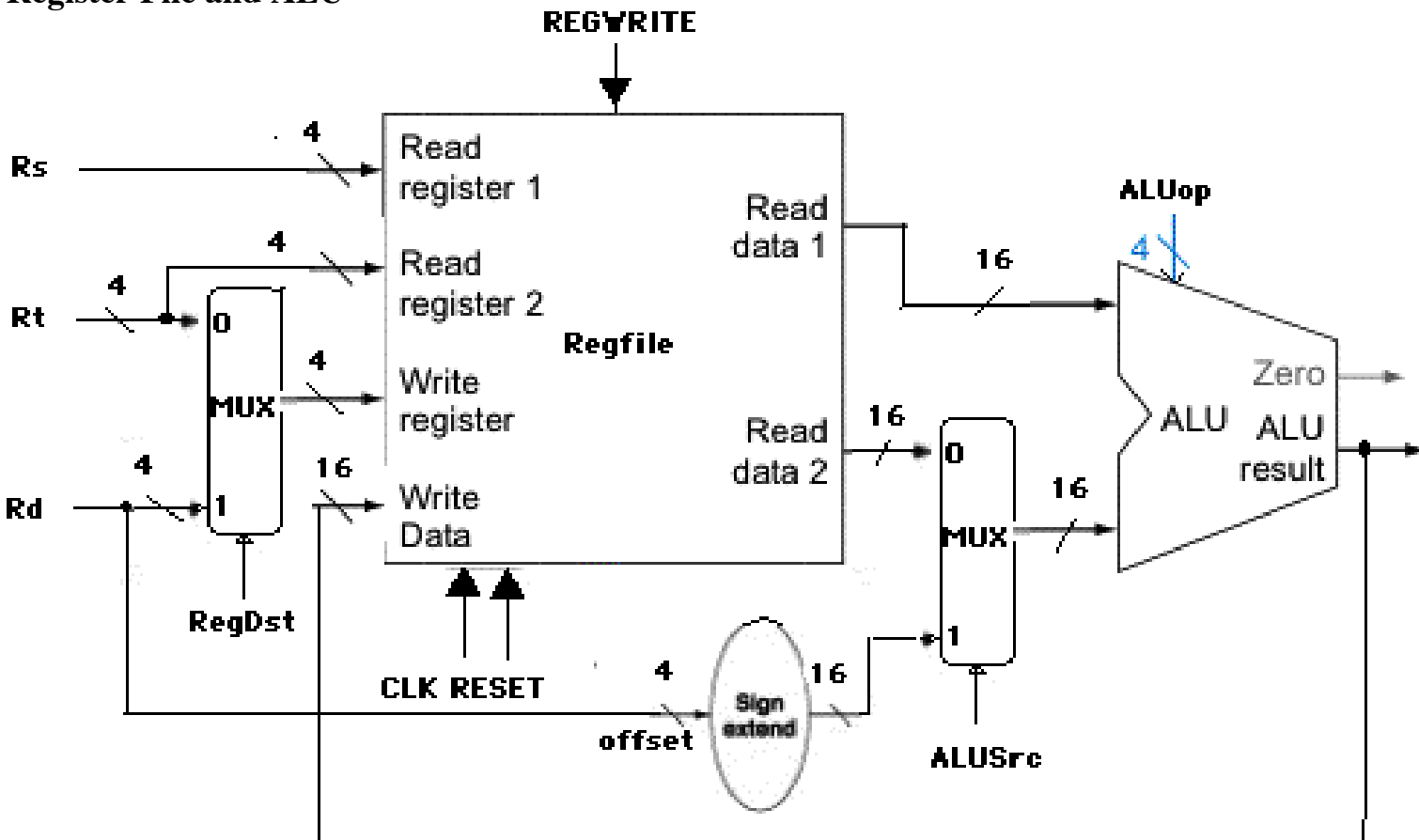

R-type instructions ADD, SUB, AND, OR, SLT (opcode Rs Rt Rd)

- read Rs and Rt from register file
- perform an ALU operation on the contents of the registers
- write the result to register Rd in register file

Memory Access instructions LW, SW (opcode Rs Rt offset)

- memory address = $Rs + \text{sign-extended 4-bit offset}$
- if **SW**, the value to be stored to memory is from Rt.
- if **LW**, Rt is loaded with the value read from memory


Register written to (**Write Register**) is Rd **or** Rt if a **LW** instruction (chosen by a 2x4 MUX which is controlled by **RegDst**)

ALU calculates $Rs + Rt$, **or** $Rs + \text{sign-extended offset}$.

- Input A of the ALU is always Rs
- Input B of the ALU is Rt **or** the offset (chosen by a 2x16 multiplexer, which is controlled by **ALUSrc**):

Data Memory

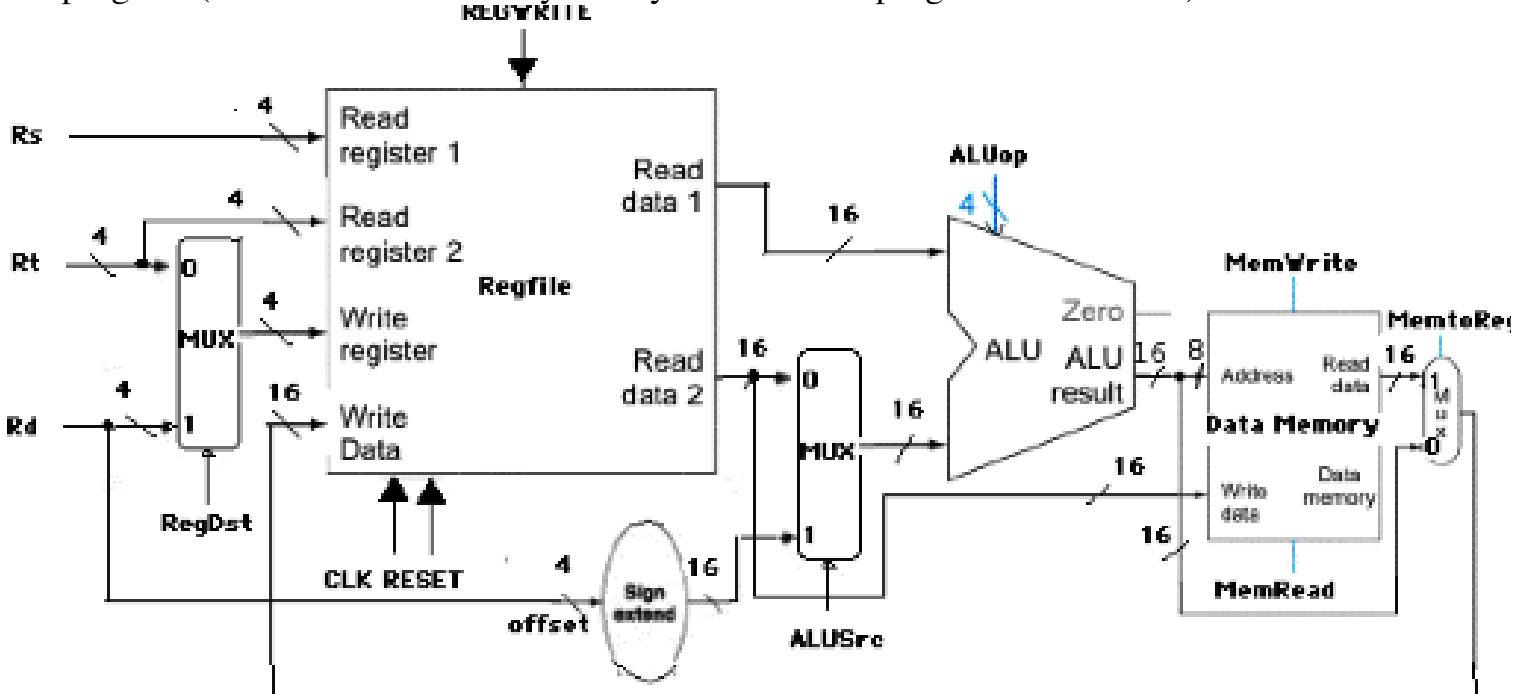We need an additional memory for values loaded or stored (**LW** or **SW**) during execution of the program (the instruction memory is only used to store program instructions).



RegDst (chooses whether Rd or Rt goes to the **Write data** input on the Regfile)

If 0, destination is Rd. If 1, destination is Rt.

RegWr (control line to RegFile)

If 1, writes the value on the **Write data** input to the register specified by **Write register**

ALUSrc (chooses the source of the second ALU operand)

If 0, the operand is the second register file output.

If 1, the operand is the sign-extended, lowest 4 bits of the instruction.

MemRd (control signal to data memory)

If 0, value stored at address in data memory is read from **Read data**.

MemWr (control signal to data memory)

If 0, data memory address written with value from **Rt** on the **Write data** input.

MemtoReg (chooses the value to be written back to the Regfile)

If 0, the value comes from the ALU (**R-type instruction**)

If 1, the value comes from data memory (**LW**)

ALUop(4 bits)	ALU function
0	a AND b
1	a OR b
2	a + b (add)
6	a - b
7	set on less than

ALU can perform 5 possible operations:

<u>ALUop</u>	<u>ALU function</u>
0	a AND b
1	a OR b
2	a + b (add)
6	a - b
7	set on less than

Need an ALU Control Unit to select the proper operation for each instruction:

Instruction	Opcode	ALU operation	ALUop
LW	0	add	2
SW	1	add	2
ADD	2	add	2
SUB	3	sub	6
AND	4	and	0
OR	5	or	1
SLT	6	slt	7
BEQ	7	sub	6
JMP	8	don't care	don't care

Op3	Op2	Op1	Op0	ALUop3	ALUop2	ALUop1	ALUop0
0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	1	1	1
0	1	1	1	0	1	1	0


Can use a 3x8 decoder to produce the ALUop

Control Unit

Must provide control signals for all other devices in datapath (MUXs, Regfile, Data Memory)

Instruction	Opcode	RegDst	RegWr	ALUSrc	MemRd	MemWr	MemtoReg
LW	0000	1	1	1	0	1	1
SW	0001	1	0	1	1	0	0
ADD	0010	0	1	0	1	1	0
SUB	0011	0	1	0	1	1	0
AND	0100	0	1	0	1	1	0
OR	0101	0	1	0	1	1	0
SLT	0110	0	1	0	1	1	0
BEQ	0111	0	0	0	1	1	0
JMP	1000	0	0	0	1	1	0

Full Implementation

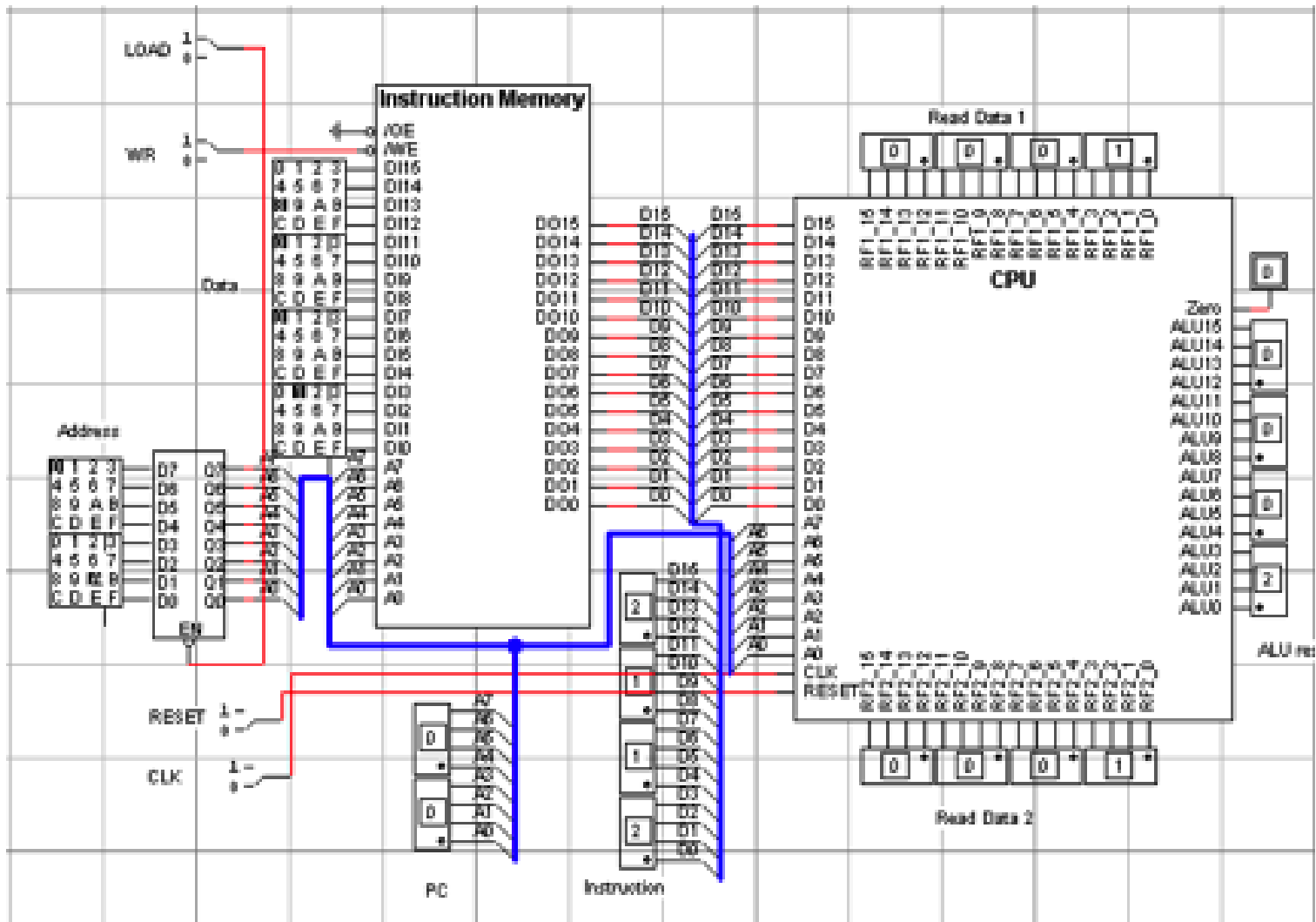

Procedure to Load/Execute a New Program

1. Disconnect the address bus of the Instruction Memory from the CPU
2. Set **LOAD** = 0
3. Set **address** and **data** switches for instruction
4. Set **WR** = 0, then back to 1
5. Repeat steps 3 and 4 until all instructions are loaded to memory
6. Set **LOAD** = 1
7. Reconnect address bus to CPU
8. Set **Reset** = 1, then back to 0
9. Set **CLK** = 1, then back to 0, for each instruction.