

CS 240 Lab 3


Basic Digital Circuits

- **Multiplexer**
- **Decoder**
- **Adder**
- **ALU**

Multiplexer


- n select lines
- 2^n input lines
- 1 output

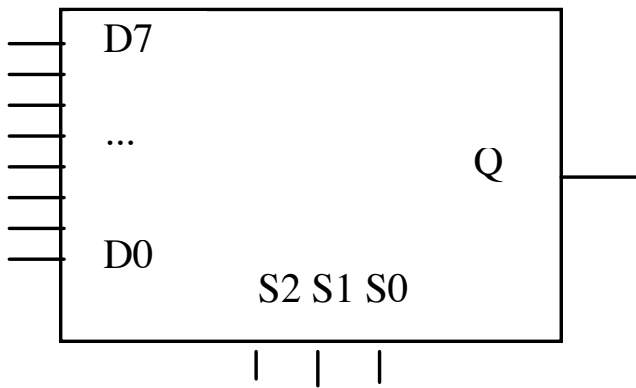One of the possible 2^n inputs is chosen by the n select lines, and gated through to the output of a multiplexer.




<u>S2</u>	<u>S1</u>	<u>S0</u>	<u>Q</u>
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

Half-Adder – adds two one-bit values

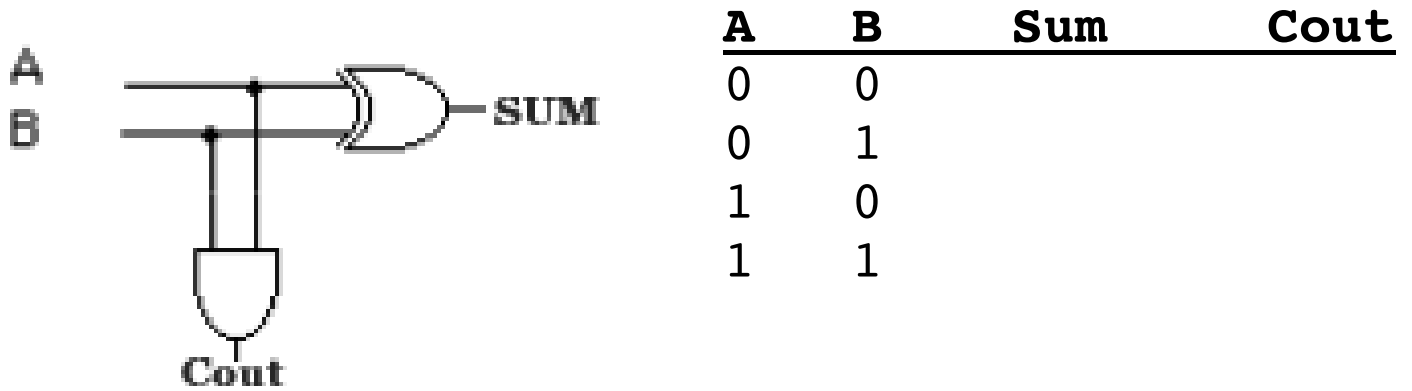

Full Adder – incorporates a carry-in

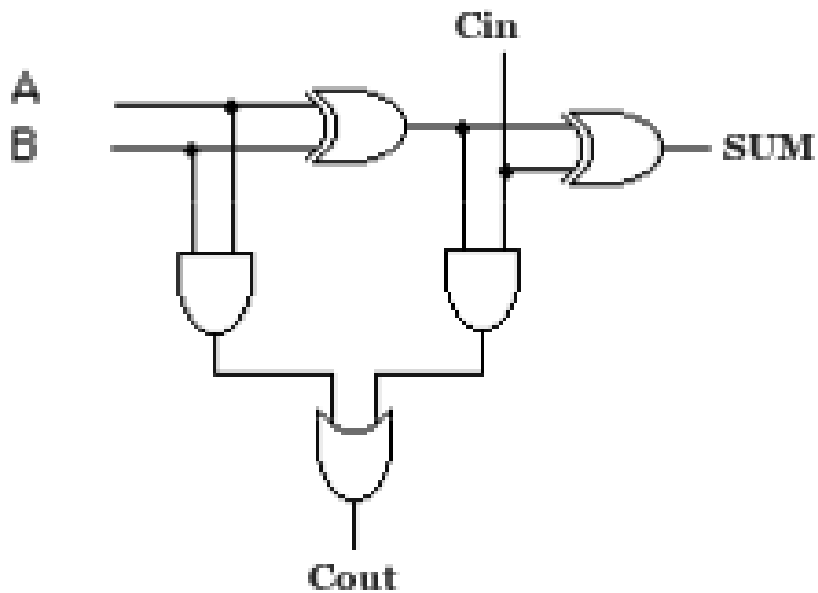


A	B	Cin	Sum	Cout	
0	0	0	0	0	Sum = $A \oplus B \oplus Cin$
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	
1	0	0	1	0	Cout = $AB + (A \oplus B)Cin$
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

n-bit adder = n 1-bit adders

Carry-out of each adder = Carry-in of the adder for next two most significant bits being added

ALU

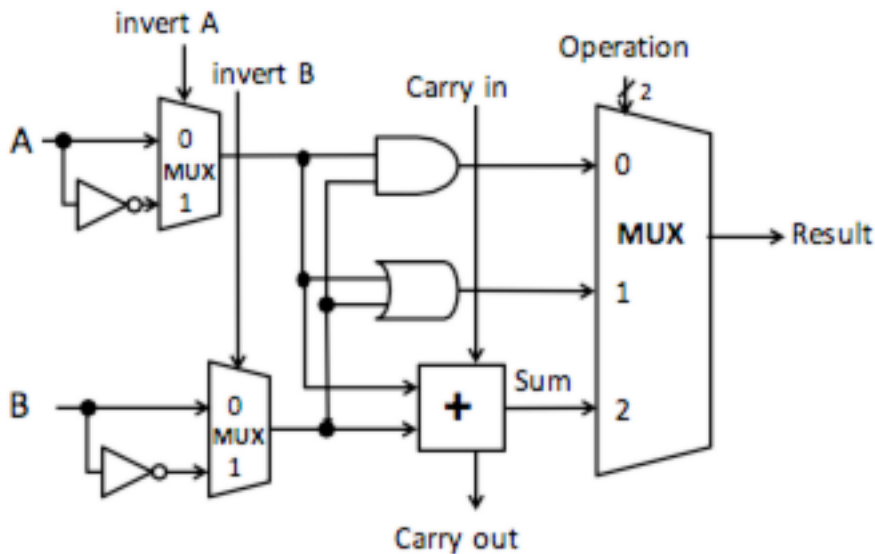Want to be able to select whether the ALU will produce the bitwise AND, OR, and sum as a result.



The basic operations and results are:

add ($a + b + \text{Cin}$),

AND ($a \text{ AND } b$),

OR ($a \text{ OR } b$),

Adding the ability to choose whether to invert A or B provides additional operations:

sub (invert b, $\text{Cin} = 1$, $a + b + \text{Cin}$)

NOR (invert a, invert b, a AND b)

invA	invB	Cin	Op1	Op0	Result
0	0	X	0	0	a AND b
0	0	X	0	1	a OR b
0	0	0/1	1	0	a + b
0	1	1	1	0	a - b
1	1	X	0	0	a NOR b