 


CS240 Laboratory 4 Memory and Datapath

Basic Memory Circuits

Latch Single-bit memory, level-triggered
Flip-Flop Also single-bit, but edge-triggered

SR (Set Reset) Latch



S	R	Q	Q'	
0	0	Qp	Qp'	remember
0	1	0	1	reset (clear)
1	0	1	0	set
1	1			unpredictable

What does **unpredictable** mean? Notice in a NOR gate, if either input = 1 to a gate, its output = 0 (1 is a deterministic input):

A	B	(A+B)'
0	0	1
0	1	0
1	0	0
1	1	0


So, although you wouldn't usually try to *set* and *reset* at the same time (it doesn't make sense), if you did, Q and Q' will both be 0 (which is not unpredictable).

However, when you go back to the *remember* state (S=R=0), Q and Q' will not stay at 0 0. The circuit passes through one of either the *set* or *reset* state on its way back to the *remember* state, and Q and Q' change to the complement of one another.

Since the final state depends on which transitional state was sensed on the way back to *remember*, you cannot predict whether the final state of Q will be 1 or 0.


Clocked SR Latch

 Incorporates a clock input/level-sensitive




Output Q can change in response to S and R whenever the CK input is asserted.

 How does Q respond to the following inputs?



D Latch

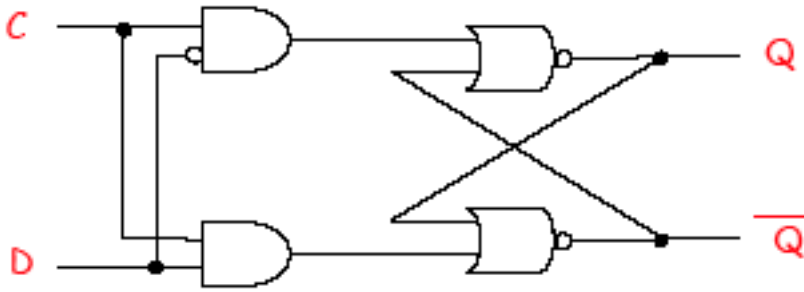Avoids unpredictable state, because a single input D determines the next state of the circuit.




<u>D</u>	<u>Q_{next}</u>
0	0
1	1

D Flip-Flop

Changes state on a clock transition (edge), rather than whenever the clock is asserted.

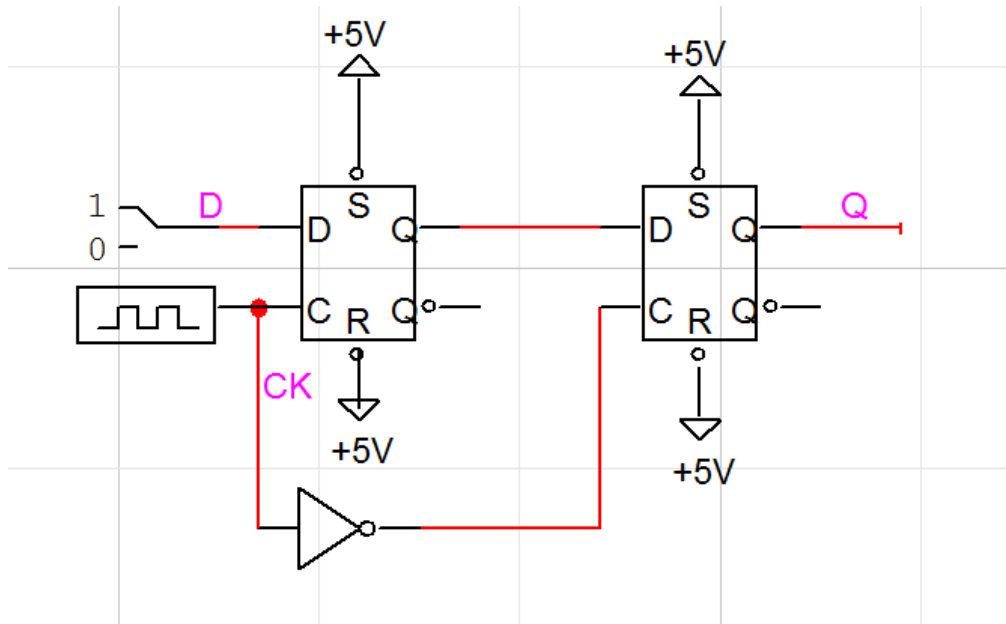Internally, a flip-flop is made from 2 latches. The first latch is controlled by the clock, but the second latch is controlled by the *inverse* of the clock:




So, the input D will not be passed from the first latch to the second latch until the clock goes low.

Once the clock is low, a new value on D will not store into the first latch. Overall, the flip-flop can change value only *exactly* at the transition of the clock from high to low.

Output Q can change in response to S and R only on the positive edge of the clock.

 
How does Q respond to the following inputs?




Notice the difference between Q and the output for the earlier clocked latch example.

Circuits using Flip-flops

 
Register - n -bit memory, uses n flip-flops, and shared *clock* and *clear* inputs



Register File set of registers

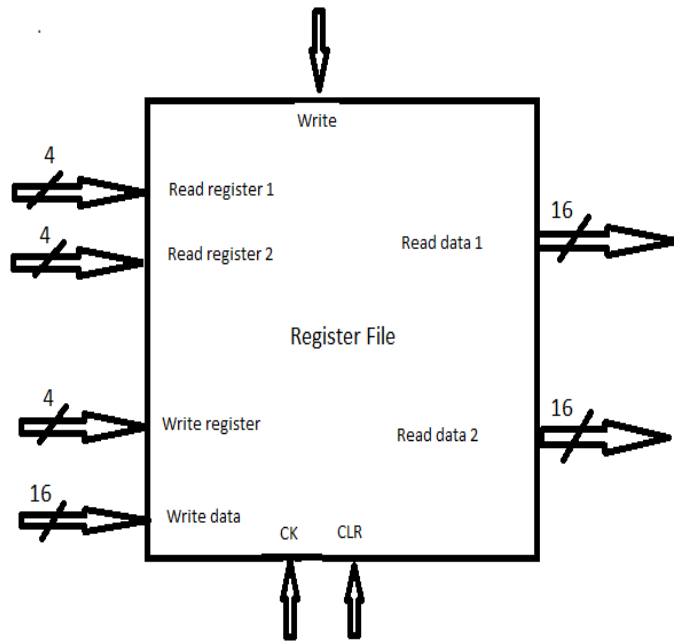


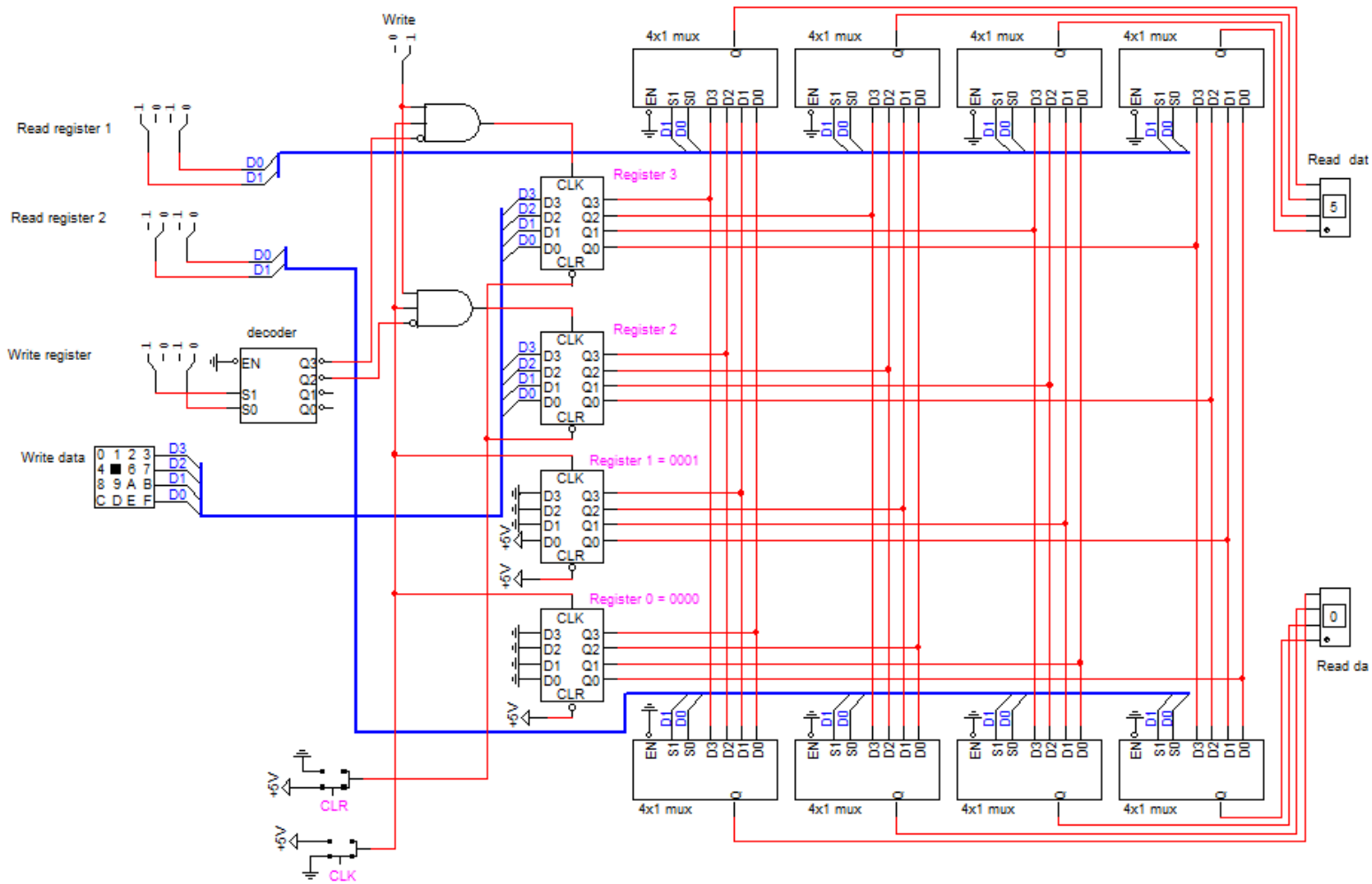- **Write** is the write control signal.
- **Write register** is the number of a register to be written with a new value
- **Read register 1** and **2** indicate which 2 registers can be read at data ports **Read data 1** and **Read data 2** at any given time
- clear and clock (**CLR** and **CLK**) are shared by all the 16 registers.




- 2 sets of 4 x 1 multiplexers select which 2 registers are currently being output at the two read ports.
- A decoder uses the write register number to select which of the 4 registers will receive a new value on a write.

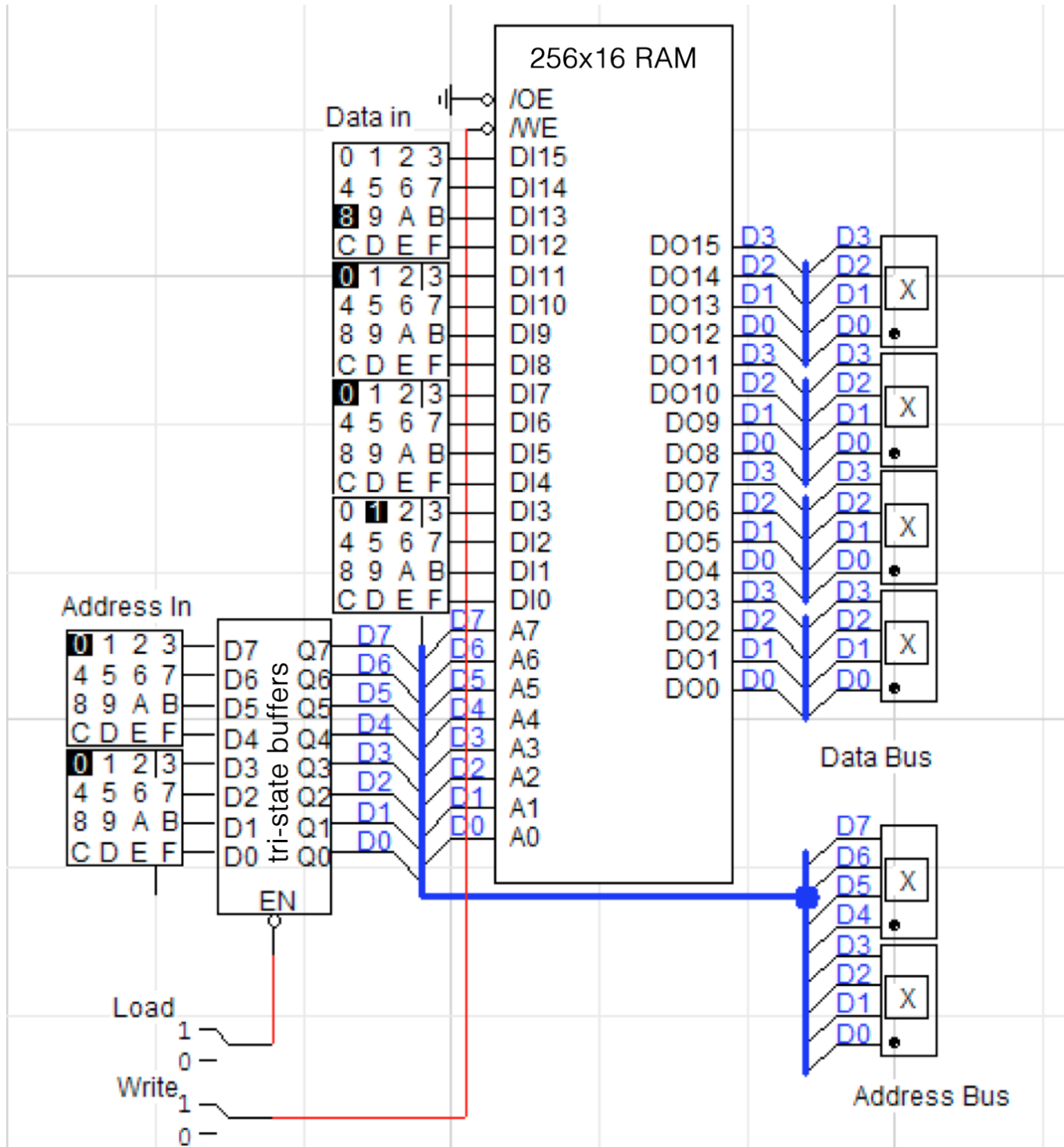RAM memory contains multiple flip-flops, organized into n-bit words, where each word can be accessed through use of an address:



Internal lay-out looks like this:

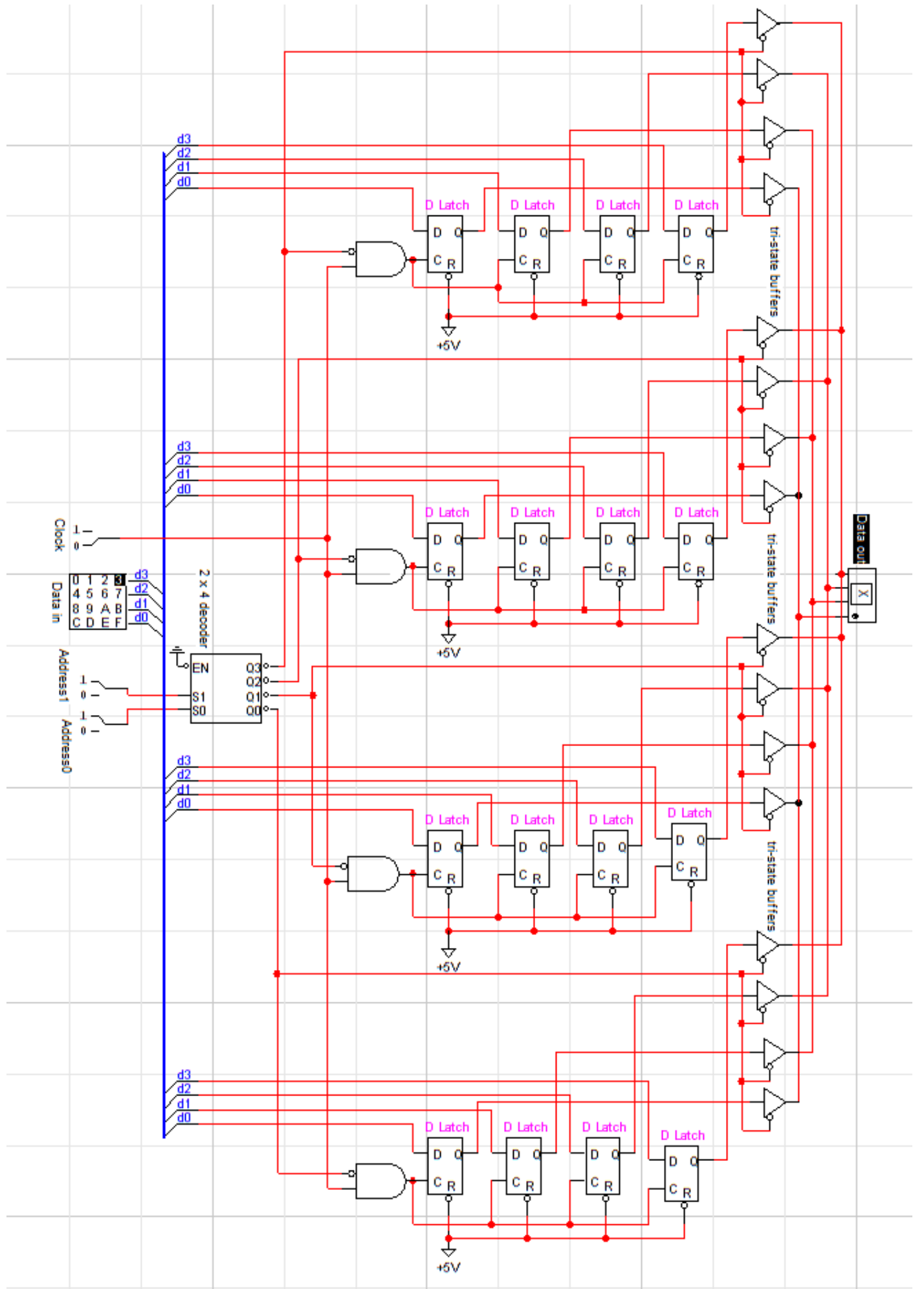


HW Instruction Set Architecture

- **16 bit data bus**
- **8 bit address bus**
- Starting address of every program = 0 (PC initialized to 0 by a reset to begin execution)
- PC incremented by 2 to move to the next instruction.
- **16 registers**
 - R0 = 0 (constant)
 - R1 = 1 (constant)
 - R2-R15 general purpose


Instruction Set

Instruction	Meaning	Op 4-bit	Rs 4-bit	Rt 4-bit	Rd 4-bit
LW Rs,Rt,offset	Rt loaded with word from Data Memory at address(Rs + offset)	0000		0-15	0-15 offset
SW Rs,Rt,offset	Data Memory address(Rs + offset) stored with word from Rt	0001		0-15	0-15 offset
ADD Rs,Rt,Rd	$Rd := R_s + R_t$	0010		0-15	0-15 0-15
SUB Rs,Rt,Rd	$Rd := R_s - R_t$	0011		0-15	0-15 0-15
AND Rs,Rt,Rd	$Rd := R_s \text{ AND } R_t$	0100		0-15	0-15 0-15
OR Rs,Rt,Rd	$Rd := R_s \text{ OR } R_t$	0101		0-15	0-15 0-15
BEQ Rs,Rt,offset	If $R_s=R_t$ then pc:=pc+2+(offset*2) else pc:=pc+2	0111		0-15	0-15 offset
JMP offset	Jump to abs. addr = offset*2	1000		---12 bit offset-----	

Instruction Fetch

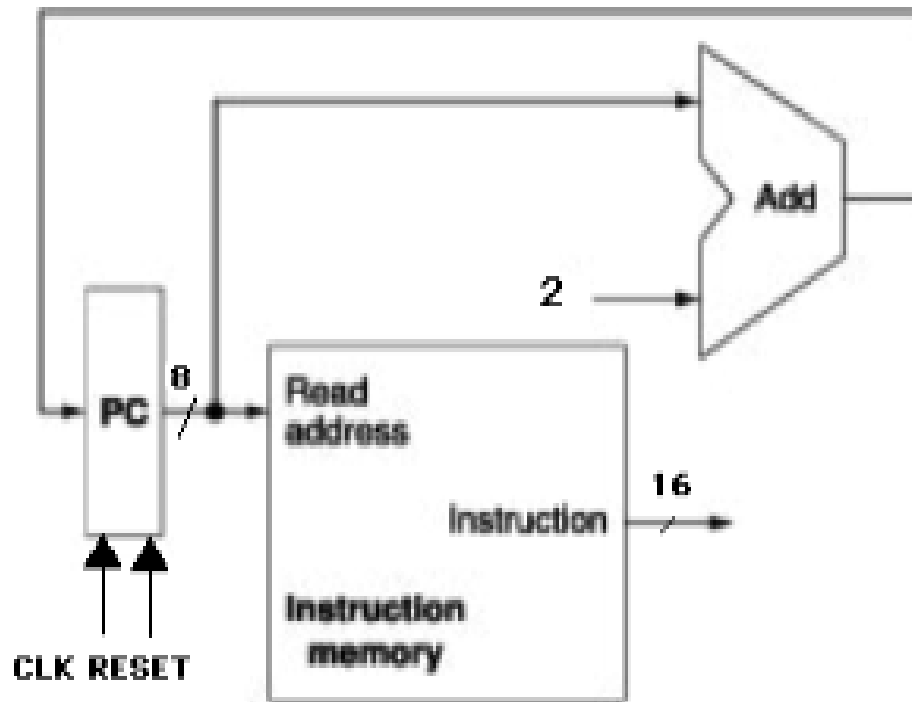

Register File and ALU

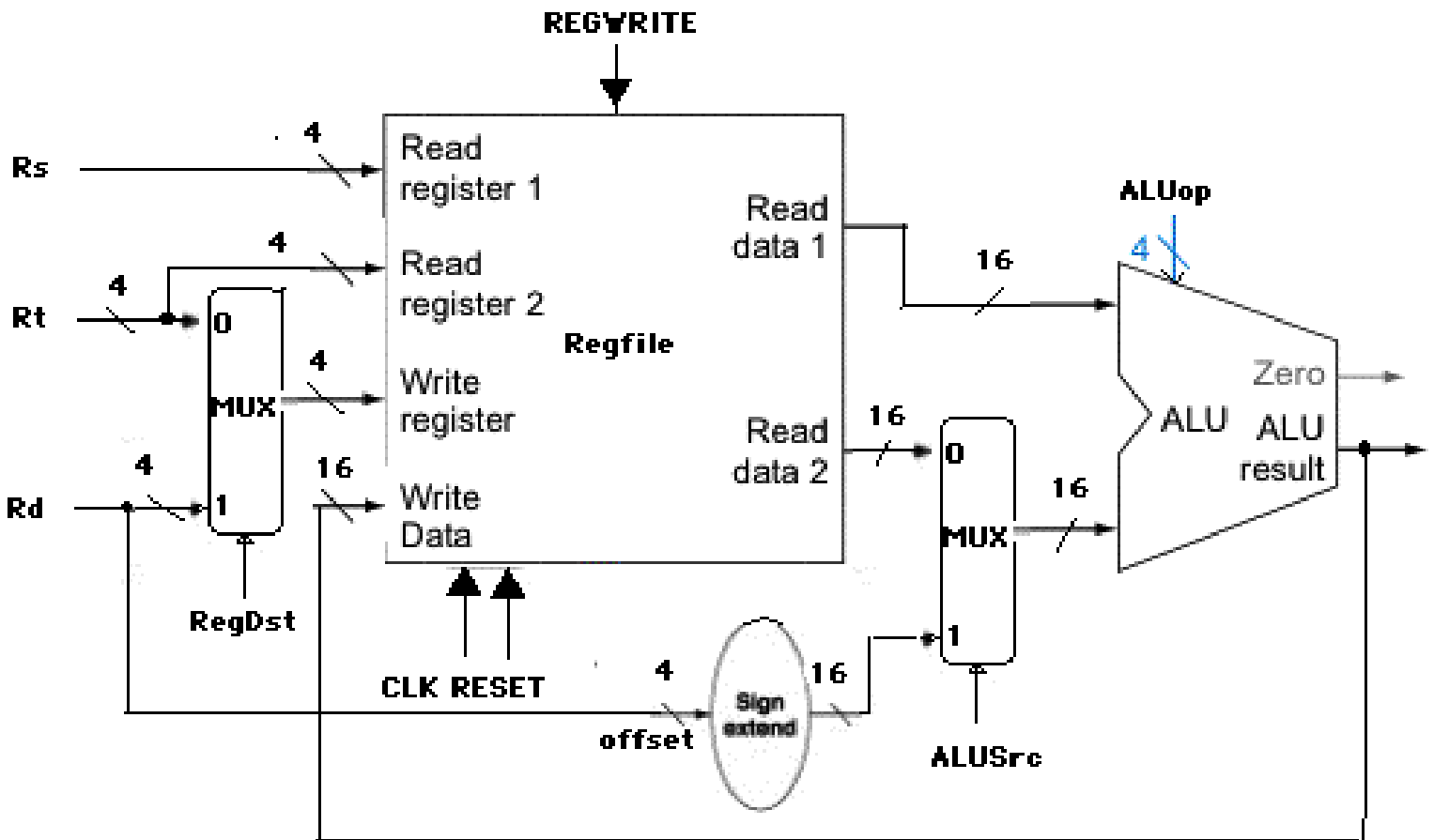

R-type instructions ADD, SUB, AND, OR, SLT (opcode Rs Rt Rd)

- read Rs and Rt from register file
- perform an ALU operation on the contents of the registers
- write the result to register Rd in register file

Memory Access instructions LW, SW (opcode Rs Rt offset)

- memory address = $Rs + \text{sign-extended 4-bit offset}$
- if SW, the value to be stored to memory is from Rt.
- if LW, Rt is loaded with the value read from memory

Register written to (**Write Register**) is Rd or Rt if a LW instruction (chosen by a 2x4 MUX which is controlled by **RegDst**)

ALU calculates $R_s + R_t$, **or** $R_s + \text{sign-extended offset}$.

- Input A of the ALU is always R_s
- Input B of the ALU is R_t **or** the offset
(chosen by a 2x16 multiplexer, which is controlled by **ALUSrc**)