



1. Basic combinational building blocks

2. Logic for arithmetic

Common combinational circuits: encoders, decoders, multiplexers, adders, Arithmetic Logic Unit

(printed together, separate sets of slides online)

But first...

Recall: *sum of products*

logical sum (OR)
of products (AND)
of inputs or their complements (NOT).

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Construct with:

- 1 code detector per 1-valued output row
- 1 large OR of all code detector outputs

Is it minimal?

Gray Codes = reflected binary codes

Alternate binary encoding
designed for electromechanical switches and counting.

00	01	11	10
0	1	2	3

000	001	011	010	110	111	101	100
0	1	2	3	4	5	6	7

How many bits change when incrementing?

Karnaugh Maps: find (minimal) sums of products



		gray code order →			
		00	01	11	10
A	B	0	0	0	0
	0	0	0	1	0
	0	0	1	0	0
	0	0	1	1	0
	0	1	0	0	0
0	0	1	0	1	0
	0	1	0	1	0
	1	0	0	0	1
	1	0	0	1	1
	1	0	1	0	1
1	0	1	1	0	1
	1	1	0	0	1
	1	1	0	1	1
	1	1	1	0	1
	1	1	1	1	0


1. Cover exactly the 1s by drawing a (minimum) number of maximally sized rectangles whose dimensions (in cells) are powers of 2. (They may overlap or wrap around!)
2. For each rectangle, make a *product* of the inputs (or complements) that are 1 for all cells in the rectangle. (*minterms*)
3. Take the *sum* of these products.

Voting again with Karnaugh Maps

ex

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Toolbox: Building Blocks

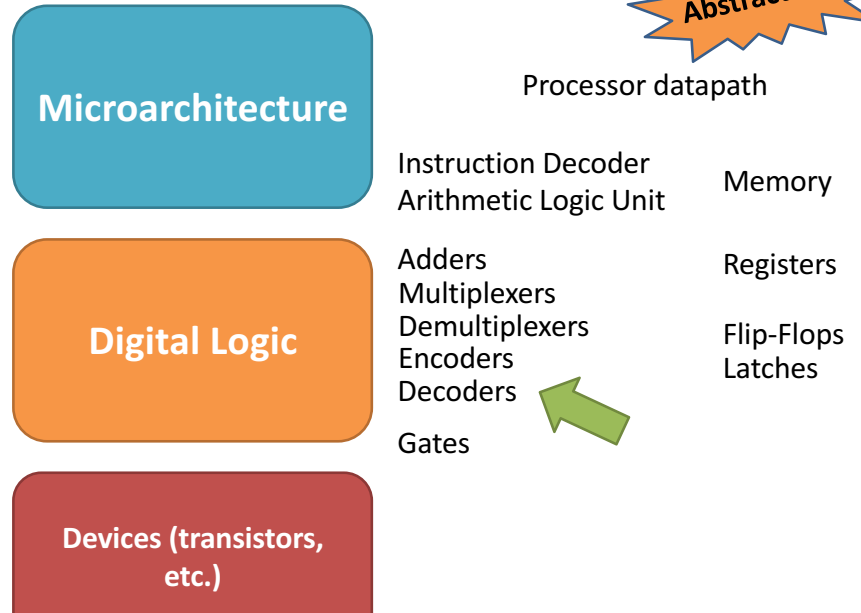

Decoders


ex

Decodes input number, asserts corresponding output.

n -bit input (an unsigned number)


2^n outputs

Built with code detectors.

 

Multiplexers

Select one of several inputs as output.

 

Build a 2-to-1 MUX from gates


ex

If $S=0$, then $F=D_0$.


If $S=1$, then $F=D_1$.

1. Construct the truth table.

2. Build the circuit.

 


8-to-1 MUX

 

Costume idea: MUX OX

MUX + voltage source = truth table

 


Buses and Logic Arrays

A **bus** is a collection of data lines treated as a single logical signal.

= **fixed-width value**

Array of logic elements applies same operation to each bit in a bus.

= **bitwise operator**

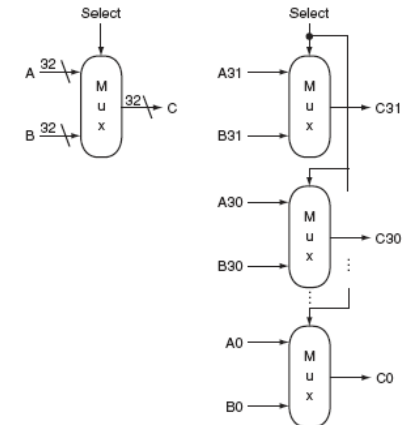


Addition: start small with a 1-bit (half) adder

ex

A	B	Carry out	Sum
0	0		
0	1		
1	0		
1	1		

1-bit full adder

 


ex

n-bit addition: $Sum_i = A_i + B_i + CarryOut_{i-1}$ Need a bigger adder!

A	B	Carry in	Carry out	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


n-bit ripple-carry adder

 

There are faster, more complicated ways too...


Processor Components

Abstraction!

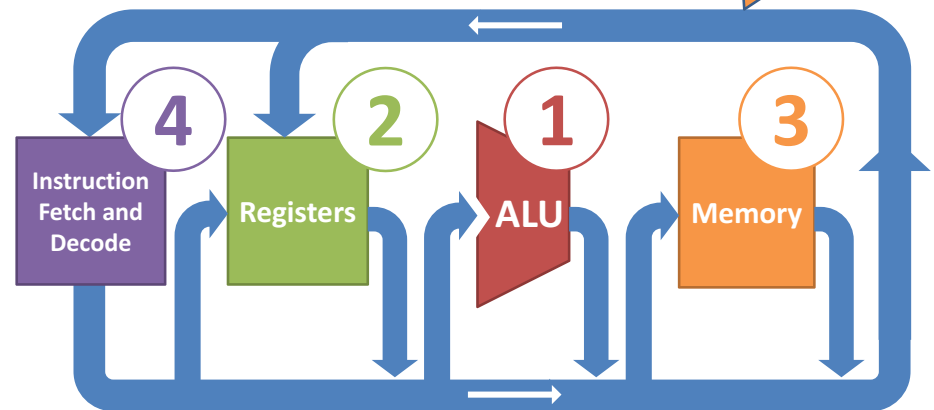

Arithmetic Logic Unit (ALU)

1

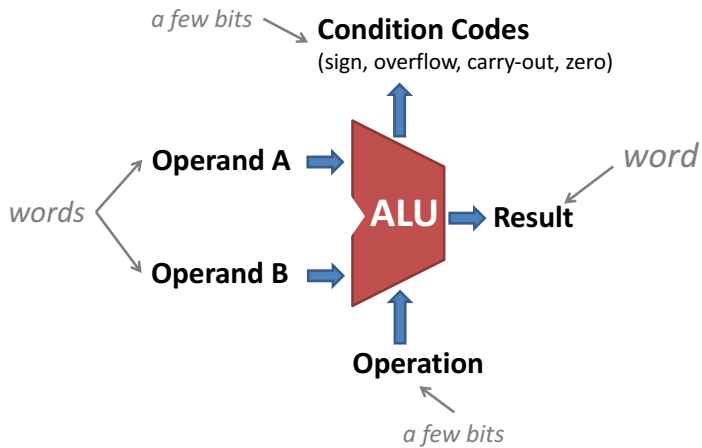


Hardware unit for arithmetic and bitwise operations.

1-bit ALU for bitwise operations

ex


Build an n-bit ALU from n 1-bit ALUs.

 Each bit i in the result is computed from the corresponding bit i in the two inputs.




Op	A	B	Result
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


1-bit ALU

 

n-bit ripple carry adder

 

n-bit ALU

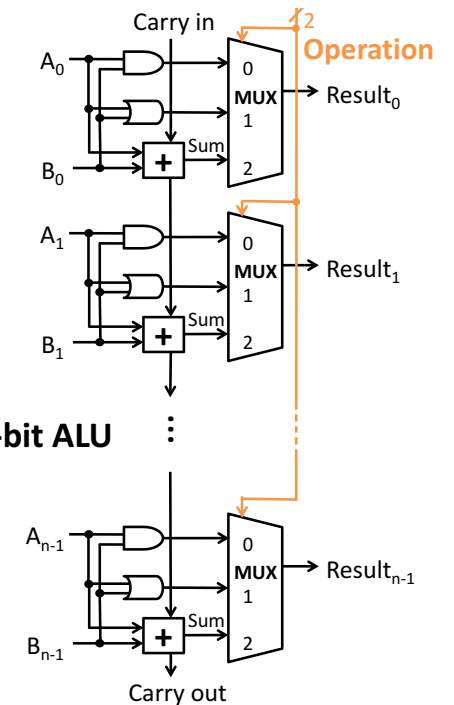

ALU conditions

Extra ALU outputs
describing properties of result.


Zero Flag:
1 if result is 00...0 else 0

Sign Flag:
1 if result is negative else 0

Carry Flag:
1 if carry out else 0


(Signed) Overflow Flag:
1 if signed overflow else 0

Implement these.

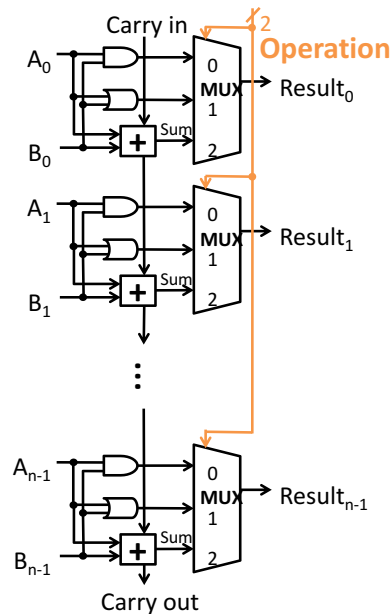

Add subtraction

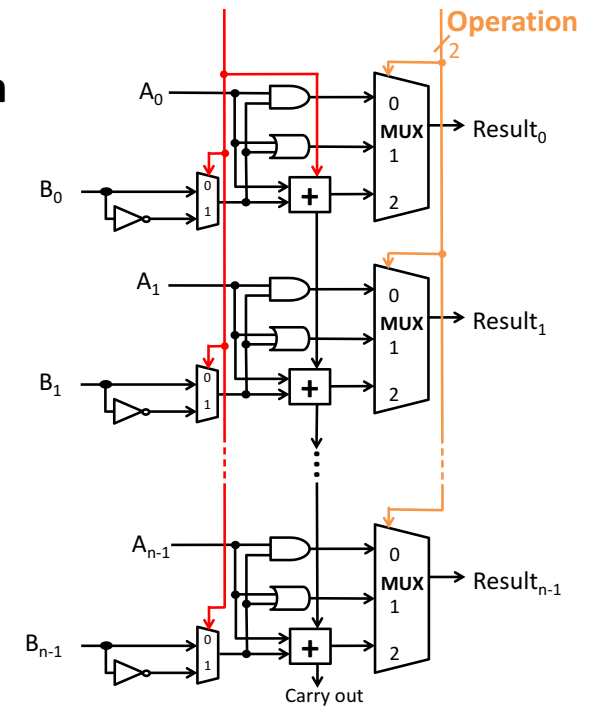How can we control ALU inputs or add minimal new logic to compute A-B?




A NAND B

A NOR B

A < B

A == B

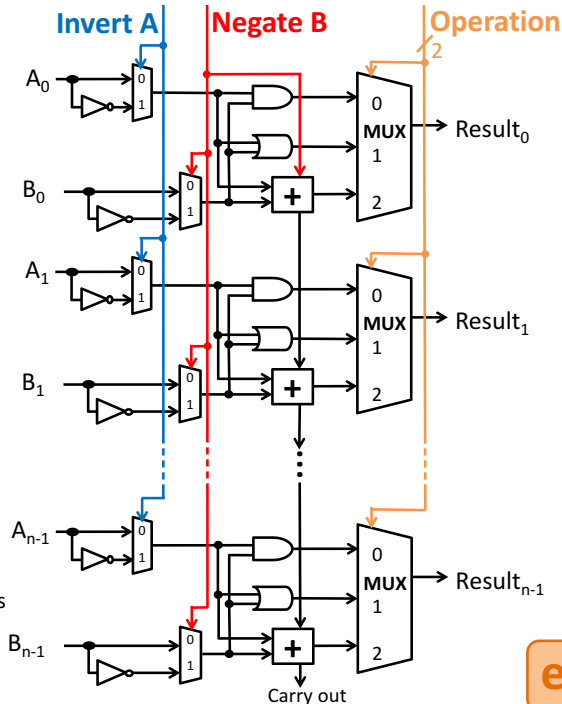How can we control ALU inputs or add minimal new logic to compute each?



Controlling the ALU

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
1100	NOR

