

Digital Logic

Gateway to computer science


Digital data/computation = Boolean

Boolean value (*bit*): 0 or 1

Boolean functions (AND, OR, NOT, ...)

Electronically:

bit = high voltage vs. low voltage

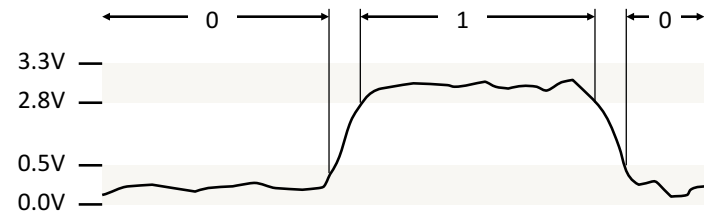


Boolean functions = logic gates, built from transistors


Transistors (more in lab)

If **Base voltage is high:**
Current may flow freely from *Collector* to *Emitter*.

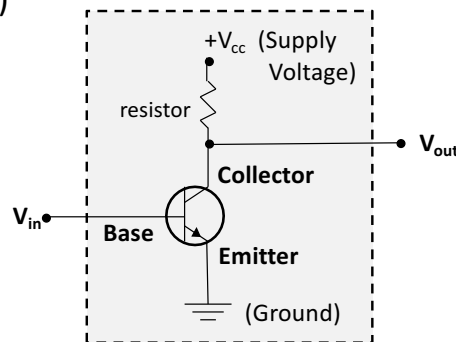If **Base voltage is low:**
Current may not flow from *Collector* to *Emitter*.



Truth table					
V_{in}	V_{out}	=	in	out	=
low	high	=	0	1	=
high	low	=	1	0	=
			F	T	
			T	F	

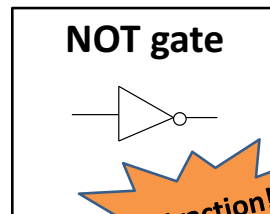


Abstraction!

Digital Logic Gates



Abstraction!

ex

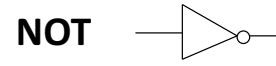
Tiny electronic devices that compute basic Boolean functions.



V_{in}	V_{out}
0	1
1	0

 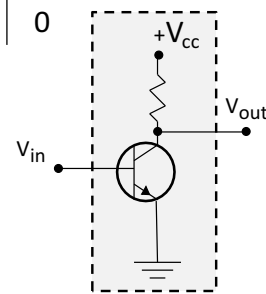


V_1	V_2	
	0	1
0	0	0
1	0	1

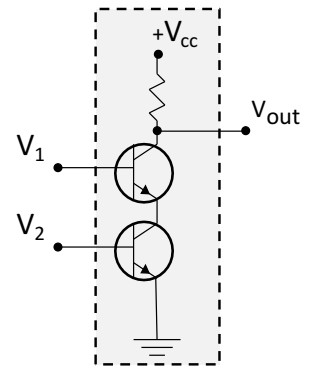


Five basic gates: define with truth tables


ex

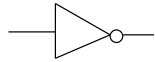


NOT	
0	1
1	0

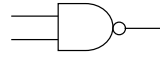


NAND		
	0	1
0	1	1
1	1	0

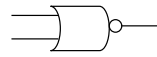

NOR		
	0	1
0	1	1
1	0	0

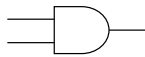

AND		
	0	1
0	0	0
1	0	1

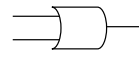


OR		
	0	1
0	0	0
1	1	1

Boolean Algebra


for combinational logic

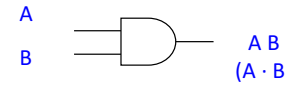inputs = variables
wires = expressions
gates = operators/functions
circuits = functions




AND = Boolean product

·	0	1
0	0	0
1	0	1

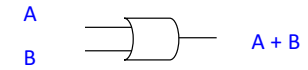

OR = Boolean sum

+	0	1
0	0	1
1	1	1

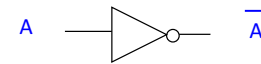

NOT = inverse or complement

	0	1
0	1	0
1	0	1




wire = identity

	0	1
0	0	0
1	1	1

Circuits

ex

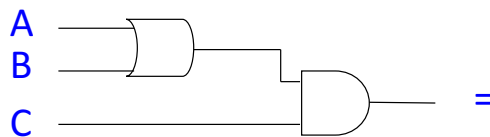Connect inputs and outputs of gates with wires.
Crossed wires touch **only if** there is a dot.



What is the output if A=1, B=0, C=1?

What is the truth table of this circuit?

What is an equivalent Boolean expression?

Translation


ex

Connect gates to implement these functions. Check with truth tables.
Use a direct translation -- it is straightforward and bidirectional.


$$F = (A\bar{B} + C)D$$

$$Z = \bar{W} + (X + \bar{W}Y)$$


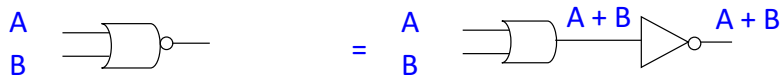
Note on notation: bubble = inverse/complement




Identity law, inverse law

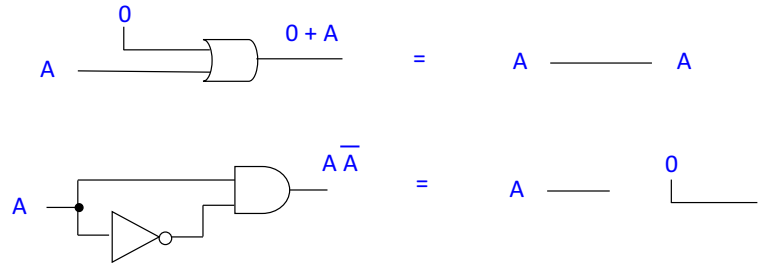


Commutativity, Associativity

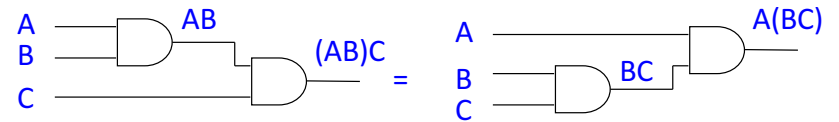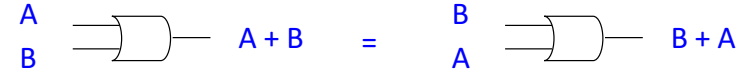

Idempotent law, Null/Zero law


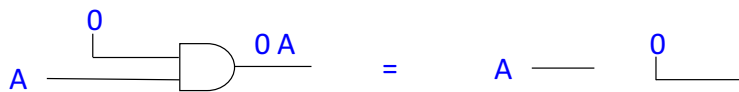


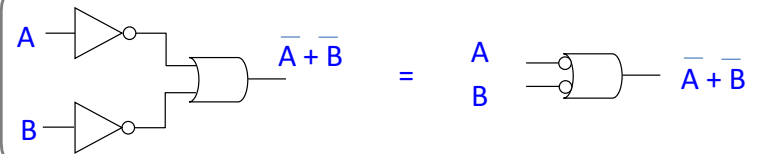Note on notation: bubble = inverse/complement



DeMorgan's Law

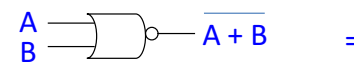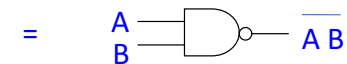
(double bubble, toil and trouble, in Randy's words...)




One law, Absorption law

ex

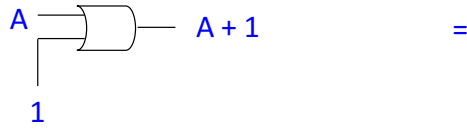Write truth tables. Do they correspond to simpler circuits?



NAND is *universal*.

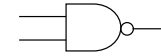


ex

All Boolean functions can be implemented using only NANDs.
Build NOT, AND, OR, NOR, using only NAND gates.

XOR: Exclusive OR

ex

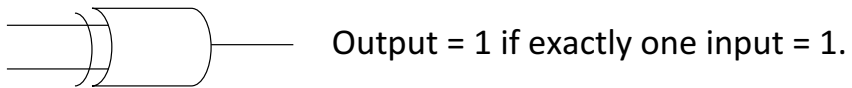

Truth table:

Build from earlier gates:


Often used as a one-bit comparator.

Video game designers, Halloween costumers extraordinaire, sci-fi/fantasy screenwriters, I have an idea...

Larger gates

ex

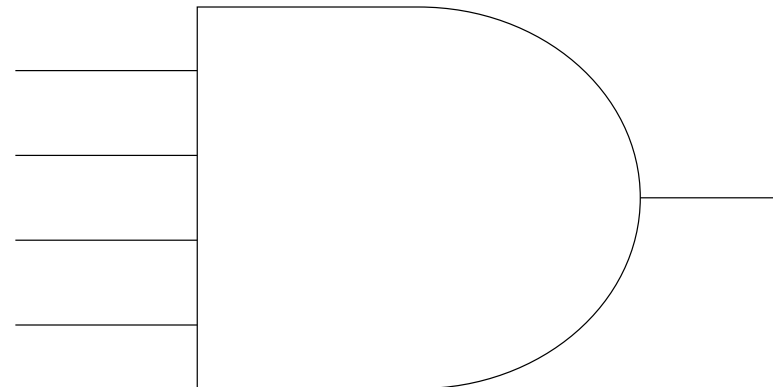Build a 4-input AND gate using any number of 2-input gates.




Why simplify?

ex

Circuit simplification

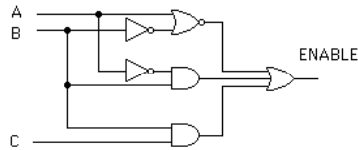Is there a simpler circuit that performs the same function?



Start with an equivalent Boolean expression, then simplify with algebra.


$F(A, B, C) =$

Check the answer with a truth table.

Circuit derivation: *code detectors*

ex

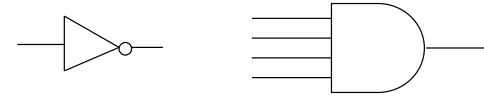AND gate + NOT gates = code detector, recognizes exactly one input code.



Design a 4-input code detector to output 1 if ABCD = 1001, and 0 otherwise.

A _____
 B _____
 C _____
 D _____

Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others. (accept = 1, reject = 0)

Circuit derivation: *sum-of-products* form

ex

logical sum (OR)
 of products (AND)
 of inputs or their complements (NOT)

Draw the truth table and design a sum-of-products circuit for a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others.

How are the truth table and the sum-of-products circuit related?

Voting machines

ex

A **majority circuit** outputs 1 if and only if a majority of its inputs equal 1.

Design a majority circuit for three inputs. **Use a sum of products.**

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Triply redundant computers in spacecraft

- Space program also hastened Integrated Circuits.