

Latch: CC-BY Rberteig@flickr




Latches, Flip-flops, Registers, Memory

Sequential logic: elements to store values
Output depends on inputs *and* stored values.


(vs. combinational logic: output depends only on inputs)

Bistable latches

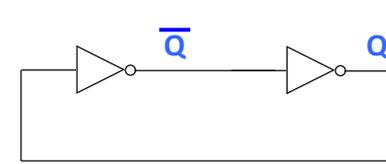Suppose we somehow get a 1 (or a 0?) on here.




=

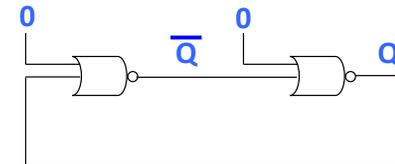


SR latch


S	R	Q	Q'	Q (stable)	Q' (stable)
0	0	0	0	?	?
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
1	0	?	?	1	0
0	1	?	?	0	1

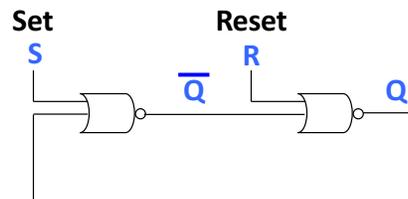

SR latch

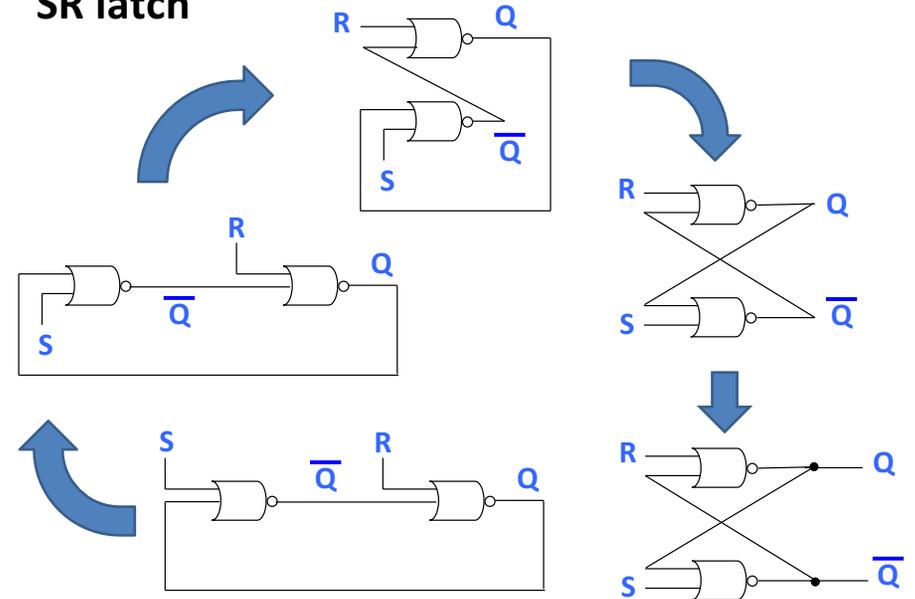

D latch

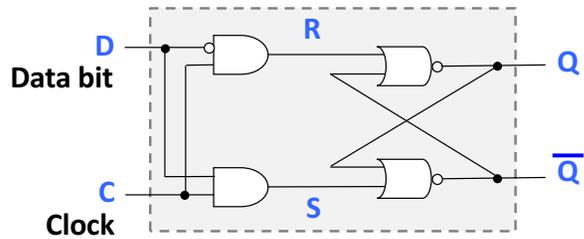

if $C = 0$, then SR latch stores current value of Q .

if $C = 1$, then D flows to Q :

if $D = 0$, then $R = 1$ and $S = 0$, $Q = 0$

if $D = 1$, then $R = 0$ and $S = 1$, $Q = 1$

Time matters!

D


C

Q

Clocks

Clock: free-running signal
with fixed **cycle** time = **clock period** = T .


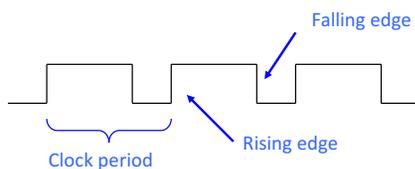
Clock frequency = $1 / \text{clock period}$



A clock controls when to update
a sequential logic element's state.




D flip-flop with falling-edge trigger

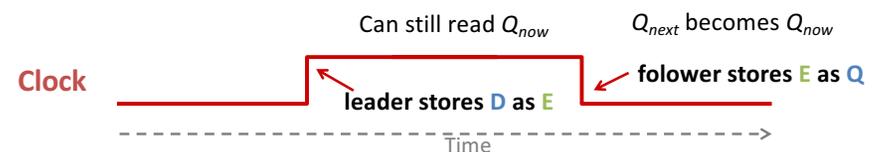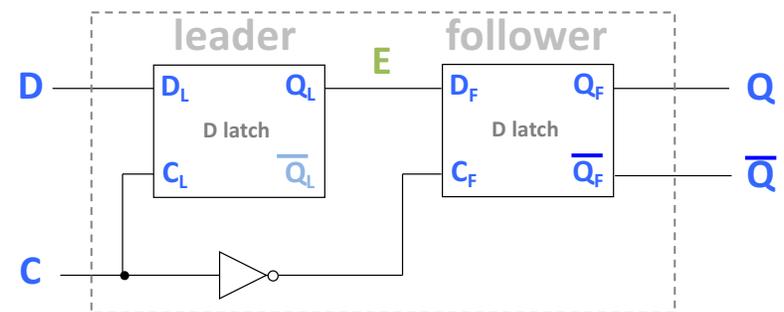

Time matters!

D
C
E
Q


Reading and writing in the same cycle

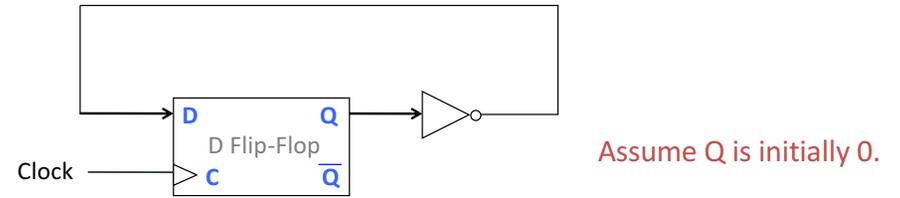


**Half a byte!* 🖱️

A 1-nybble* register

(a 4-bit hardware storage cell)

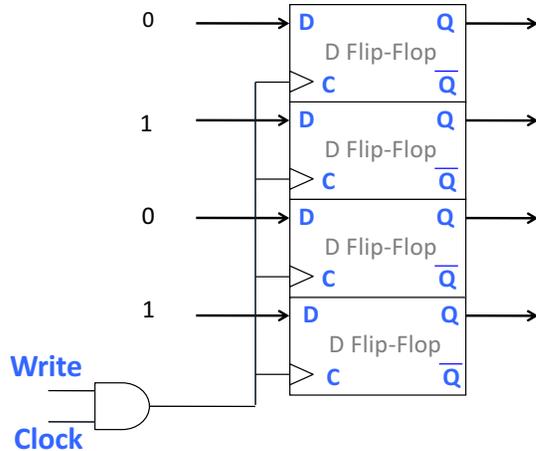


Register file

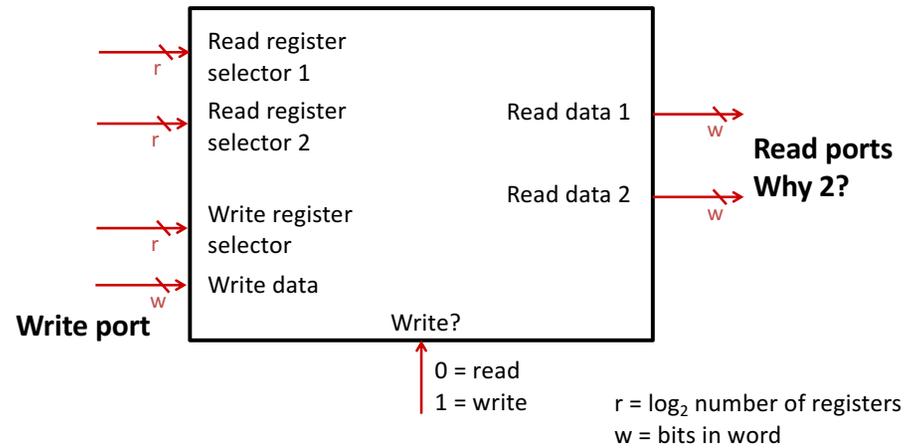


Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.


Read ports (data out)

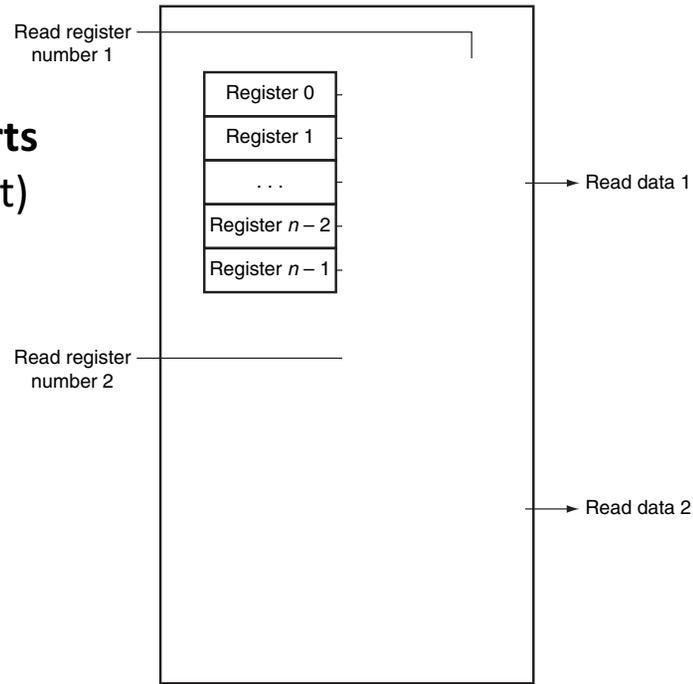

Write port (data in)

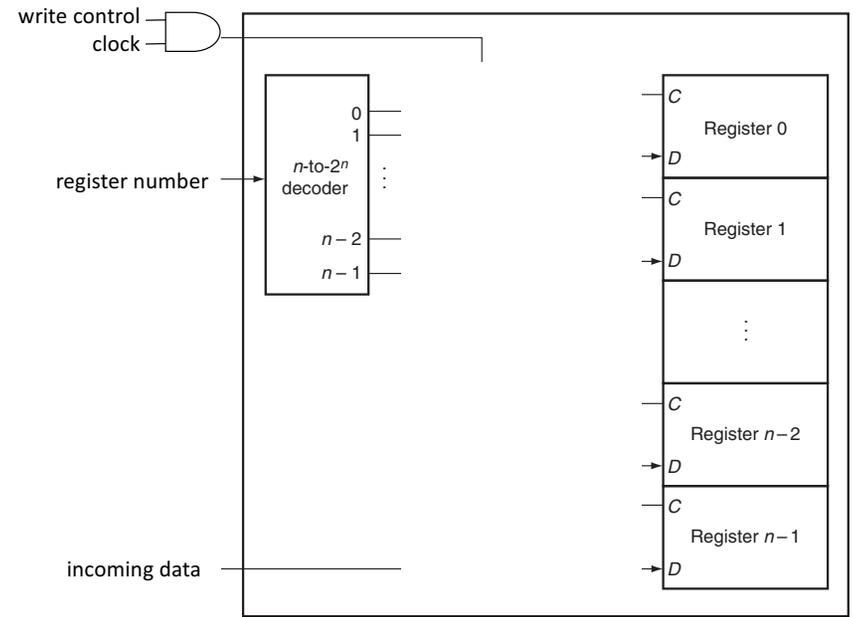

RAM (Random Access Memory)

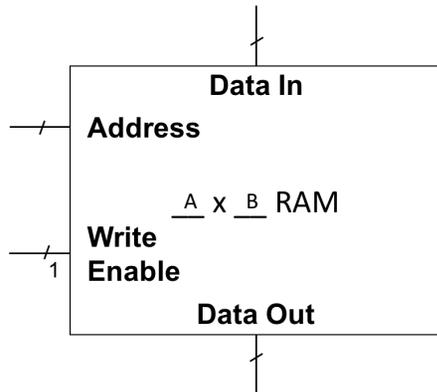

Similar to register file, except...

16 x 4 RAM

