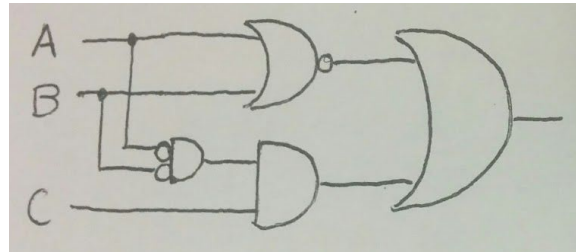


**Digital Logic (Part 1)**

1. For the following circuit:



a. Write its truth table:

A	B	C	F (output)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Are there any shortcuts?

**If output = 1, then either  $(A+B)' = 1$  ( $A = 0, B = 0, C = 0$  or  $1$ )  
 or  $A'B'C = 1$  ( $A = 0, B = 0, C = 1$ )**


b. What is the equivalent, unsimplified Boolean expression?

$$(A + B)' + A'B'C = \overline{A+B} + \overline{A} \overline{B} C$$

c. Simplify or shorten your answer in part c, using boolean algebra laws, and write the laws you used next to each step.

$A'B' + A'B'C$	<b>DeMorgan's</b>
$A'B'$	<b>Absorption</b>

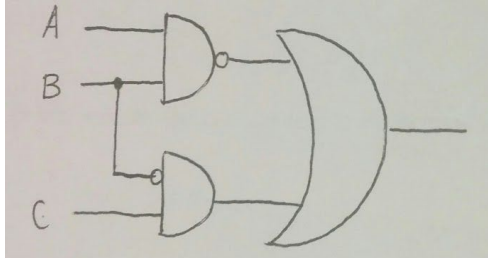Extra practice: (repeat #1 for this circuit)



A	B	C	F (output)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


$(AB)' + B'C$   
 $A' + B' + B'C$   
 $A' + B'$

(original)  
 DeMorgan's  
 Absorption

2. For the boolean equation:  $F = (A'A + (BC'))' + B$

$$\overline{\overline{AA + \overline{BC} + B}}$$

a. Draw the unsimplified circuit:

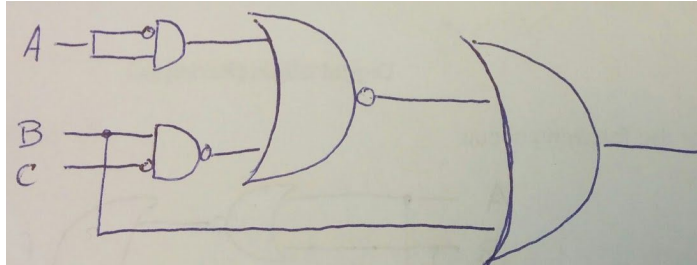

What was your thought process in implementing this circuit?  
**(ideally) inside-out or outside-in**

b. Write its truth table:


A	B	C	F (output)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

c. Simplify the expression by using boolean algebra laws to shorten the number of terms, and write the corresponding laws next to each step:

$$\begin{aligned}
 F &= (A'A + (BC'))' + B && \text{(original)} \\
 F &= (0 + (BC'))' + B = ((BC'))' + B && \text{Inverse} \\
 F &= BC' + B && \text{Involution} \\
 F &= B && \text{Absorption}
 \end{aligned}$$

Extra practice:  $(A + ABC')B$

(repeat #2 for this expression)

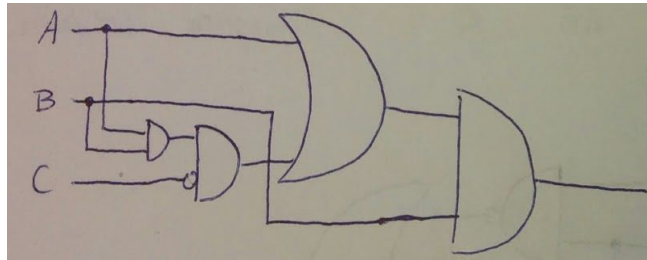

A	B	C	F (output)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

**$(A + ABC')B$**   
**AB**

**(original)**  
**Absorption again**

3. What are the different levels of abstraction in the hardware/software interface?  
(Hint: the rainbow)

**[This is just to help you keep the overall context and big idea of the class in mind.]**

