
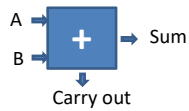


## Addition: 1-bit *half* adder

ex

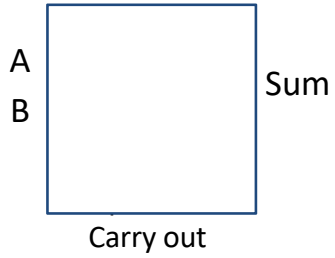


A	B	Carry out	Sum
0	0		
0	1		
1	0		
1	1		




## Addition: 1-bit *full* adder

ex

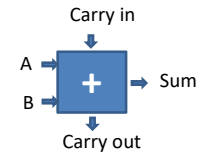

Carry in	A	B	Carry out	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

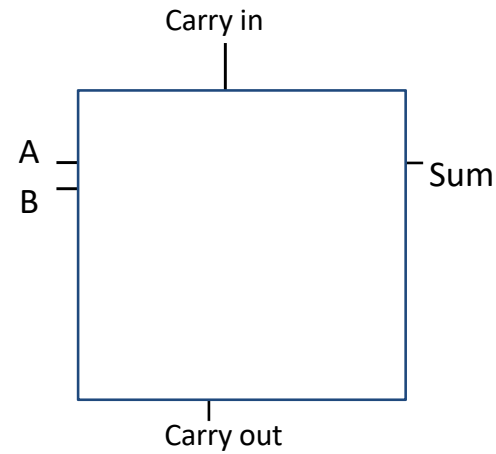


## 1-bit ALU for bitwise operations

ex


Build an n-bit ALU from n 1-bit ALUs.

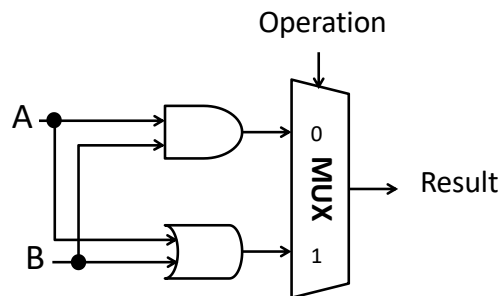Each bit  $i$  in the result is computed from the corresponding bit  $i$  in the two inputs.



Op	A	B	Result
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

## 1-bit ALU

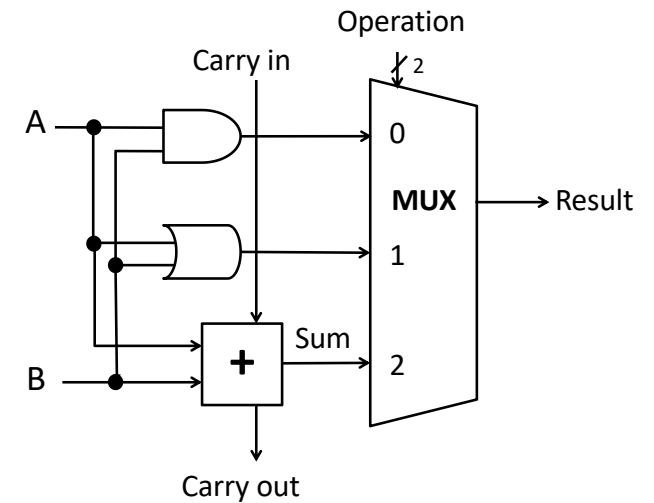

# ALU conditions

## Extra ALU outputs

describing properties of result.

**Zero Flag:** ex

1 if result is 00...0 else 0

**Sign Flag:** ex

1 if result is negative else 0


**Carry Flag:**

1 if carry out else 0

**(Signed) Overflow Flag:**


1 if signed overflow else 0

Implement these.

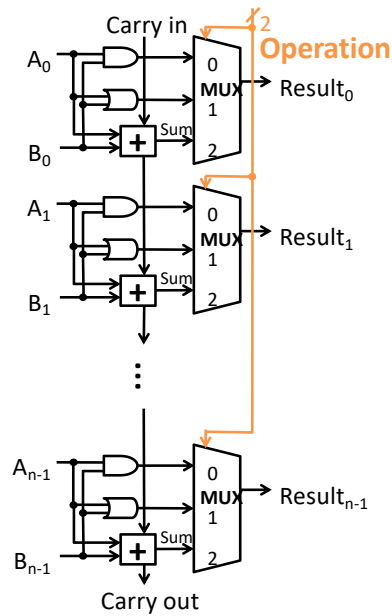
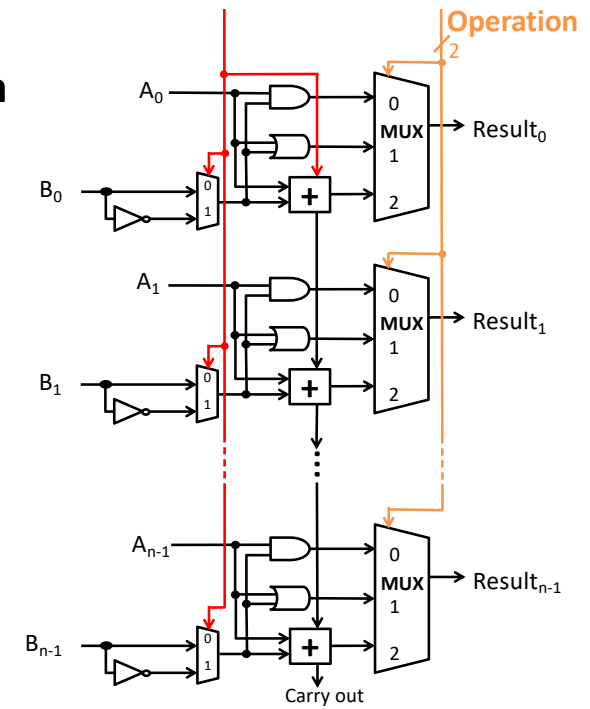
# Add subtraction

How can we control ALU inputs or add minimal new logic to compute A-B?



## A NAND B

## A NOR B

## A < B

## A == B

How can we control ALU inputs or add minimal new logic to compute each?

