


# Digital Logic

Gateway to computer science
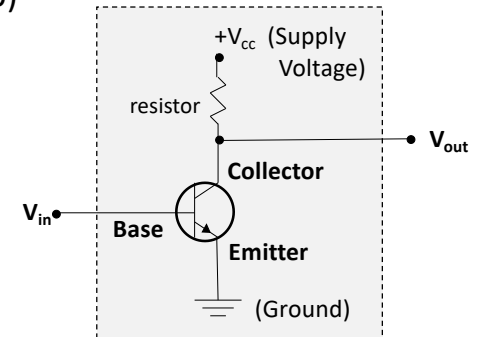
## Transistors (more in lab)

**If Base voltage is high:**  
Current may flow freely from *Collector* to *Emitter*.

**If Base voltage is low:**  
Current may not flow from *Collector* to *Emitter*.





## Digital Logic Gates

Tiny electronic devices that compute basic Boolean functions.

**Abstraction!**



ex

**NOT**

 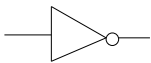


$V_{in}$	$V_{out}$
0	1
1	0

$V_1$	$V_2$	
	0	1
0		
1		

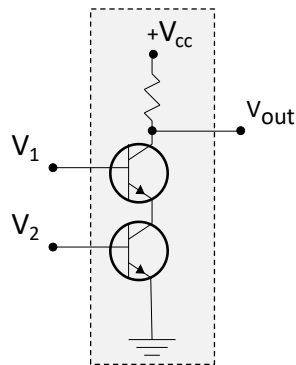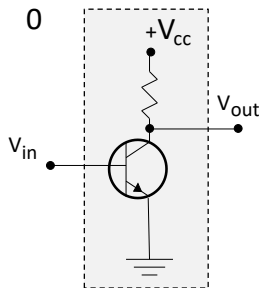


## Five basic gates: define with truth tables


ex

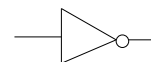


<b>NOT</b>	
0	1
1	0

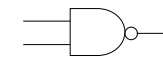


<b>NAND</b>		
	0	1
0	1	1
1	1	0

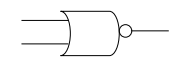

<b>NOR</b>		
	0	1
0		
1		

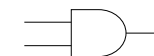

<b>AND</b>		
	0	1
0		
1		

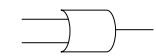


<b>OR</b>		
	0	1
0		
1		

ex
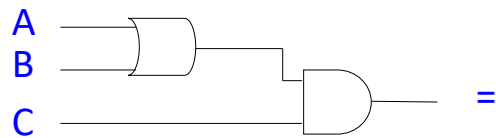
## Circuits

Connect inputs and outputs of gates with wires.  
Crossed wires touch **only if** there is a dot.



What is the output if A=1, B=0, C=1?  
What is the truth table of this circuit?  
What is an equivalent Boolean expression?

ex

## Translation

Connect gates to implement these functions. Check with truth tables.  
Use a direct translation -- it is straightforward and bidirectional.




$$F = (\overline{A}B + C)D$$

$$Z = \overline{W} + (X + \overline{W}Y)$$

ex

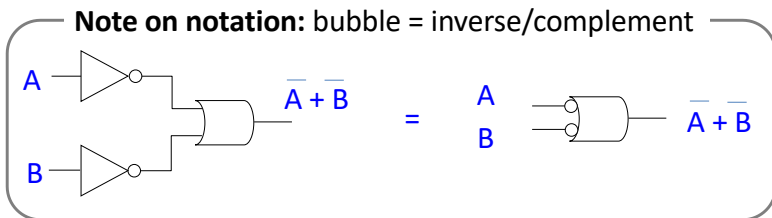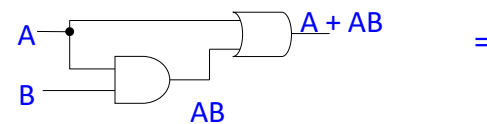
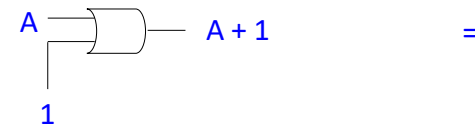
## One law, Absorption law

Write truth tables. Do they correspond to simpler circuits?



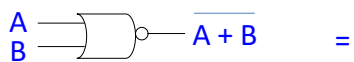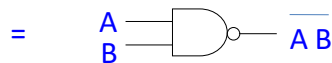
## DeMorgan's Law

(double bubble, toil and trouble, in Randy's words...)



## NAND is *universal*.

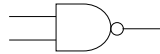


ex

All Boolean functions can be implemented using only NANDs.  
Build NOT, AND, OR, NOR, using only NAND gates.

## XOR: Exclusive OR

ex

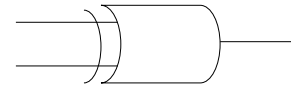

Output = 1 if exactly one input = 1.

Truth table:

Build from earlier gates:


Often used as a one-bit comparator.

*Video game designers, Halloween costumers extraordinaire, sci-fi/fantasy screenwriters, I have an idea...*
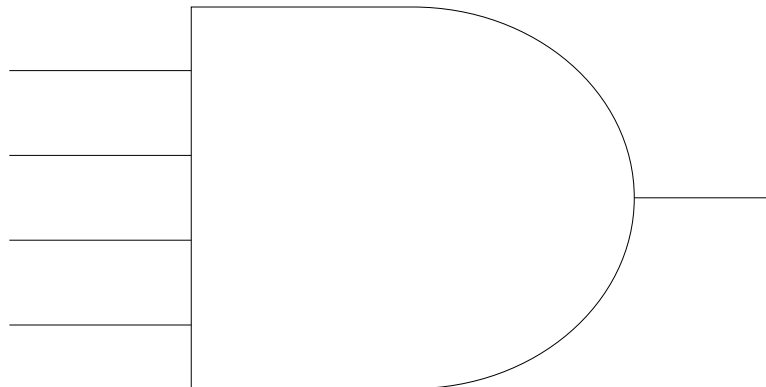
## Larger gates

ex

Build a 4-input AND gate using any number of 2-input gates.




Why simplify?

ex
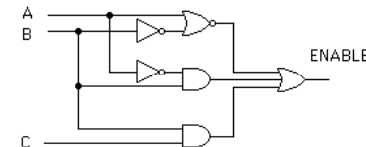
## Circuit simplification

Is there a simpler circuit that performs the same function?



Start with an equivalent Boolean expression, then simplify with algebra.


$$F(A, B, C) =$$

Check the answer with a truth table.
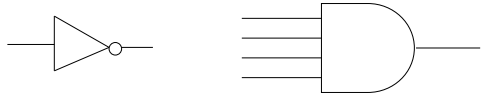
## Circuit derivation: *code detectors*

ex

AND gate + NOT gates = code detector, recognizes exactly one input code.



Design a 4-input code detector to output 1 if ABCD = 1001, and 0 otherwise.

A \_\_\_\_\_  
B \_\_\_\_\_  
C \_\_\_\_\_  
D \_\_\_\_\_

Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others. (accept = 1, reject = 0)

## Circuit derivation: *sum-of-products* form

ex

logical sum (OR)  
of products (AND)  
of inputs or their complements (NOT)

**Draw the truth table and design a sum-of-products circuit** for a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others.

**How are the truth table and the sum-of-products circuit related?**

## Voting machines

ex

A **majority circuit** outputs 1 if and only if a majority of its inputs equal 1.

Design a majority circuit for three inputs. **Use a sum of products.**

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

**Triply redundant computers in spacecraft**

- Space program also hastened Integrated Circuits.