

CS 240 Lab 2

More Digital Logic and Combinational Circuits

- **Binary and Hex Numbers/Binary Counter**
- **Multiplexer**
- **Decoder**
- **Adder**

Binary and Hexadecimal Numbers

Hex	Binary			
	QD	QC	QB	QA
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
A	1	0	1	0
B	1	0	1	1
C	1	1	0	0
D	1	1	0	1
E	1	1	1	0
F	1	1	1	1

Hex can be converted to binary and vice versa by grouping into 4 bits.


$$11110101_2 = F5_{16}$$

$$37_{16} = 00110111_2$$

Binary Counter




NOTE: logic diagram is not the same as pin-outs! Shows information about the logical operation of the device.

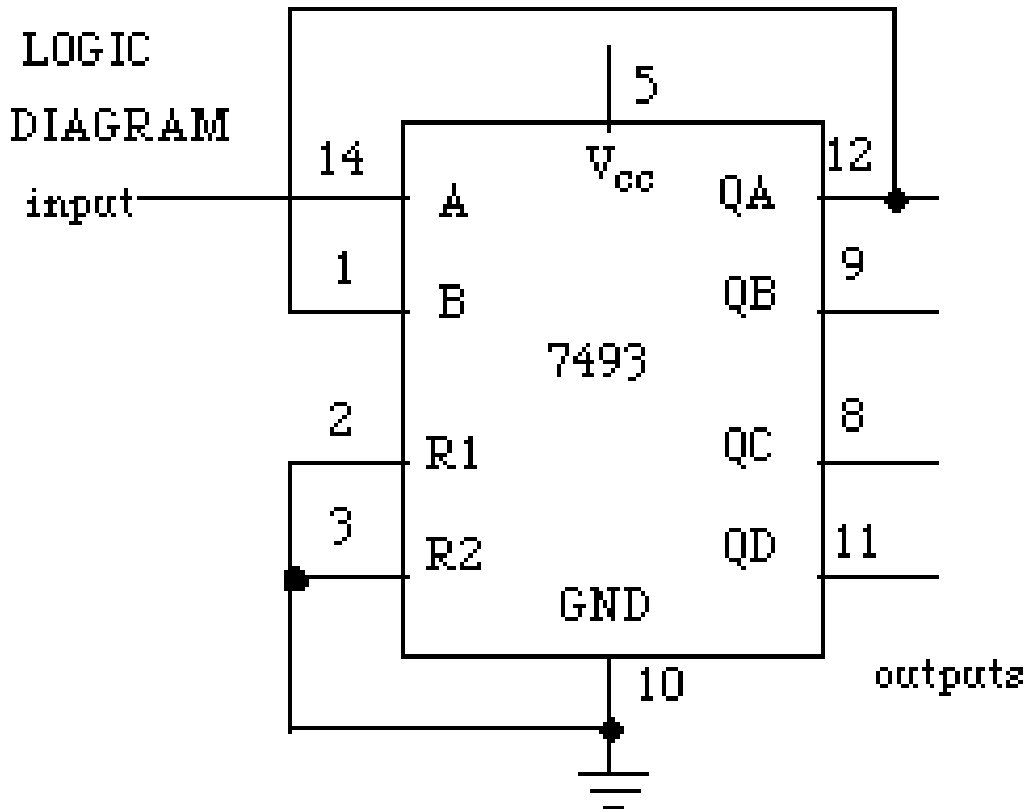- Inputs on left side of diagram
- Outputs on right
- Voltage shown on top
- Ground shown on bottom



Multiplexer

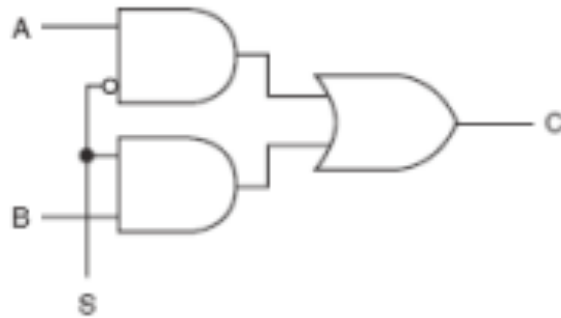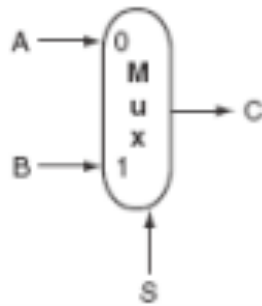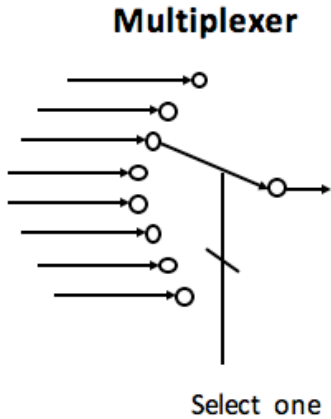A multiplexer can be thought of as a **steering circuit**, which steers a single input from a set of inputs through to the output, based on the select line.



- n select lines
- 2^n input lines
- 1 output

One of the possible 2^n inputs is chosen by the n select lines, and gated through to the output of a multiplexer. The truth table for an 8x1 MUX is:


<u>S2</u>	<u>S1</u>	<u>S0</u>	<u>Q</u>
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

Decoder


A decoder translates an binary number input to the select lines, and asserts the corresponding numbered output.

- n input/select lines
- 2^n outputs
- only one of the outputs is active at any given time, based on the value of the n select lines.

2x4 Decoder

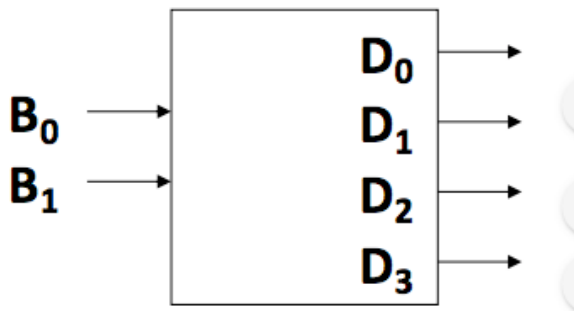


Built with code detectors:

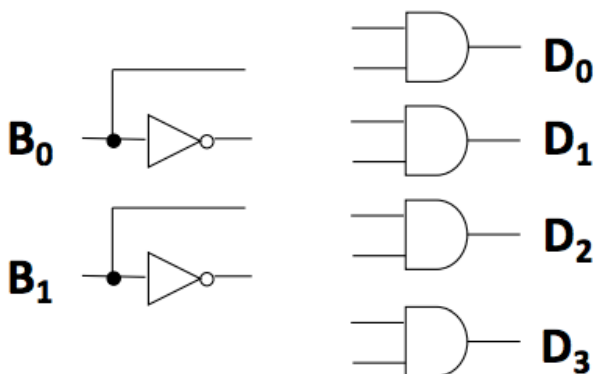

Adder


Addition is a very important arithmetic operation, and uses the Exclusive OR gate!

Half-Adder – adds two one-bit values

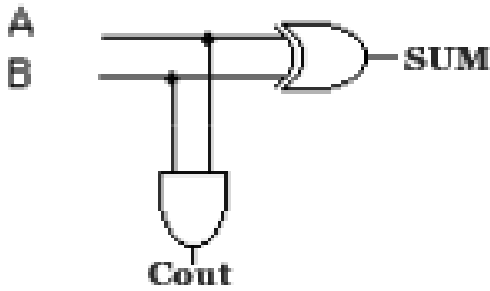

<u>A</u>	<u>B</u>	<u>Cout</u>	<u>Sum</u>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

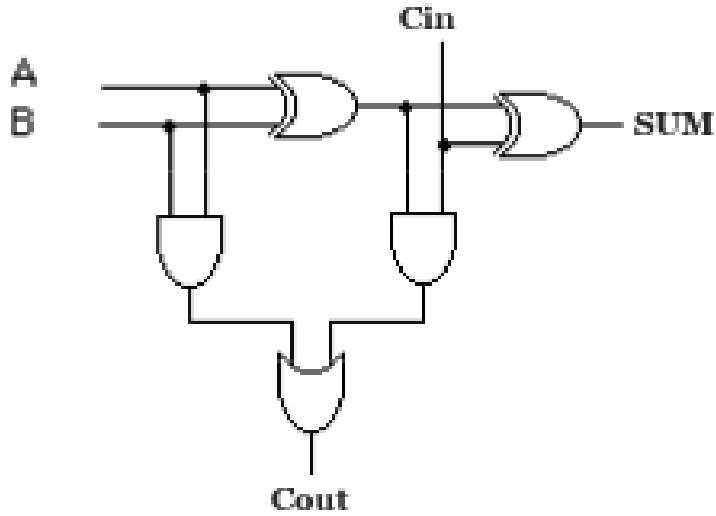Full Adder – uses two half-adders and incorporates a carry-in



Cin	A	B	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = AB + (A \oplus B) \text{Cin}$$