

# Laboratory 5

## Processor Datapath

### Description of HW Instruction Set Architecture

- **16 bit data bus**
- **8 bit address bus**
- **16 registers**
  - R0 = 0 (constant)
  - R1 = 1 (constant)
  - R2-R15 general purpose


## HW ISA Instructions

MSB
**16-bit Encoding**
LSB

Assembly Syntax	Meaning	Opcode	Rs	Rt	Rd
ADD <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] + R[t]$	0010	<i>s</i>	<i>t</i>	<i>d</i>
SUB <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] - R[t]$	0011	<i>s</i>	<i>t</i>	<i>d</i>
AND <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] \& R[t]$	0100	<i>s</i>	<i>t</i>	<i>d</i>
OR <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s]   R[t]$	0101	<i>s</i>	<i>t</i>	<i>d</i>
BEQ <i>Rs, Rt, offset</i>	If $R[s] == R[t]$ then $PC \leftarrow PC + offset * 2$	0111	<i>s</i>	<i>t</i>	<i>offset</i>
JMP <i>offset</i>	$PC \leftarrow offset * 2$	1000	<i>o</i>	<i>f</i>	<i>f s e t</i>
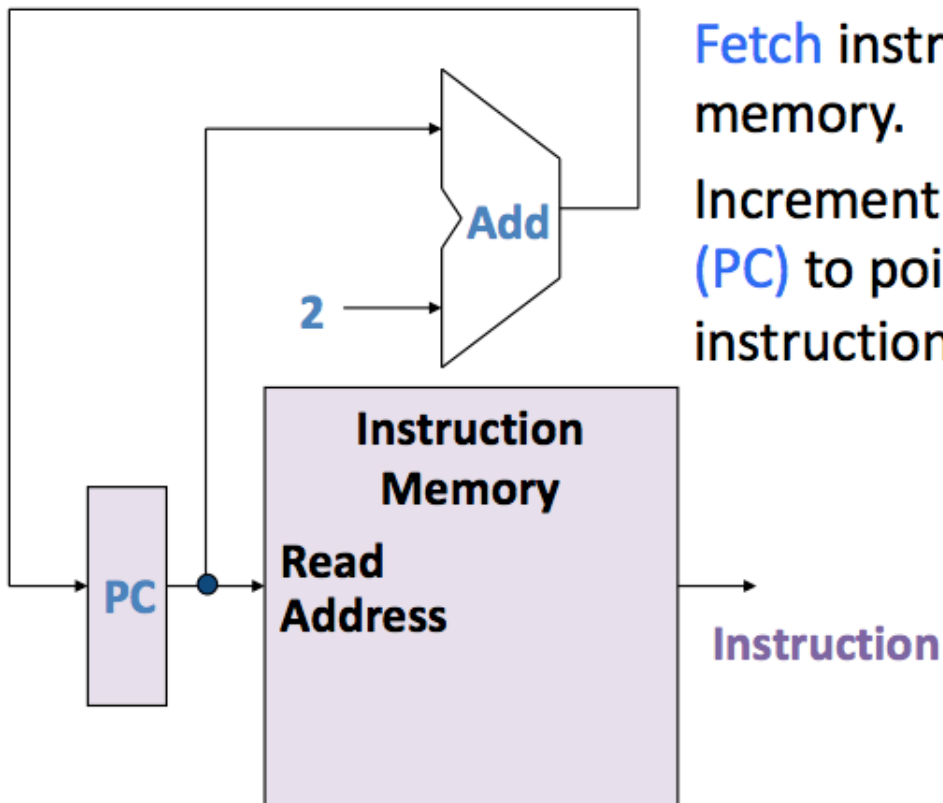
## Fetch Instruction from Memory

- **PC** register holds address of currently executing instruction
- Programs are assumed to start at address 0
- **PC** initialized to 0 by a reset to begin execution
- Next instruction located at current **PC + 2**



Fetch instruction from memory.

Increment program counter (PC) to point to the next instruction.

## Branch Address


Programs do not always execute in sequential order.

When the **BEQ** instruction is executed, the next instruction to be executed is either:

$$PC = PC + 2$$

or

$$PC = PC + 2 + (2 * \text{offset})$$

 

### BEQ Rs,Rt,offset

- The **offset** = number of instructions away from the next value of the PC to branch to, so must be multiplied by 2.
- Since **offset** is 4 bits, it must be sign-extended to 8 bits to be added to the PC.

A **MUX** selects the next value of the PC. The value of the **Branch** and **Zero** bits are used to determine which is used:

- The **Branch** control line = 1 if a BEQ instruction is being executed.
- The **Zero** bit from the ALU is used to check whether  $R_s = R_t$ : it is 1 if  $R_s - R_t = 0$  (meaning they're equal). If **Branch** = 1 and **Zero** = 1, then the next value of the PC will be the branch address ; otherwise, it will simply be **PC + 2**

In the HW computer, there is also an unconditional branch instruction called **JMP** (jump):

### **JMP offset**


where the *offset* is a 12-bit value which specifies the number of instructions from the beginning of the program to jump to:

$$\text{PC} = \text{offset} * 2$$

For example, **JMP 3** sets the **PC** to 0x6, causing the instruction stored at address 0x6 (*i.e.*, the 3rd instruction in the program) to be executed next.
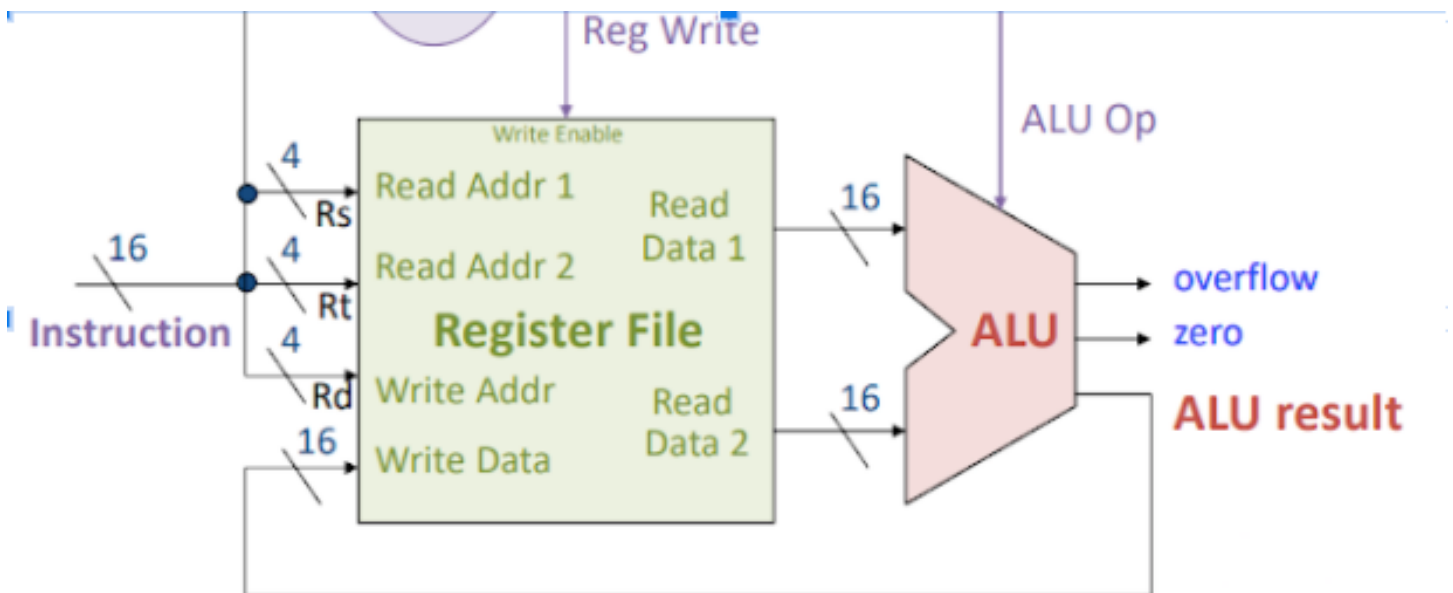
## **Datapath**

The following diagram describes the basic datapath for executing the arithmetic and logic instructions:



**R-type instructions** ADD,SUB,AND,OR have format: **opcode Rs Rt Rd**

- read **Rs** and **Rt** from register file
- perform an ALU operation on the contents of the registers
- write the result to register **Rd** in register file

ALU can perform 4 possible operations,


**BEQ** is accomplished by subtraction (which sets the **Zero** bit).

**BEQ** and **JMP** do not change the value of a register.

<b>Instruction</b>	<b>Opcode</b>	<b>ALUop</b>	<b>RegWrite</b>
ADD	0010	0010	1
SUB	0011	0110	1
AND	0100	0000	1
OR	0101	0001	1
BEQ	0111	0110	0
JMP	1000	don't care	0

Can use decoders or simple logic to produce these signals.

## Full Implementation

 

## Procedure to Load/Execute a New Program

1. Disconnect the address bus of the Instruction Memory from the CPU
2. Set **LOAD** = 0
3. Set **address** and **data** switches for instruction
4. Set **WR** = 0, then back to 1
5. Repeat steps 3 and 4 until all instructions are loaded to memory
6. Set **LOAD** = 1
7. Reconnect address bus to CPU
8. Set **Reset** = 1, then back to 0
9. Set **CLK** = 1, then back to 0, for each instruction.

Address	Instruction	op	Rs	Rt	Rd/offset
0:		ADD	R1	R1	R2 # initialize R2
2:		ADD	R2	R1	R3 # initialize R4
4:		AND	R2,	R2,	R4 # copy R2 to R4
6:		AND	R3,	R3,	R5 # copy R3 to R5
8: (LOOP)		BEQ	R5,	R0,	3 # if R5 is 0, branch to end
A:		SUB	R5,	R1,	R5 # decrement R5
C:		ADD	R4,	R4,	R4 # update result in R4
E:		JMP	4		# repeat loop
10: (END)		AND	R4,	R4,	R4 #program will end here with value of R4 # displayed at outputs of ALU