




# Arithmetic Logic

adders  
Arithmetic Logic Unit

<https://cs.wellesley.edu/~cs240/>

Arithmetic Logic 1

## Addition: 1-bit *half* adder

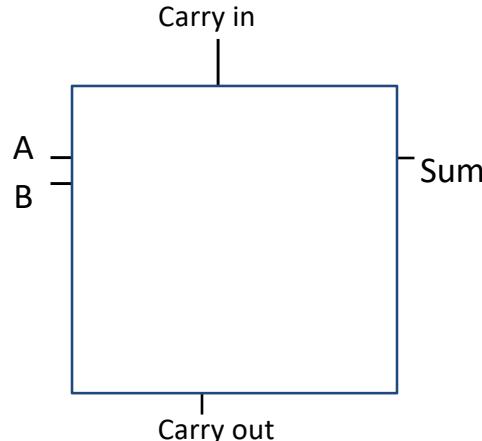


ex

Carry in	A	B	Carry out	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Arithmetic Logic 3

## Addition: 1-bit *half* adder

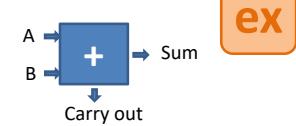


ex

A	B	Carry out	Sum
0	0		
0	1		
1	0		
1	1		

Arithmetic Logic 2

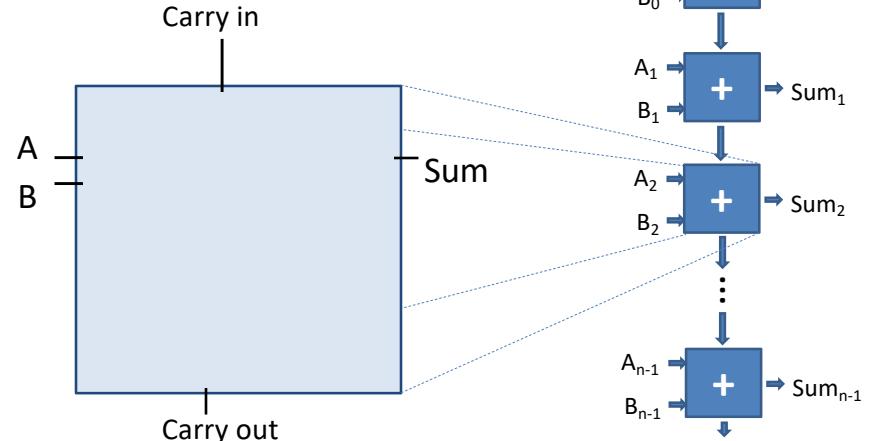
## Addition: *n*-bit *ripple-carry* adder



There are faster, more complicated ways too...


Arithmetic Logic 4

## Processor Components

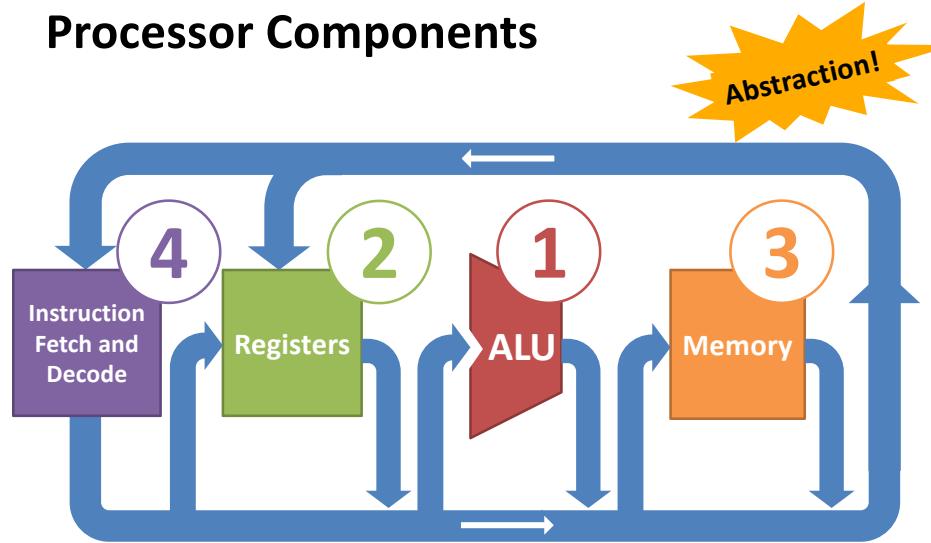

Arithmetic Logic 5

## Arithmetic Logic Unit (ALU)

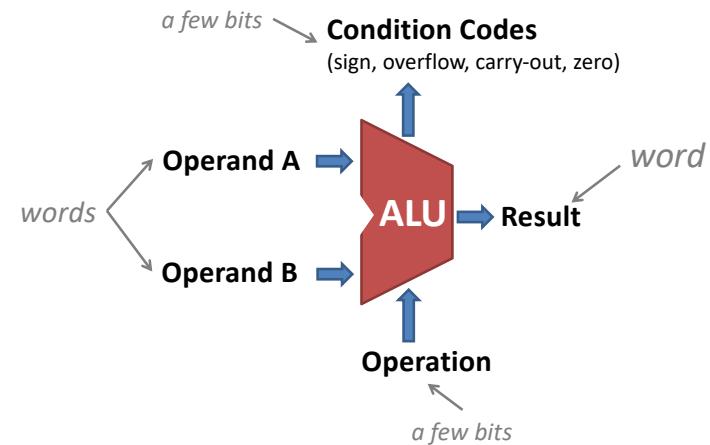


Hardware unit for arithmetic and bitwise operations.

Arithmetic Logic 6


## 1-bit ALU for bitwise operations

**ex**

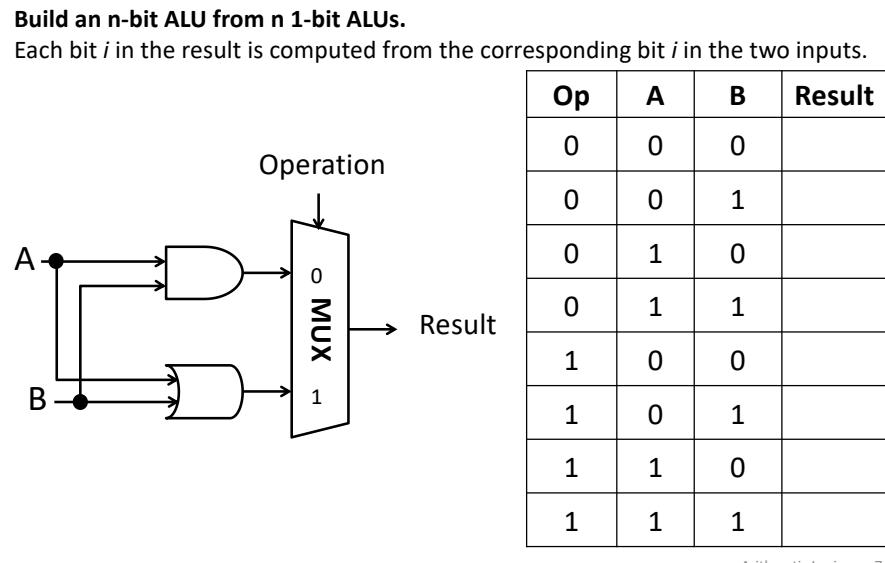

Arithmetic Logic 7



## 1-bit ALU

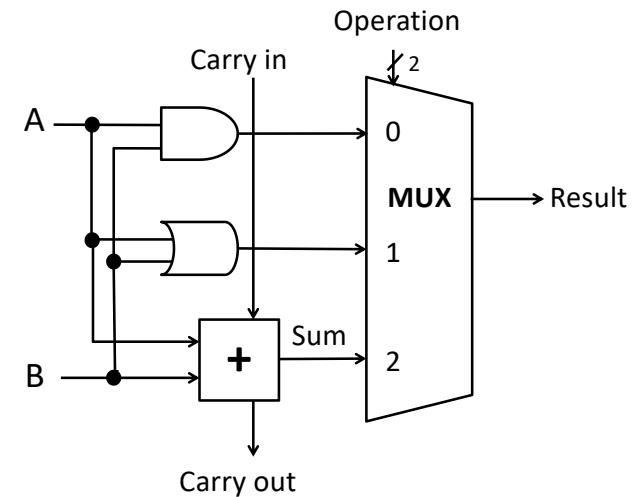

Arithmetic Logic 8

1

## n-bit ripple carry adder

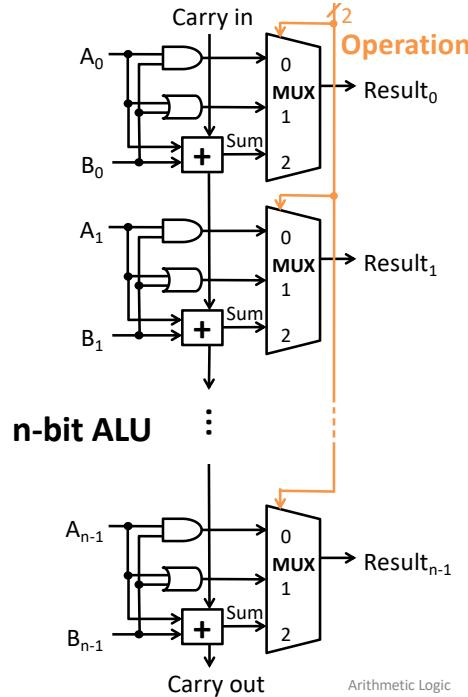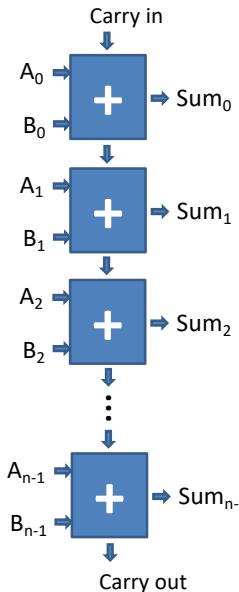

## ALU conditions

Extra ALU outputs  
describing properties of result.

**Zero Flag:** ex

1 if result is 00...0 else 0

**Sign Flag:** ex

1 if result is negative else 0


**Carry Flag:**

1 if carry out else 0

**(Signed) Overflow Flag:**


1 if signed overflow else 0

Implement these.

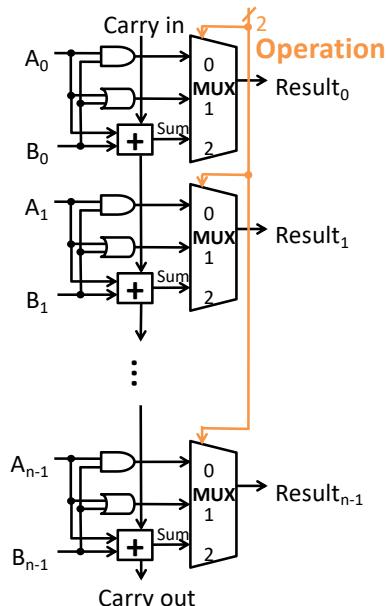
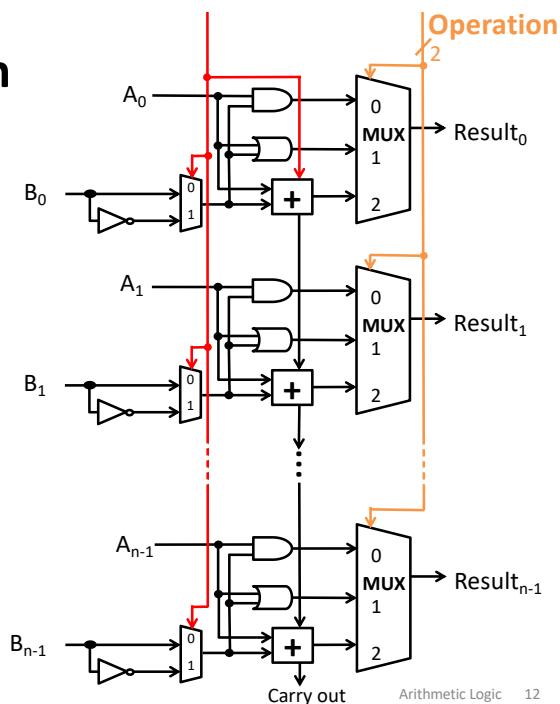
## Add subtraction

How can we control ALU inputs  
or add minimal new logic  
to compute A-B?



ex


A NAND B

A NOR B

A<B

A==B

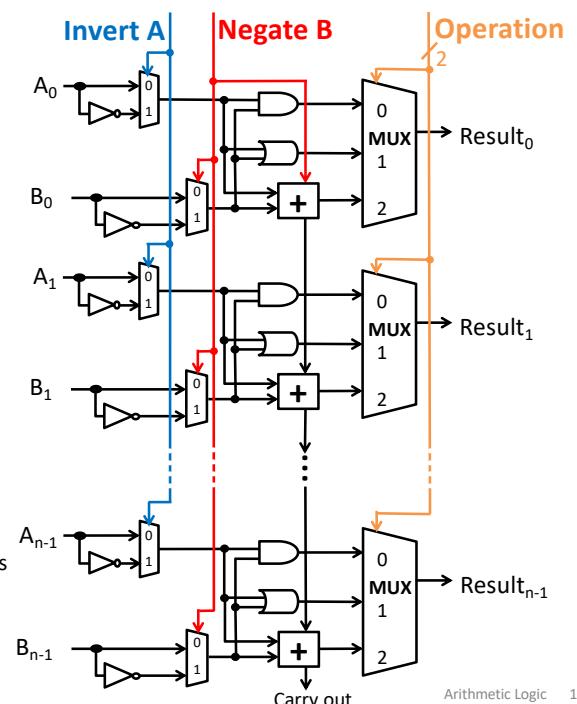How can we control ALU inputs  
or add minimal new logic  
to compute each?



# Controlling the ALU

Abstraction!

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
1100	NOR

