



Sequential Logic and State


Latch: CC-BY Rberteig@flickr



Output depends on inputs *and* stored values.
(vs. combinational logic: output depends only on inputs)


Elements to store values: latches, flip-flops, registers, memory

Processor: Data Path Components

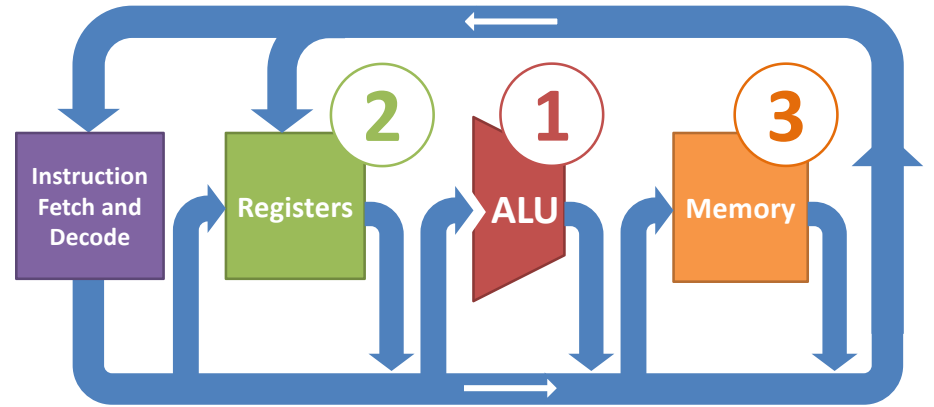


Bistable latches

 Suppose we somehow get a 1 (or a 0?) on here.




==

 


SR latch

S	R	Q	Q'	Q (stable)	Q' (stable)
0	0	0	1	0	1
0	0	1	0	1	0
1	0	?	?	1	0
0	1	?	?	0	1

 


SR latch

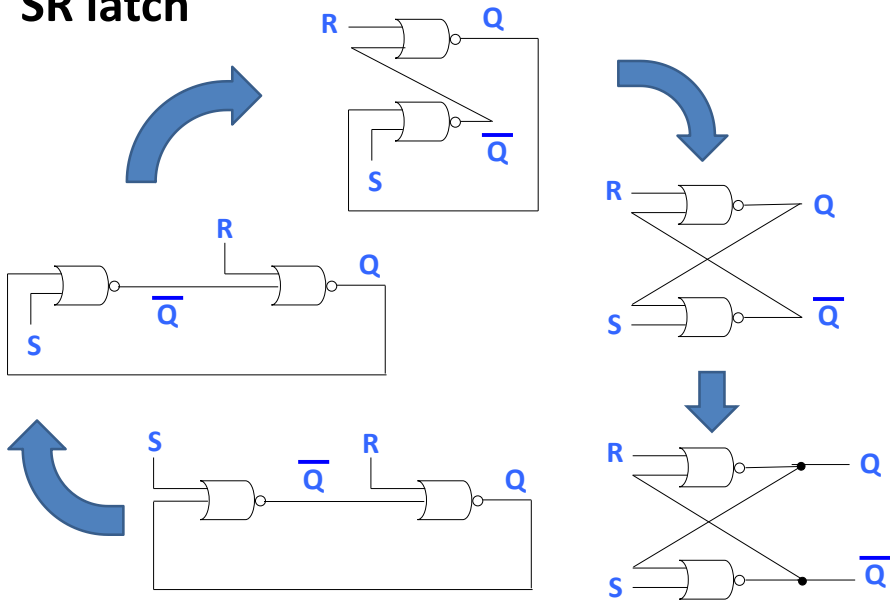

Sequential Logic 5

D latch

 

if $C = 0$, then SR latch stores current value of Q .

if $C = 1$, then D flows to Q :


if $D = 0$, then $R = 1$ and $S = 0$, $Q = 0$

if $D = 1$, then $R = 0$ and $S = 1$, $Q = 1$

Sequential Logic 6

Time matters!

ex

 


Assume Q has an initial state of 0

Sequential Logic 7

Clocks

Clock: free-running signal
with fixed cycle time = clock period = T .

 Clock frequency = $1 / \text{clock period}$




A clock controls when to update a sequential logic element's state.





Sequential Logic 8

Synchronous systems

 Inputs to state elements must be **valid** on active clock edge.




D flip-flop with falling-edge trigger

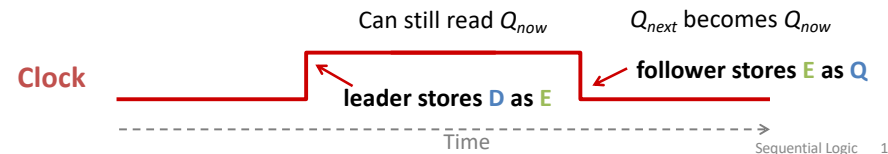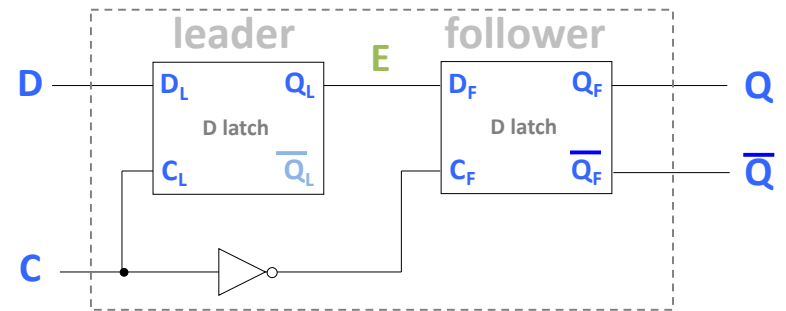


Time matters!

ex

 


Assume Q and E have an initial state of 0

Reading and writing in the same cycle

 

Assume Q is initially 0.


D flip-flop = one bit of storage

 


A 1-nybble* register

(a 4-bit hardware storage cell)

*Half a byte!

 


Register file

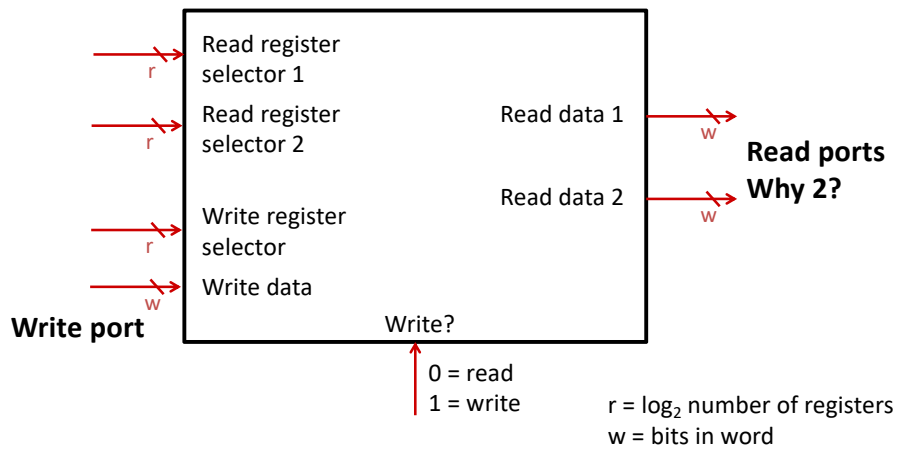


Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.


Read ports (data out)

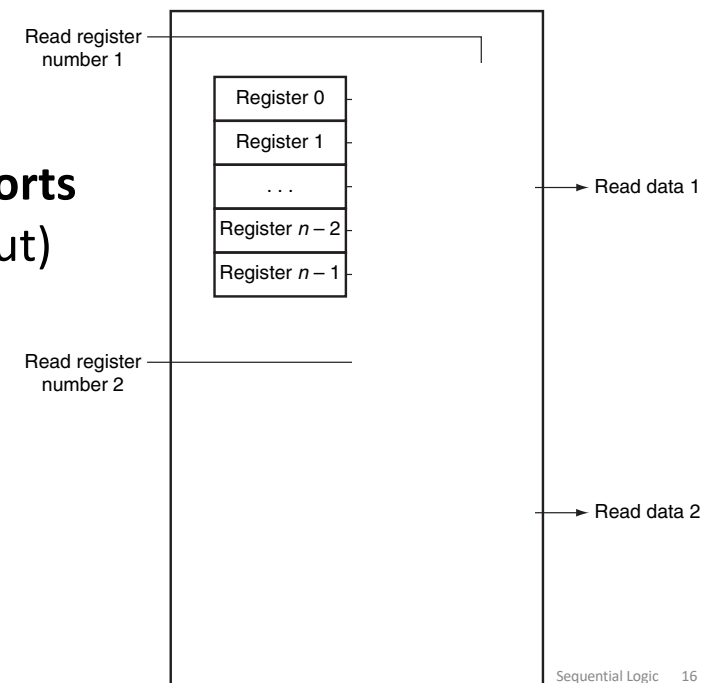

Write port (data in)

 

RAM (Random Access Memory)

 

Similar to register file, except...

16 x 4 RAM

