


CS 240 Lab 3

Combinational and Arithmetic Circuits

- **Multiplexer**
- **Decoder**
- **Adder**

Multiplexer

 A multiplexer can be thought of as a **selection circuit**, which steers a single input from a set of inputs through to the output, based on the select line.



- n select lines
- 2^n input lines
- 1 output

One of the possible 2^n inputs is chosen by the n select lines, and gated through to the output of a multiplexer. The truth table for an 8x1 MUX is:


<u>S2</u>	<u>S1</u>	<u>S0</u>	<u>Q</u>
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

Decoder


A decoder takes an n-bit binary number as an input, and asserts the corresponding numbered output from the set of 2^n outputs.

- n input/select lines
- 2^n outputs
- only one of the outputs is active at any given time, based on the value of the n select lines.


2x4 Decoder

 

Built with code detectors:

 


Half-Adder – adds two one-bit values

 

A	B	Cout	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 Full Adder – uses two half-adders and incorporates a carry-in




Cin	A	B	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = AB + (A \oplus B)\text{Cin}$$

4-bit Ripple-Carry Adder

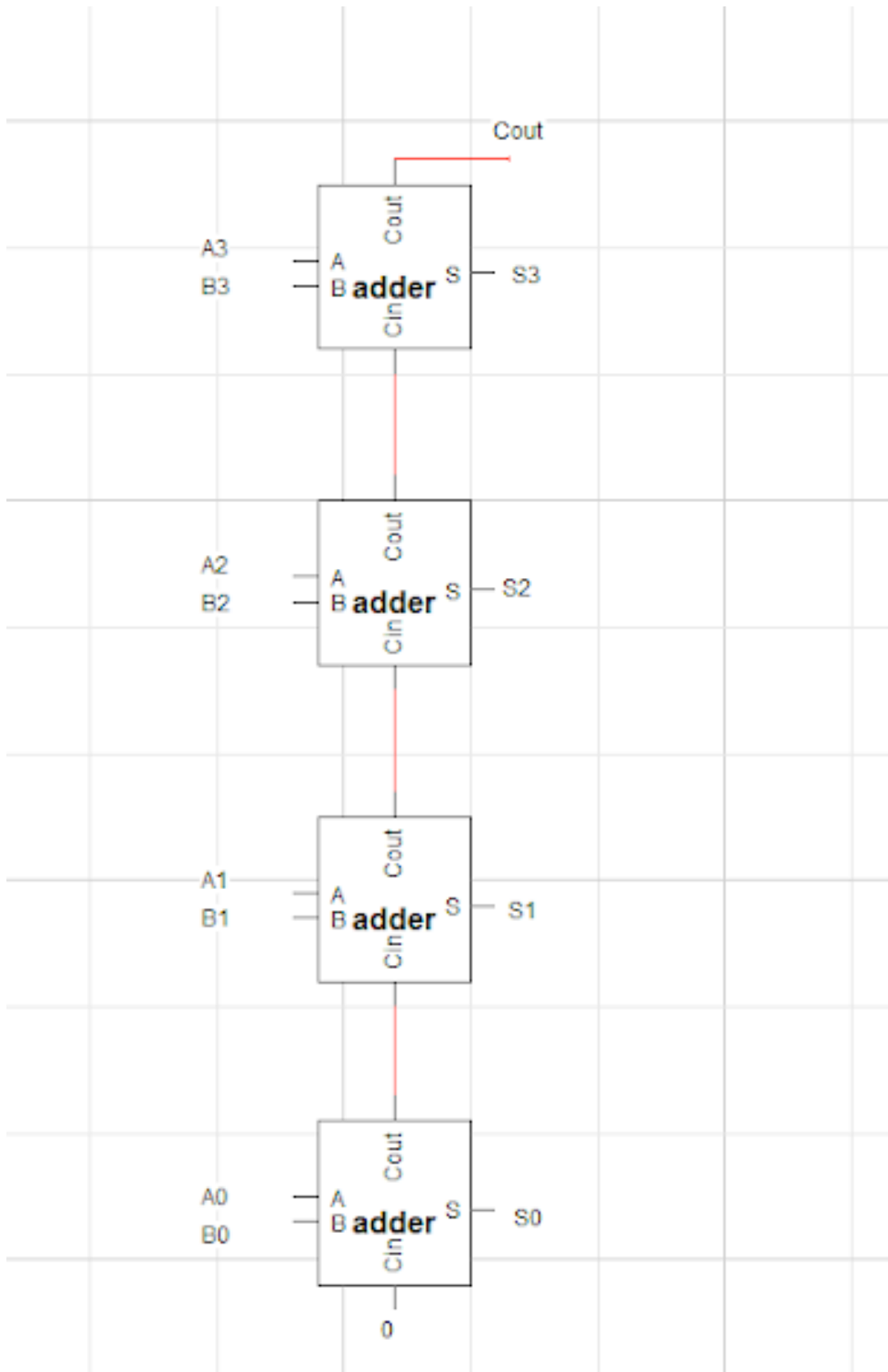

Overflow when Adding

An overflow occurs when adding two n-bit numbers if the result will not fit in n bits.

An overflow can be detected when:

- Two positive numbers added together yield a negative result, or
- Two negative numbers added together yield a positive result.

Overflow can also be detected when:

- The Cin and Cout bits to the most significant pair of bits being added are not the same.

An overflow cannot result if a positive and negative number are added.

Example: given 4 bits:

$$\begin{array}{r} 0111_2 \\ + 0001_2 \\ \hline 1000_2 \end{array} = \text{overflow} \quad \text{NOTE: there is not a carry-out!}$$

In two's complement representation, a carry-out does not indicate an overflow, as it does in unsigned representation.

Example: given 4 bits,

$$\begin{array}{r} 1001_2 (-7_{10}) \\ + 1111_2 (-1_{10}) \\ \hline 1\ 1000_2 (-8_{10}) \end{array} \quad \text{no overflow, even though there is a carry-out}$$