




CS 240
Foundations of Computer Systems



Digital Logic

Gateway to computer science

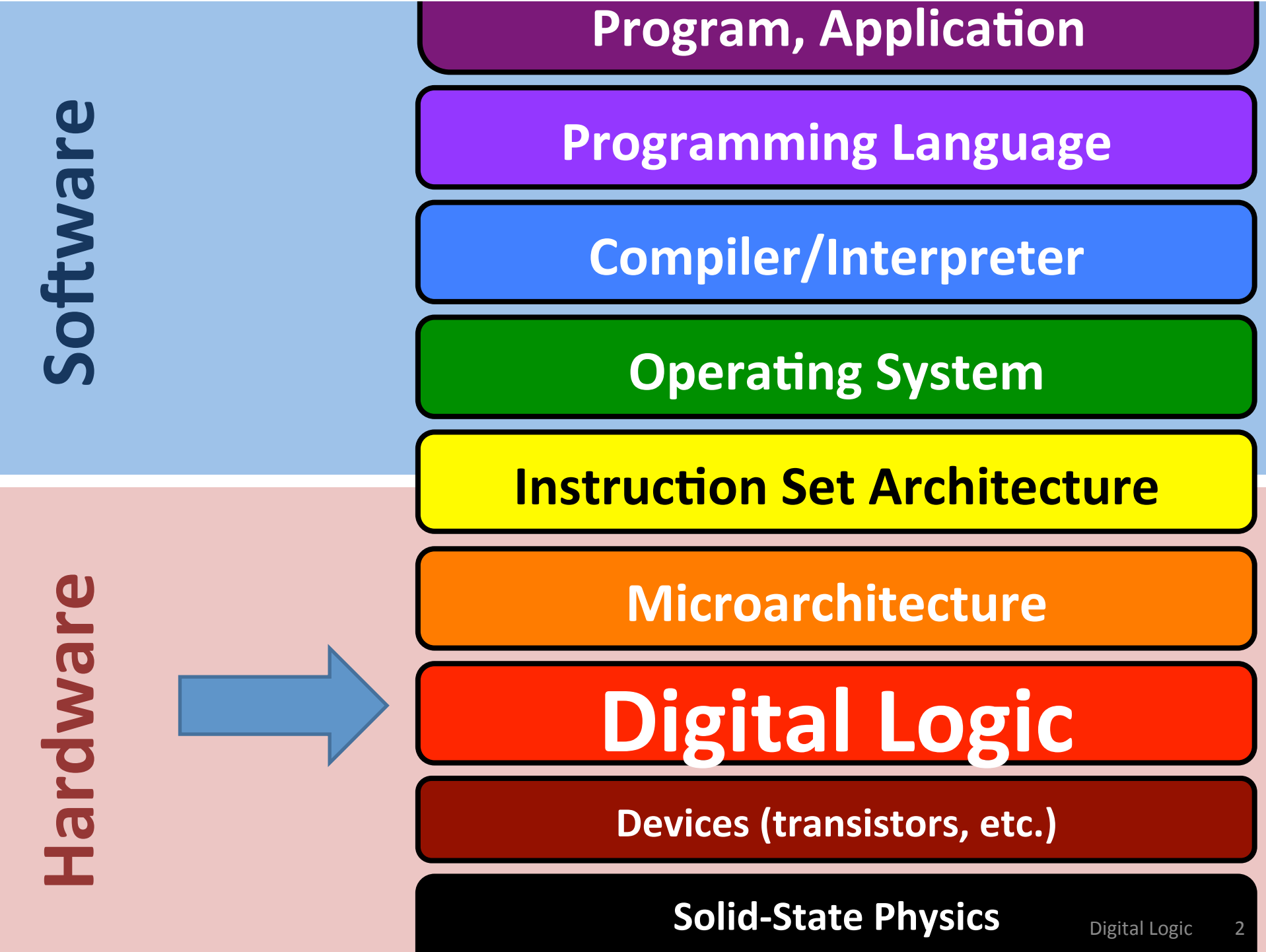transistors, gates, circuits, Boolean algebra




Digital data/computation = Boolean

Boolean value (*bit*): 0 or 1

Boolean functions (AND, OR, NOT, ...)

Electronically:

bit = high voltage vs. low voltage

 

Abstraction!




Boolean functions = logic gates, built from transistors


Transistors (more in lab)

If **Base voltage is high:**
Current may flow freely
from *Collector* to *Emitter*.

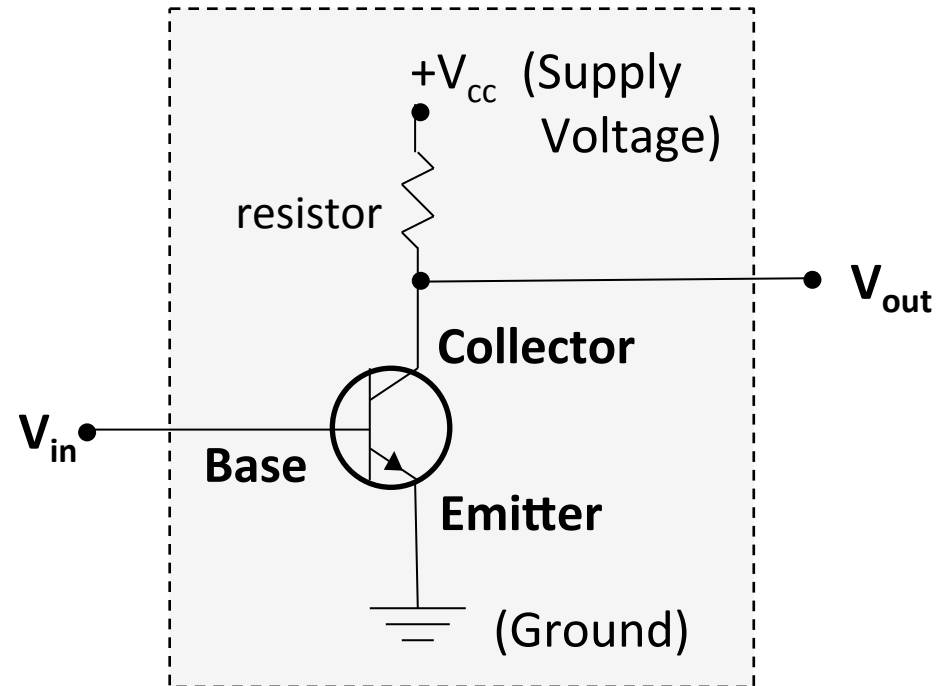If **Base voltage is low:**
Current may not flow
from *Collector* to *Emitter*.



Truth table							
V_{in}	V_{out}	=	in	out	=	in	out
low	high	=	0	1	=	F	T
high	low		1	0		T	F

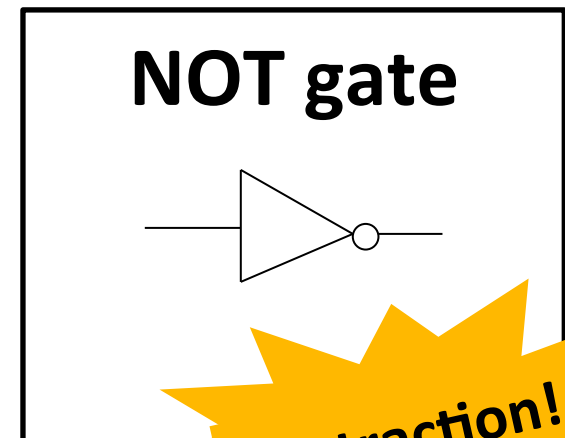

Abstraction!


Digital Logic Gates

Abstraction!

ex



Tiny electronic devices that compute basic Boolean functions.

NOT

 


V_{in}	V_{out}
0	1
1	0

	V_2	
V_1	0	1
0		
1		

  


Integrated Circuits (1950s -)


Early (first?) transistor

 


Chip

 


Wafer

 


Small integrated circuit

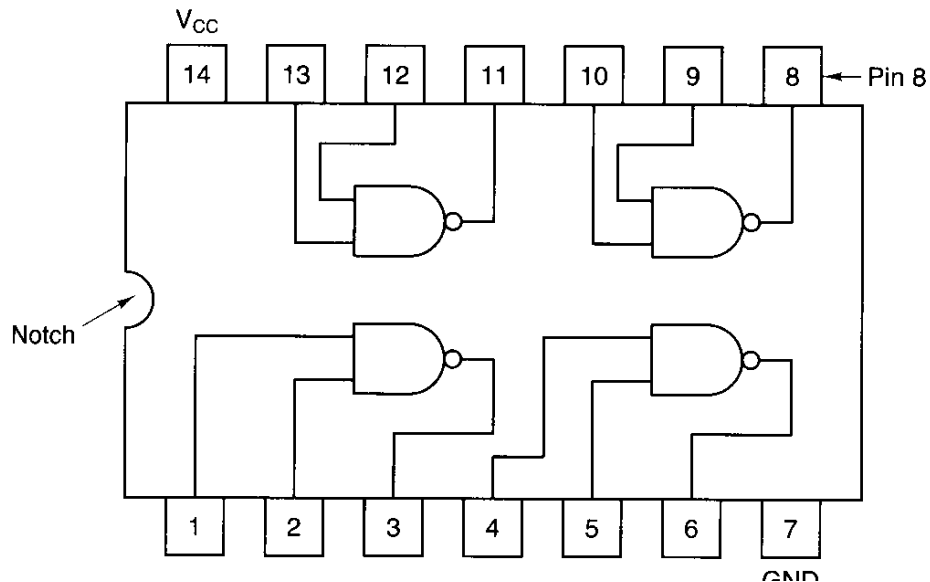

 
Five basic gates: define with truth tables




NOT	
0	1
1	0

 


NAND	0	1
0	1	1
1	1	0

 

NOR	0	1
0		
1		

 

AND	0	1
0		
1		

 


OR	0	1
0		
1		


Simple Boolean Expressions

for combinational logic

 
inputs = *variables*
wires = *expressions*
gates = *operators/functions*
circuits = *functions*




wire: identity

 

NOT: inverse or complement

 

OR = Boolean sum

 

AND = Boolean product

Orange forms are most convenient in text editors.

A **boolean literal** is a variable or its complement.

E.g., A, A', B, B' are literal boolean expressions, but $A + B, AB,$ and $(AB)'$ are not.

General Boolean Expressions

Boolean expressions are generated by this context free grammar:

$$BE ::= \textit{variable} \mid 0 \mid 1 \mid BE' \mid BE + BE \mid BE * BE \mid (BE)$$

Precedence: (...) > NOT > AND > OR


E.g., $A'B + CD'$ means $((A')*B) + (C*(D'))$

Circuits & Boolean Expressions



Given input variables, **circuits** specify outputs as functions of inputs using wires & gates.

 - Crossed wires touch *only if* there is a dot.
- T intersections don't need a dot.



Each output can be translated to a boolean expression in terms of the input variables.

What is a boolean expression for Q in the above circuit?

What is the truth table for Q in the example circuit?

A	B	C	Q



Translation Exercise

Connect gates to implement these functions. Check with truth tables.

Use a direct translation -- it is straightforward and bidirectional.

$$F = (\overline{A}\overline{B} + C)D$$

$$Z = \overline{W} + (X + \overline{W}Y)$$



Sum-of-products Form

A **sum-of-product** form is a boolean expression for a circuit output that is expressed as a sum of **minterms**, one for each row whose output is 1.

A **minterm** for a row is a product of literals (variables or their negations) whose value is 1 for that row.

What is the sum-of-products expression for this truth table?

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1



Product-of-sums Form

A **product-of-sums** form is a boolean expression for a circuit output that is expressed as a product of **maxterms**, one for each row whose output is 0.

A **maxterm** for a row is a sum of literals (variable or their negations) whose value is 0 for that row.

What is the sum-of-product expression for this truth table?

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Boolean Algebra: Simple laws

Boolean algebra laws can be proven by truth tables and used to show equivalences between boolean expressions.

For all laws in one place, see the [Boolean Laws Reference Sheet](#)

Name of Law / Theorem	Form	Equivalent/Dual form (interchange AND and OR, and 0 and 1)
Involution (or double negation)	$\overline{\overline{A}} = A$	none
Identity	$0+A = A$	$1*A = A$
Inverse (or Complements)	$A\overline{A} = 0$	$A+\overline{A} = 1$
Commutativity	$A+B = B+A$	$AB = BA$
Associativity	$(AB)C = A(BC)$	$(A+B)+C = A+(B+C)$
Idempotent	$A+A = A$	$AA = A$
Null (or Null Element)	$0*A = 0$ (the Zero Law)	$1+A = 1$ (the One Law)

Boolean Algebra: Distributivity

Distributive	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
---------------------	---------------------------	----------------------

Boolean Algebra: Absorption

Absorption 1 (Covering)	$A + AB = A$	$A(A + B) = A$
Absorption 2	$A + \bar{A}B = A + B$	$A(\bar{A} + B) = AB$


Boolean Algebra: DeMorgan's laws

DeMorgan's	$\overline{A+B+C+\dots} = \overline{A} \overline{B} \overline{C} \dots$	$\overline{\overline{A+B+C+\dots}} = A B C \dots$
------------	---	---

Boolean Algebra: Some Other Laws

Combining	$AB + A\bar{B} = A$	$(A + B)(A + \bar{B}) = A$
Consensus	$AB + \bar{A}C + BC = AB + \bar{A}C$	$(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$

XOR: Exclusive OR

 

Output = 1 if exactly one input = 1.

Truth table:


Build from earlier gates:



XOR	0	1
0		
1		


Often used as a one-bit comparator.

NAND is *universal*

 

All Boolean functions can be implemented using only NANDs.
Build NOT, AND, OR, NOR, using only NAND gates.

NOR is also *universal*

 


All Boolean functions can also be implemented using only NORs. Build NAND using only NOR gates; then since NAND is universal, NOR must be too! (Why?)



Larger gates

 
Build a 4-input AND gate using any number of 2-input gates.





Circuit simplification

 Is there a simpler circuit that performs the same function?




Start with an equivalent Boolean expression, then simplify with algebra.

$$F(A, B, C) =$$

Check the answer with a truth table.

Circuit derivation: *code detectors*

 some NOT gates followed by multi-input AND gate = **code detector**:
recognizes exactly one input code.



Design a 4-input code detector to output 1 if ABCD = 1001, and 0 otherwise.

A _____
B _____
C _____
D _____

Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111)
and reject all others. (accept = 1, reject = 0)



Circuit derivation: *sum-of-products* form

logical sum (OR)

of products (AND)

of inputs or their complements (NOT)

Draw the truth table and design a sum-of-products circuit for a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others.

How are the truth table and the sum-of-products circuit related?



Voting machines

A majority circuit outputs 1 if and only if a majority of its inputs equal 1.

Design a majority circuit for three inputs. Use a sum of products.

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Triply redundant computers in spacecraft

- Space program also hastened Integrated Circuits.



Computers

- Manual calculations
- powered all early US **space** missions.
- Facilitated transition to digital computers.

Katherine Johnson

- Supported Mercury, Apollo, Space Shuttle, ...





Mary Jackson

- NASA's first black female engineer
- Studied air around airplane via wind tunnel experiments.

Dorothy Vaughan

  - First black supervisor within NACA
- Early self-taught FORTRAN programmer for NASA move to digital computers.



Early pioneers in reliable computing



Katherine Johnson

- Calculated first US human space flight trajectories
- Mercury, Apollo 11, Space Shuttle, ...
- Reputation for accuracy in manual calculations, verified early code
- Called to verify results of code for launch calculations for first US human in orbit
- Backup calculations helped save Apollo 13
- Presidential Medal of Freedom 2015




Margaret Hamilton

- Led software team for Apollo 11 Guidance Computer, averted mission abort on first moon landing.
- Coined “software engineering”, developed techniques for correctness and reliability.
- Presidential Medal of Freedom 2016

Apollo 11 code print-out



 Wellesley Connection: Mary Allen Wilkes '59



Created LAP operating system at MIT Lincoln Labs for Wesley A. Clark's LINC computer, widely regarded as the first personal computer (designed for interactive use in bio labs). Work done 1961—1965.



Created first interactive keyboard-based text editor on 256 character display. LINC had only 2K 12-bit words; (parts of) editor code fit in 1K section; document in other 1K.

In 1965, she developed LAP6 with LINC in Baltimore living room. First home PC user!



Early versions of LAP developed using LINC simulator on MIT TX2 compute, famous for GUI/PL work done by Ivan and Bert Sutherland at MIT.



Later earned Harvard law degree and headed Economic Crime and Consumer Protection Division in Middlesex (MA) County District Attorney's office.