



# Combinational Logic

Karnaugh maps

Building blocks: encoders, decoders, multiplexers

**Abstraction!**

But first...

## Recall: *sum of products*

logical sum (OR)

of products (AND)

of inputs or their complements (NOT).

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Construct with:


- 1 code detector per 1-valued output row
- 1 large OR of all code detector outputs

Is it minimal?
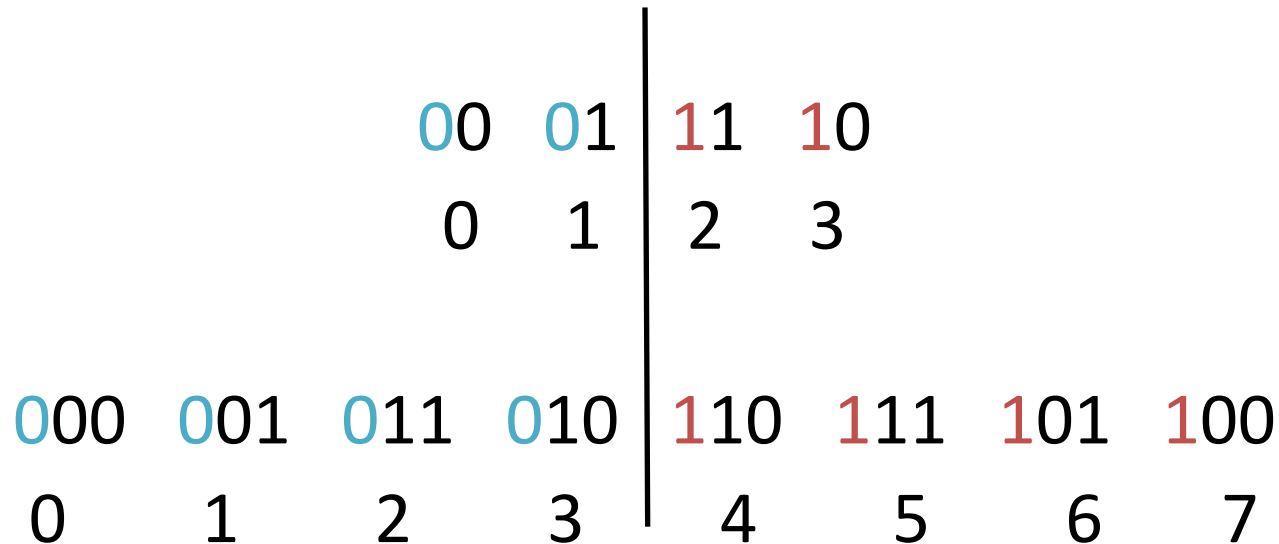
# Gray Codes = reflected binary codes

Alternate binary encoding

designed for electromechanical switches and counting.



How many bits change when incrementing?



# Karnaugh Maps: find (minimal) sums of products

A	B	C	D	F(A, B, C, D)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		CD			
		gray code			
		order →			
		00	01	11	10
AB ↓	00	0	0	0	0
	01	0	0	0	1
	11	1	1	0	1
	10	1	1	1	1

1. Cover exactly the 1s by drawing a (minimum) number of maximally sized rectangles whose dimensions (in cells) are powers of 2. (They may overlap or wrap around!)
2. For each rectangle, make a *product* of the inputs (or complements) that are 1 for all cells in the rectangle. (*minterms*)
3. Take the *sum* of these products.



# Karnaugh Maps and Wrapping

Blocks of 1s in Karnaugh maps can wrap around sides and even 4 corners.

Give the minimal sum-of-products for the Karnaugh map to the left.

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	0
	11	1	0	0	1
	10	1	0	0	1

The grouping and ordering of variables in a Karnaugh map doesn't matter, but the **AB/CD** ordering is easier to read from a truth table.

Convince yourself that the **AC/DB** table is equivalent to the **AB/CD** table and has the same sum-of-products expression. In this particular AC/DB table, no wrapping is required for the rectangles!

		DB			
		00	01	11	10
AC	00	1			
	01	1			
	11	1	1		
	10	1	1		



# Karnaugh Maps and Ambiguity

The minimal sum-of-products expression for a Karnaugh map may not be unique.

Ambiguity is introduced when an arbitrary choice needs to be made.

An example of ambiguity is this Karnaugh map. Give four different minimal sum-of-product expressions for this map


		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	1	0	1
	11	1	1	1	1
	10	0	0	0	0

# Voting again with Karnaugh Maps



A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
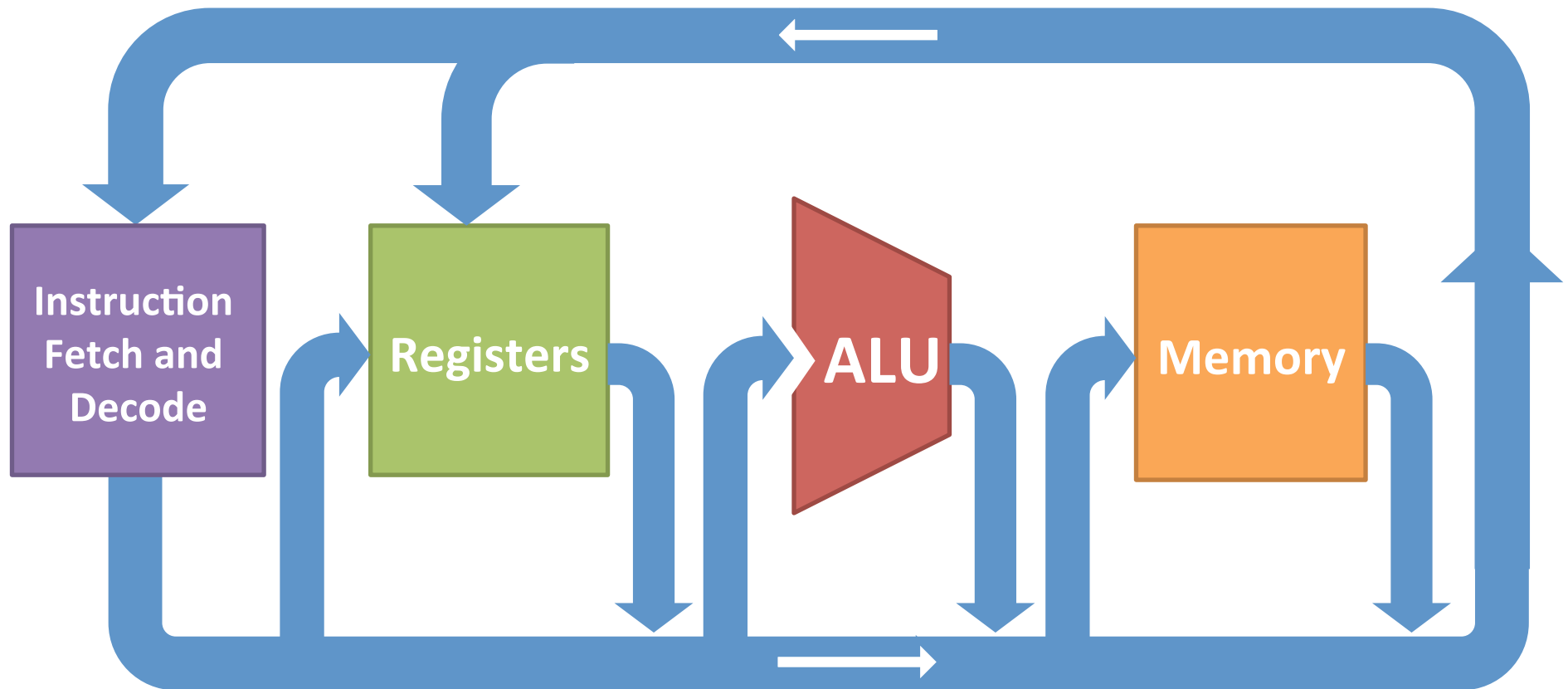
# Goal for next 2 weeks: **Simple Processor**





# Toolbox: Building Blocks



Microarchitecture

Processor datapath

Instruction Decoder  
Arithmetic Logic Unit

Memory

Digital Logic

Adders  
Multiplexers  
Demultiplexers  
Encoders  
Decoders

Registers

Flip-Flops  
Latches

Gates



Devices (transistors,  
etc.)





# Decoders

Decodes input number, asserts corresponding output.

$n$ -bit input (an unsigned number)


$2^n$  outputs

Built with code detectors.

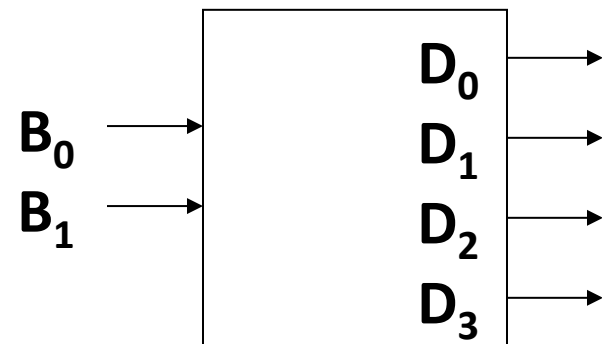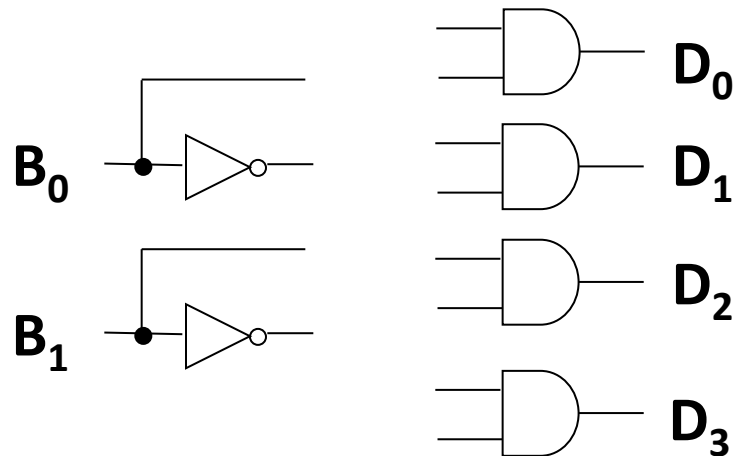

# Multiplexers

Select one of several inputs as output.

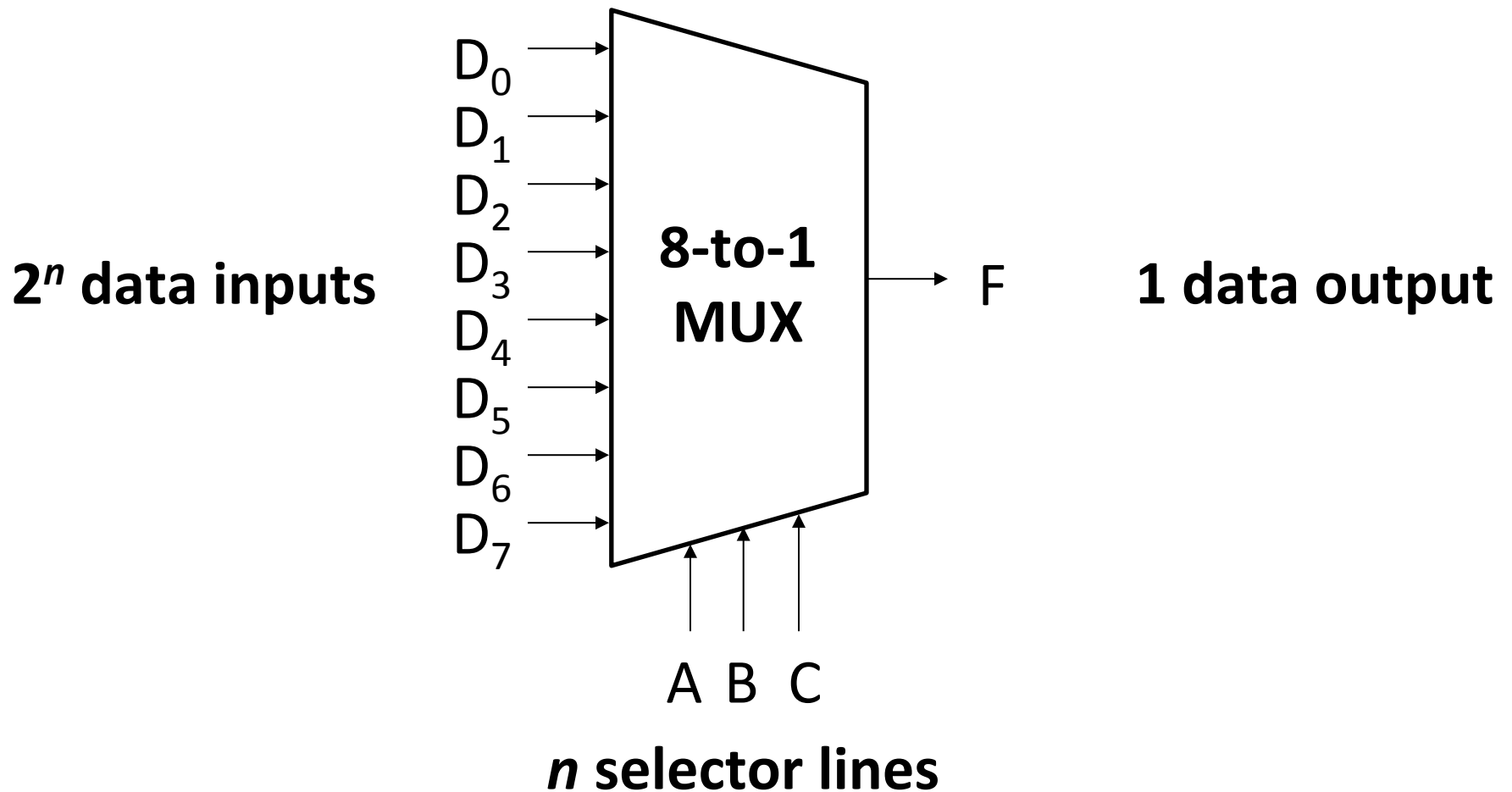




# Build a 2-to-1 MUX from gates

If  $S=0$ , then  $F=D_0$ .


If  $S=1$ , then  $F=D_1$ .

1. Construct the truth table.

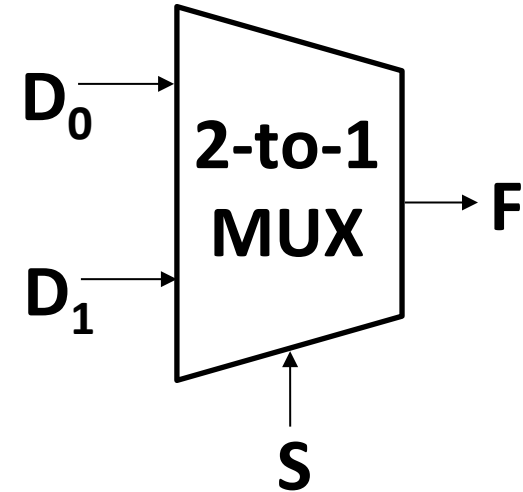


2. Build the circuit.

# 8-to-1 MUX

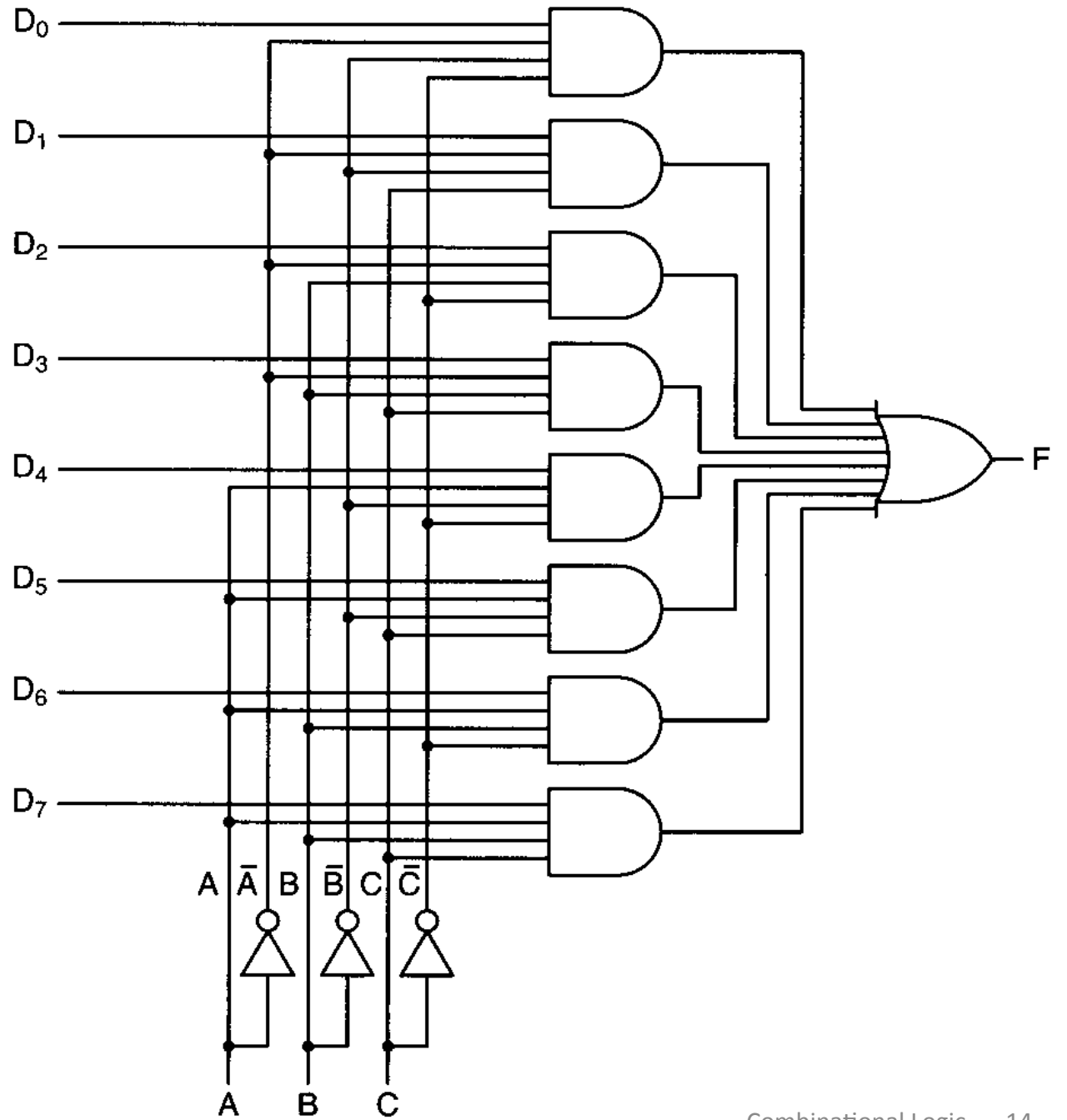

Costume idea: MUX OX

# MUX + voltage source = truth table

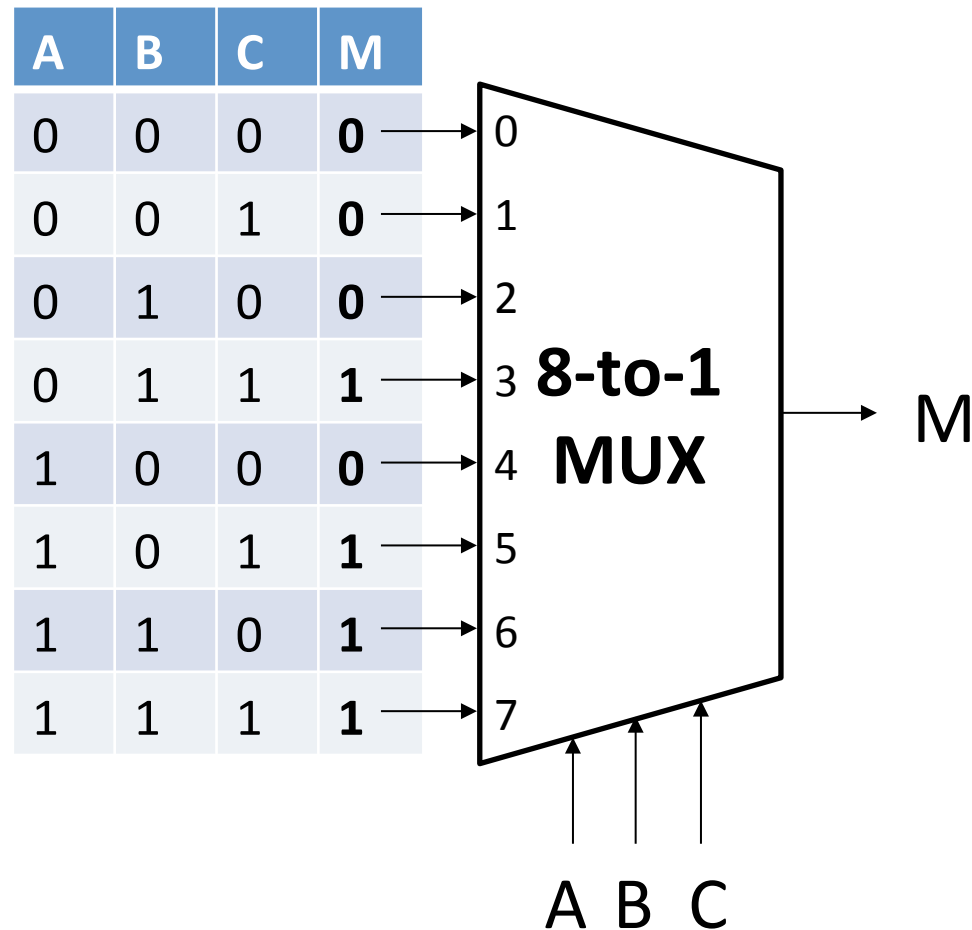

# Buses and Logic Arrays

A bus is a collection of data lines treated as a single logical signal.

= fixed-width value

Array of logic elements applies same operation to each bit in a bus.

= bitwise operator

