

About how many total hours did you spend actively working on this assignment? _____

Q1 [4 points] Time spent on Q1: _____

F1 =

F2 =

A	B	C		F1	F2
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Q2 [6 points] Time spent on Q2: _____

Draw your three circuits here:

Q3 [5 points] *Time spent on Q3:* _____

a [2] $\text{bexp}_3 =$

b [3] circuit diagram:

Q4 [5 points] *Time spent on Q4:* _____

a [2] $\text{bexp}_4 =$

b [3] circuit diagram:

Q5 [10 points] *Time spent on Q5:* _____

Truth table for parts a [2] and c [2]

A	B	AB	A'B'	AB + A'B'	bexp_{5b}	AB + bexp_{5b}
0	0					
0	1					
1	0					
1	1					

Below, show steps in deriving the answer expressions

b [1] $\text{bexp}_{5b} =$

d [2] $\text{bexp}_{5d} =$

e [3] $\text{bexp}_{5e} =$

Q7 [8 points] *Time spent on Q7:* _____

Q7a [4] Express XOR in terms of 2-input NAND gates.

Time spent on Q7a:

Q7b [4] Express XOR in terms of 2-input NOR gates.

Time spent on Q7b:
