



# Combinational Logic

Karnaugh maps

Building blocks: encoders, decoders,  
multiplexers



But first...

# Recall: *sum of products*

logical sum (OR)

of products (AND)

of inputs or their complements (NOT).

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Construct with:

- 1 code detector per 1-valued output row
- 1 large OR of all code detector outputs

Is it minimal?



# Karnaugh Maps:

find (minimal) sums of products



Truth table:

A	B	C	D	F(A, B, C, D)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
0	1	1	1	0
<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
1	1	1	1	0

K-map:

gray code

	order →	00	01	11	10
AB ↓	00	0	0	0	0
01	0	0	0	1	
11	1	1	0	1	
10	1	1	1	1	

To build a k-map (best for functions of 2-4 inputs)

1. Split the inputs, half as the header row and half as the header column.
2. Put the input *values* as products in **gray code order**.
3. Fill in each cell based on the truth table.

# Karnaugh Maps:

find (minimal) sums of products



Truth table:

A	B	C	D	F(A, B, C, D)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
0	1	1	1	0
<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
1	1	1	1	0

K-map:

gray code

	order →	00	01	11	10
AB ↓	00	0	0	0	0
01	0	0	0	0	1
11	1	1	1	0	1
10	1	1	1	1	1

To derive a minimal expression from a k-map

1. Cover **exactly** the **1s** by drawing a (minimum) number of (maximally sized) rectangles whose dimensions are **powers of 2**.
  - They may overlap or wrap around!
2. For each, make a **product** of the inputs (or complements) that are 1 for all cells in the rectangle. (*minterms*)
3. Take the **sum** of these products.

# Karnaugh Maps: find (minimal) sums of products



Truth table:

A	B	C	D	F(A, B, C, D)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
0	1	1	1	0
<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
1	1	1	1	0

K-map:

$$AC' + AB' + BCD'$$

gray code

	order →	00	01	11	10
AB ↓	00	0	0	0	0
01	0	0	0	0	1
11	1	1	1	0	1
10	1	1	1	1	1

To convert to algebra:

1. Any literals that *change* are excluded from the product.
2. A literal that is always 1 should be included as is.
3. A literal that is always 0 should be negated and included.
4. Take the **sum** of these products.

# Karnaugh Maps and Wrapping



Blocks of 1s in Karnaugh maps can wrap around sides and even 4 corners.

Give the minimal sum-of-products for the Karnaugh map to the left.

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	0
	11	1	0	0	1
	10	1	0	0	1

---

The grouping and ordering of variables in a Karnaugh map doesn't matter, but the **AB/CD** ordering is easier to read from a truth table.

Convince yourself that the **AC/DB** table is equivalent to the **AB/CD** table and has the same sum-of-products expression. In this particular AC/DB table, no wrapping is required for the rectangles!

		DB			
		00	01	11	10
AC	00	1			
	01	1			
	11	1	1		
	10	1	1		

# Karnaugh Maps and Ambiguity

The minimal sum-of-products expression for a Karnaugh map may not be unique.

Ambiguity is introduced when an arbitrary choice needs to be made.

An example of ambiguity is this Karnaugh map. Give four different minimal sum-of-product expressions for this map.

		<b>CD</b>			
		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>AB</b>	<b>00</b>	1	1	1	1
	<b>01</b>	1	1	0	1
	<b>11</b>	1	1	1	1
	<b>10</b>	0	0	0	0






# Voting again with Karnaugh Maps



A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
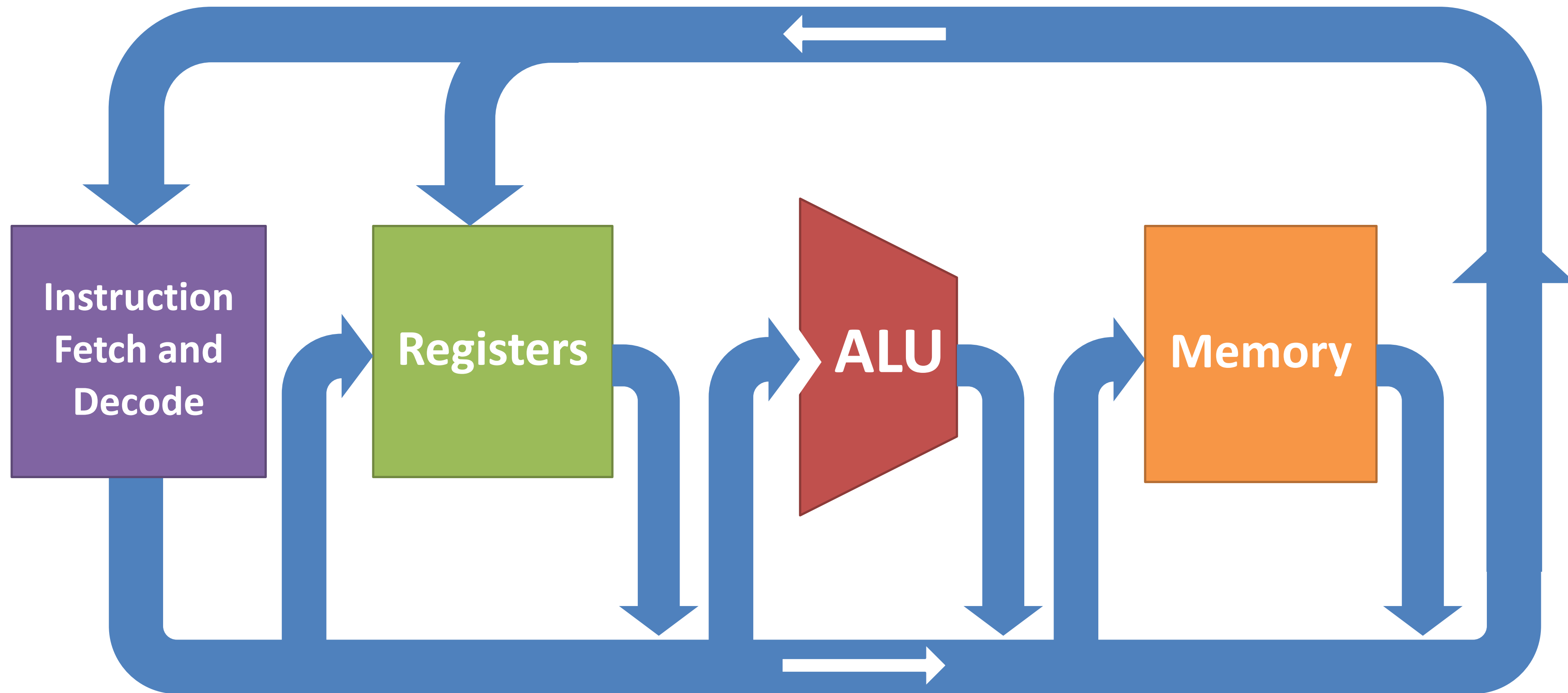
# Goal for the next 3 weeks: Simple Processor



# Toolbox: Building Blocks

Microarchitecture

Digital Logic

Devices (transistors, etc.)

## Processor datapath

Instruction Decoder

Arithmetic Logic Unit

Adders

Multiplexers

Demultiplexers

Encoders

Decoders


Gates

Memory

Registers

Flip-Flops

Latches

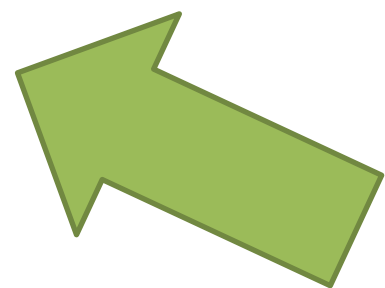

# Decoders


ex

Decodes input number, asserts corresponding output.


$n$ -bit input (an unsigned number)

$2^n$  outputs


Built with code detectors.

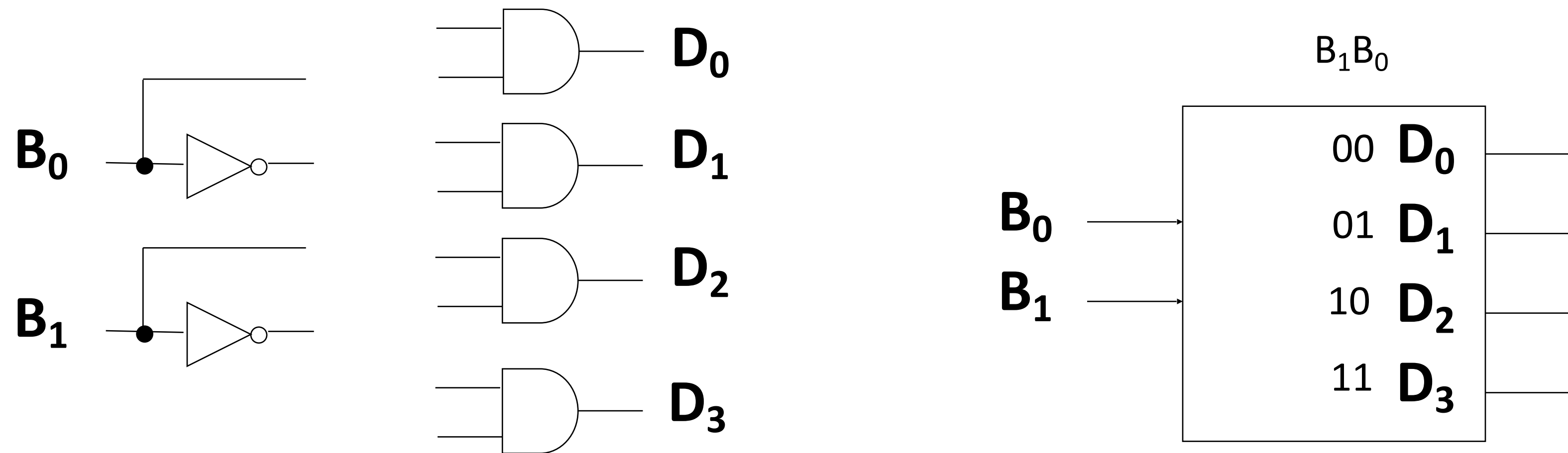

# 3-bit decoder

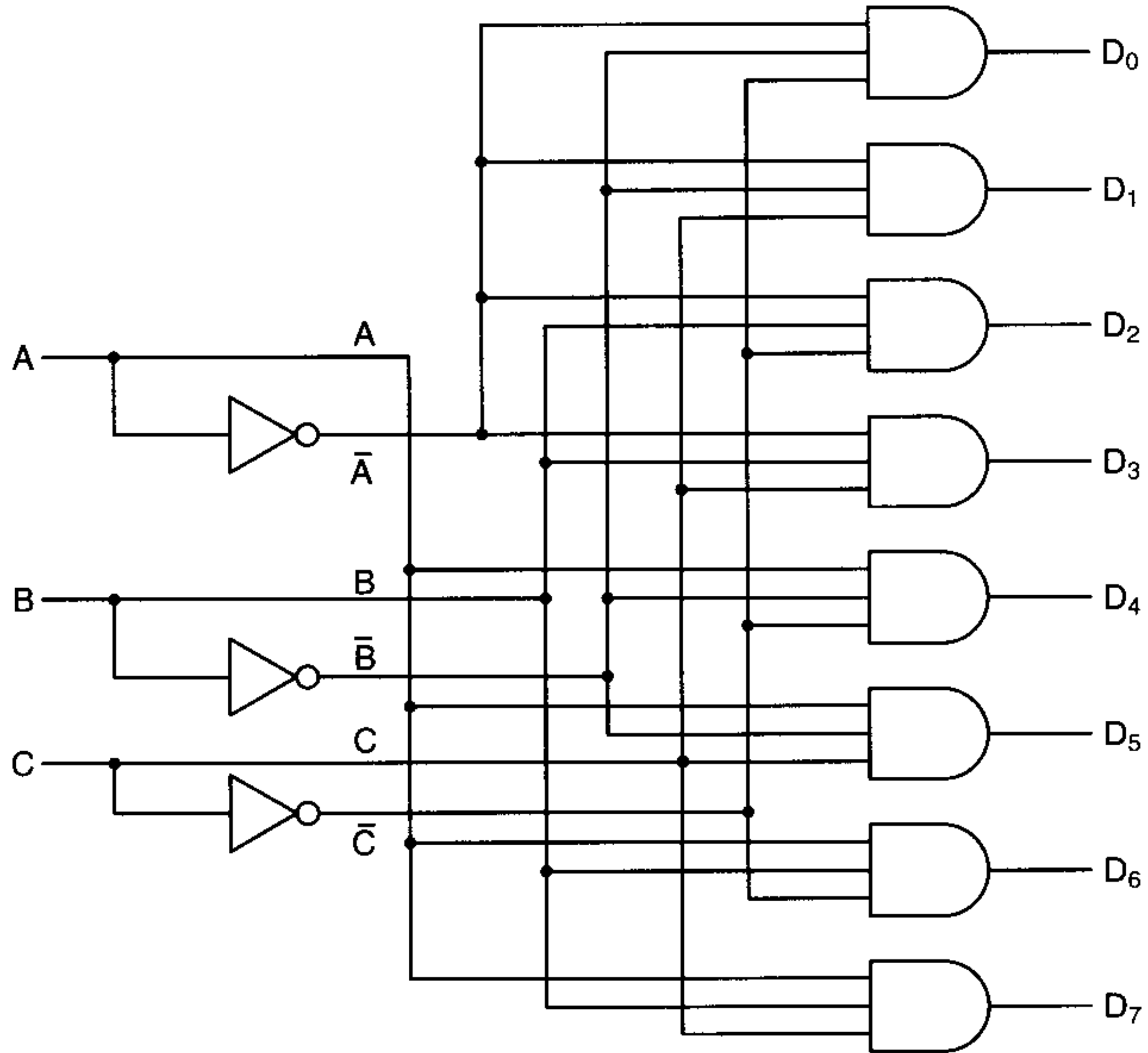
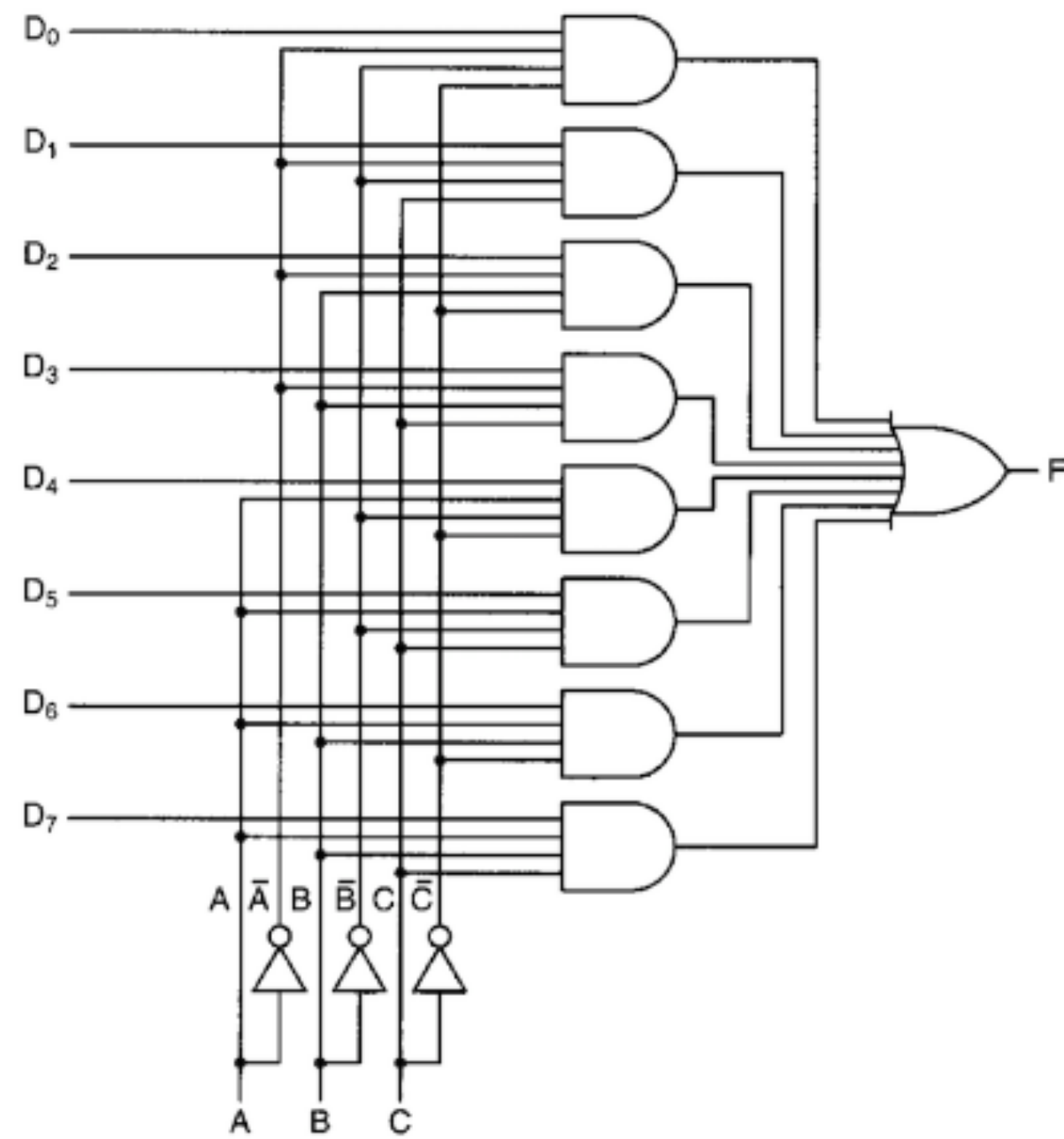
# Warmup question: is the following a *decoder* or a *multiplexer*?




Decoder

Multiplexer (mux)


None of the above
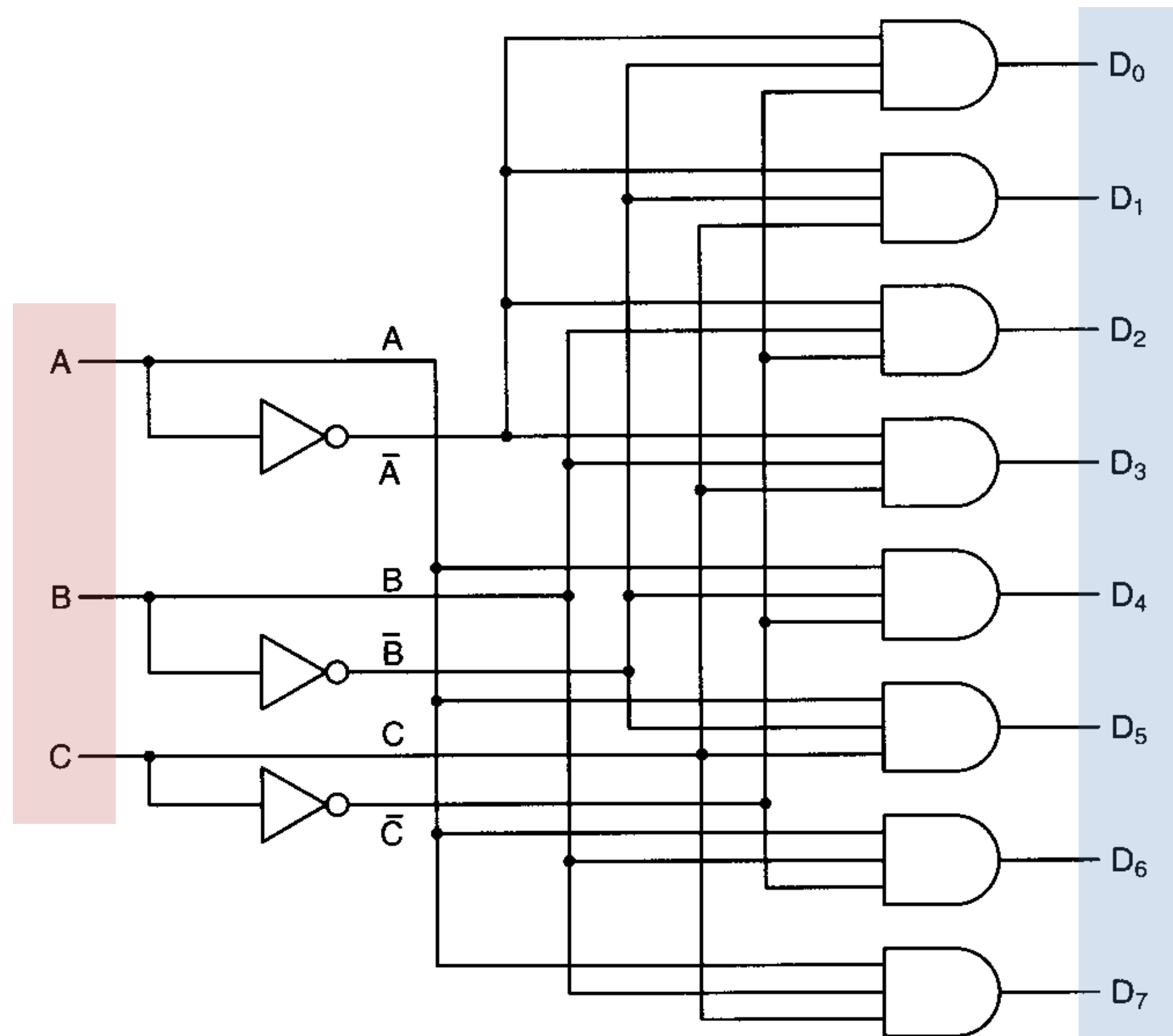
# Recall: decoders and multiplexers


A decoder has an  $n$ -bit input and  $2^n$  outputs. Only 1 output active at once.



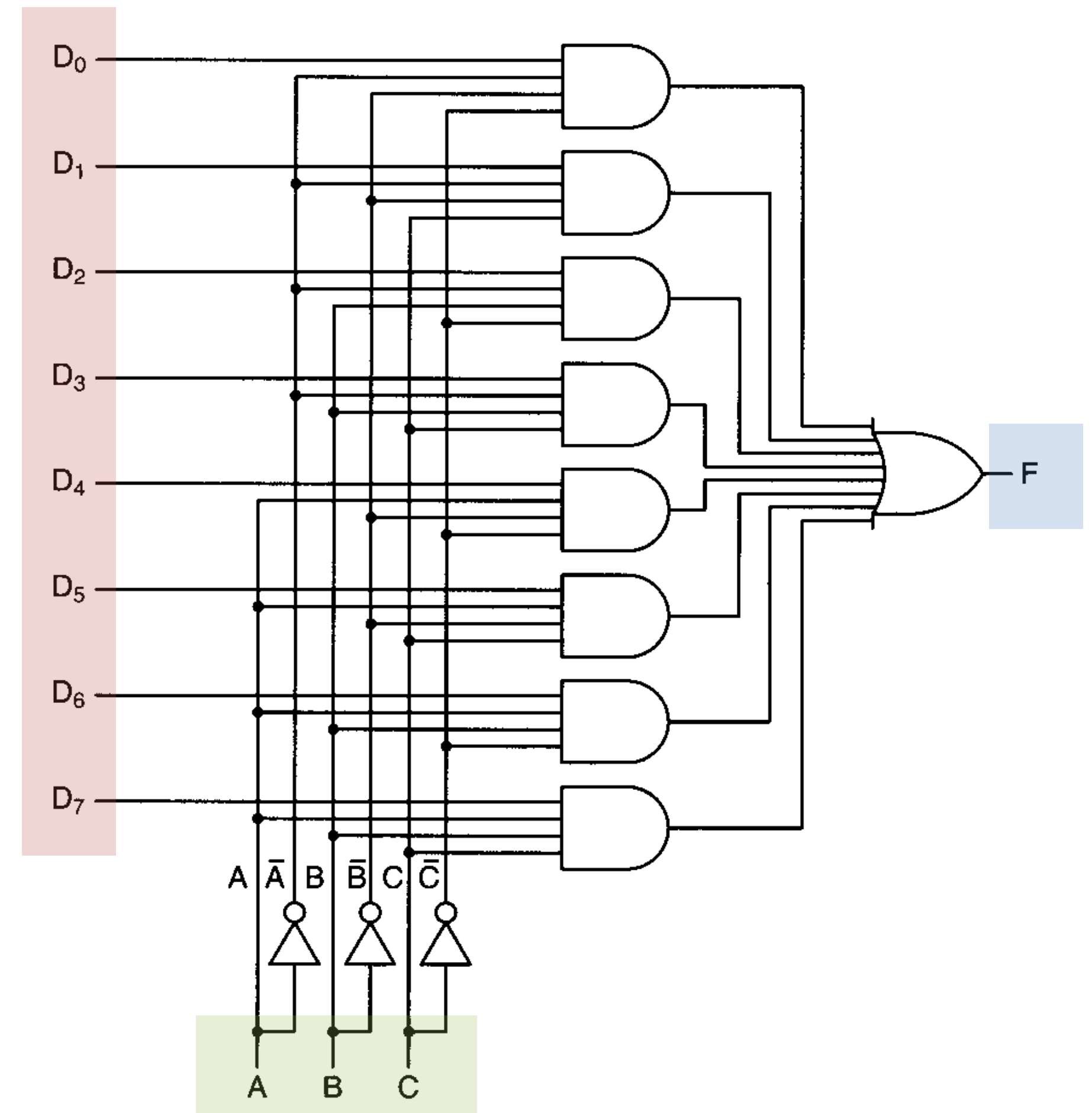A multiplexer has  $2^n$  inputs,  $n$  selector wires, and 1 output.




# 8-to-1 MUX

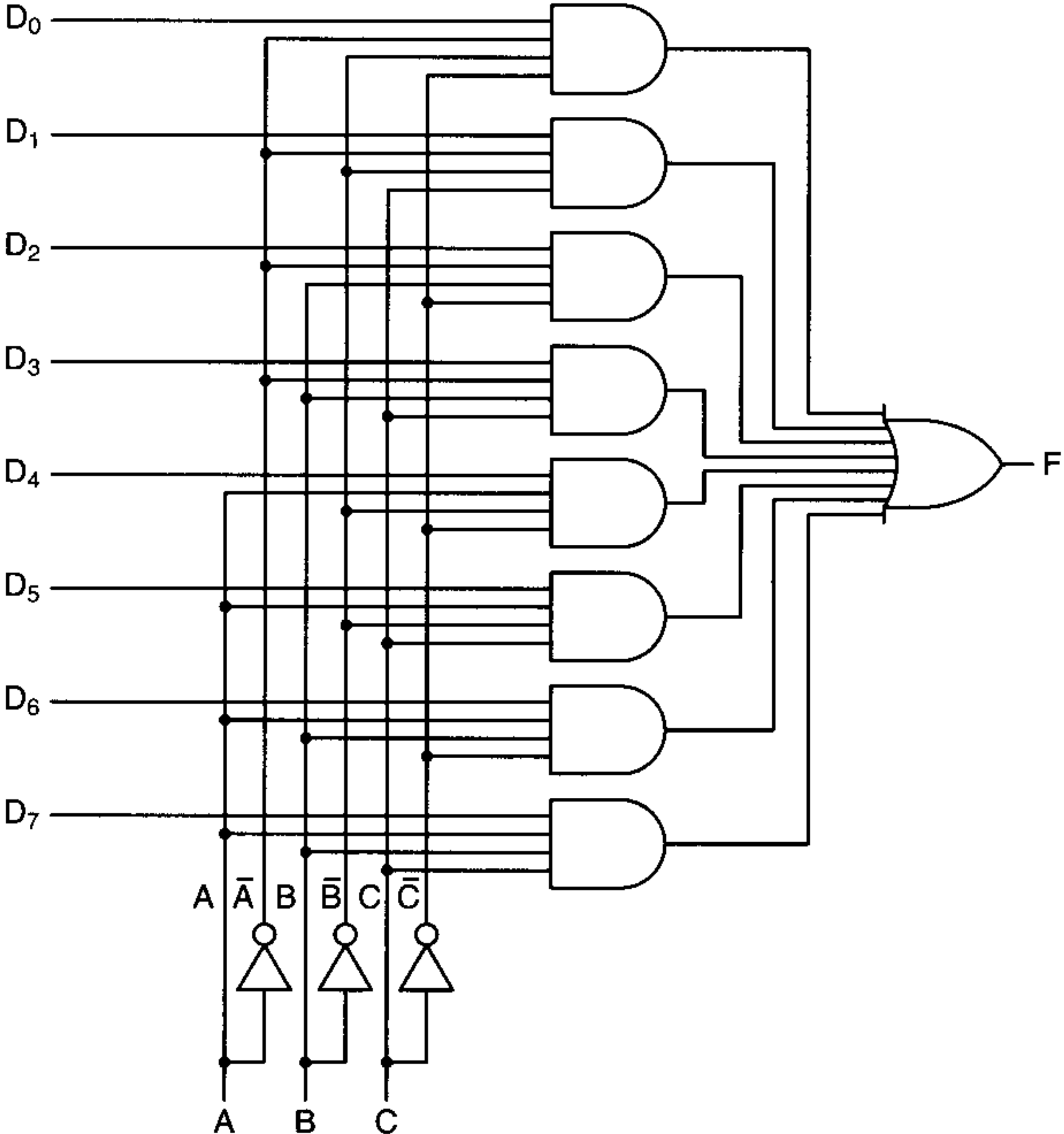



# Multiplexers

Select one of several inputs as output.

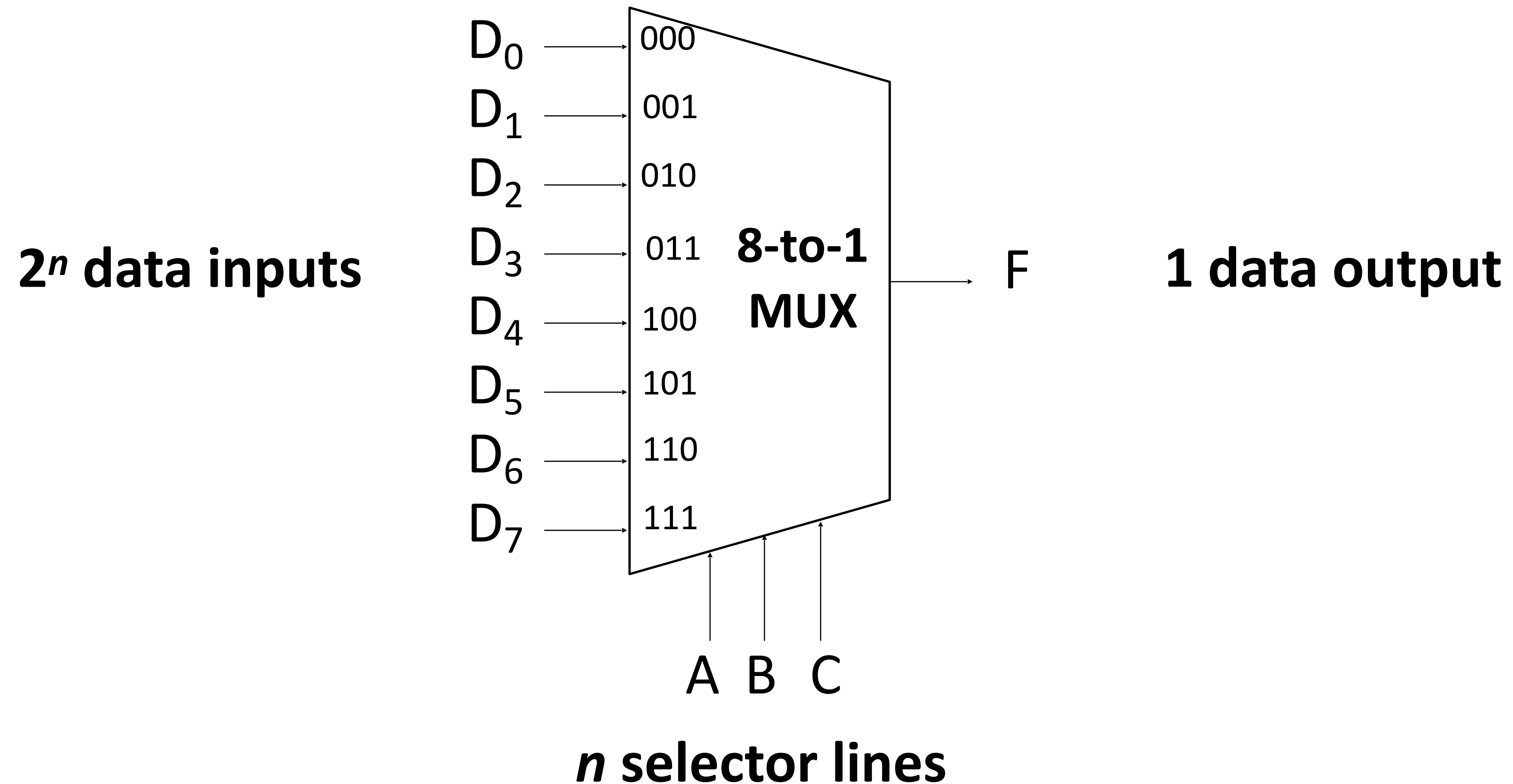


# Build a 2-to-1 MUX from gates

If  $S=0$ , then  $F=D_0$ .

If  $S=1$ , then  $F=D_1$ .


1. Construct the truth table.

2. Build the circuit.

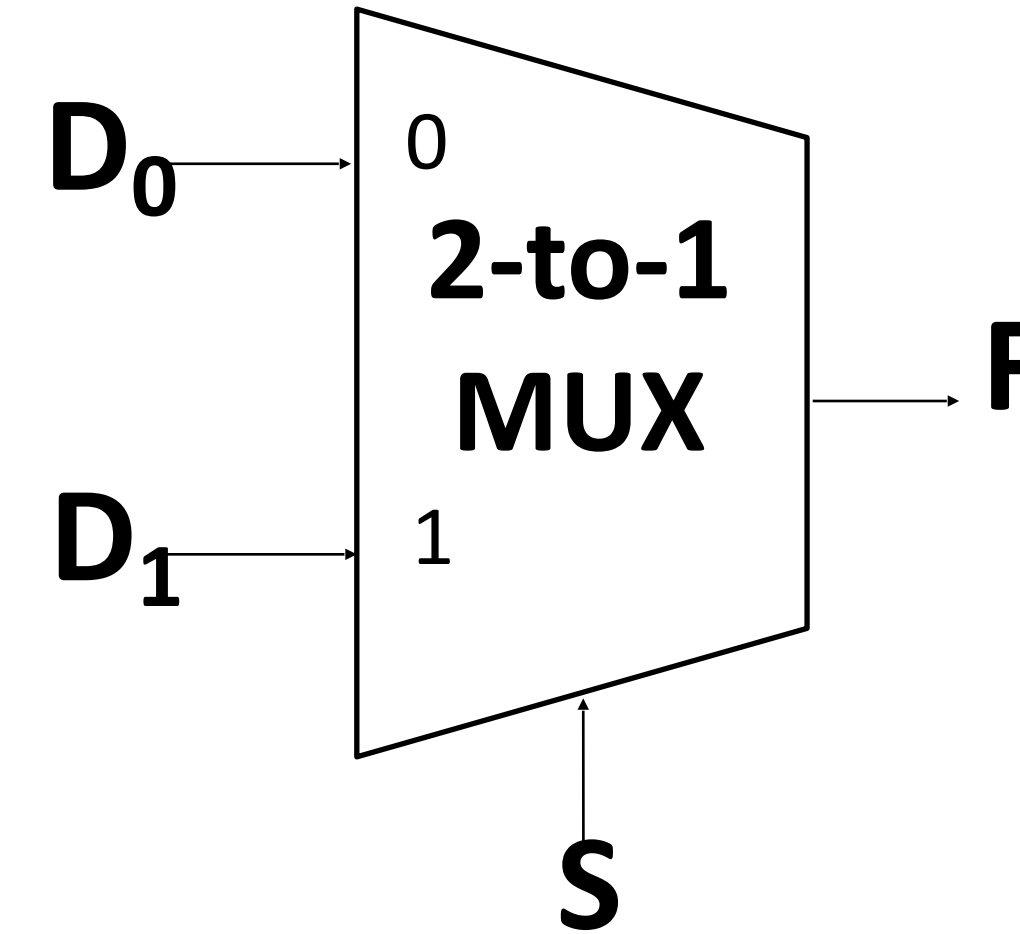

ex

# MUX + voltage source = truth table

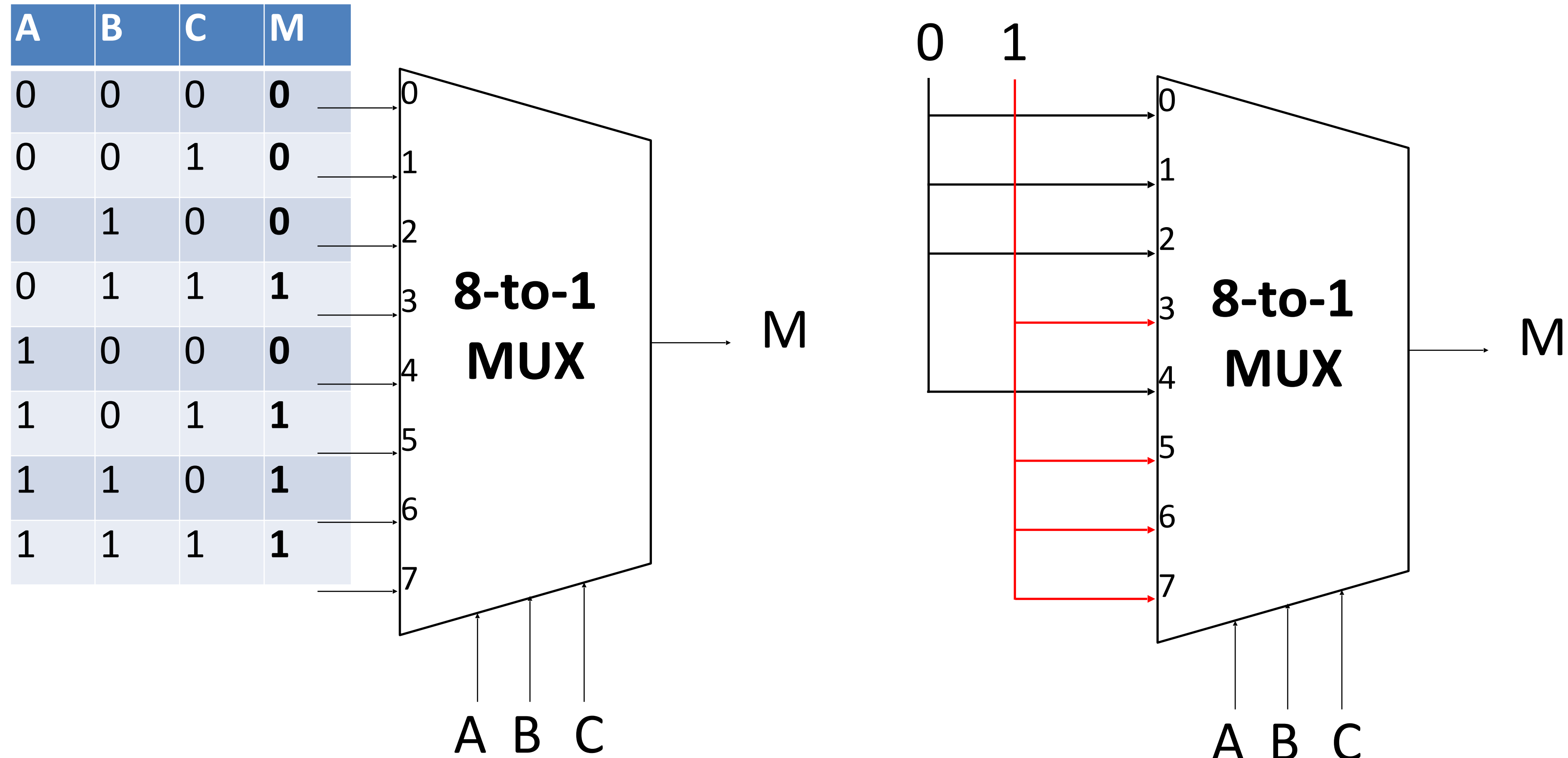

# Buses and Logic Arrays

A bus is a collection of data lines treated as a single logical signal.

= *fixed-width value*

An array of logic elements (logical array) applies same operation to each bit in a bus.

= *bitwise operator*

