

About how many hours did you spend actively working on this assignment? _____

Q1 vALUe Judgement [22 points]

Draw circuits on next page, text answers here.

1.1 Condition Flags [5 points]
(draw circuits on next page)

1.2. (a) [3 points] A, B with correct result

A	B	A - B	sign(A-B)	Is A < B?
positive	positive			no
negative	negative			yes
different signs	different signs			

1.2. (b) [2 points] A, B with incorrect result

A	B	A - B	sign(A-B)	Is A < B?
positive				no
negative				yes

1.2. (c) [1 point] Key effect

1.2. (d) [5 points] Draw your circuit for the *Less-Than* on the next page.

1.2. (e) [1 points] Control lines for *Less-Than*

Invert A = *Negate B* = *Operation* =

1.3. (a) [4 points] Draw your *Equals* Flag design on the next page.

1.3. (b) [1 points] Control lines for *Equals*


Invert A = *Negate B* = *Operation* =

Q2. Flop-flip-flopping [10 points]

Q2.2 Explanation (You need not fill this entire space.)

Cycles Completed	Q ₂	Q ₁	Q ₀
0 (initial)	0	0	0
1			
2			
3			
4			
5			
6			
7			
8			
9			
10			

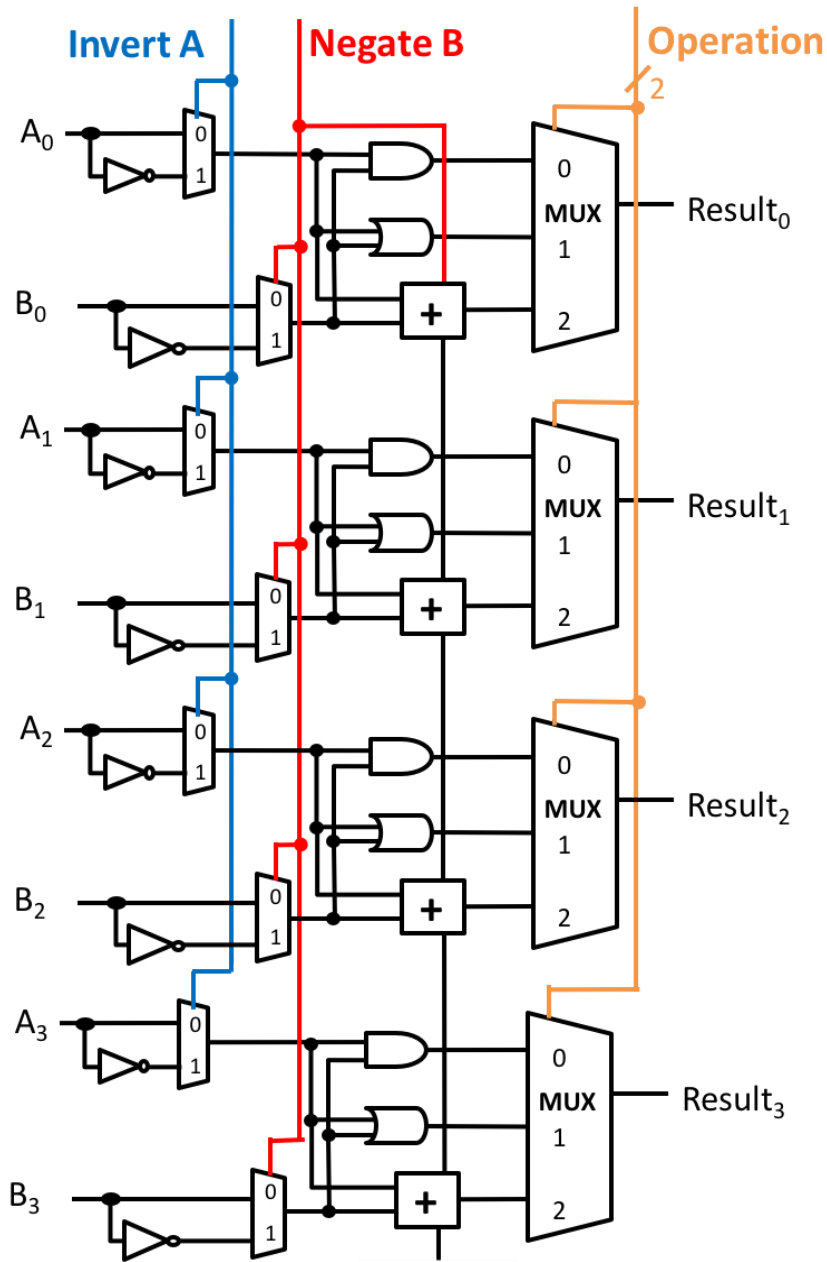1.1. (a-d) Condition Flags, 1.2. (d) Less-Than Flag, 1.3. (a) Equals Flag. Label outputs clearly.



Q3 Some Loopy Programs [14 points]

3.1 [8 points] Execution Table for P1

<i>PC</i>	<i>Instruction</i>	<i>State Changes</i>

3.2 [3 points] Final contents, P1	R2:	R3:	R4:
--	------------	------------	------------

3.3 [3 points] C statements equivalent to P1:

```
int R0 = 0;
int R1 = 1;
int R2 = R0+R1;
```

3.4 (a) [3 points] Result of P2

Execute this code, assuming R2 holds 2 and R3 holds 3. Indicate the final register values when the code reaches **HALT**.

```

0x0:  AND R2, R2, R4
0x2:  AND R3, R3, R5
0x4:  BEQ R5, R0, 3
0x6:  SUB R5, R1, R5
0x8:  ADD R4, R4, R4
0xA:  JMP 2
0xC:  HALT # Stops execution.

```

R2: R3: R4: R5:

3.4 (b) [2 points] C line for P2

Single line of C code equivalent to P2.
Use only basic C operations (no function calls).

R4 =

Q4 Taking Control [8 points]**Control Unit Truth Table**

Instruction Name	Opcode _[3:0] (4 bits)	Reg Write (1 bit)	ALU Op _[3:0] (4 bits)	Mem Store (1 bit)	Mem (1 bit)	Branch (1 bit)	Jump (Q6.2 [1pt]) (1 bit)
LW	0000	1	0010	0	1	0	0
SW							
ADD							
SUB							
AND							
OR							
BEQ							
NAND (Q5.2 [3 pts])							
JMP (Q6.3 [1 pt])							

Q5 Instruction Not Missing [8 points]

Fill in, following the format of slide 14 of the A Simple Processor lecture notes.

----- 16-bit encoding -----

Assembly	Meaning	Opcode [15:12]	Rs [11:8]	Rt [7:4]	Rd [3:0]
5.1 [3 points] NAND Rs ,Rt ,Rd	$R[d] \leftarrow \sim(Rs \& Rt)$				
5.3 [2 points] NOT Rs ,Rd	$R[d] \leftarrow \sim Rs$				

Q6 Jumping into the Unknown [8 points]

6.1 [6 points]. Below, add a `Jump` output wire from the Control Unit and modify logic to use it to implement `JMP` instruction. Note: if you use the new red write split off from `Inst`, be sure to label which range ([?, ?]) of bits you use.

