

About how many total hours did you spend actively working on this assignment? _____

Q1 [6 points] Time spent on Q1: _____

Truth Tables

A	B	C		P	Q
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Unsimplified Boolean Expressions

P =

Q =

Q2 [6 points] Time spent on Q2: _____

Q3 [4 points]*Time spent on Q3:* _____**a [1]****Counterexample or explanation:**

- ☐ Equivalent
☐ Not equivalent

b [1]**Counterexample or explanation:**

- ☐ Equivalent
☐ Not equivalent

c [1] [Independent]**Counterexample or explanation:**

- ☐ Equivalent
☐ Not equivalent

d [1] [Independent]**Counterexample or explanation:**

- ☐ Equivalent
☐ Not equivalent

Q4 [5 points] *Time spent on Q4:* _____**a [2]** $\text{bexp}_4 =$ **b [3]** circuit diagram:**Q5 [5 points]** *Time spent on Q5:* _____**a [2]** $\text{bexp}_5 =$ **b [3]** circuit diagram:

Q6 [12 points] *Time spent on Q6:* _____

Q6a [6 points] *Time spent on Q6a:* _____

Truth table

A	B	C	output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Derivation (you are given more rows than you need; box, underline, or color all redexes)

Simplification steps	Law(s) used to simplify redex in previous line
$ABC + ABC' + A'C + A'B'C + AB'C$	

Q6b [Independent] [6 points] *Time spent on Q6b:* _____

Truth table

A	B	C	output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Derivation (you are given more rows than you need; box, underline, or color all redexes)

Simplification steps	Law(s) used to simplify redex in previous line
$A'B' + A'BC' + (A + C)'$	

Q7 [10 points]

Time spent on Q7: _____

Truth table for parts a [1] and c [1]

A	B	AB	A'B'	AB + A'B'	bexp _{7b}	AB + bexp _{7b}
0	0					
0	1					
1	0					
1	1					

Below, show steps in deriving the answer expressions

b [1] bexp_{7b} =

d [2] bexp_{7d} =

e [2] [independent]
bexp_{7e} =

f [3] [Independent]
bexp_{7f} =

Q8 [12 points] *Time spent on Q8:* _____

Q8a [6] Express XOR in terms of 2-input NAND gates. Show both the final circuit *and* your derivation/explanation

Time spent on Q8a: _____

Q8b [Independent] [6] Express XOR in terms of 2-input NOR gates.

Show both the final circuit *and* your derivation/explanation

Time spent on Q8b: _____

Q9 Decoding a T-Shirt [8 points] *Time spent on Q9:* _____

1a [2 points] Message in base of flag:

Hex pairs: 43 53 33 34 32 20 43 6f 6d 70 75 74 65 72 20 53 65 63 75 72 69 74 79
ASCII:

Decoded message from base of flag:

1b [6 points] Message in binary bits of the flag. Write down the bits and show your decoding details.

Q10 Decoding a Unicode Message [12 points] *Time spent on Q10:* _____

2a [10 points] Show how to decode the Unicode message in the hex bytes 49 E2 99 A5 CF 80 21 to Unicode code points. Write the **message bits** corresponding to the hex bytes, distinguish **header** bits from **content** bits, and indicate **the number of bytes in each code point**. Show the **code points** determined by the content bits.

2b [2 points]. What would the message look like in a Unicode enabled application?