 


Computer Science 240

Assignment for Lab 7

NOTE: You should not try to do the problems on flip-flops until after lecture on Friday.


- Given the following diagram for the ALU, and assuming A and B are 4-bit hexadecimal values, fill the table below:




Function	Test Inputs	Output	Carry-out	Zero	Overflow
A + B	A = 3, B = 7				
A + B	A = F, B = E				
A AND B	A = 1, B = F				
A AND B	A = 7, B = 8				
A OR B	A = 3, B = C				
A NOR B	A = 6, B = 9				
SLT	A = 3, B = 9				
SLT	A = C, B = 7				

2. Assume you have an SR latch, $S=0$ and $R=0$. Do you know if the output Q is 0 or 1? Explain.

 3. Assume you have a clocked SR **latch**. Draw Q , given the following CK, S, and R:



 4. Assume you have a clocked SR **flip-flop**, that is activated on the positive edge of the clock. Draw Q given the same CK, S, and R:



5. Explain why your outputs are different for the latch and the flip-flop: