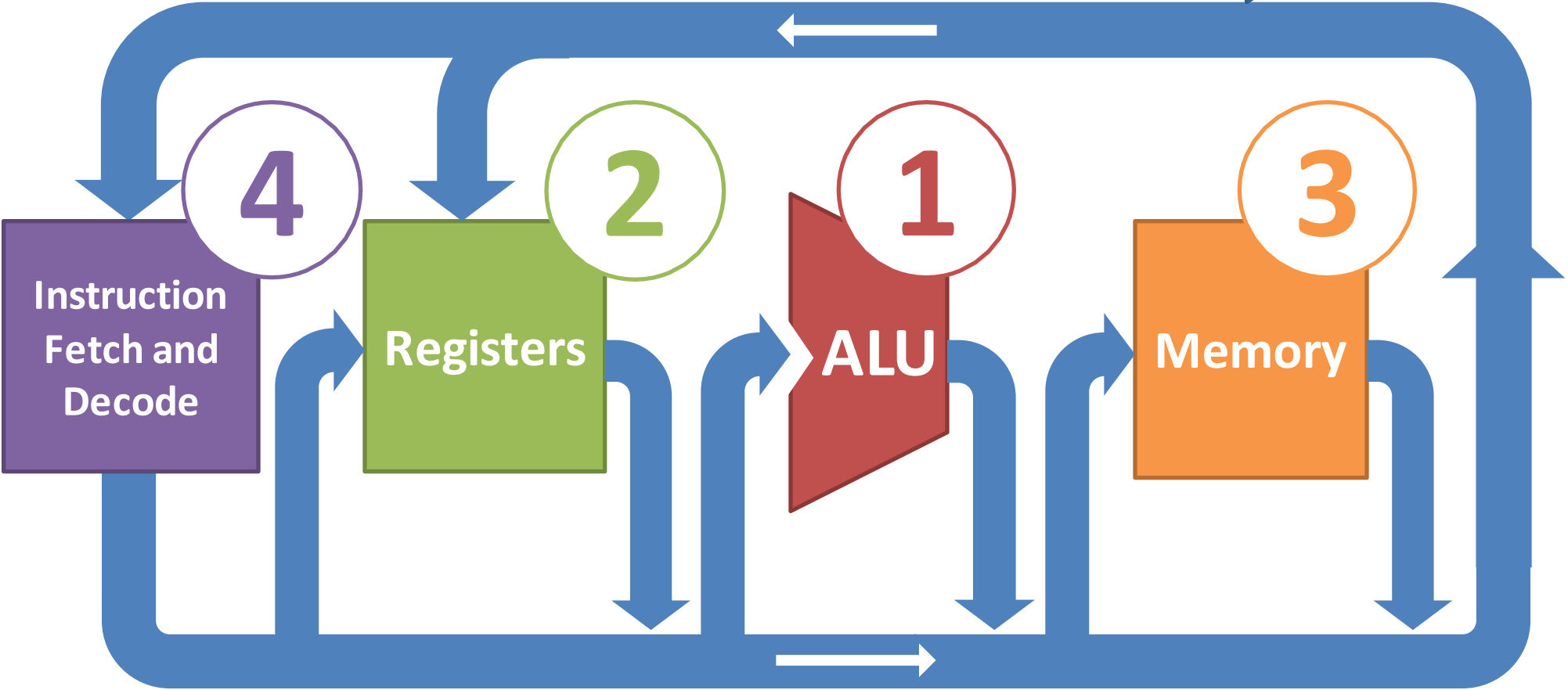


Processor: Data Path Components

Abstraction!



Building Blocks

Microarchitecture

Digital Logic

Devices (transistors,
etc.)



Processor datapath

Instruction Decoder
Arithmetic Logic Unit


Memory

Adders
Multiplexers
Demultiplexers
Encoders
Decoders


Registers

Flip-Flops
Latches

Gates

 

Arithmetic Logic Unit (ALU)

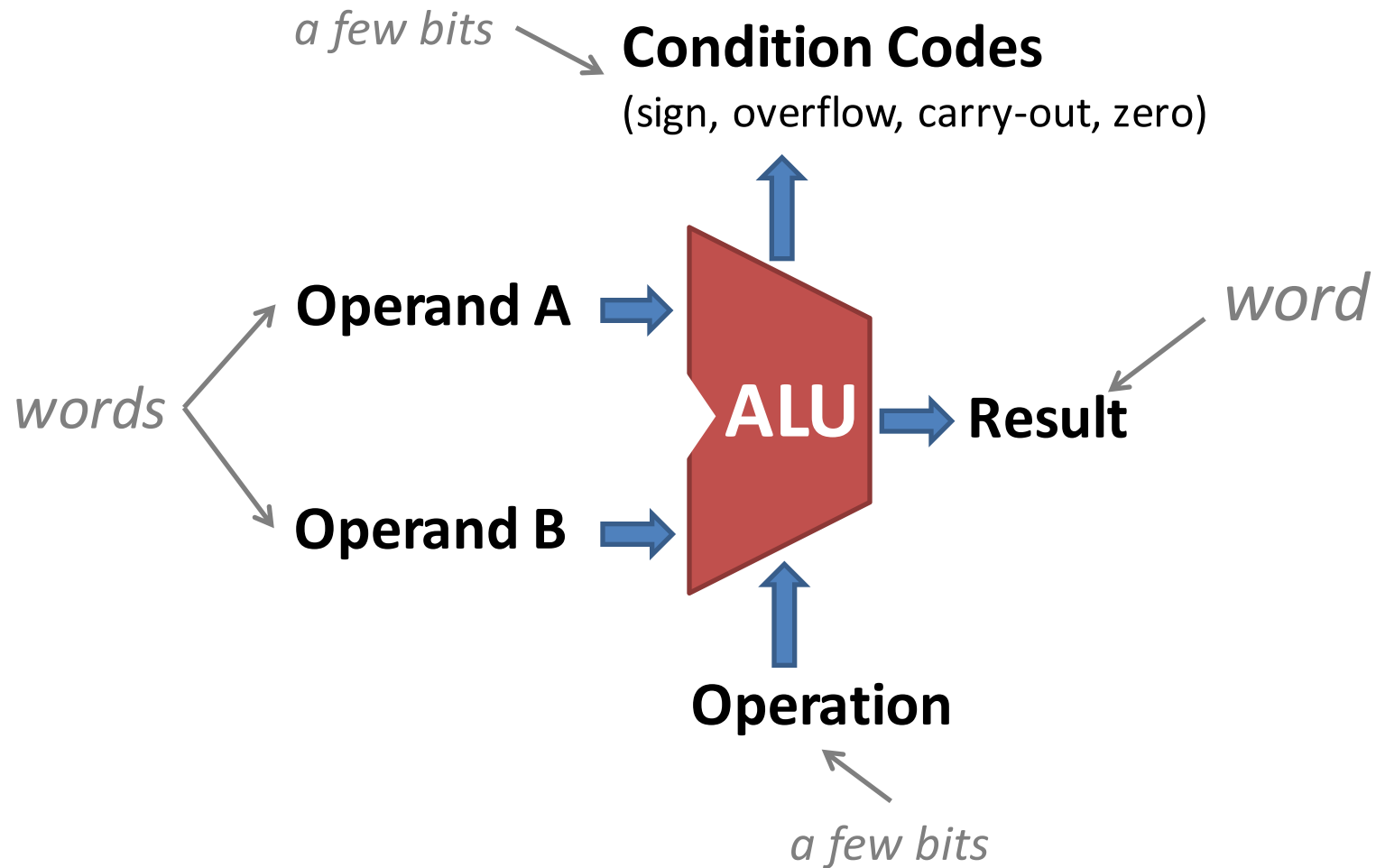


Hardware unit for arithmetic and bitwise operations.

1-bit ALU for bitwise operations



Build an n-bit ALU from n 1-bit ALUs.

 Each bit i in the result is computed from the corresponding bit i in the two inputs.




Op	A	B	Result
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

1-bit adder


Build an n-bit adder from n 1-bit adders.

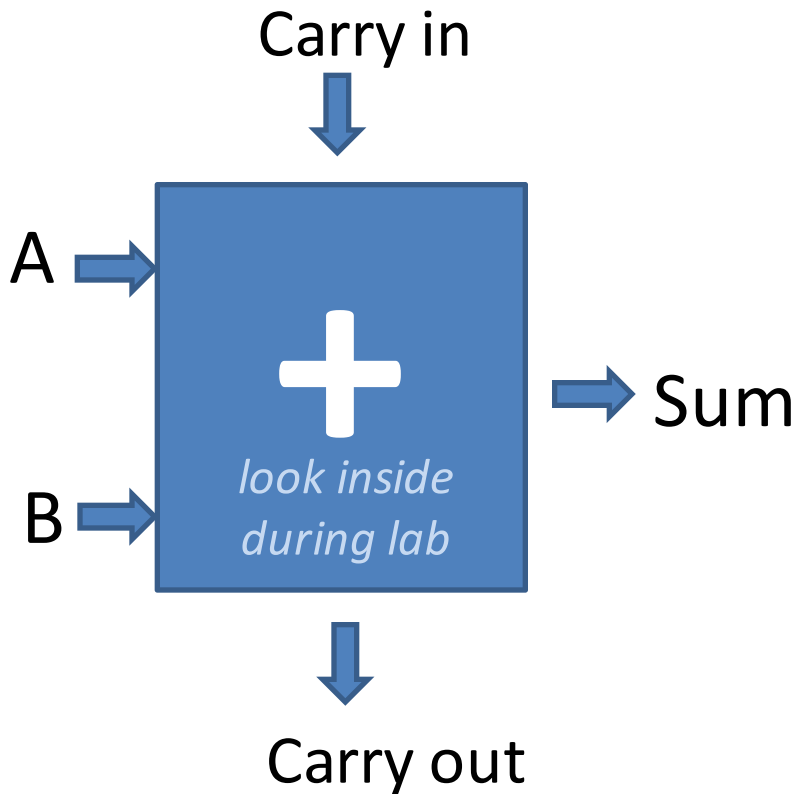Each bit i in the result is computed from the corresponding bit i in the two inputs and the carry out of bit $i-1$.




A	B	Carry in	Carry out	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

n-bit ripple-carry adder

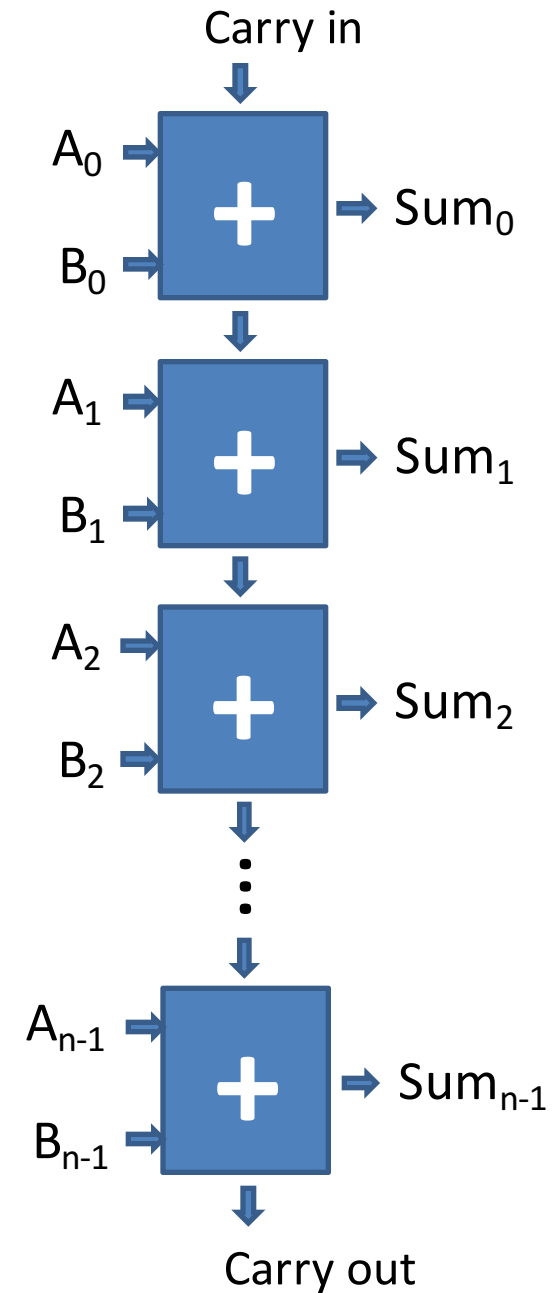


There are faster, more complicated ways too...

1-bit ALU

 


n-bit ALU

with ripple carry

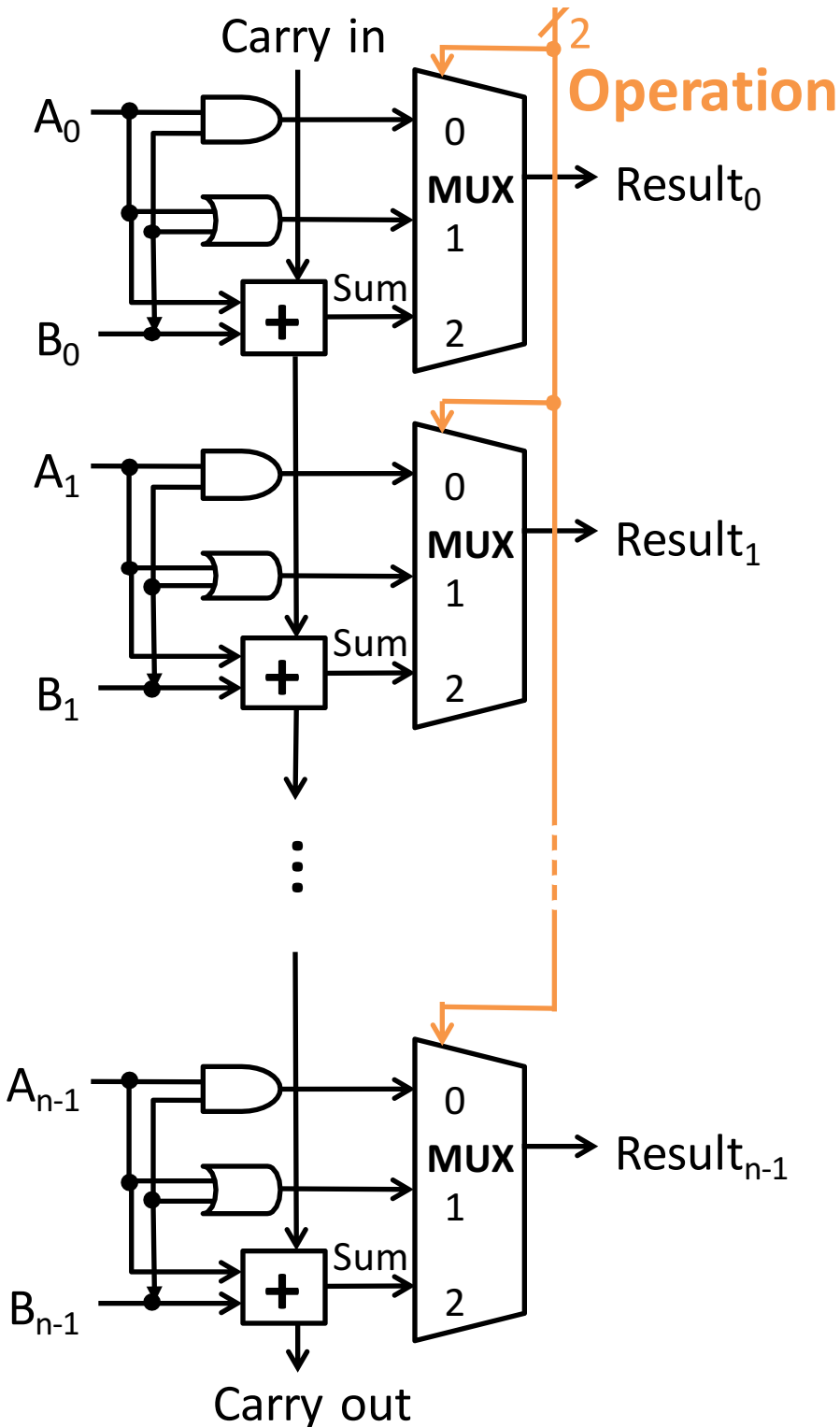

Adding subtraction

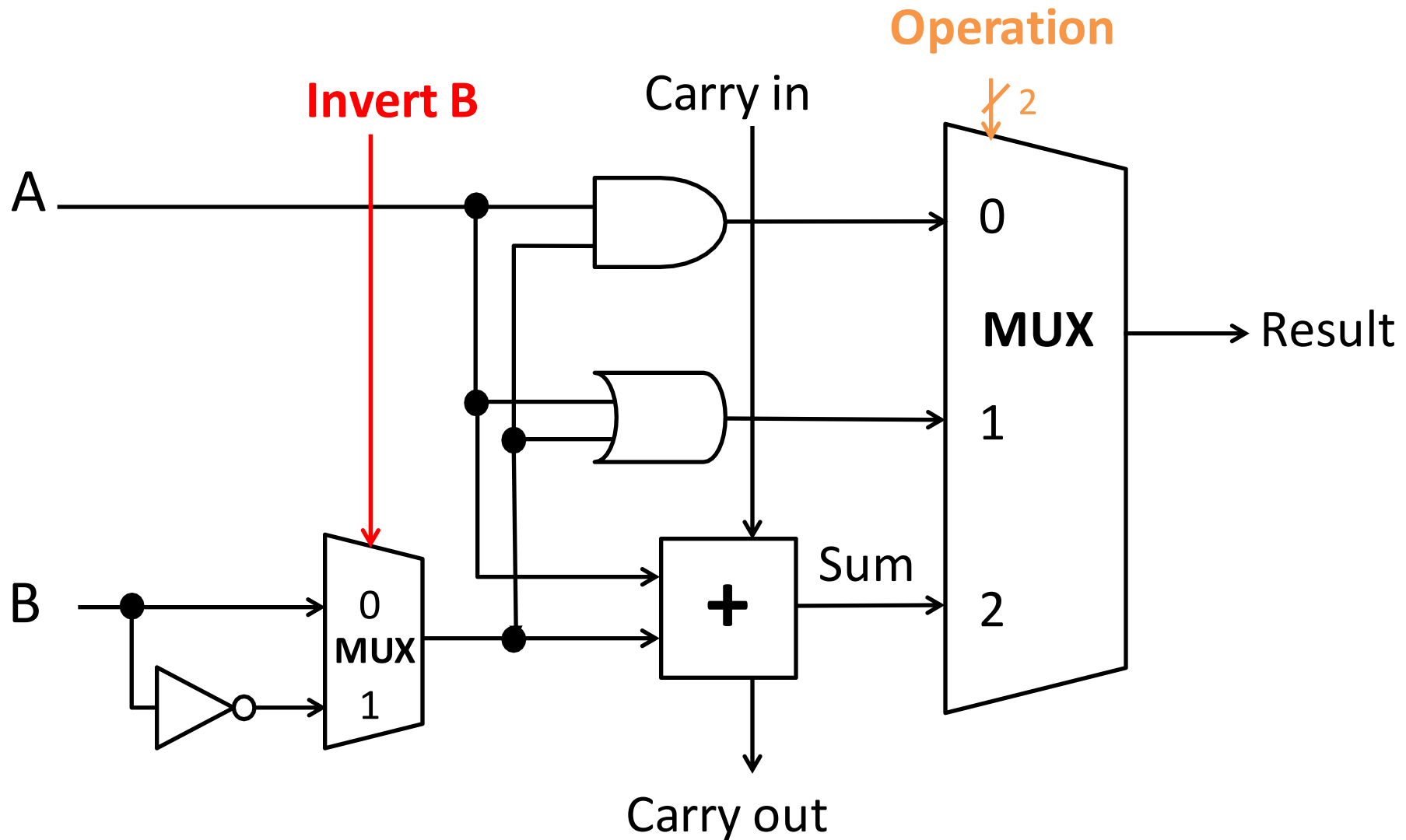

Different than in SCO book.

ALU Condition Codes (x86)

Extra ALU outputs describing properties of result.

Zero Flag: 1 if result is 00...0 else 0


Sign Flag: sign bit of result

Carry Flag: 1 if unsigned overflow else 0
carry-out bit of result

Overflow Flag: 1 if signed overflow else 0

Compute NAND, NOR, NOT A,


Set inputs as needed.

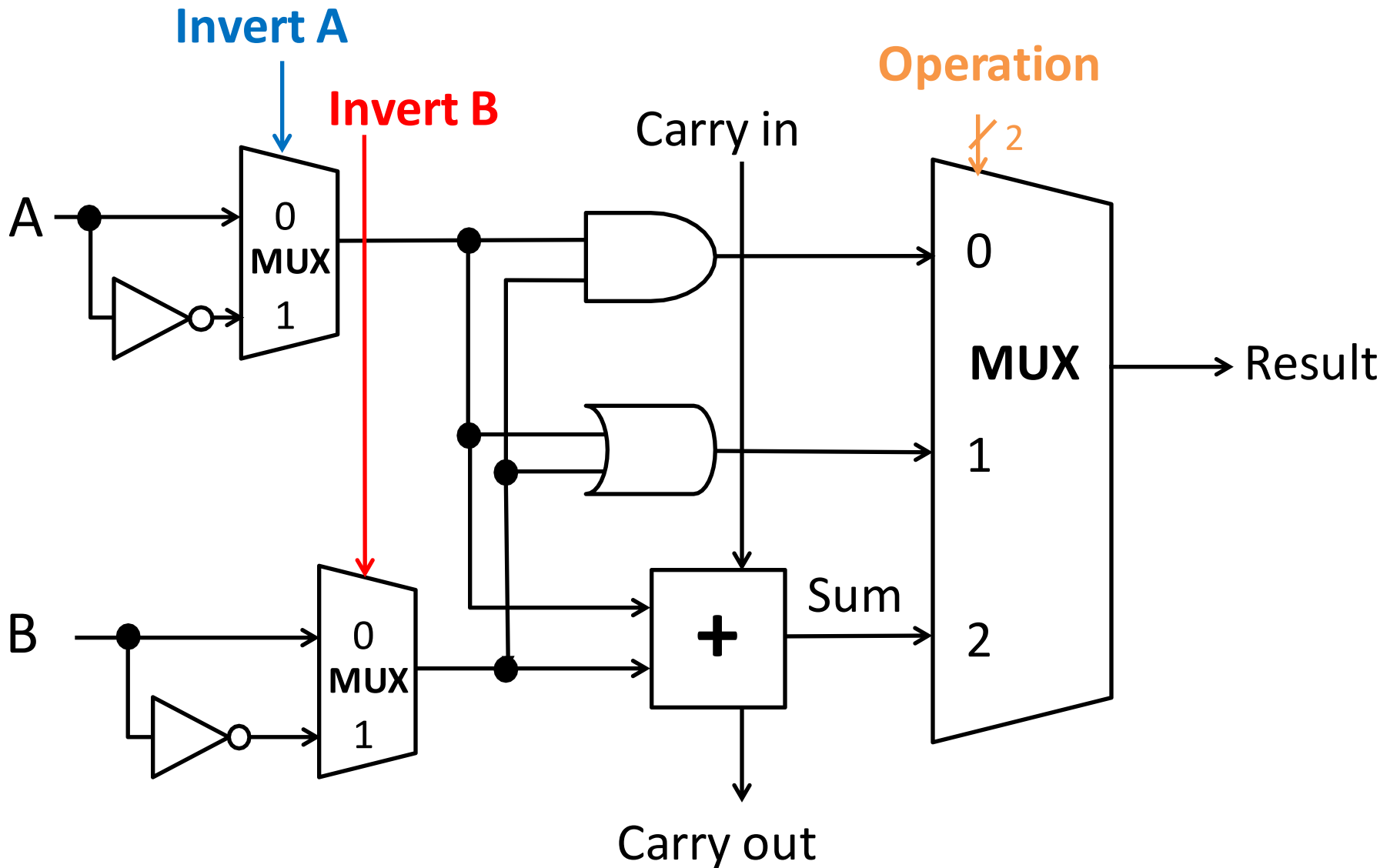


Compute $<$, $==$? Detect overflow?



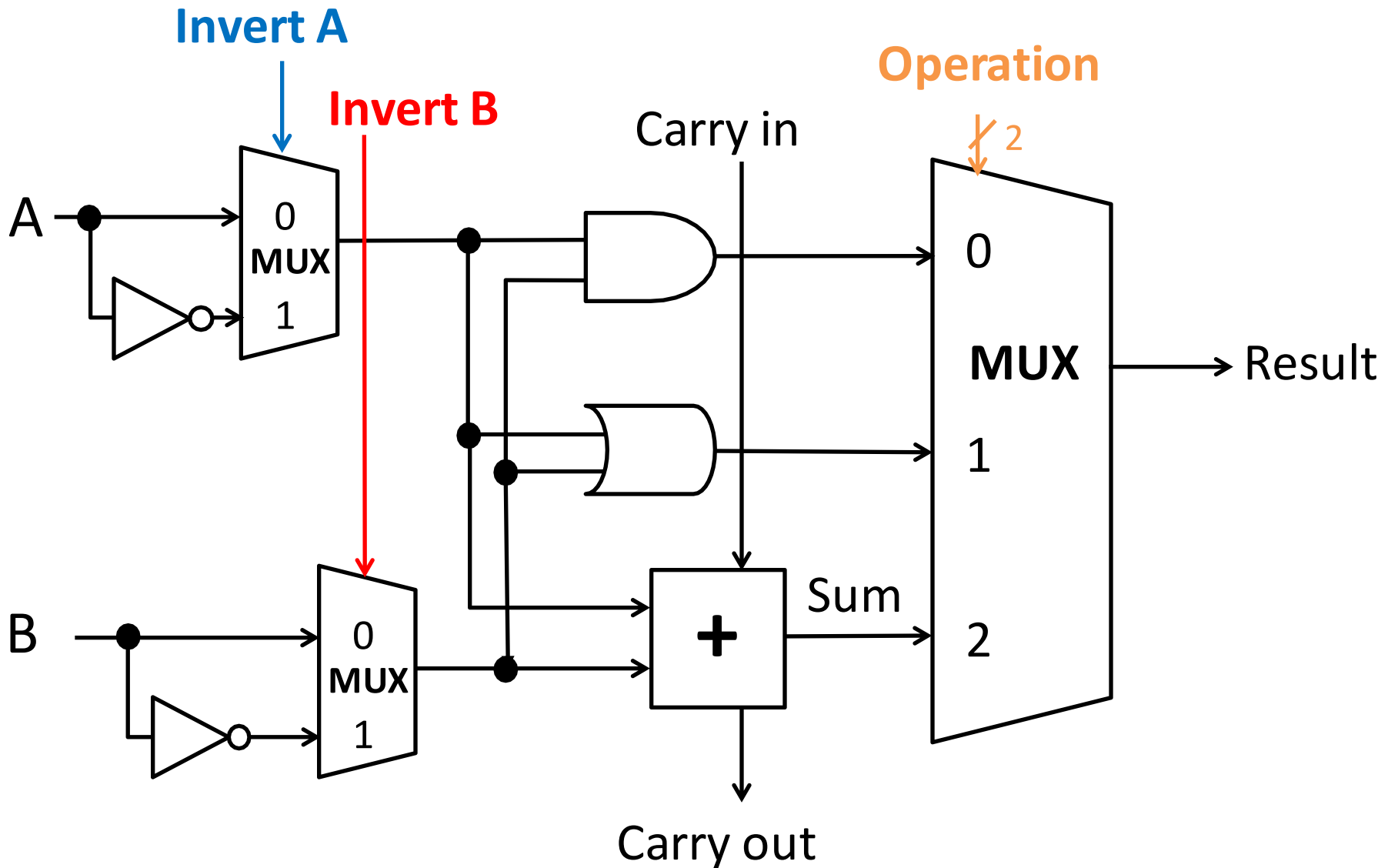Set inputs as needed, add minimal logic for overflow.



n-bit ALU

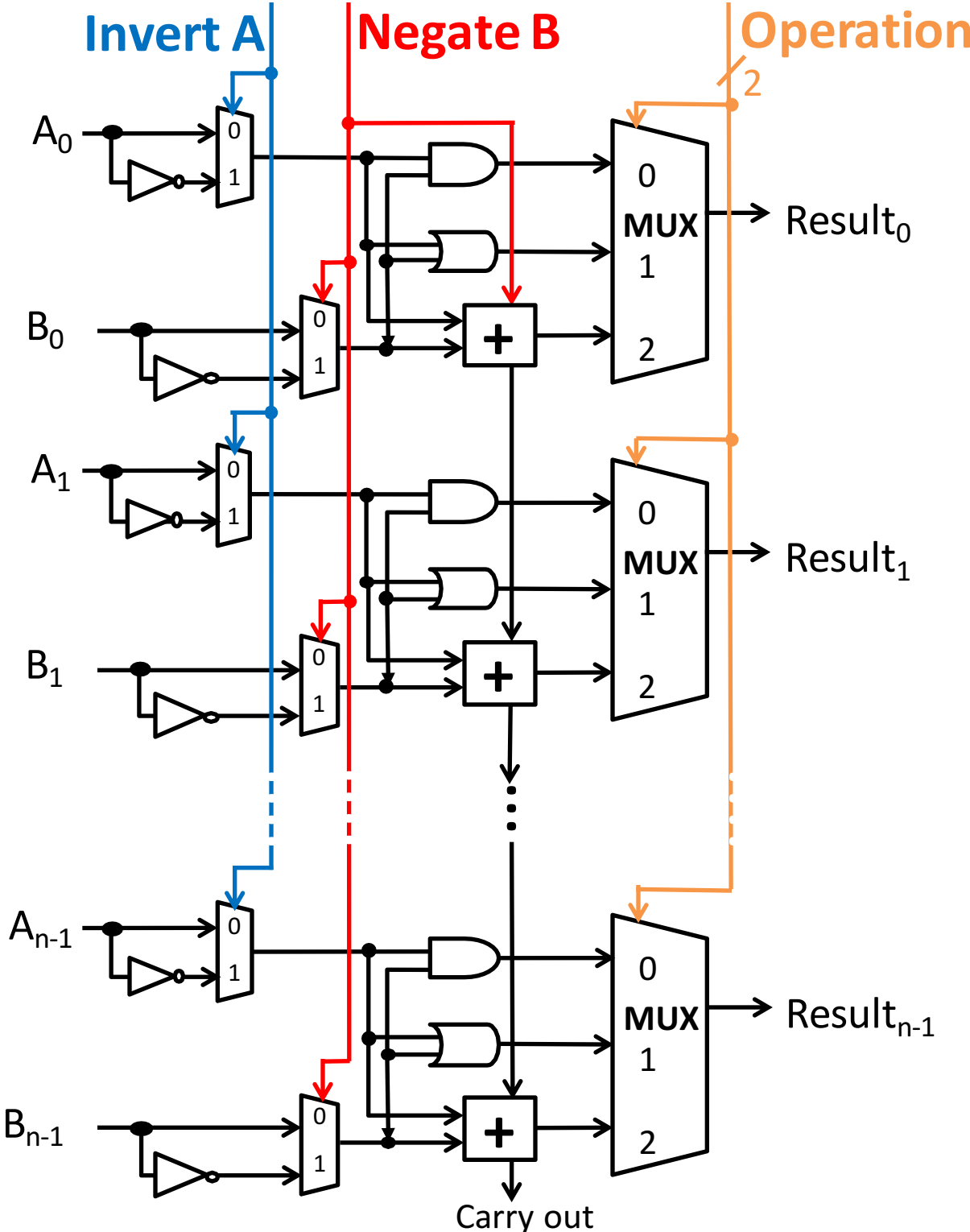

Controlling the ALU



ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
1100	NOR

