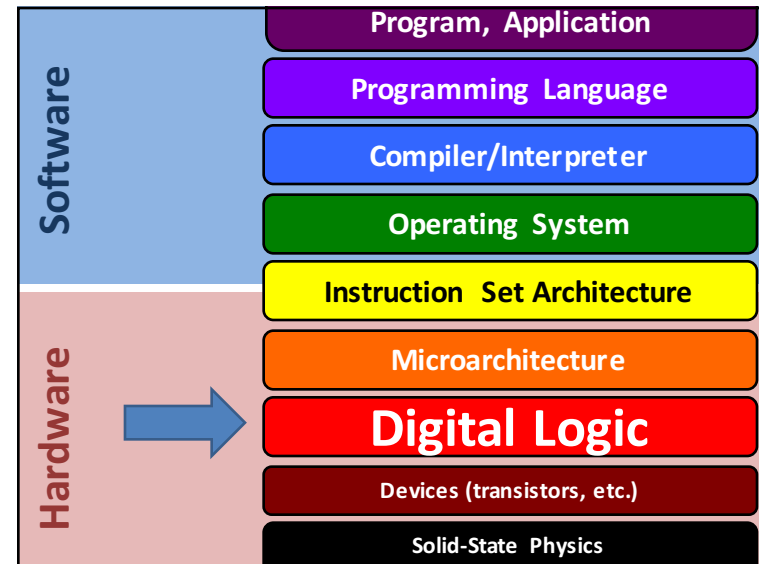


Digital Logic

Gateway to computer science



Boolean value (*bit*): 0 or 1

basis of all digital data representations

Boolean functions (AND, OR, NOT, ...):

basis of all digital computations

Electronically:
bit = high voltage vs. low voltage

Boolean functions = logic gates, built from transistors

Abstraction!

Transistors (more in lab)

If Base voltage is high:
Current may flow freely from *Collector* to *Emitter*.

If Base voltage is low:
Current may not flow from *Collector* to *Emitter*.

V_{in}		V_{out}	
low	high	in	out
low	high	0	1
high	low	1	0

Truth table

in	out
F	T
T	F


NOT gate

Abstraction!


Digital Logic Gates

Abstraction! ex


Tiny electronic devices that compute basic Boolean functions.

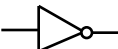NOT 

V _{in}	V _{out}
0	1
1	0

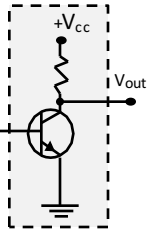



V ₂	
0	1
V ₁	0
1	1

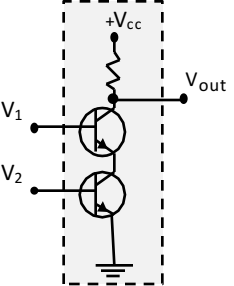


Integrated Circuits (invented 1950s)

Gates are manufactured in units called *integrated circuits*.
From SSI (tens) to VLSI (hundreds of thousands to billions)

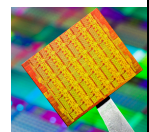
Chip 

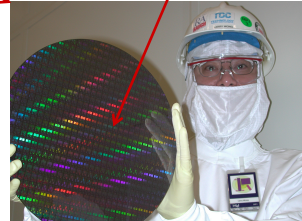Wafer 

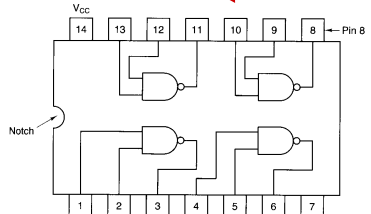


Five basic gates: define with truth tables


ex




NOT	
0	1
1	0




NAND	0	1
0	1	1
1	1	0



NOR	0	1
0	1	1
1	1	0

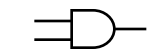

AND	0	1
0	0	0
1	0	1

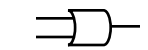


OR	0	1
0	0	1
1	1	1

Boolean Algebra


for combinational logic

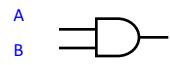inputs = variables
wires = expressions
gates = operators/functions
circuits = functions




AND = Boolean product

·	0	1
0	0	0
1	0	1

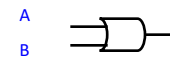

OR = Boolean sum

+	0	1
0	0	1
1	1	1

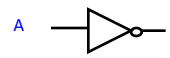

NOT = inverse or complement

	0	1
	1	0

wire = identity


	0	1
	0	1

Circuits

ex

Connect inputs and outputs of gates with wires.
Crossed wires touch *only* if there is a dot.

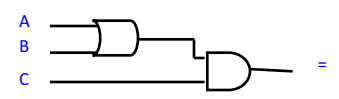What is the output if A=1, B=0, C=1?
What is the truth table of this circuit?
What is an equivalent Boolean expression?



Translation


ex

Connect gates to implement these functions. Check with truth tables.
A one-to-one translation is straightforward and bidirectional.


$$F = (A\bar{B} + C)D$$

$$Z = \bar{W} + (X + \bar{W}Y)$$

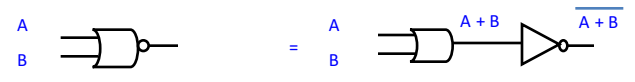
Note on notation: bubble = inverse/complement




Identity law, inverse law

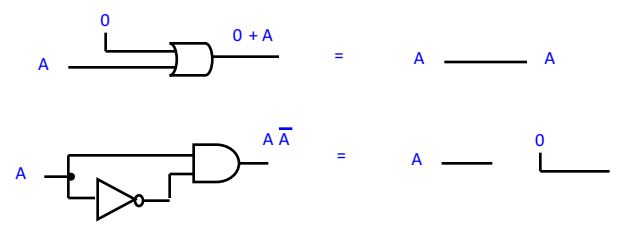


Commutativity, Associativity

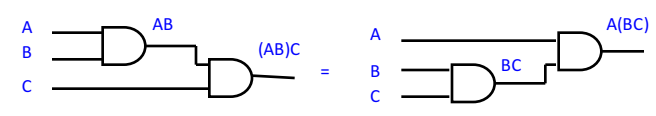


Idempotent law, Null/Zero law


 $A + A = A$



 $A \cdot 0 = 0$


Note on notation: bubble = inverse/complement

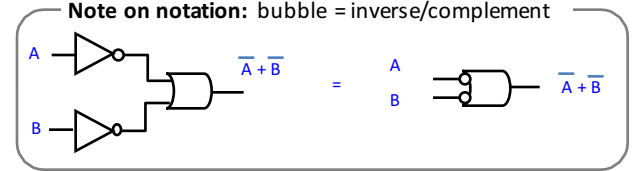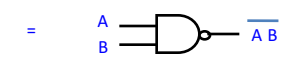
 $\overline{A+B} = \overline{A} \cdot \overline{B}$

DeMorgan's Law


(double bubble, toil and trouble, in Randy's words...)



 $\overline{A \cdot B} = \overline{A} + \overline{B}$

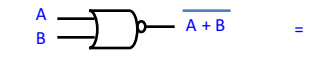
 $\overline{A+B} =$


One law, Absorption law

Write truth tables. Do they correspond to simpler circuits?

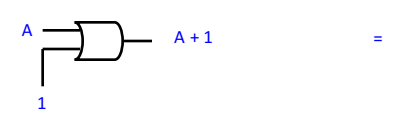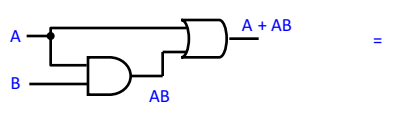
 $A + 1 =$

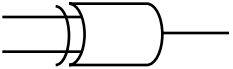

 $A + AB =$

NAND is universal.



All Boolean functions can be implemented using only NANDs.
Let's prove it! Build NOT, AND, OR, NOR, using only NAND gates.

XOR: Exclusive OR ex




Output = 1 if exactly one input = 1.

Truth table: Build from earlier gates:


Often used as a one-bit comparator.

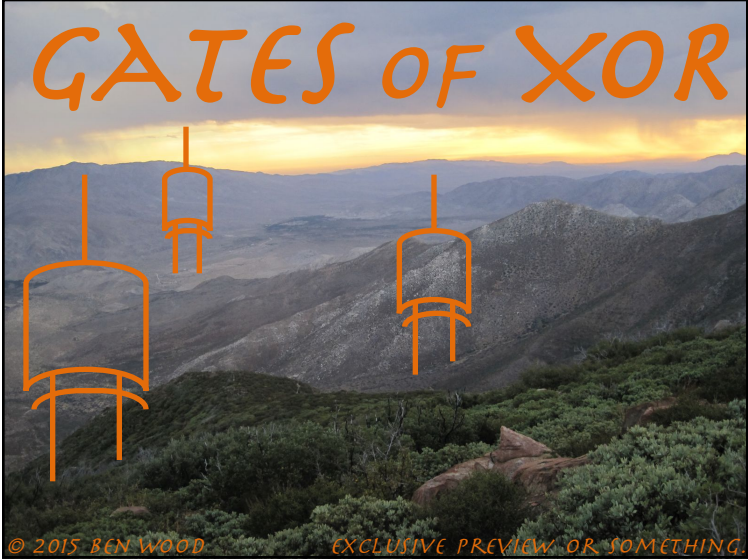Video game designers, Halloween costumers extraordinaire, sci-fi/fantasy screenwriters, I have an idea...



Larger gates ex

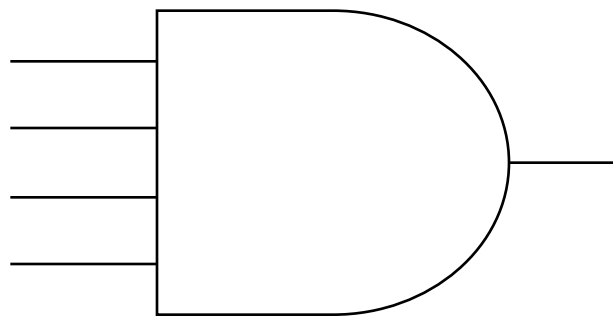
Build a 4-input AND gate using any number of 2-input gates.



Circuit simplification ex

Why simplify?
Smaller = cheaper, faster, cooler, easier to design/build.

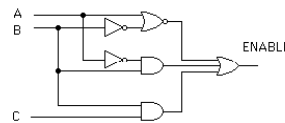Can we find a simpler circuit that performs the same function?



Start with an equivalent Boolean expression, then simplify with algebra.


$F(A, B, C) =$

Check the answer with a truth table.

Circuit derivation: *code detectors*

ex

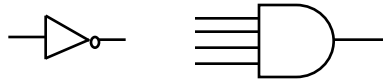AND gate + NOT gates = code detector, recognizes exactly one input code.



Design a 4-input code detector to output 1 if ABCD = 1001, and 0 otherwise.



Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others. (accept = 1, reject = 0)

Circuit derivation: *sum-of-products* form

ex

logical sum (OR)
of products (AND)
of inputs or their complements (NOT)

Draw the truth table and design a sum-of-products circuit for a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others.
How are the truth table and the sum-of-products circuit related?

Voting machines

ex

A **majority circuit** outputs 1 if and only if a majority of its inputs equal 1.
Design a majority circuit for three inputs. **Use a sum of products.**

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Triply redundant computers in spacecraft

- Compute everything on three separate devices and compare answers. Majority wins.
- Cosmic rays can flip bits on wires, especially in space.
- Triple redundancy survives failure in one device.
- Space program also hastened Integrated Circuits.

Margaret Hamilton *(speaking of space and reliability)*

Led software team for **Apollo 11** Guidance Computer.
Developed software engineering techniques for correctness and reliability.
Coined "software engineering".
Software avoided mission abort on first moon landing!

Apollo 11 code print-out

