

Introductory Concepts and Tools

Computer Science 240

Laboratory 1

- Administrivia
- Lab Environment
- Basic Electronics (Ohm's law, transistors, logic gates)

Lab Environment

- All lab exercises and reports will be *Google Docs*, and should be shared with lab partner and the instructor
- Bring a laptop to lab if you have it (helpful to use a second computer for the lab report)
- From lab machine booted to Linux, you can enter Linux commands using a **terminal / shell**
- You can also use a terminal from either Mac (*Terminal*) or PC (*PuTTY*) to open a remote connection to a Linux machine for command-line entry


NOTE: for some exercises and assignments, you will be required to use the lab machines to compile and run your programs

Basic Concepts of Electricity

Electricity = **the movement of electrons** in a material


Materials tend to have a net negative or positive charge

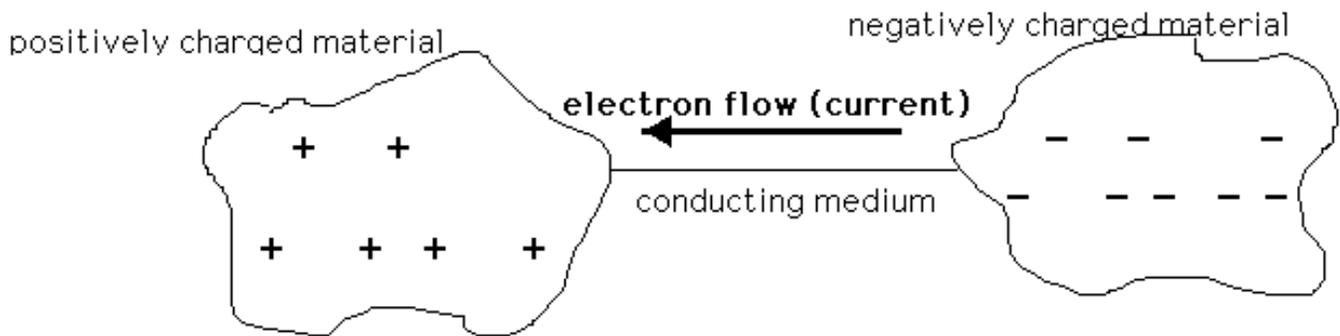Difference of charge between two points = **potential difference (V)**




Rate at which electrons flow through = **current (A)**.

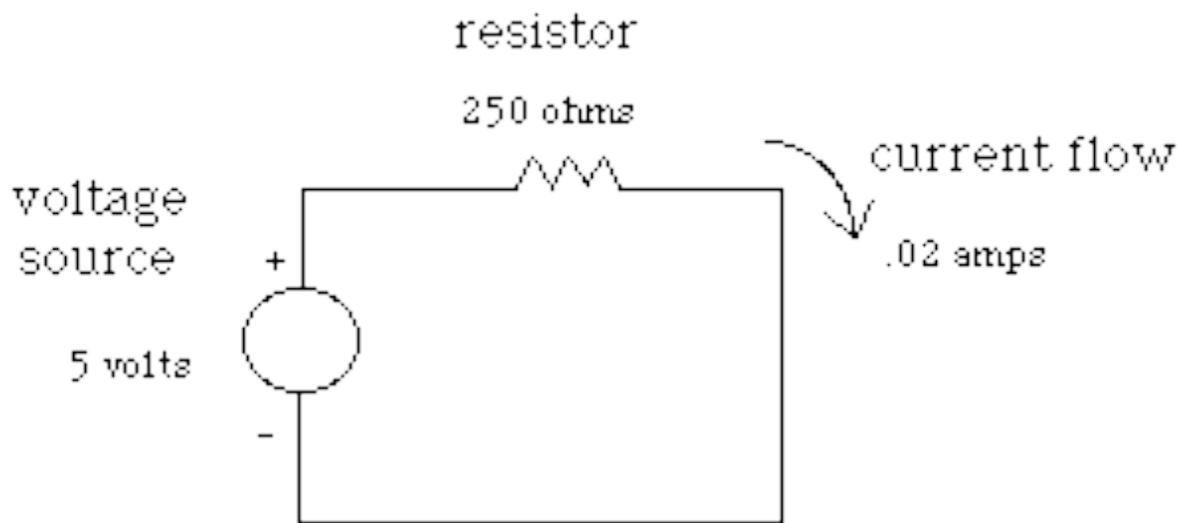Ease of conduction, or current flow = **resistance (Ω)**



Ohm's Law, $V = IR$.

Open circuit = no current

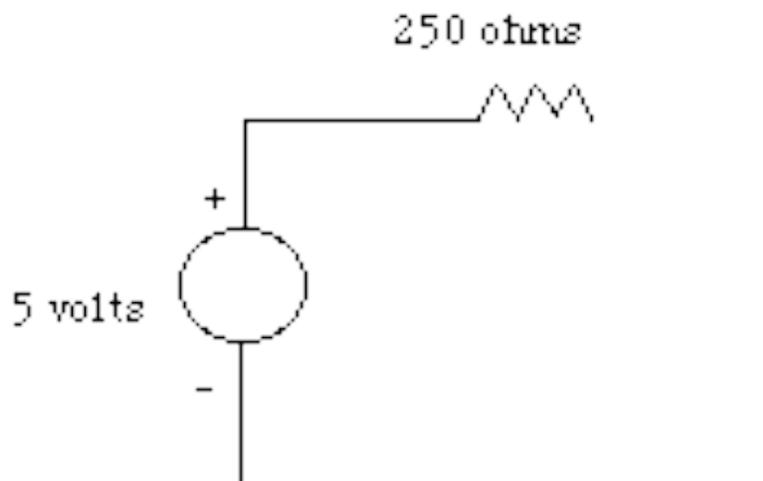


Short circuit = infinite current, since $V/0 = \text{infinite current}$:



Infinite current swiftly results in the destruction of the circuit!

Basic Gate Symbols

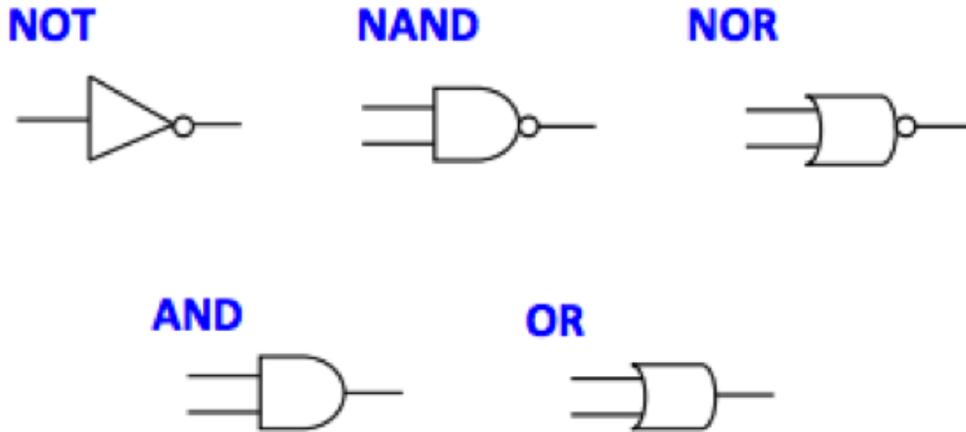


Notation and Truth Tables for Basic Logic Gates

NOT $F = A'$		NAND $F = (AB)'$			NOR $F = (A+B)'$			AND $F = AB$			OR $F = A + B$		
<u>A</u>	<u>F</u>	<u>A</u>	<u>B</u>	<u>F</u>	<u>A</u>	<u>B</u>	<u>F</u>	<u>A</u>	<u>B</u>	<u>F</u>	<u>A</u>	<u>B</u>	<u>F</u>
0	1	0	0	1	0	0	1	0	0	0	0	0	0
1	0	0	1	1	0	1	0	0	1	0	0	1	1
		1	0	1	1	0	0	1	0	0	1	0	1
		1	1	0	1	1	0	1	1	1	1	1	1


Basic Gates are built using Transistors

You have seen the circuits for NOT and NAND in lecture:


NOT – 1 transistor

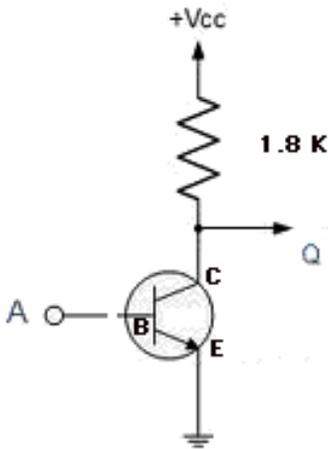

NAND - 2 transistors

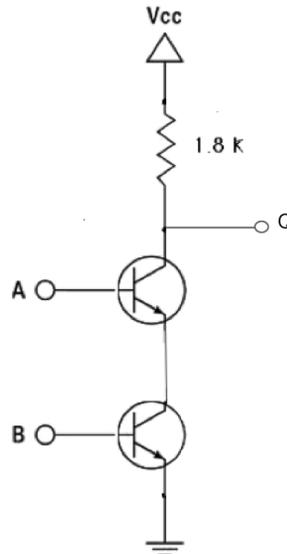


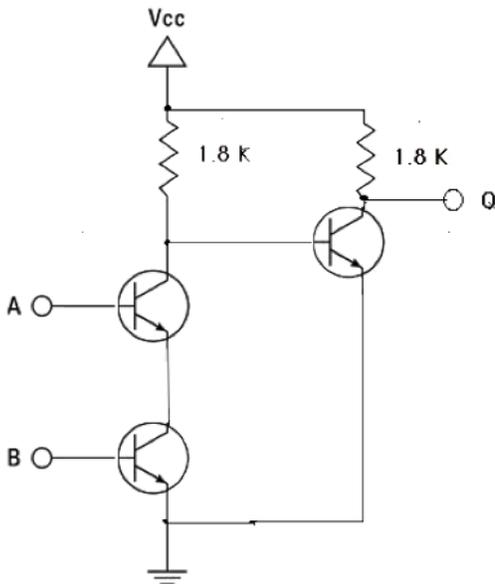AND – uses 3 transistors (send the output of a NAND through another transistor acting as a NOT gate to complement the result):



Similarly, these are the transistor circuits for a NOR and OR gate:

NOR – 2
transistors

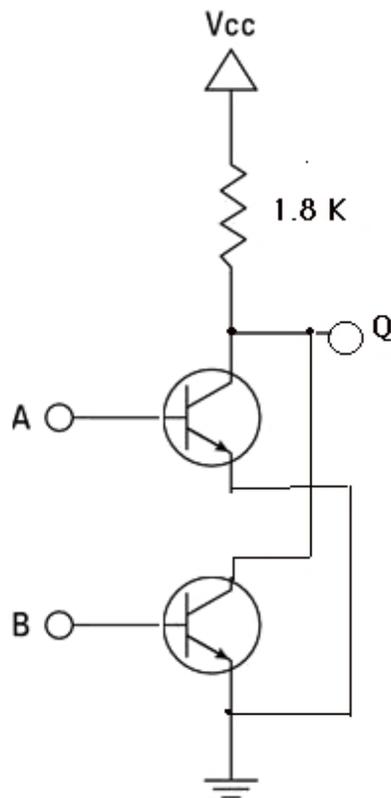

OR – 3 transistors

