

CS240 Laboratory 2

Digital Logic

- **Circuit equivalence**
- **Boolean Algebra/Universal gates**
- **Linux, C, Emacs**
- **Bitbucket, Mercurial**

Circuit Equivalence

Two boolean functions with same truth table = **equivalent**

When there is an equivalent circuit that uses fewer gates, transistors, or chips, it is preferable to use that circuit in the design

Example:

Given: $F = A'B' + A'B$

$$Q = A' + A'B + A'B'$$

<u>A</u>	<u>B</u>	<u>A'B'</u>	<u>A'B</u>	<u>F</u>
0	0	1	0	1
0	1	0	1	1
1	0	0	0	0
1	1	0	0	0

<u>A</u>	<u>B</u>	<u>A'</u>	<u>A'B</u>	<u>A'B'</u>	<u>Q</u>
0	0	1	0	1	1
0	1	1	0	0	1
1	0	0	0	0	0
1	1	0	0	0	0

F and Q are equivalent because they have the same truth table.

Identities of Boolean Algebra

- Identity law $1A = A$ $0 + A = A$
- Null law $0A = 0$ $1 + A = 1$
- Idempotent law $AA = A$ $A + A = A$
- Inverse law $AA' = 0$ $A + A' = 1$
- Commutative law $AB = BA$ $A + B = B + A$
- Associative law $(AB)C = A(BC)$
 $(A + B) + C = A + (B + C)$
- Distributive law $A + BC = (A + B)(A + C)$
 $A(B + C) = AB + AC$
- Absorption law $A(A + B) = A$
 $A + AB = A$
- De Morgan's law $(AB)' = A' + B'$
 $(A + B)' = A'B'$

Example:

$$\begin{aligned} F &= A'B' + A'B \\ &= A'(B' + B) \text{ distributive} \\ &= A'(1) \text{ inverse} \\ &= A' \text{ identity} \end{aligned} \qquad \begin{aligned} Q &= A' + A'B + A'B' \\ &= A' + A'B' \text{ absorption} \\ &= A' \text{ absorption} \end{aligned}$$

Universal Gates

Any Boolean function can be constructed with NOT, AND, and OR gates

NAND and NOR = **universal gates**


DeMorgan's Law shows how to make **AND** from **NOR** (and vice-versa)

$$AB = (A' + B)'$$
 (**AND** from **NOR**)


$$A + B = (A'B)'$$
 (**OR** from **NAND**)



NOT from a **NOR**

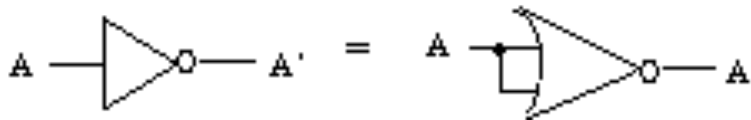

OR from a **NOR**

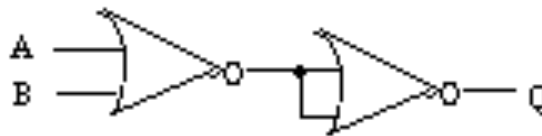

To implement a function using only **NOR** gates:

- apply DeMorgan's Law to each **AND** in the expression until all **ANDs** are converted to **NORs**
- use a **NOR** gate for any **NOT** gates, as well.
- remove any redundant gates (**NOT NOT**, may remove both)

Implementing the circuit using only **NAND** gates is similar.

Example: $Q = (AB)'B'$

$$= (A' + B')B'$$

$$= ((A'+B')' + B)'$$
 NOTE: you can use a NOR gate to produce A'
and you can do the same for B'

Simplifying Circuits or Proving Equivalency

General rule to simplify circuits or prove equivalency:

1. Distribute if possible, and if you can't, apply DeMorgan's Law so that you can.
2. Apply other identities to remove terms, and repeat step 1.

EXAMPLE: Is $(A'B)'(AB)' + A'B'$ equivalent to $(AB)'$?

$F = (A'B)'(AB)' + A'B'$	-- can't distribute
$= (A + B')(A' + B') + A'B'$	DeMorgan's
$= AA' + AB' + A'B + B'B' + A'B'$	distributive
$= 0 + AB' + A'B + B' + A'B'$	inverse and idempotent
$= AB' + A'B + A'B'$	identity
$= B'(A + A') + A'B$	distributive
$= B'(1) + A'B$	inverse
$= B' + A'B$	identity
$= B' + (A + B)'$	DeMorgan's
$= (B(A + B'))'$	DeMorgan's
$= (AB + BB')'$	distributive
$= (AB + 1)'$	inverse
$= (AB)'$	identity

Demo LogicWorks