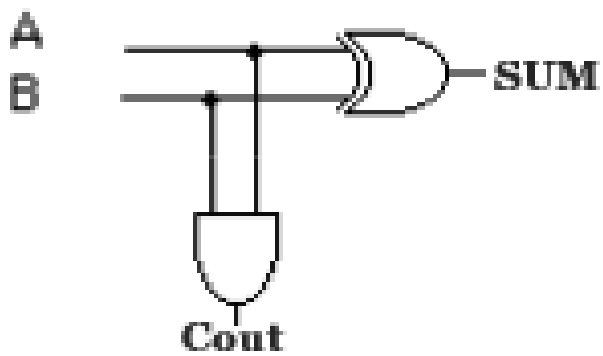


# CS 240 Lab 4


## Adders and ALU

**Half-Adder** – adds two one-bit values



<b>A</b>	<b>B</b>	<b>Sum</b>	<b>Cout</b>
0	0		
0	1		
1	0		
1	1		

**Full Adder** – incorporates a carry-in

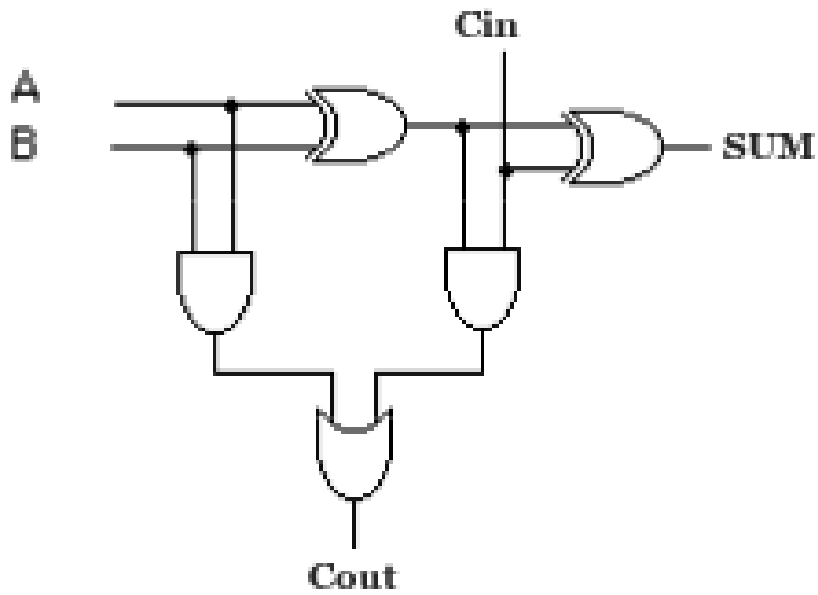


<b>A</b>	<b>B</b>	<b>Cin</b>	<b>Sum</b>	<b>Cout</b>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = AB + (A \oplus B) \text{Cin}$$

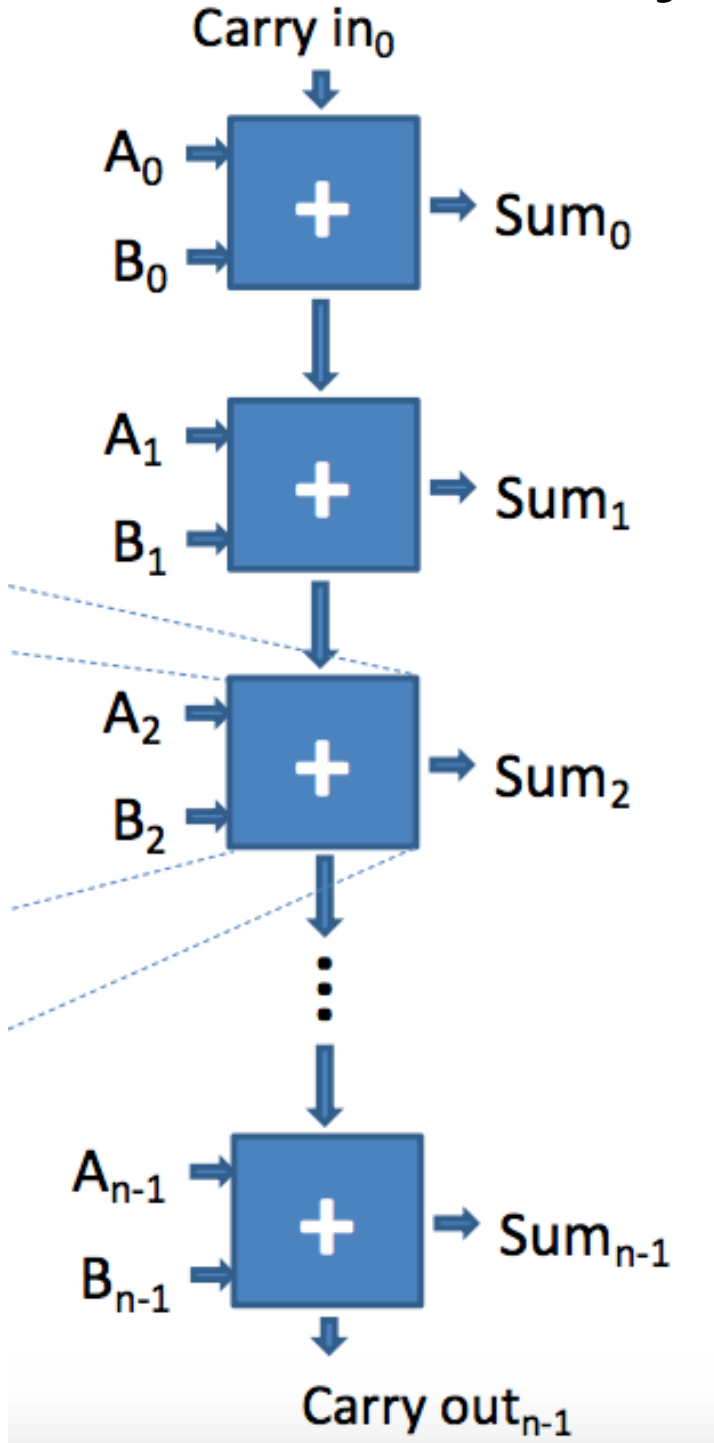
**n-bit adder = n 1-bit adders**

Carry-out of each adder = Carry-in of the adder for next two most significant bits being added


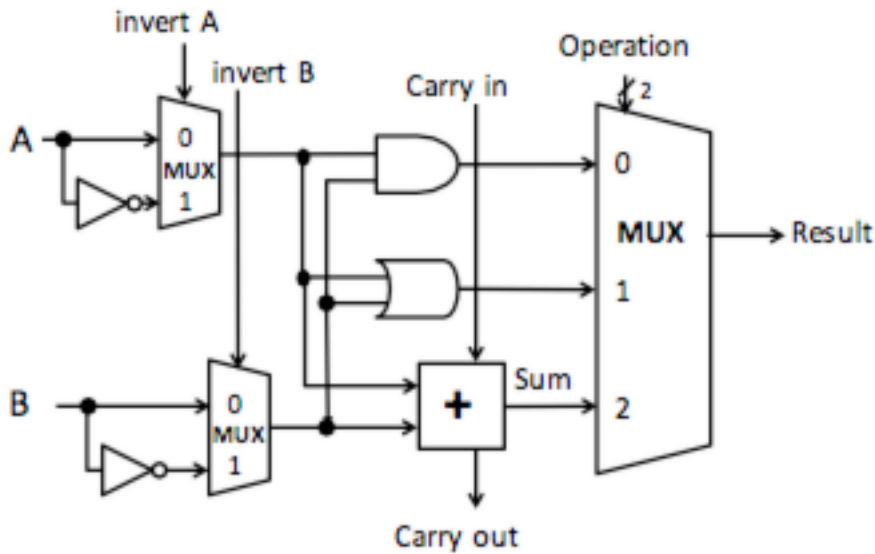
# ALU

Want to be able to select whether the ALU will produce the bitwise AND, OR, and sum as a result.



**add**  $(A + B + \text{Cin})$ ,  
**AND**  $(A \text{ AND } B)$ ,  
**OR**  $(A \text{ OR } B)$ ,

Adding the ability to choose whether to invert A or B provides additional operations:

**sub** (invert B, Cin = 1,  $A + B + \text{Cin}$ )

**NOR** (invert a, invert b,  $a \text{ AND } b$ )

<b>invA</b>	<b>invB</b>	<b>Cin</b>	<b>Op1</b>	<b>Op0</b>	<b>Result</b>
0	0	N/A	0	0	A AND B
0	0	N/A	0	1	A OR B
0	0	0/1	1	0	A + B
0	1	1	1	0	A - B
1	1	N/A	0	0	A NOR B

# n-bit ALU

