

Laboratory 6

Processor Datapath

Description of HW Instruction Set Architecture

- 16 bit data bus
- 8 bit address bus
- 16 registers
 - R0 = 0 (constant)
 - R1 = 1 (constant)
 - R2-R15 general purpose


HW ISA Instructions

		16-bit Encoding			
		MSB			LSB
Assembly Syntax	Meaning	Opcode	Rs	Rt	Rd
ADD <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] + R[t]$	0010	<i>s</i>	<i>t</i>	<i>d</i>
SUB <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] - R[t]$	0011	<i>s</i>	<i>t</i>	<i>d</i>
AND <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] \& R[t]$	0100	<i>s</i>	<i>t</i>	<i>d</i>
OR <i>Rs, Rt, Rd</i>	$R[d] \leftarrow R[s] R[t]$	0101	<i>s</i>	<i>t</i>	<i>d</i>
LW <i>Rt, offset(Rs)</i>	$R[t] \leftarrow M[R[s] + offset]$	0000	<i>s</i>	<i>t</i>	<i>offset</i>
SW <i>Rt, offset(Rs)</i>	$M[R[s] + offset] \leftarrow R[t]$	0001	<i>s</i>	<i>t</i>	<i>offset</i>
BEQ <i>Rs, Rt, offset</i>	If $R[s] == R[t]$ then $PC \leftarrow PC + offset * 2$	0111	<i>s</i>	<i>t</i>	<i>offset</i>
JMP <i>offset</i>	$PC \leftarrow offset * 2$	1000	<i>o</i>	<i>f</i>	<i>f</i> <i>s</i> <i>e</i> <i>t</i>

(R = register file, M = memory)

Fetch Instruction from Memory

 - **PC** register holds address of currently executing instruction
- Programs are assumed to start at address 0
- **PC** initialized to 0 by a reset to begin execution
- Next instruction located at current **PC + 2**



Fetch instruction from memory.

Increment program counter (PC) to point to the next instruction.

Branch Address


Programs do not always execute in sequential order.

When the **BEQ** instruction is executed, the next instruction to be executed is either:

$$PC = PC + 2$$

or

$$PC = PC + 2 + (2 * \text{offset})$$

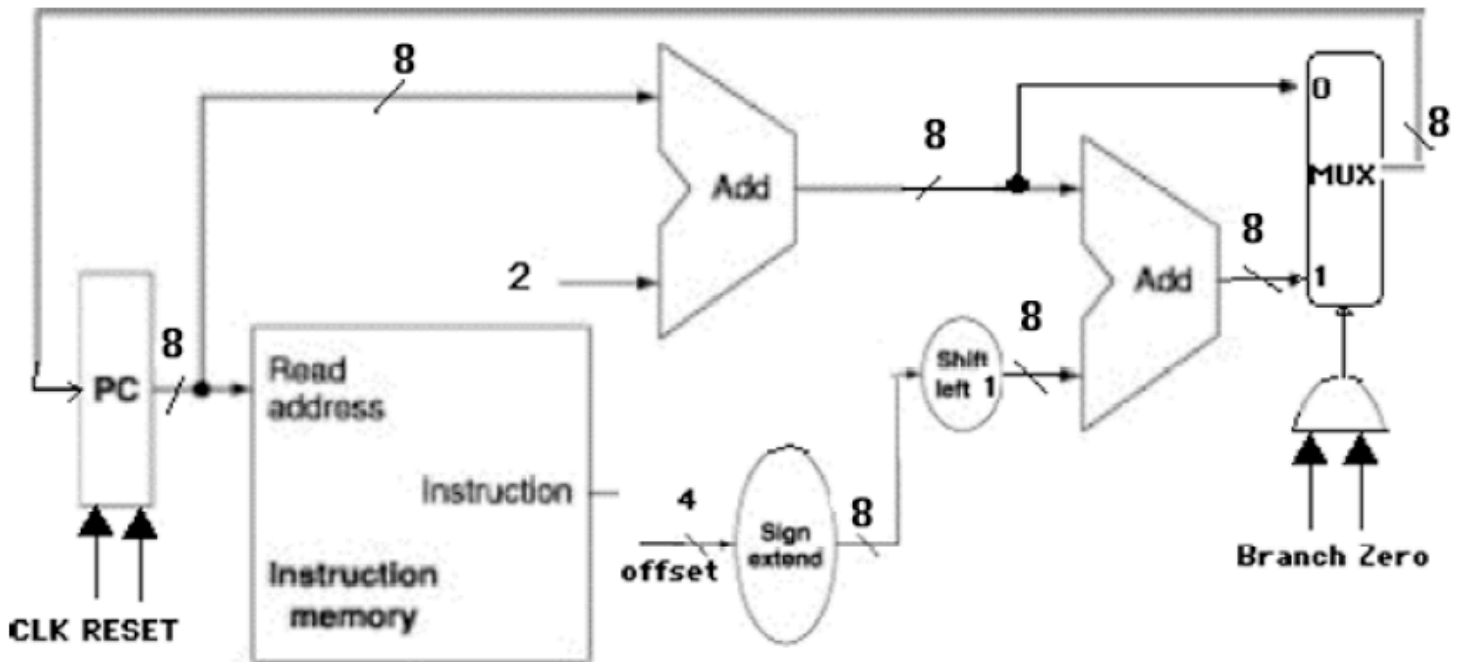


BEQ Rs,Rt,offset

- The **offset** = number of instructions away from the next value of the PC to branch to, so must be multiplied by 2.
- Since **offset** is 4 bits, it must be sign-extended to 8 bits to be added to the PC.

A **MUX** selects the next value of the PC. The value of the **Branch** and **Zero** bits are used to determine which is used:

- The **Branch** control line = 1 if a BEQ instruction is being executed.
- The **Zero** bit from the ALU is used to check whether $R_s = R_t$: it is 1 if $R_s - R_t = 0$ (meaning they're equal). If **Branch** = 1 and **Zero** = 1, then the next value of the PC will be the branch address ; otherwise, it will simply be **PC + 2**

Datapath

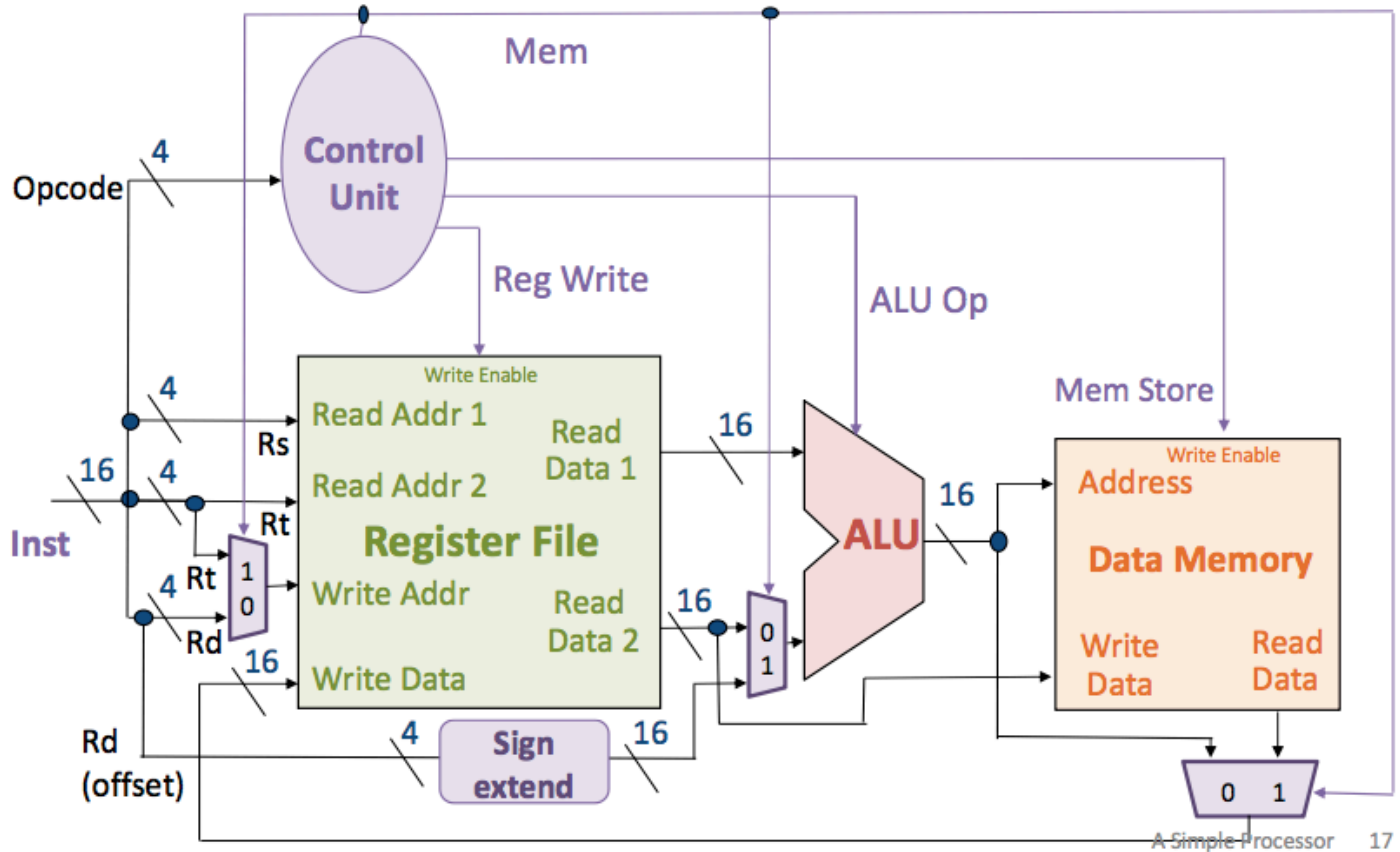

R-type instructions ADD,SUB,AND,OR have format: **opcode Rs Rt Rd**

- read **Rs** and **Rt** from register file
- perform an ALU operation on the contents of the registers
- write the result to register **Rd** in register file

Memory Access instructions LW,SW have format: **opcode Rt offset(Rs)**

- **offset** is in the position in the instruction where **Rd** is for R-type instructions
- memory address = **Rs** + sign-extended 4-bit offset
- if **SW**, the value to be stored to memory is from **Rt**
- if **LW**, **Rt** is loaded with the value read from memory

Register written to in regfile is specified by **Write Addr**, which is either **Rd** or **Rt** (chosen by MUX which is controlled by **MemLoad**)

ALU operates on **Rs** and **Rt**, or on **Rs** and the sign-extended **offset**

- Input A of the ALU is always **Rs**
- Input B of the ALU is **Rt** or the **offset** (chosen by a MUX controlled by **MemLoad**)

Control Unit

ALU can perform 4 possible operations:


<u>ALUop</u>	<u>ALU function</u>
0000	a AND b
0001	a OR b
0010	a + b (add)
0110	a - b

The Control Unit select the proper ALU operation for each instruction, along with the proper control signals, based on the opcode:

<u>Instruction</u>	<u>Opcode</u>	<u>ALUop</u>	<u>RegWrite</u>	<u>MemLoad</u>	<u>MemStore</u>	<u>Branch</u>	<u>Jump</u>
LW	0000	0010	1	1	0	0	0
SW	0001	0010	0	1	1	0	0
ADD	0010	0010	1	0	0	0	0
SUB	0011	0110	1	0	0	0	0
AND	0100	0000	1	0	0	0	0
OR	0101	0001	1	0	0	0	0
BEQ	0111	0110	0	0	0	1	0
JMP	1000	don't care	0	0	0	0	1

Can use decoders or simple logic to produce these signals.

Full Implementation

 

Procedure to Load/Execute a New Program

1. Disconnect the address bus of the Instruction Memory from the CPU
2. Set **LOAD** = 0
3. Set **address** and **data** switches for instruction
4. Set **WR** = 0, then back to 1
5. Repeat steps 3 and 4 until all instructions are loaded to memory
6. Set **LOAD** = 1
7. Reconnect address bus to CPU
8. Set **Reset** = 1, then back to 0
9. Set **CLK** = 1, then back to 0, for each instruction.

Address	Instruction	Rs	Rt	Rd/offset	Purpose
0:	ADD	R1	R1	R2	; R2 = 2
2:	ADD	R2	R2	R3	; R3 = 4
4:	ADD	R3	R3	R3	; R3 = 8
6:	SW	R0	R3	0	; data address 0: 8
8:	SW	R0	R2	2	; data address 2: 2
A:(LOOP)	LW	R0	R5	0	; R5 <- 8 from address 0
C:	LW	R0	R4	2	; R4 <- 2 from address 2
E:	SUB	R5	R4	R5	; R5 <- 8 - 2 = 6
10:	SW	R0	R5	4	; data address 4: 6
12:	LW	R0	R15	4	; R15 <- contents of address 4
14:	OR	R15	R15	R15	; displays R15 at ALU result
16:	BEQ	R2	R15	LOOP	; repeat the starting at label loop
18:	J			END	; jump to end of program

...

1E: (END):