





Logic for Arithmetic

adders



Arithmetic Logic Unit

Addition: 1-bit *half* adder

  


A	B	Carry out	Sum
0	0		
0	1		
1	0		
1	1		

Addition: 1-bit *full* adder

  

Carry in	A	B	Carry out	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


Addition: *n*-bit *ripple-carry* adder

 


There are faster, more complicated ways too...

Processor Components

Abstraction!

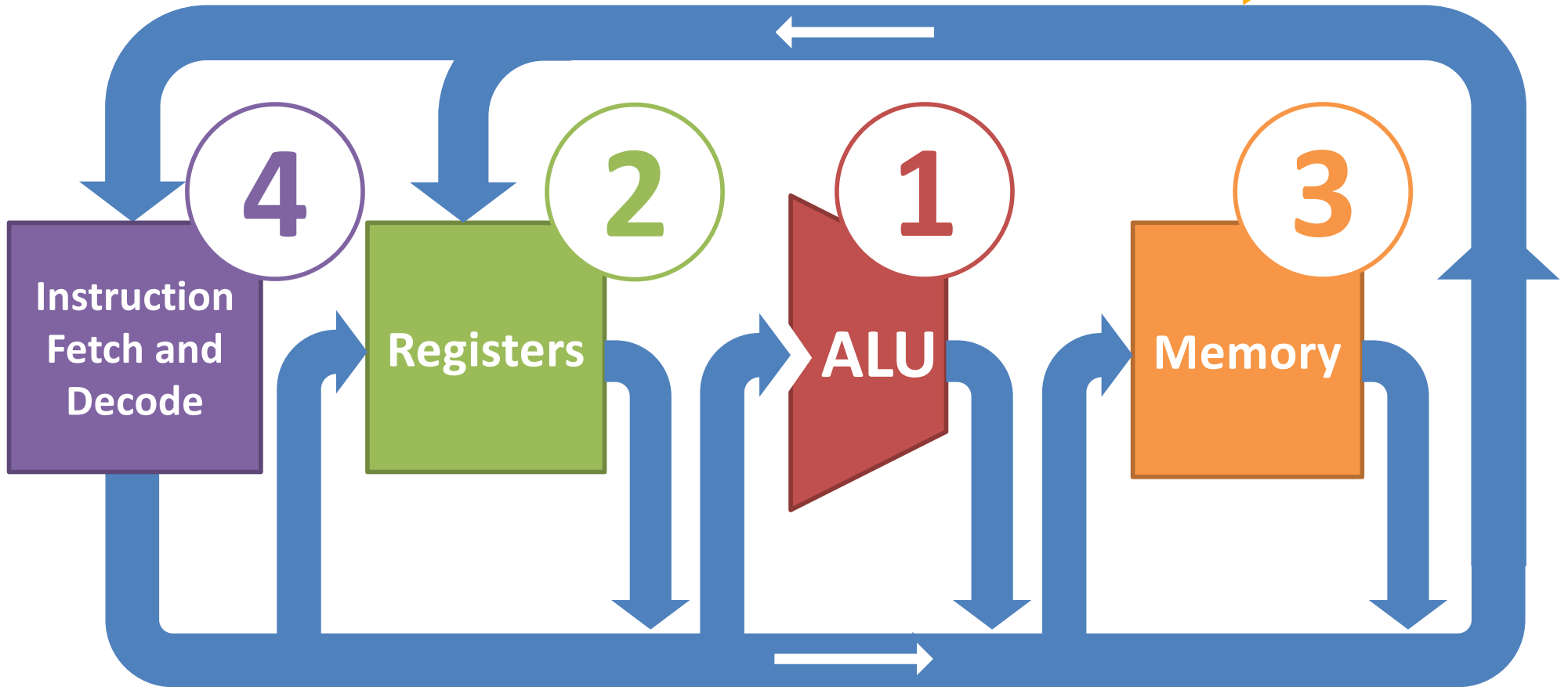

Arithmetic Logic Unit (ALU)

 


Hardware unit for arithmetic and bitwise operations.

1-bit ALU for bitwise operations




Build an n-bit ALU from n 1-bit ALUs.

 Each bit i in the result is computed from the corresponding bit i in the two inputs.




Op	A	B	Result
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


1-bit ALU

 

n-bit ripple carry adder

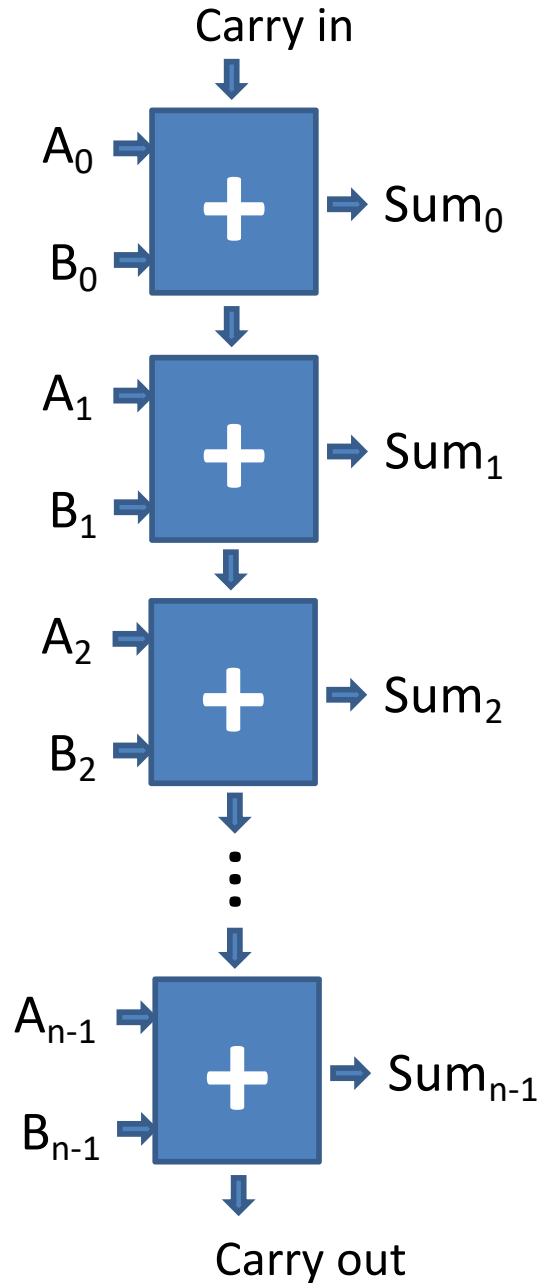

n-bit ALU

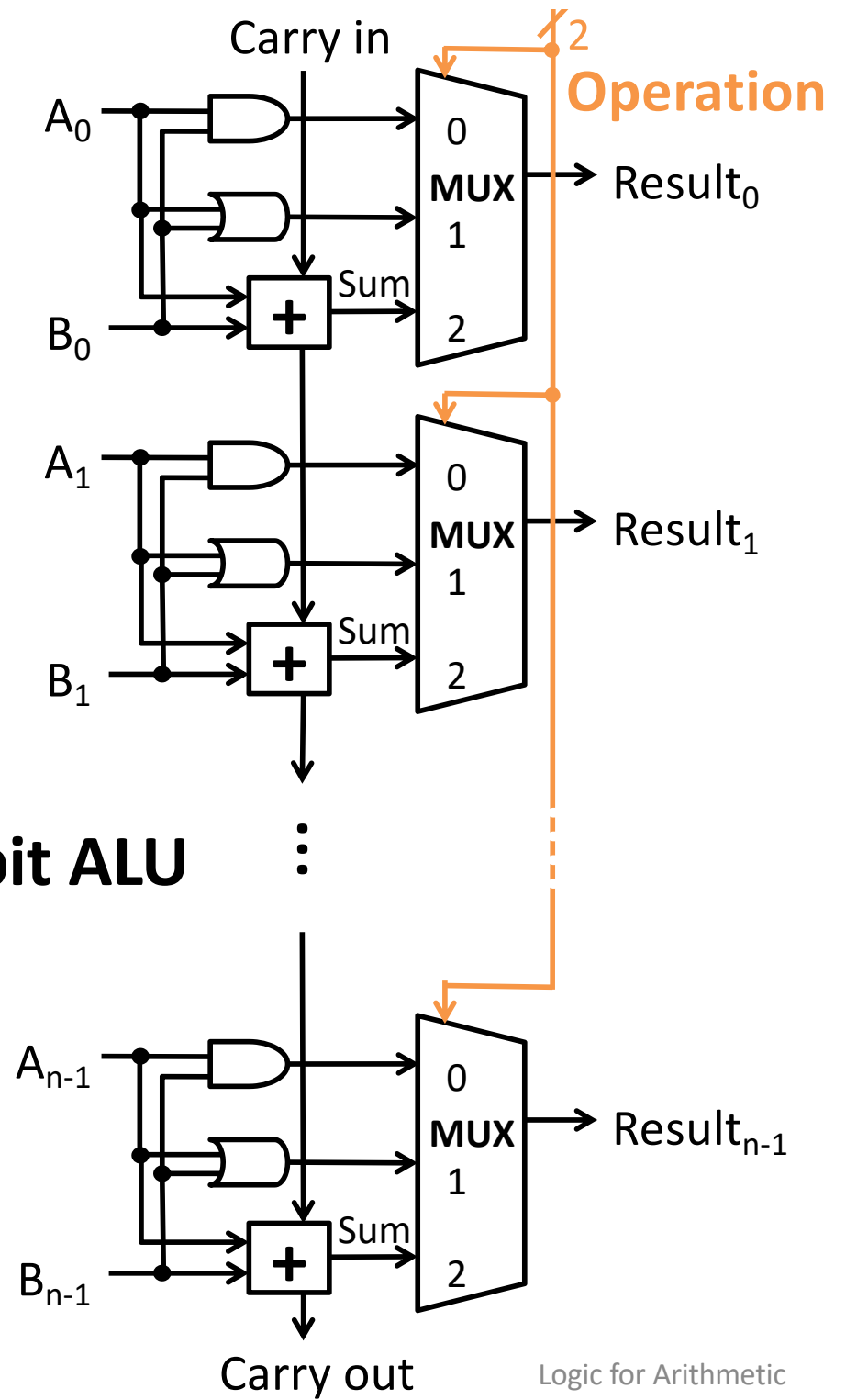

ALU conditions

Extra ALU outputs

describing properties of result.

Zero Flag: ex

1 if result is 00...0 else 0

Sign Flag: ex

1 if result is negative else 0


Carry Flag:

1 if carry out else 0

(Signed) Overflow Flag:


1 if signed overflow else 0

Implement these.

 

Add subtraction

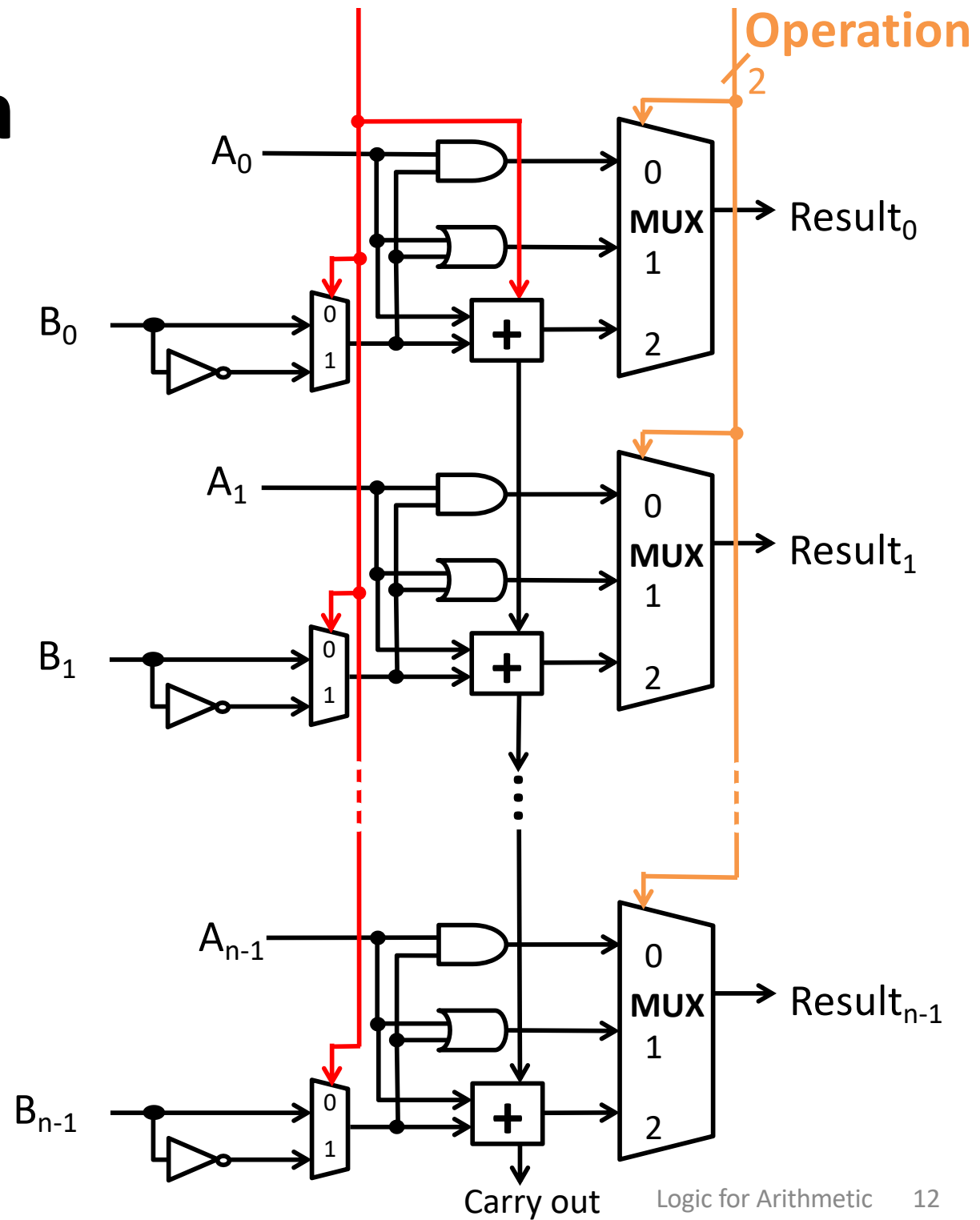How can we control ALU inputs or add minimal new logic to **compute A-B**?



ex


A NAND B

A NOR B

A < B

A == B

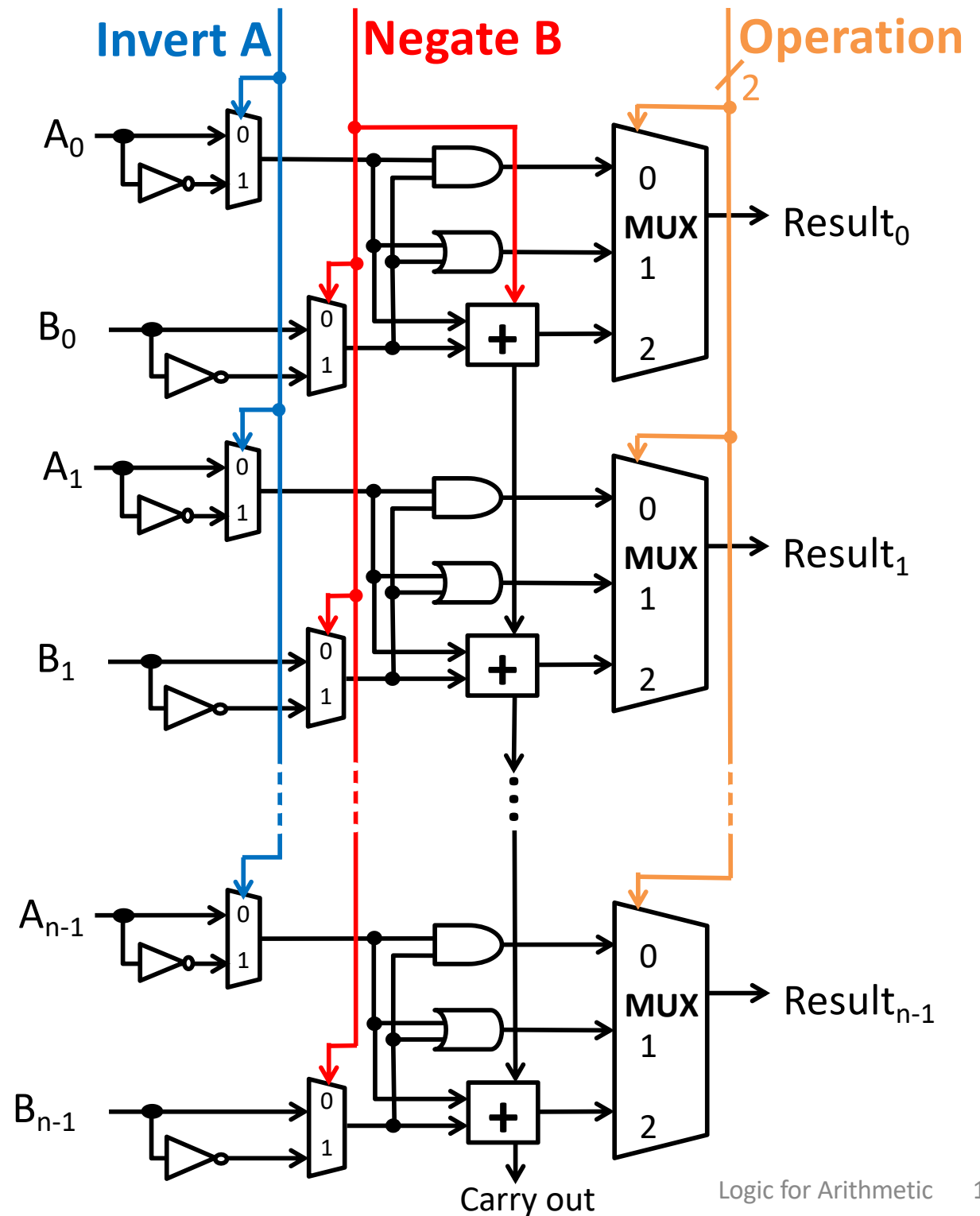How can we control ALU inputs or add minimal new logic to compute each?



Controlling the ALU



ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
1100	NOR

