



Digital Logic

Gateway to computer science

transistors, gates, circuits, Boolean algebra

Software

Program, Application

Programming Language

Compiler/Interpreter

Operating System

Instruction Set Architecture


Microarchitecture

Digital Logic

Devices (transistors, etc.)

Solid-State Physics

Hardware

 


Digital data/computation = Boolean

Boolean value (*bit*): 0 or 1

Boolean functions (AND, OR, NOT, ...)

Electronically:

bit = high voltage vs. low voltage

 

Boolean functions = logic gates, built from transistors




Transistors (more in lab)

If **Base voltage is high:**

Current may flow freely from *Collector* to *Emitter*.

If **Base voltage is low:**

 
Current may not flow from *Collector* to *Emitter*.



Truth table

V_{in}	V_{out}	=	in	out	=	in	out
low	high	=	0	1	=	F	T
high	low		1	0		T	F

NOT gate

 

Abstraction!


Digital Logic Gates

Abstraction!

ex



Tiny electronic devices that compute basic Boolean functions.

NOT

 


V_{in}	V_{out}
0	1
1	0

	V_2	
V_1	0	1
0		
1		

  


Integrated Circuits (1950s -)


Early (first?) transistor

 


Chip

 


Wafer

 


Small integrated circuit

 

 
Five basic gates: define with truth tables




NOT	
0	1
1	0

 


NAND	0	1
0	1	1
1	1	0

 

NOR	0	1
0		
1		

 

AND	0	1
0		
1		

 


OR	0	1
0		
1		

Boolean Algebra


for combinational logic

 inputs = *variables*
wires = *expressions*
gates = *operators/functions*
circuits = *functions*




AND = Boolean product

·	0	1
0	0	0
1	0	1

 


OR = Boolean sum

+	0	1
0	0	1
1	1	1

 

NOT = inverse or complement

0	1
1	0

 


wire = identity

0	0
1	1

Circuits

 Connect inputs and outputs of gates with wires.
Crossed wires touch *only if* there is a dot.



What is the output if $A=1$, $B=0$, $C=1$?

What is the truth table of this circuit?

What is an equivalent Boolean expression?


Translation

Connect gates to implement these functions. Check with truth tables.
Use a direct translation -- it is straightforward and bidirectional.



$$F = (A\bar{B} + C)D$$

$$Z = \bar{W} + (X + \bar{W}Y)$$

 
Note on notation: bubble = inverse/complement




Identity law, inverse law

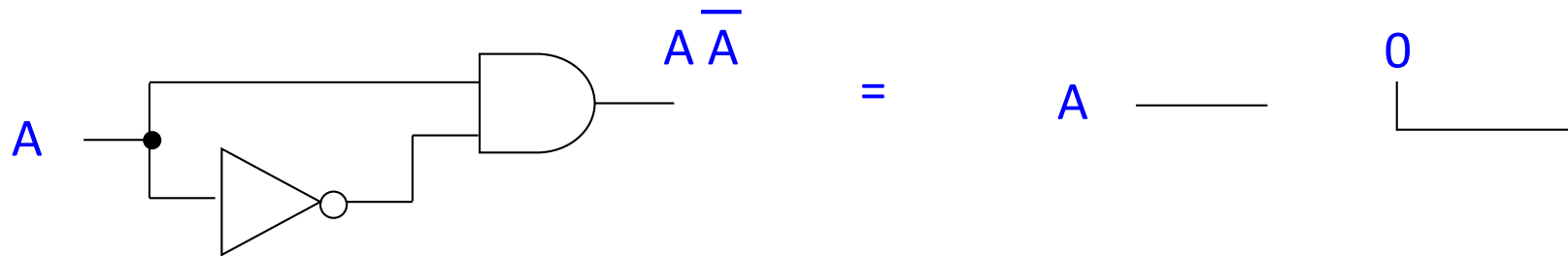 


Commutativity, Associativity

 

Idempotent law, Null/Zero law


 


 Note on notation: bubble = inverse/complement



DeMorgan's Law

 
 
(double bubble, toil and trouble, in Randy's words...)




One law, Absorption law



  Write truth tables. Do they correspond to simpler circuits?




NAND is *universal*.

 

All Boolean functions can be implemented using only NANDs.
Build NOT, AND, OR, NOR, using only NAND gates.

XOR: Exclusive OR

 

Output = 1 if exactly one input = 1.

Truth table:


Build from earlier gates:

Often used as a one-bit comparator.

Larger gates



 
Build a 4-input AND gate using any number of 2-input gates.





Circuit simplification

 Is there a simpler circuit that performs the same function?



Start with an equivalent Boolean expression, then simplify with algebra.


$$F(A, B, C) =$$

Check the answer with a truth table.

Circuit derivation: *code detectors*



 AND gate + NOT gates = code detector, recognizes exactly one input code.



Design a 4-input code detector to output 1 if ABCD = 1001, and 0 otherwise.

A _____
B _____
C _____
D _____

Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others. (accept = 1, reject = 0)

Circuit derivation: *sum-of-products* form



logical sum (OR)

of products (AND)

of inputs or their complements (NOT)

Draw the truth table and design a sum-of-products circuit for a 4-input code detector to accept two codes (ABCD=1001, ABCD=1111) and reject all others.

How are the truth table and the sum-of-products circuit related?

Voting machines

A majority circuit outputs 1 if and only if a majority of its inputs equal 1.
Design a majority circuit for three inputs. Use a sum of products.

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Triply redundant computers in spacecraft

- Space program also hastened Integrated Circuits.

Computers

- Manual calculations
- powered all early US **space** missions.
- Facilitated transition to digital computers.



Mary Jackson




Katherine Johnson

- Supported Mercury, Apollo, Space Shuttle, ...

Dorothy Vaughn

 - First black supervisor within NACA
- Early self-taught FORTRAN programmer for NASA move to digital computers.



Early pioneers in reliable computing



Katherine Johnson

- Calculated first US human space flight trajectories
- Mercury, Apollo 11, Space Shuttle, ...
- Reputation for accuracy in manual calculations, verified early code
- Called to verify results of code for launch calculations for first US human in orbit
- Backup calculations helped save Apollo 13
- Presidential Medal of Freedom 2015



Margaret Hamilton

- Led software team for Apollo 11 Guidance Computer, averted mission abort on first moon landing.
- Coined “software engineering”, developed techniques for correctness and reliability.
- Presidential Medal of Freedom 2016

Apollo 11 code print-out

