



# Sequential Logic and State


Latch: CC-BY Rberteig@flickr



Output depends on inputs *and* stored values.  
 (vs. combinational logic: output depends only on inputs)


Elements to store values: latches, flip-flops, registers, memory

## Processor: Data Path Components

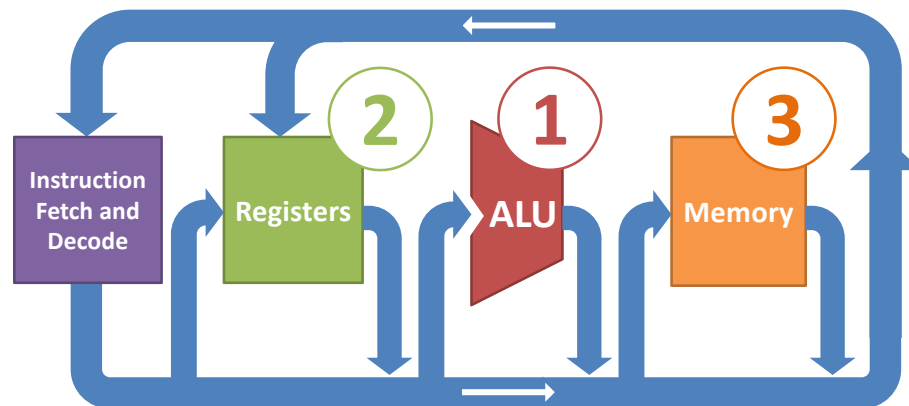

 
## Bistable latches

Suppose we somehow get a 1 (or a 0?) on here.




==

 


## SR latch

| S | R | Q | Q' | Q (stable) | Q' (stable) |
|---|---|---|----|------------|-------------|
| 0 | 0 | 0 | 1  | 0          | 1           |
| 0 | 0 | 1 | 0  | 1          | 0           |
| 1 | 0 | ? | ?  | 1          | 0           |
| 0 | 1 | ? | ?  | 0          | 1           |

 


## SR latch

 

Sequential Logic 5

## D latch

 

if  $C = 0$ , then SR latch stores current value of  $Q$ .

if  $C = 1$ , then  $D$  flows to  $Q$ :


if  $D = 0$ , then  $R = 1$  and  $S = 0$ ,  $Q = 0$

if  $D = 1$ , then  $R = 0$  and  $S = 1$ ,  $Q = 1$

Sequential Logic 6

## Time matters!

ex

 


Assume  $Q$  has an initial state of 0

Sequential Logic 7
 
## Clocks

**Clock:** free-running signal  
with fixed cycle time = clock period =  $T$ .

Clock frequency =  $1 / \text{clock period}$




A clock controls when to update a sequential logic element's state.





Sequential Logic 8
 
# Synchronous systems

Inputs to state elements must be **valid** on active clock edge.




# D flip-flop with falling-edge trigger

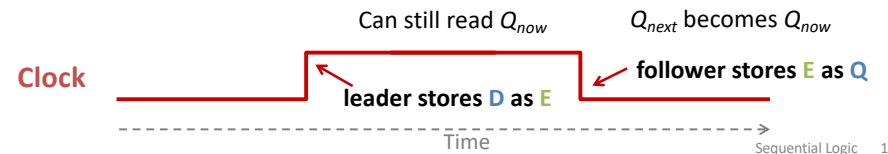 


# Time matters!

ex

 


Assume Q and E have an initial state of 0

# Reading and writing in the same cycle

 

Assume Q is initially 0.


# D flip-flop = one bit of storage

 


# A 1-nybble\* register

(a 4-bit hardware storage cell)

\*Half a byte!

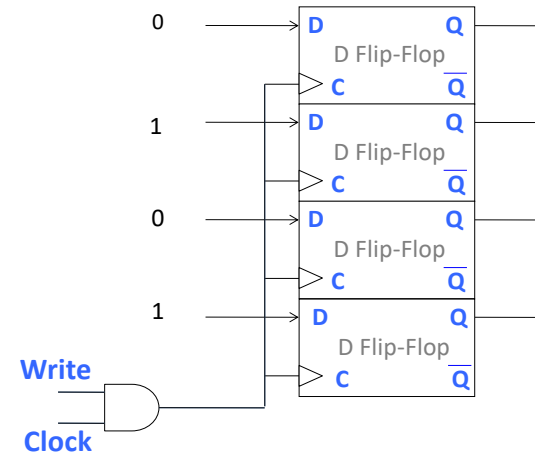


# Register file

 


Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.


# Read ports (data out)

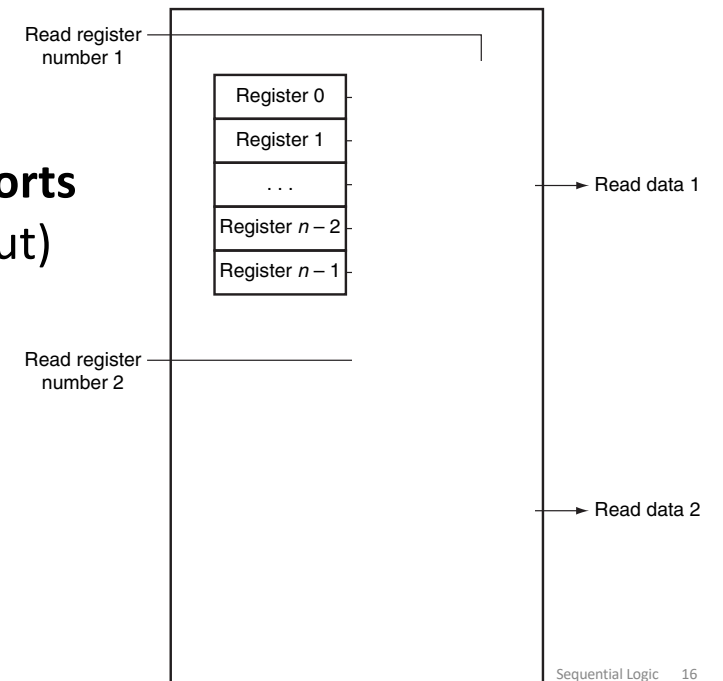

## Write port (data in)

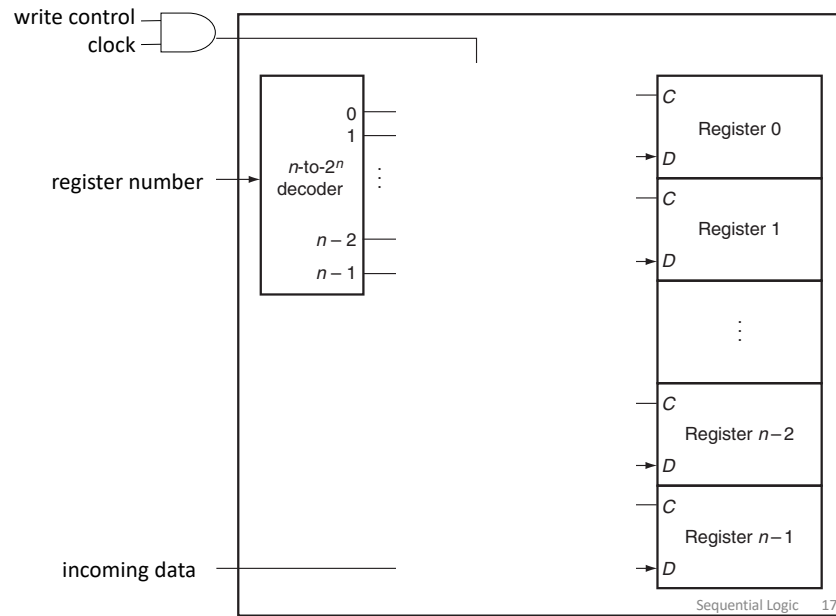

## RAM (Random Access Memory)

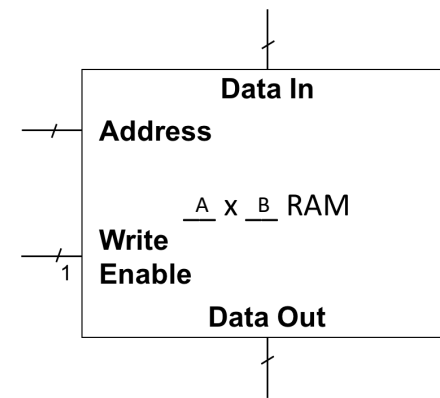

Similar to register file, except...

## 16 x 4 RAM

