

**CS240 Laboratory 3**  
**Arithmetic Logic Unit (ALU)**  
**and**  
**Introduction to Memory**

- **Signed Representation Review**
- **4-bit Addition with Ripple-Carry**
- **Arithmetic Logic Unit**
- **1-bit Memory Circuit (Latch)**

## Signed Representation

Given  $n$  bits, the range of binary values which can be represented using:

**Unsigned representation:**  $0 \rightarrow 2^n - 1$

**Signed representation:**  $-2^{n-1} \rightarrow 2^{n-1} - 1$ , MSB is used for sign

**Two's Complement** (signed representation):

Most significant /leftmost bit (0/positive, 1/negative)

Example: given a fixed number of 4 bits:

$1000_2$  is negative.

$0111_2$  is positive.

## Overflow

Given a fixed number of  $n$  available bits, overflow occurs if a value cannot fit in  $n$  bits.

For example, given 4 bit representation:

The largest negative value we can represent is  $-8_{10}$  ( $1000_2$ )

The largest positive value we can represent is  $+7_{10}$  ( $0111_2$ )

## Overflow when Adding

An overflow occurs when adding two n-bit numbers if the result will not fit in n bits.

An overflow can be detected when:

- Two positive numbers added together yield a negative result, or
- Two negative numbers added together yield a positive result.

Overflow can also be detected when:

- The Cin and Cout bits to the most significant pair of bits being added are not the same.

An overflow cannot result if a positive and negative number are added.

Example: given 4 bits:


$$0111_2$$
$$+ 0001_2$$
$$1000_2 = \text{overflow} \quad \text{NOTE: there is not a carry-out!}$$

In two's complement representation, a carry-out does not indicate an overflow, as it does in unsigned representation.

Example: given 4 bits,

$$1001_2 (-7_{10})$$
$$+ 1111_2 (-1_{10})$$
$$1\ 1000_2 (-8_{10}) \quad \text{no overflow, even though there is a carry-out}$$


# 4-bit Ripple-Carry Adder

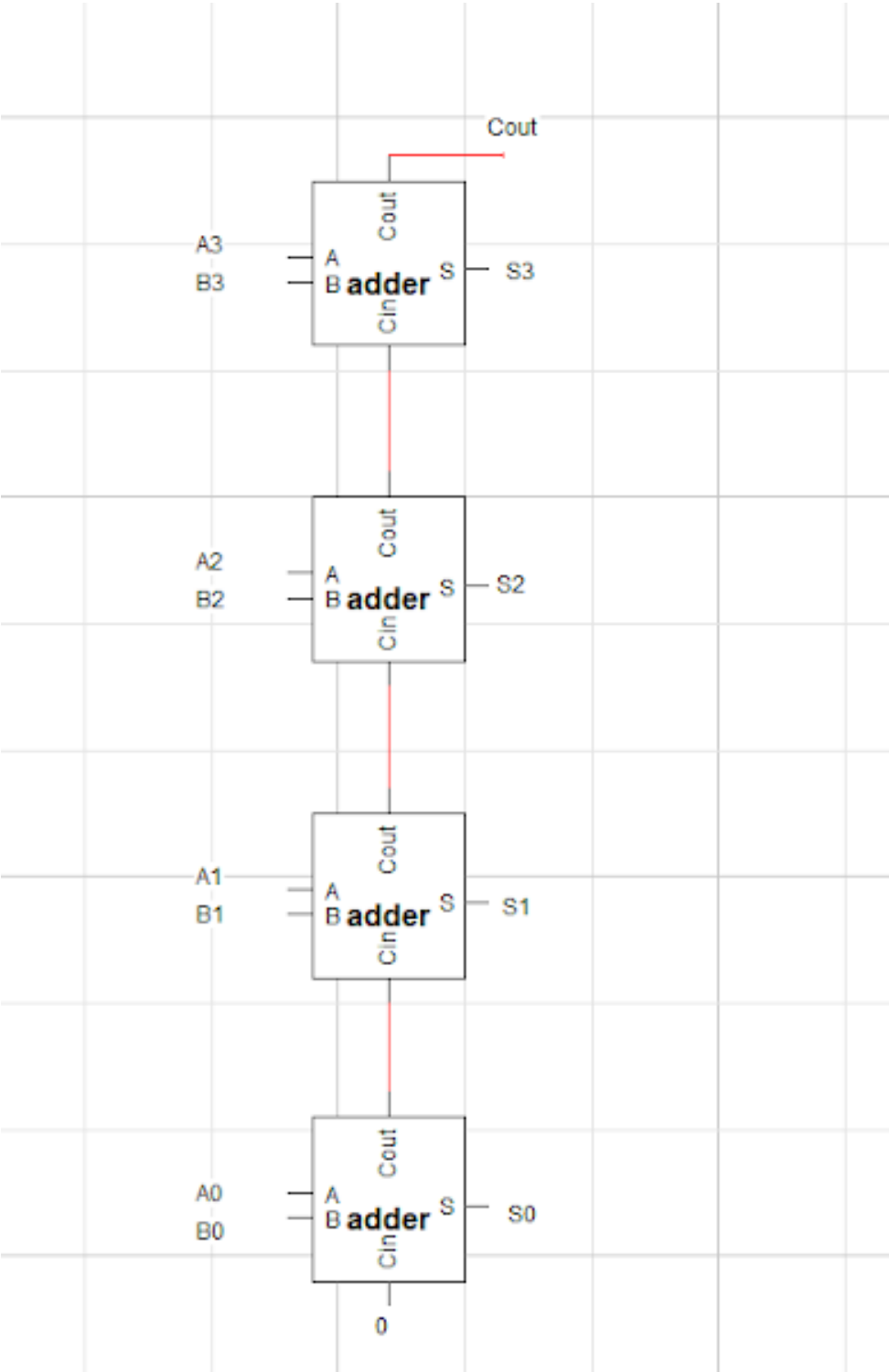
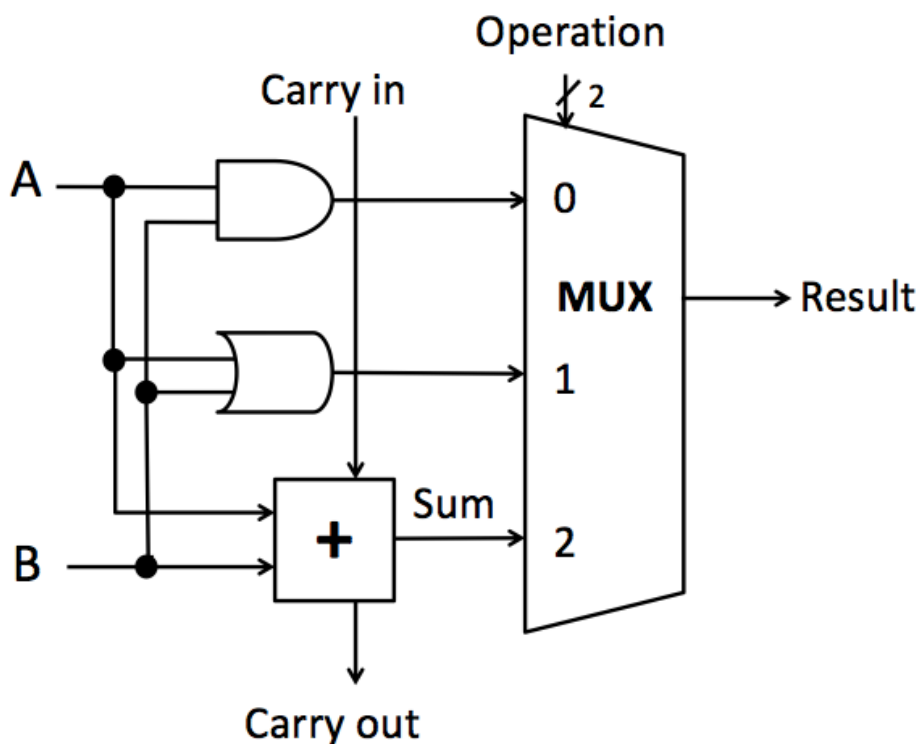
## Arithmetic Logic Unit

An **ALU** is a combinational circuit used to perform all the arithmetic and logical operations for a computer processor.

A simple 1-bit ALU can be built using the basic components you have learned about: **AND** gate, **OR** gate, **1-bit adder**, and **multiplexer**:



Arithmetic Logic


The **Operation** (a 2-bit value), selects which operation should be produced as the **Result**:

<u>Operation bits</u>	<u>Result</u>
0 0	A AND B
0 1	A OR B
1 0	A + B

By adding some additional control inputs, it is possible to get produce additional functions with the ALU.

**Invert A** is used to complement the input A.

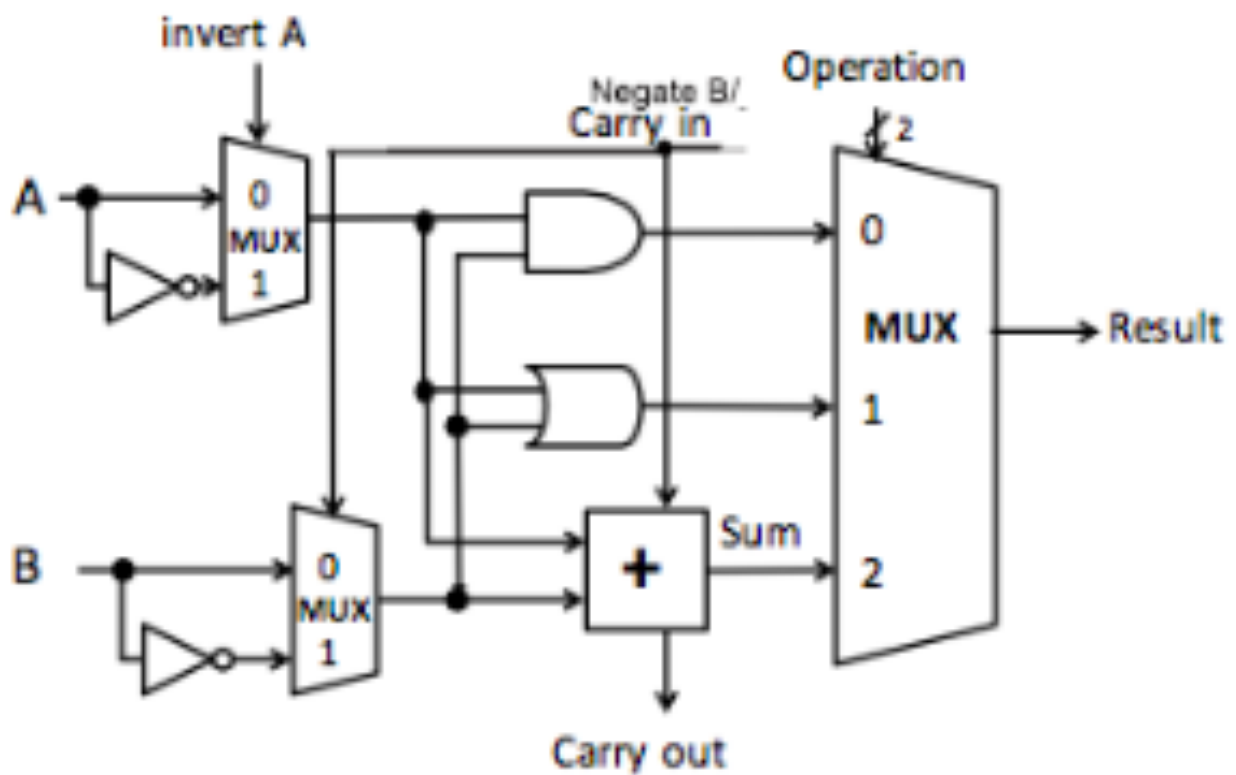**Negate B/Carry in** used to complement input B for logical operations, and as a carry-in when addition is performed.




## Basic Operations

- **add** (operation = add)
- **sub** (negate B/Carry in = 1, operation = ADD)
- **AND** (operation = AND)
- **OR** (operation = OR)
- **NOR** (invertA=1, negateB=1, operation = AND)

<b>Control Inputs</b>				<b>Result</b>
<u>invertA</u>	<u>negateB</u>	<u>Operation</u>		
0	0	0	0	a AND b
0	0	0	1	a OR b
0	0	1	0	a + b
0	1	1	0	a - b
1	1	0	0	a NOR b

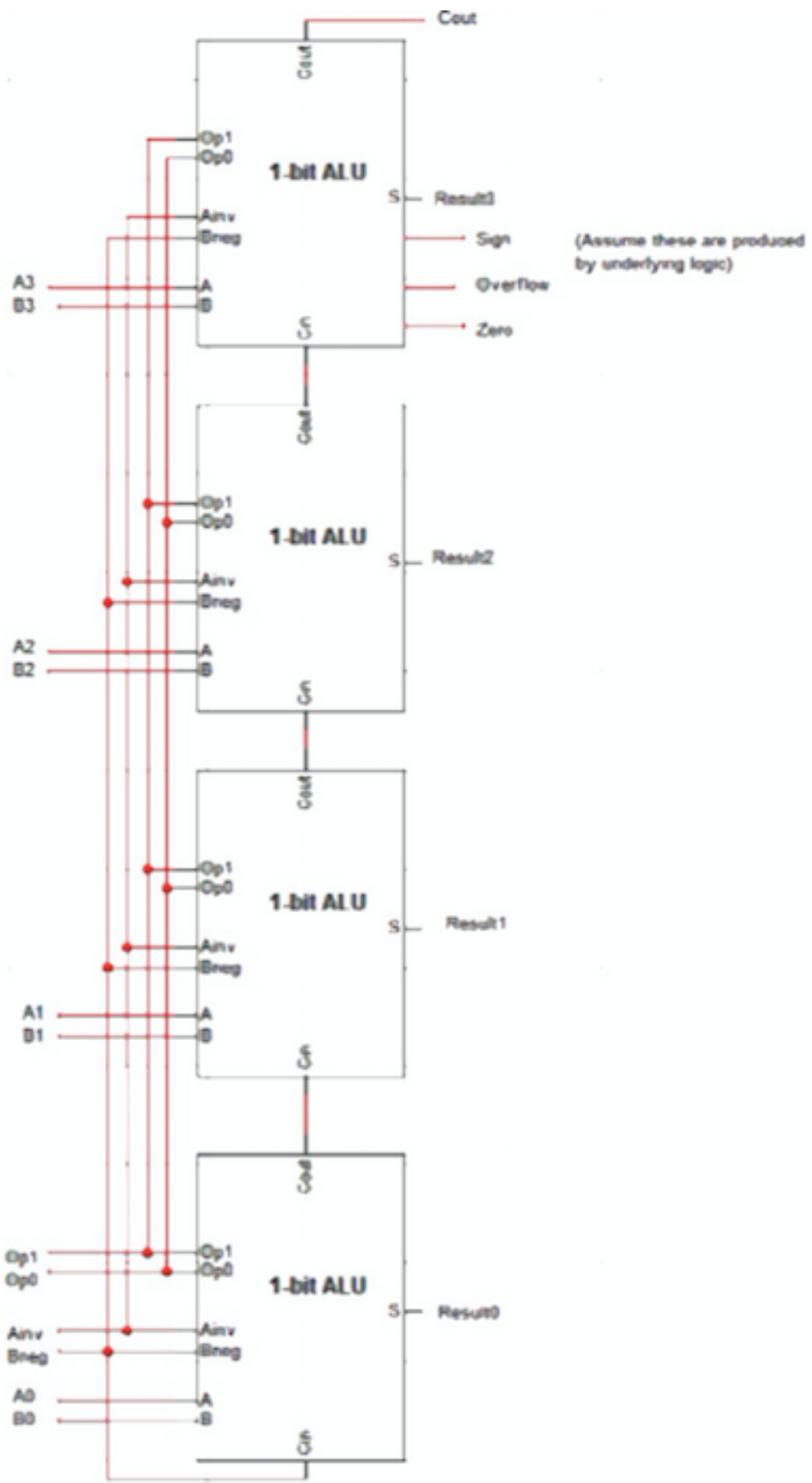A 4-bit ALU can be built from 4 1-bit ALUs in the same way that a 4-bit adder can be built from 1-bit adders:






How do you produce the Sign, Overflow, and Zero bits?

## Basic Memory Circuit

**Latch** Single-bit memory, level-triggered

### SR (Set Reset) Latch

 

<b>S</b>	<b>R</b>	<b>Q</b>	<b>Q'</b>	
0	0	Q <sub>p</sub>	Q <sub>p</sub> '	remember
0	1	0	1	reset/clear
1	0	1	0	set
1	1			unpredictable

What does **unpredictable** mean? Notice in a NOR gate, if either input = 1 to a gate, its output = 0 (1 is a deterministic input):

<b>A</b>	<b>B</b>	<b>(A+B)'</b>
0	0	1
0	1	0
1	0	0
1	1	0


So, although you wouldn't usually try to *set* and *reset* at the same time (it doesn't make sense), if you did, Q and Q' will both be 0 (which is not unpredictable).

However, when you go back to the *remember* state ( $S=R=0$ ),  $Q$  and  $Q'$  will not stay at 0. The circuit passes through one of either the *set* or *reset* state on its way back to the *remember* state, and  $Q$  and  $Q'$  change to the complement of one another.

Since the final state depends on which transitional state was sensed on the way back to *remember*, you cannot predict whether the final state of  $Q$  will be 1 or 0.

### **Clocked SR Latch**

Incorporates a clock input.

 

Output  $Q$  can change in response to  $S$  and  $R$  whenever the  $CK$  input is asserted.