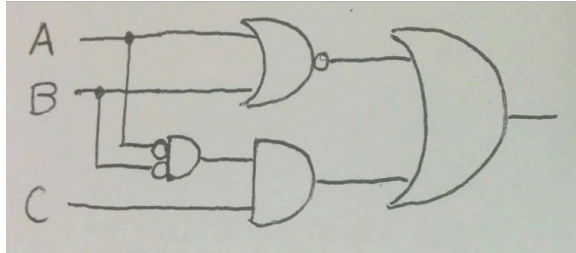


CS240 Supplemental Practice – Gates

1) For the following circuit, answer the following questions



a. Write out its truth table:

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

b. What is the equivalent, unsimplified Boolean expression? In other words, what is the Boolean algebra translation of the circuit above?

$$(A + B)' + (A'B')C$$

c. What is the sum of products expression of the truth table?

$$A'B'C + A'B'C'$$

d. Simplify your answer from part b using Boolean algebra laws. As a sanity check, you should be able to simplify your expression from part c and arrive at the same answer.

$$(A + B)' + (A'B')C \text{ - Original equation from part b}$$


$$A'B' + (A'B')C \text{ - DeMorgan's Law}$$

$$A'B' \text{ - Absorption}$$

$$A'B'C + A'B'C' \text{ - Original equation from part c}$$

$$A'B' \text{ - Combining}$$

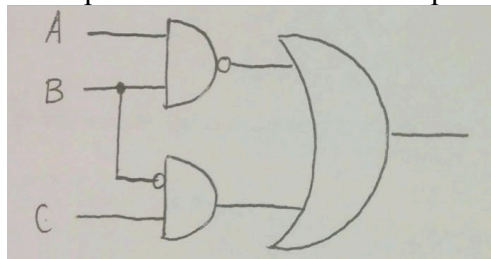Extra practice: answer the same questions above with this circuit



a. Write out its truth table:

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

b. What is the equivalent, unsimplified Boolean expression? In other words, what is the Boolean algebra translation of the circuit above?

$$(AB)' + B'C$$

c. What is the sum of products expression of the truth table?

$$A'B'C' + A'B'C + A'BC' + A'BC + AB'C' + AB'C$$

d. Simplify your answer from part b using Boolean algebra laws. As a sanity check, you should be able to simplify your expression from part c and arrive at the same answer.


$$\begin{aligned} &(AB)' + B'C - \text{Original equation from part b} \\ &A' + B' + B'C - \text{DeMorgan's} \\ &A' + B' - \text{Absorption} \end{aligned}$$

$$\begin{aligned} &A'B'C' + A'B'C + A'BC' + A'BC + AB'C' + AB'C - \text{Original equation from} \\ &\text{part c} \\ &A'B' + A'BC' + A'BC + AB'C' + AB'C - \text{Absorption} \\ &A'B' + A'B + AB'C' + AB'C - \text{Absorption} \\ &A'B' + A'B + AB' - \text{Absorption} \\ &A' + AB' - \text{Absorption} \\ &(A' + A)(A' + B') - \text{Distributive} \end{aligned}$$

(1)(A' + B') – Inverse
A' + B' - Identity

2) For the Boolean expression: $(A'A + (BC)')' + B$

a. Draw the unsimplified circuit:

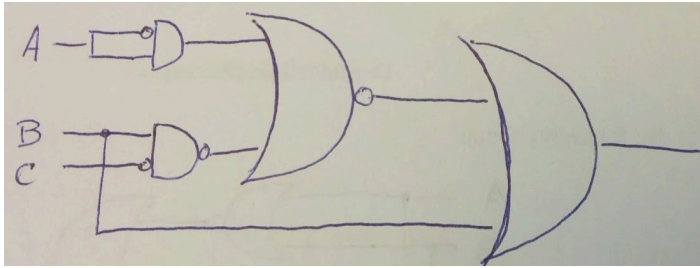

b. Write out its truth table:

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

c. Simplify or shorten the expression step-by-step using Boolean algebra laws, and write the corresponding laws next to each step

$(A'A + (BC)')' + B$ – Original equation

$(0 + (BC)')' + B$ – Inverse


$((BC)')' + B$ – Identity

$(BC) + B$ – Negation

B – Absorption

Extra practice: answer the questions above with this Boolean algebra expression $(A + ABC')B$

a. Draw the unsimplified circuit:

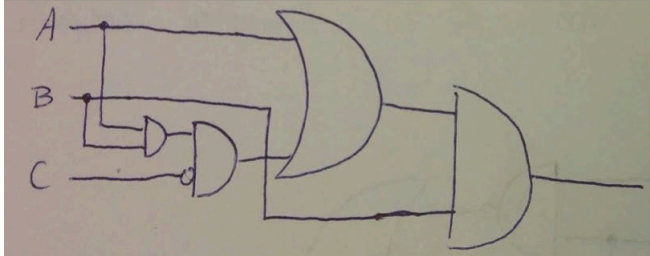

b. Write out its truth table:

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

c. Simplify or shorten the expression step-by-step using Boolean algebra laws, and write the corresponding laws next to each step

$(A + ABC')B$ – Original Equation

AB – Absorption