

About how many total hours did you spend actively working on this assignment? \_\_\_\_\_

**Q1 [4 points]** Time spent on Q1: \_\_\_\_\_

**F1 =**

**F2 =**

A	B	C		F1	F2
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

**Q2 [6 points]** Time spent on Q2: \_\_\_\_\_

**Draw your three circuits here:**

**Q3 [5 points]** *Time spent on Q3:* \_\_\_\_\_

**a [2]**  $\text{bexp}_3 =$

**b [3]** circuit diagram:

**Q4 [5 points]** *Time spent on Q4:* \_\_\_\_\_

**a [2]**  $\text{bexp}_4 =$

**b [3]** circuit diagram:

**Q5 [10 points]** *Time spent on Q5:* \_\_\_\_\_

**Truth table for parts a [2] and c [1]**

A	B	AB	A'B'	AB + A'B'	$\text{bexp}_{5b}$	AB + $\text{bexp}_{5b}$
0	0					
0	1					
1	0					
1	1					

*Below, show steps in deriving the answer expressions*

**b [1]**  $\text{bexp}_{5b} =$

**d [1.5]**  $\text{bexp}_{5d} =$

**e [2]**  $\text{bexp}_{5e} =$

**f [2.5]**  $\text{bexp}_{5f} =$







**Q7 [12 points]** *Time spent on Q7: \_\_\_\_\_*

**Q7a [6]** Express XOR in terms of 2-input NAND gates. Show both the final circuit  
\*and\* your derivation/explanation

*Time spent on Q7a: \_\_\_\_\_*

**Q7b [6] Express XOR in terms of 2-input NOR gates. Show both the final circuit  
\*and\* your derivation/explanation.**

*Time spent on Q7b: \_\_\_\_\_*