



Latch: CC-BY Rberteig@flickr



# Sequential Logic and State



Output depends on inputs *and stored values*.  
(vs. combinational logic: output depends only on inputs)

Elements to store values: latches, flip-flops, registers, memory



Latch: CC-BY Rberteig@flickr




# Sequential Logic and State




Output depends on inputs *and stored values*.  
(vs. combinational logic: output depends only on inputs)

Elements to store values: latches, flip-flops, registers, memory

## Processor: Data Path Components

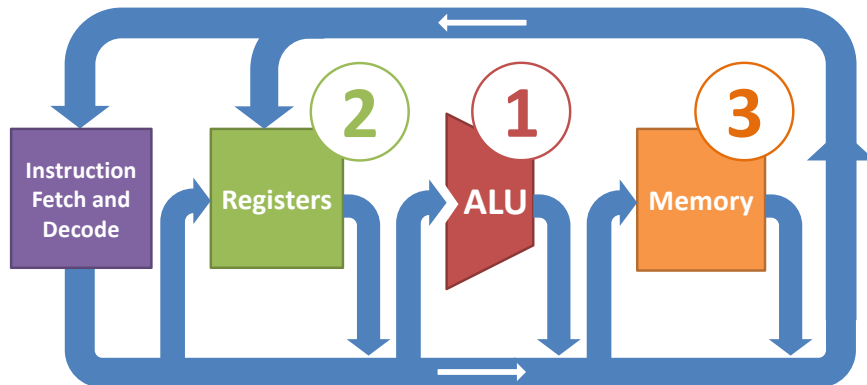

## Unstable circuit

 


Have this issue with any **odd** number of inverters in a loop.

 
# Bistable latches

Things are more sensible with an **even** number of inverters in a loop.

Suppose we somehow get a 1 (or a 0?) on here.




# SR latch

 


S	R	Q <sub>prev</sub>	Q' <sub>prev</sub>	Q <sub>next</sub> (stable)	Q' <sub>next</sub> (stable)
0	0	0	1	0	1
0	0	1	0	1	0
1	0	any	any	1	0
0	1	any	any	0	1
1	1	any	any	0	0

violates invariant that Q and Q' are inverses!

# SR latch

 

# D latch

 


if C = 0, then SR latch stores current value of Q.  
 if C = 1, then D flows to Q:  
 if D = 0, then R = 1 and S = 0, Q = 0  
 if D = 1, then R = 0 and S = 1, Q = 1

Notes:

- Data bit D replaces S & R: it's the bit value we want to store when Clock = 1
  - Internally, Data bit D prevents bad case of S = R = 1
- This logic is **level-triggered**; as long as Clock = 1, changes to D have impact


# Time matters!

 

Assume Q has an initial state of 0
 
# Clocks

Clock: free-running signal with fixed cycle time = clock period = T.  
 Clock frequency = 1 / clock period




A clock controls when to update a sequential logic element's state.




 
# Synchronous systems


Inputs to state elements must be valid on active clock edge.



# D flip-flop with falling-edge trigger

 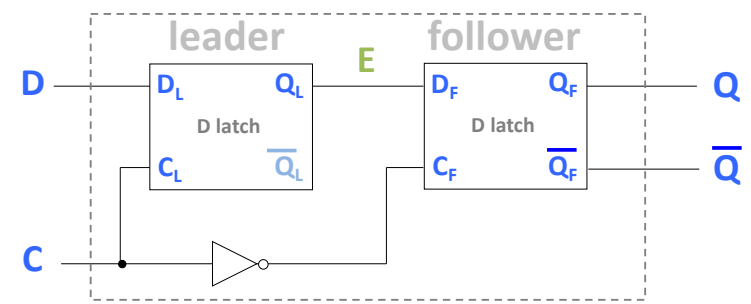


# Time matters!

 

Assume Q and E have an initial state of 0


# Reading and writing in the same cycle

 

Assume Q is initially 0.

Moral: It's OK to use the current output Q of a flip-flop as part of the the next data input D to the same flip-flop.

# D flip-flop = one bit of storage

 


The bit value of D when C has a falling edge is remembered at Q until the next falling edge of C.


# A 1-nybble\* register

(a 4-bit hardware storage cell)

\*Half a byte!

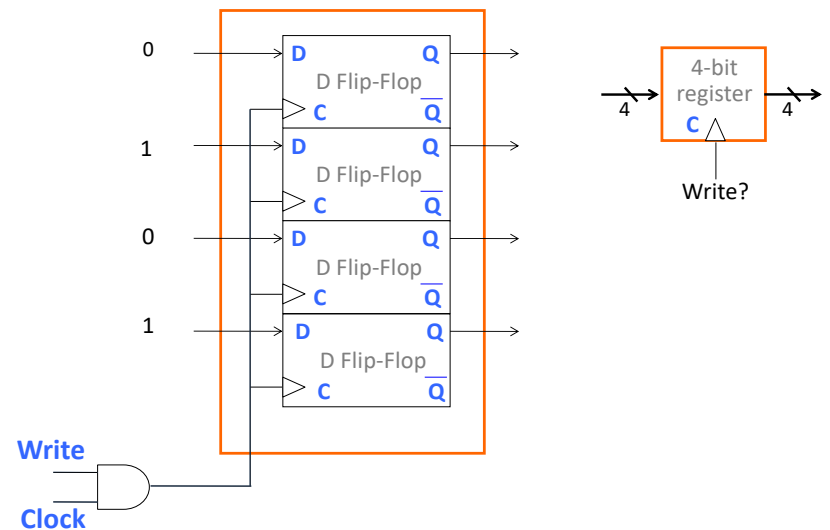


# Register file

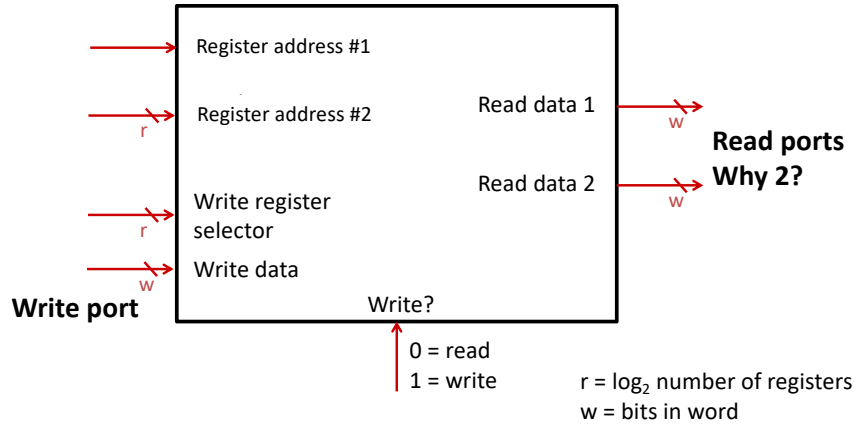


Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.


# Read ports (data out)

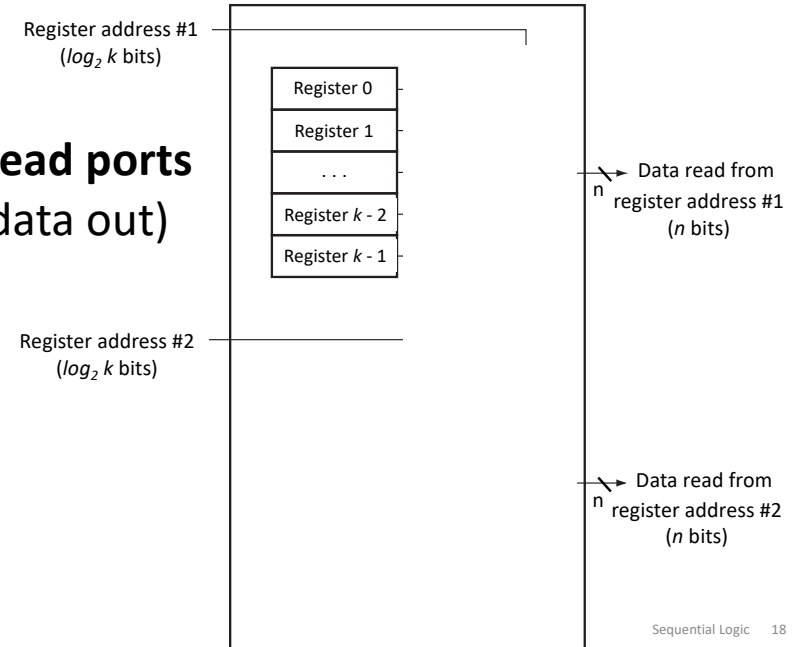


# Read ports (data out)

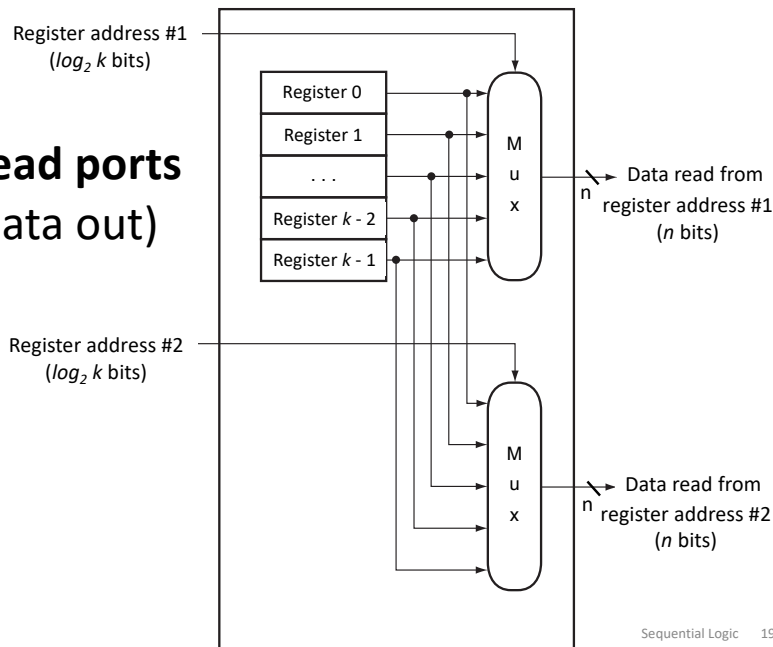


# Write port (data in)

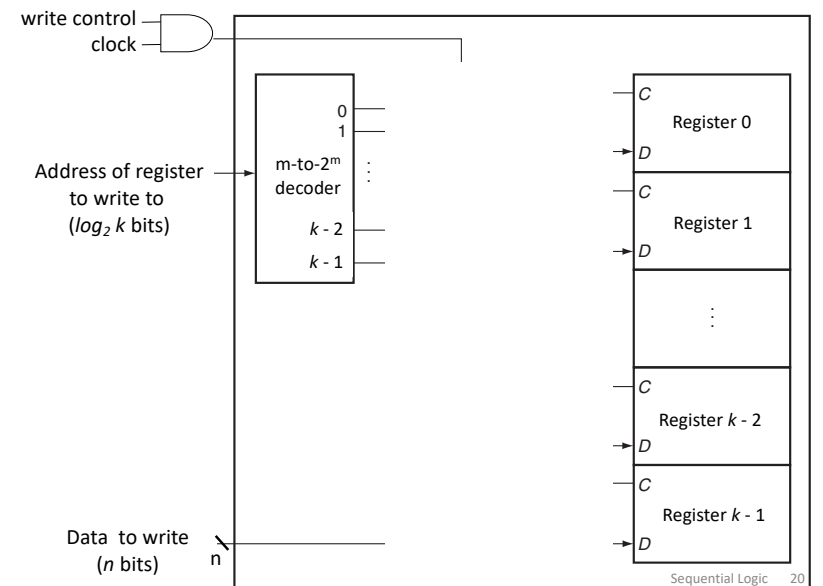

## Write port (data in)

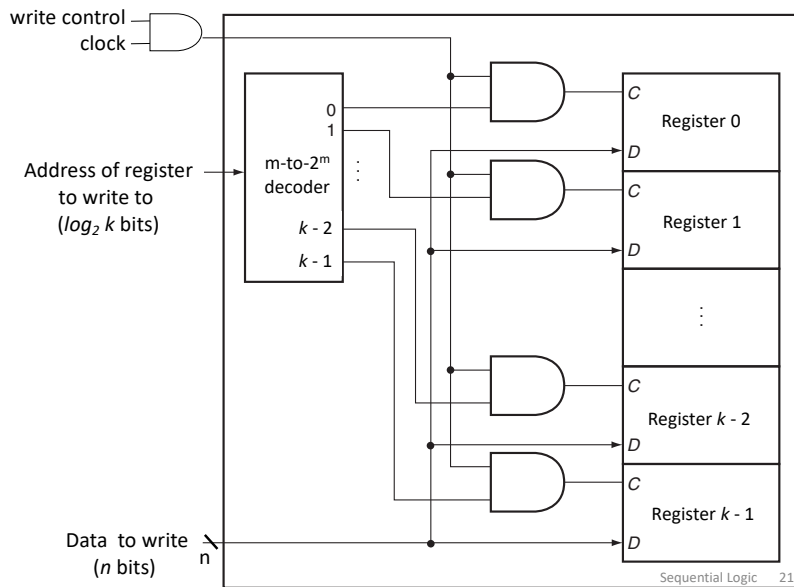

## RAM (Random Access Memory)

 

- A is number of words in RAM
- Specify the desired word by an address of size  $\log_2 A$
- B is the width of each word (in bits)

Similar to register file, except...

## 16 x 4 RAM

