 




Sequential Logic and State

Latch: CC-BY Rberteig@flickr



Output depends on inputs *and stored values*.

(vs. combinational logic: output depends only on inputs)

Elements to store values: latches, flip-flops, registers, memory



Sequential Logic and State

Latch: CC-BY Rberteig@flickr




Output depends on inputs *and stored values*.


(vs. combinational logic: output depends only on inputs)

Elements to store values: latches, flip-flops, registers, memory

Processor: Data Path Components

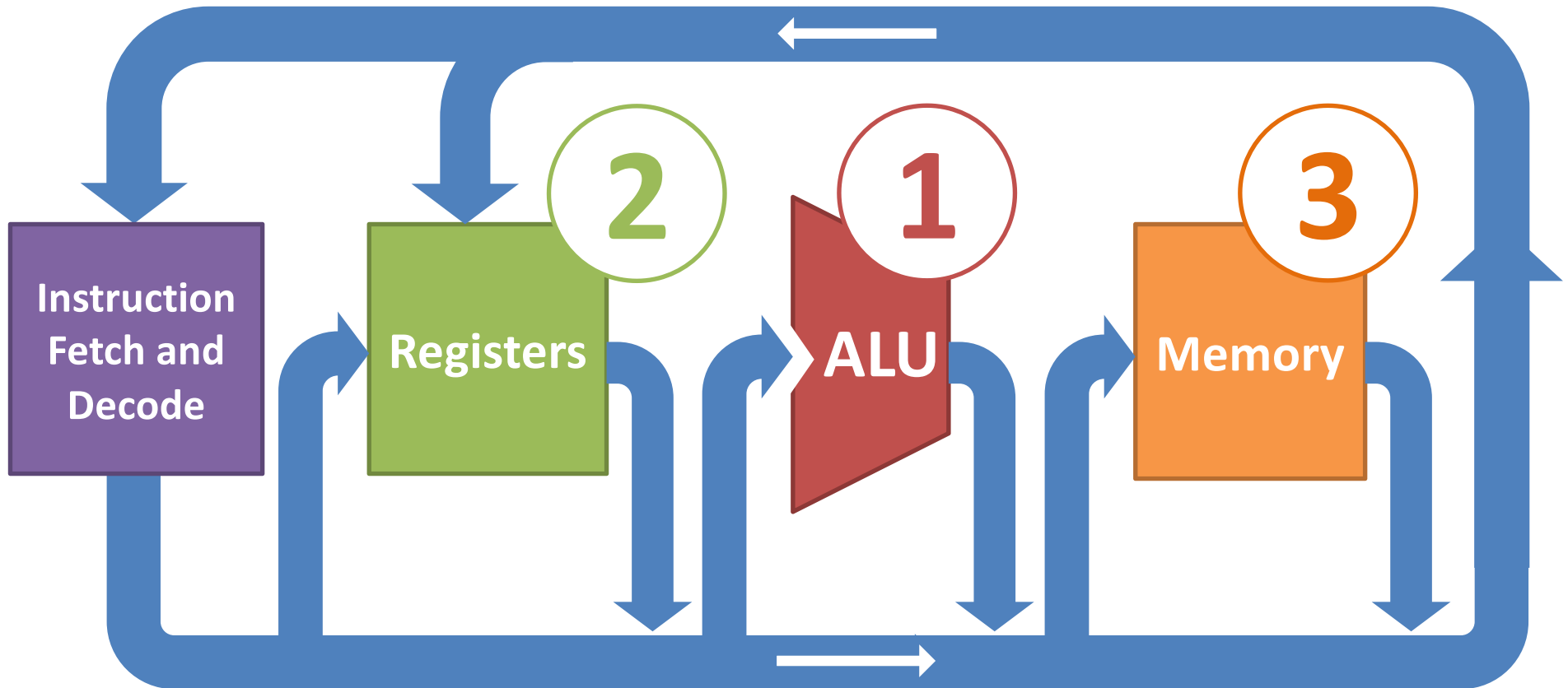

Unstable circuit

 


Have this issue with any **odd** number of inverters in a loop.


Bistable latches

Things are more sensible with an **even** number of inverters in a loop.

 
Suppose we somehow get a 1 (or a 0?) on here.



=

 



SR latch

 


S	R	Q _{prev}	Q' _{prev}	Q _{next} (stable)	Q' _{next} (stable)
0	0	0	1	0	1
0	0	1	0	1	0
1	0	<i>any</i>	<i>any</i>	1	0
0	1	<i>any</i>	<i>any</i>	0	1
1	1	<i>any</i>	<i>any</i>	0	0

← violates invariant that Q and Q' are inverses!

SR latch

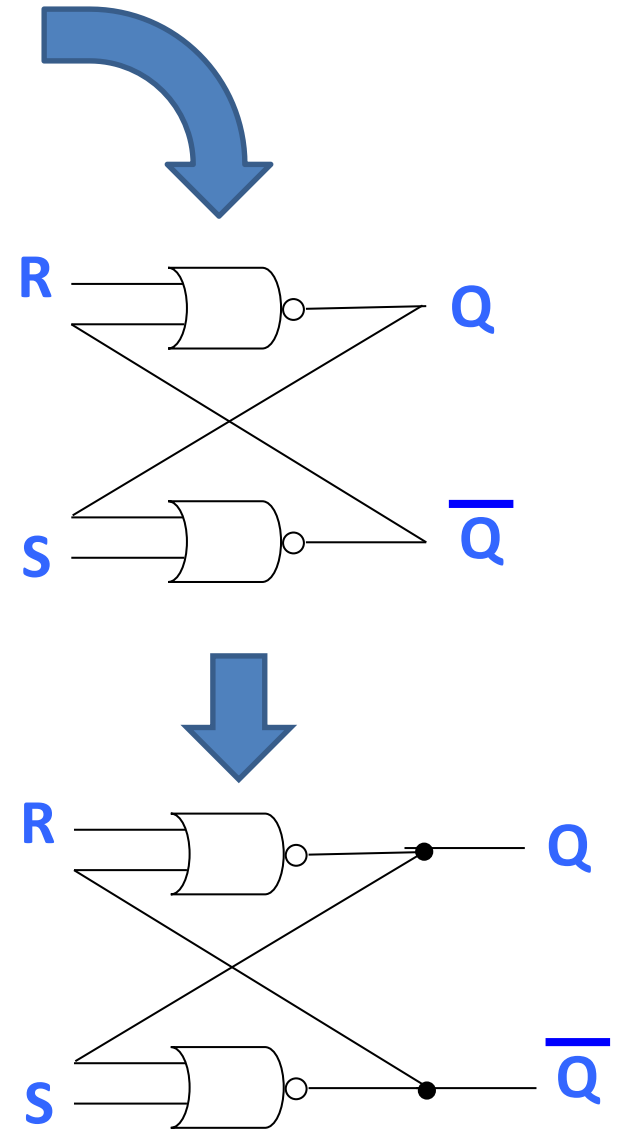 

D latch

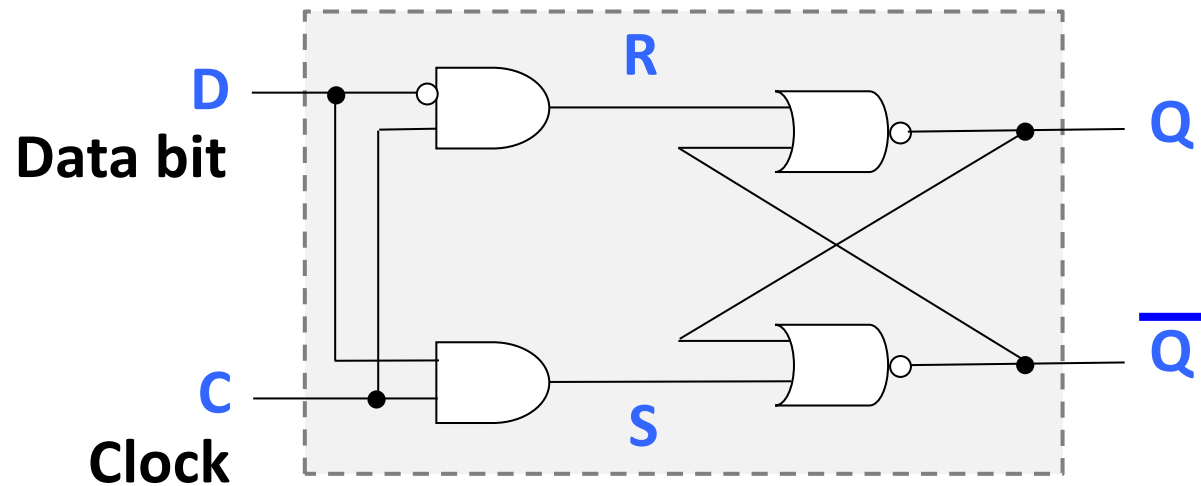

if $C = 0$, then SR latch stores current value of Q.

if $C = 1$, then D flows to Q:


if $D = 0$, then $R = 1$ and $S = 0$, $Q = 0$

if $D = 1$, then $R = 0$ and $S = 1$, $Q = 1$

Notes:

- Data bit D replaces S & R: it's the bit value we want to store when Clock = 1
 - Internally, Data bit D prevents bad case of $S = R = 1$
- This logic is **level-triggered**; as long as Clock = 1, changes to D have impact

Time matters!

 


Assume Q has an initial state of 0

Clocks

Clock: free-running signal
with fixed **cycle** time = **clock period** = T .

 Clock frequency = $1 / \text{clock period}$




A clock controls when to update
a sequential logic element's state.





Synchronous systems

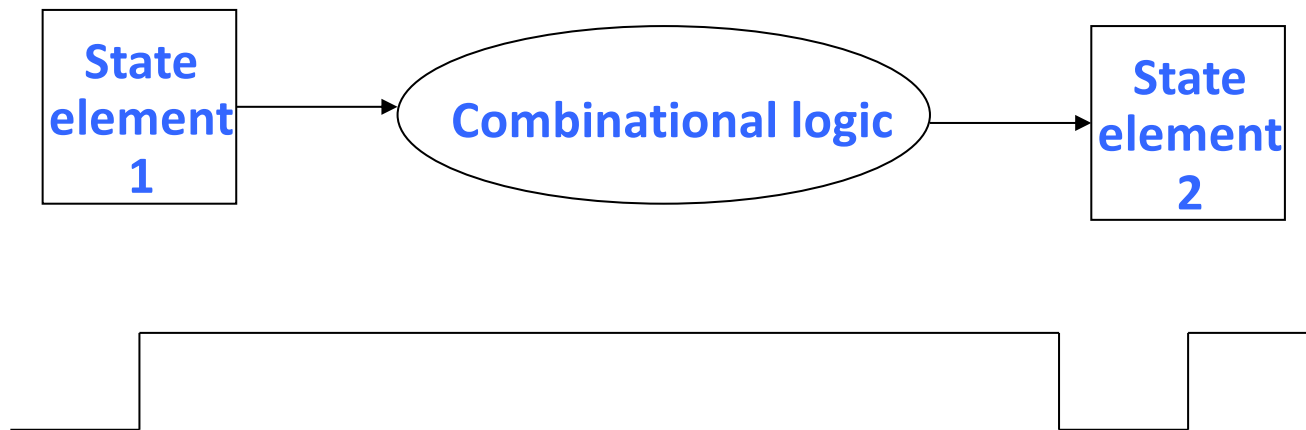
Inputs to state elements must be **valid** on active clock edge.



D flip-flop with falling-edge trigger

 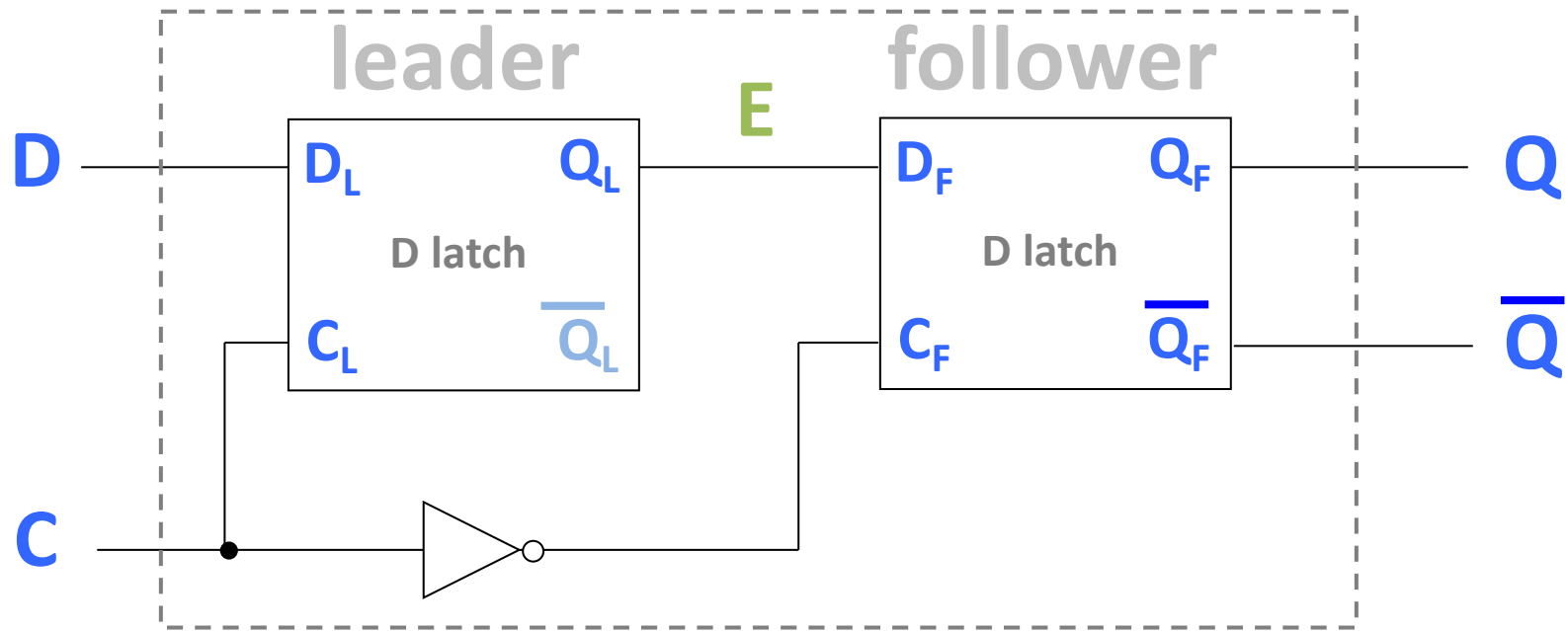


Time matters!

 

Assume Q and E have an initial state of 0

Reading and writing in the same cycle

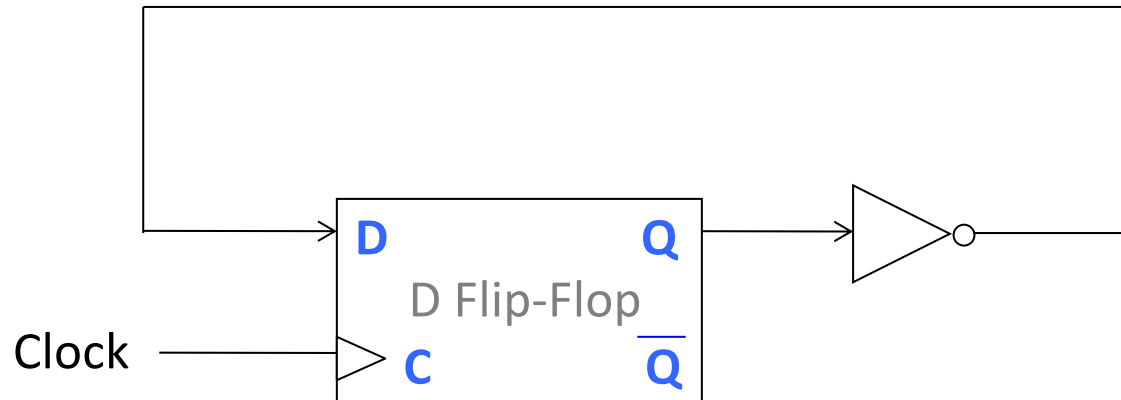

Assume Q is initially 0.

Moral: It's OK to use the current output Q of a flip-flop as part of the the next data input D to the same flip-flop.

D flip-flop = one bit of storage





The bit value of D when C has a falling edge is remembered at Q until the next falling edge of C.


*Half a byte! 

A 1-nybble* register

(a 4-bit hardware storage cell)

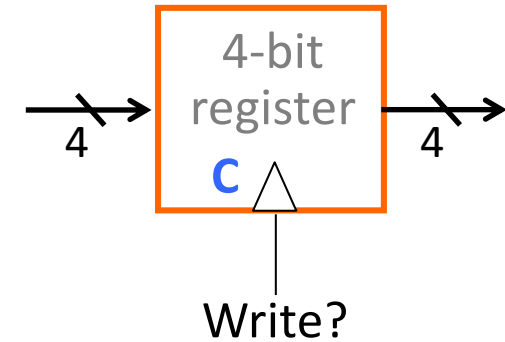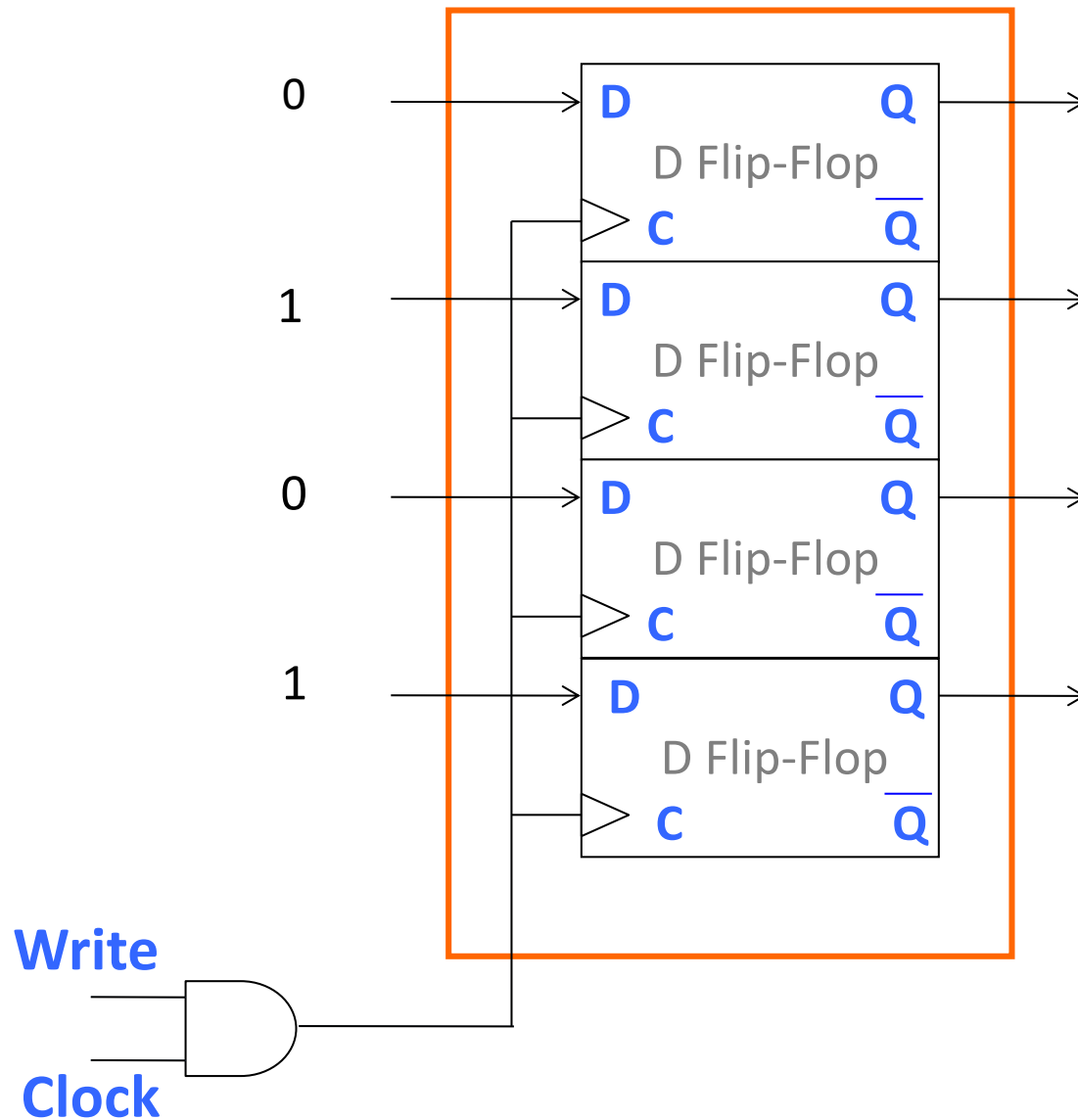


Register file

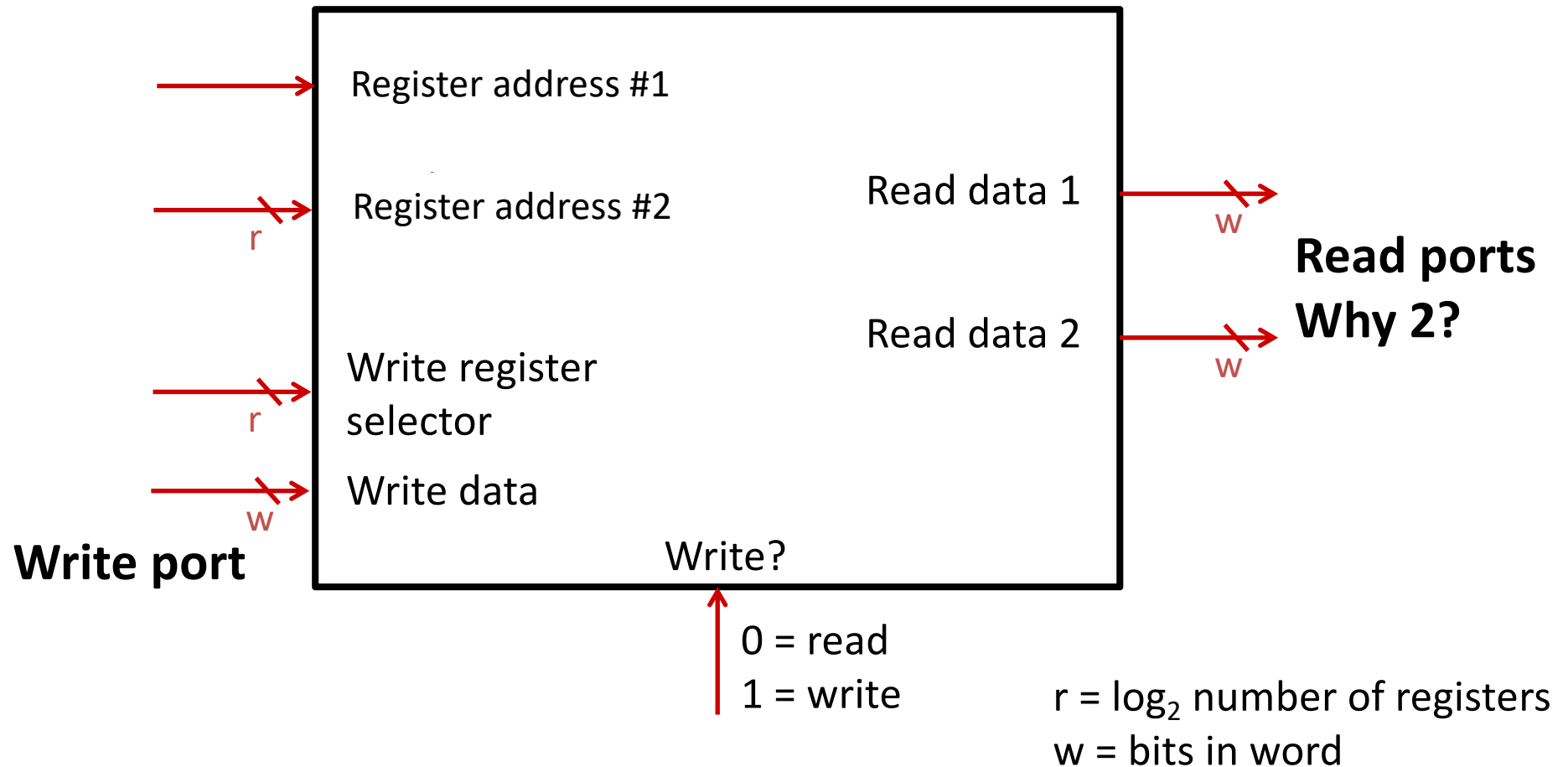

Array of registers, with register selectors, write/read control, input port for writing data, output ports for reading data.

Read ports (data out)

Register address #1
($\log_2 k$ bits)

 

Register address #2
($\log_2 k$ bits)


n → Data read from
register address #1
(n bits)

n → Data read from
register address #2
(n bits)


Read ports (data out)

Register address #1
($\log_2 k$ bits)


Register address #2
($\log_2 k$ bits)

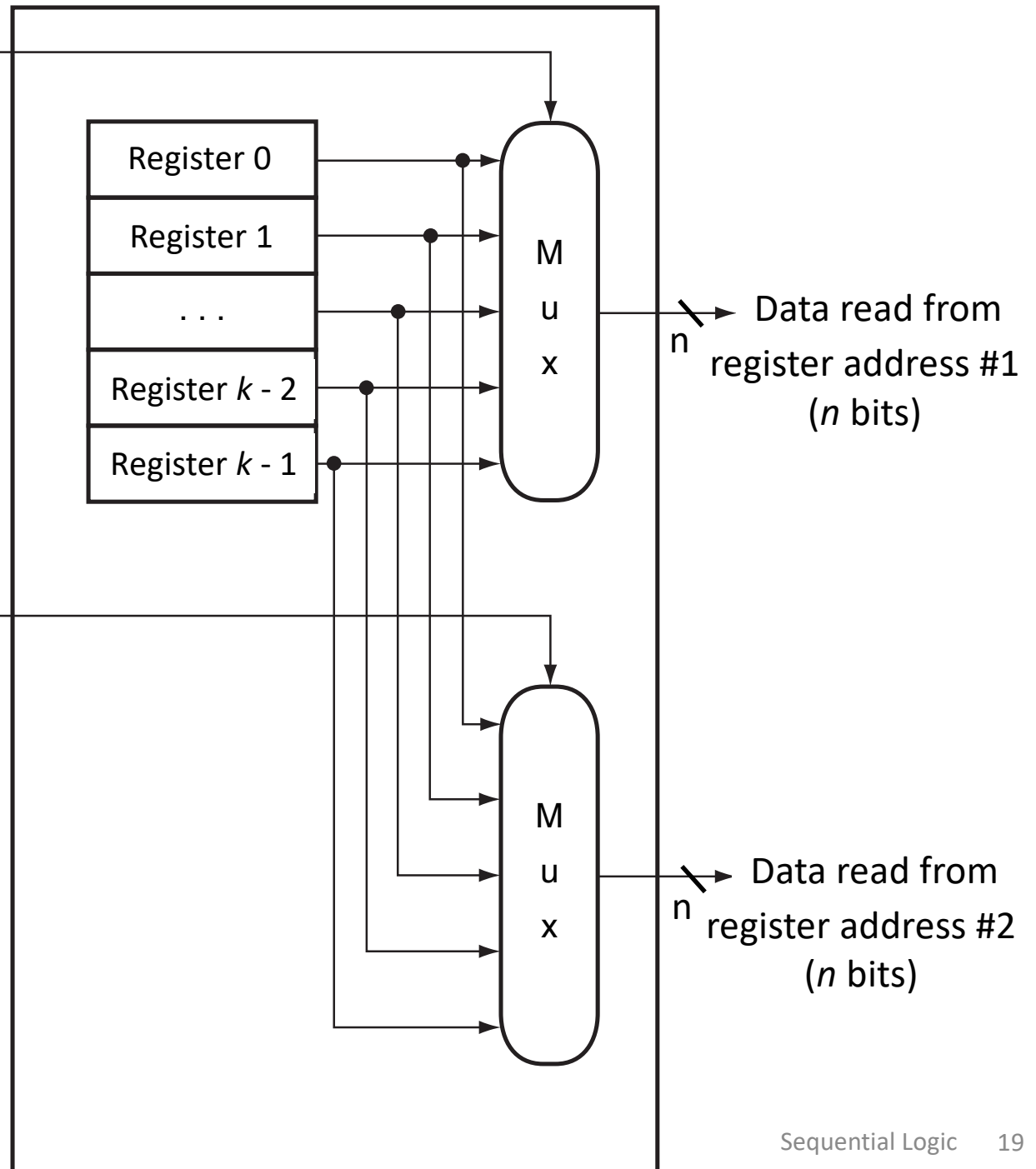


Write port (data in)

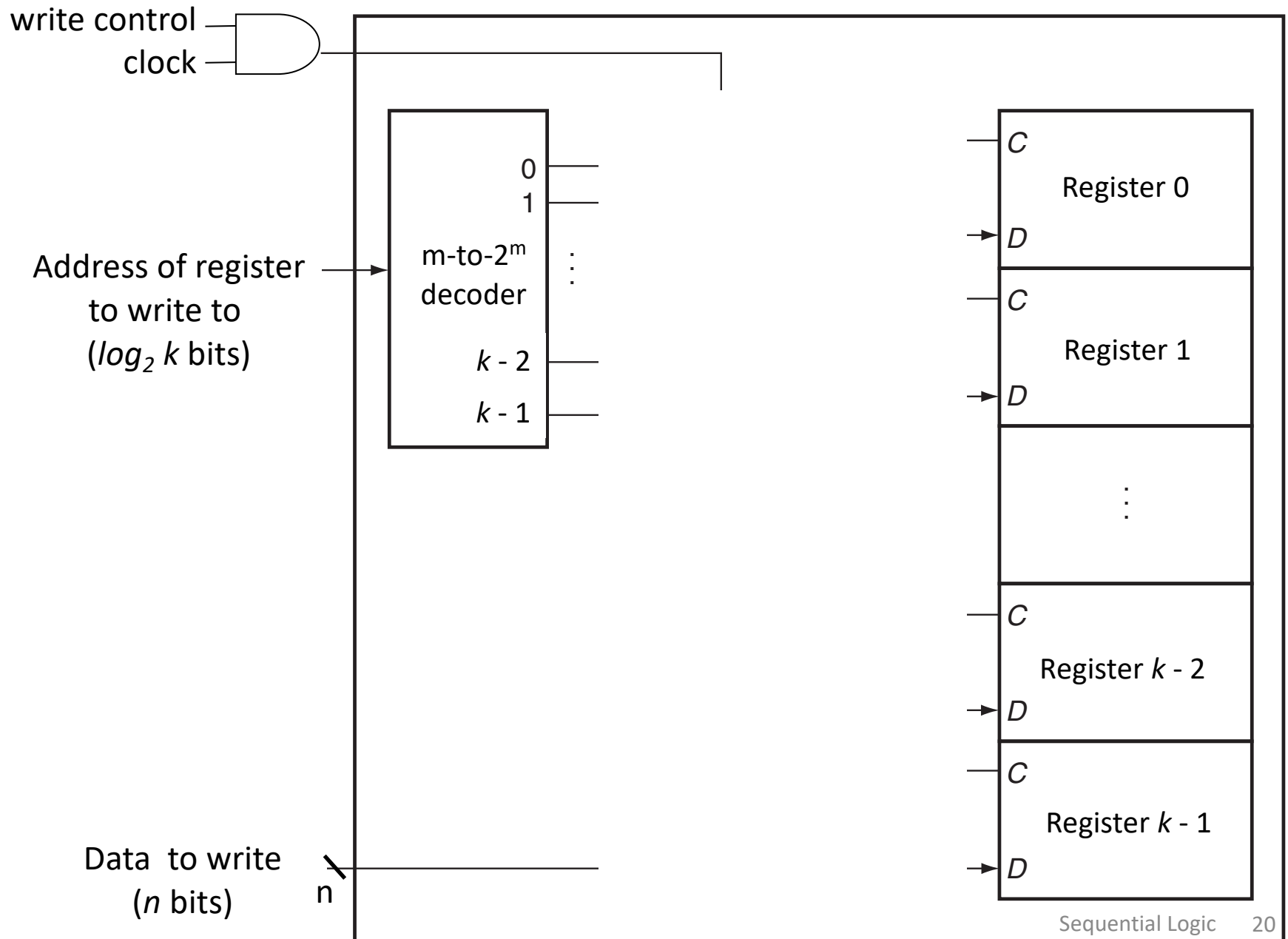

Write port (data in)

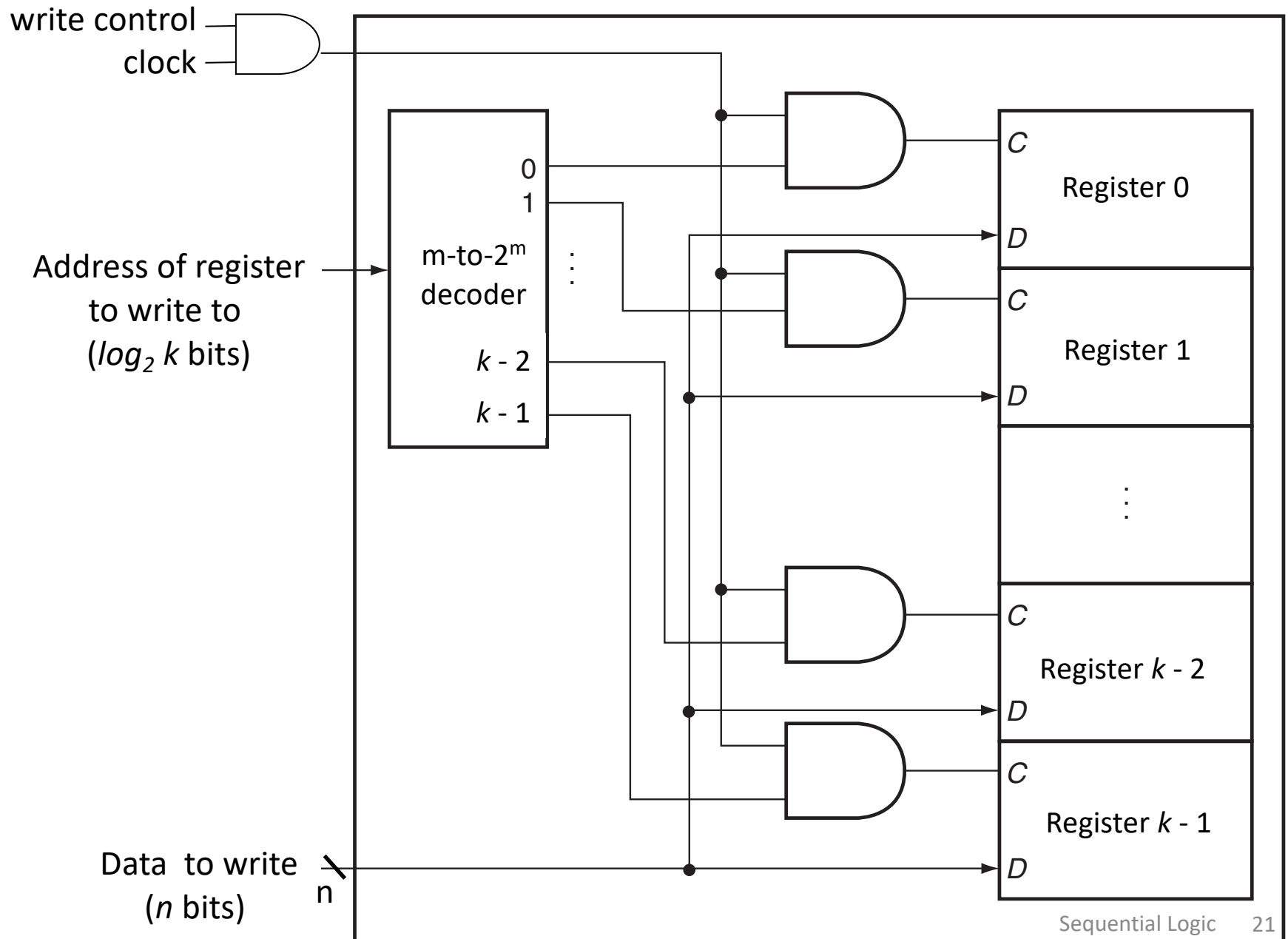

RAM (Random Access Memory)

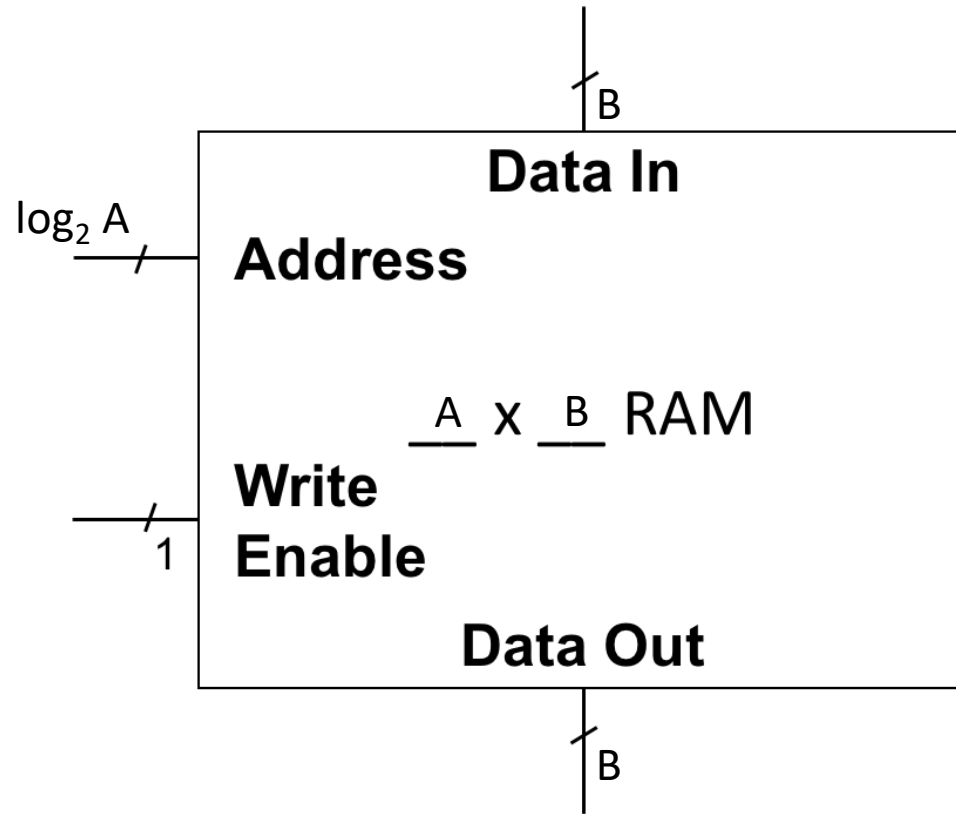

- A is number of words in RAM
- Specify the desired word by an address of size $\log_2 A$
- B is the width of each word (in bits)

Similar to register file, except...

16 x 4 RAM

