

About how many hours did you spend actively working on this assignment? \_\_\_\_\_

**Q1 Universal Muxification of Gates [10 points]**

*Time spent on Q1:* \_\_\_\_\_

<b>1.1 NOT A</b> (one 2:1 mux) [1]	<b>1.2. A AND B</b> (one 2:1 mux) [1]	<b>1.3 A NOR B</b> (two 2:1 muxes) [2]
<b>1.4 A XOR B</b> (two 2:1 muxes) [Independent] [3]	<b>1.5 A XOR B</b> (one 2:4 decoder and one 2:1 mux) [Independent] [3]	

**Q2 vALUe Judgement [28 points]**

Draw circuits on next page, text answers (except 2.1b) go here.

Time spent on Q2: \_\_\_\_\_

**2.1 Condition Flags [5]**

(draw circuits for (a) and give explanation for (b) on the next page)

**2.2 Result of the ALU when *Invert A = 1*, *Negate B = 1*, and *Operation ID = 10*. [4]**

(a) [2] Result =

(b) [2] Derivation of Result:

**2.3 (a) [3 points] A, B with correct result**  
(multiple answers shown; you only needed one)

A	B	A - B	sign(A-B)	Is A < B?
positive	positive			
negative	negative			
different signs	different signs			

**2.3. (b) [2 points] A, B with incorrect result**

A	B	A - B	sign(A-B)	Is A < B?
positive				
negative				

**2.3. (c) [1 point] Key reason(s) why 2.3(b) examples are incorrect.**

**2.3 (d) [3 points]** Draw your circuit for the Less-Than Flag on the next page.

**2.3. (e) [1 point]** Control lines for Less-Than Flag:  
*Invert A* =      *Negate B* =      *Operation* =


**2.3. (f) [2 points]** Explain why your Less-Than Flag circuit on the next page gives the correct result.

**2.4. (a) [3 points]** Draw your Equals Flag design on the next page.

**2.4. (b) [1 point]** Explain why your Equals Flag circuit correctly calculates  $A == B$ .

**2.4. (c) [1 points]** Control lines for the Equals Flag  
*Invert A* =      *Negate B* =      *Operation* =

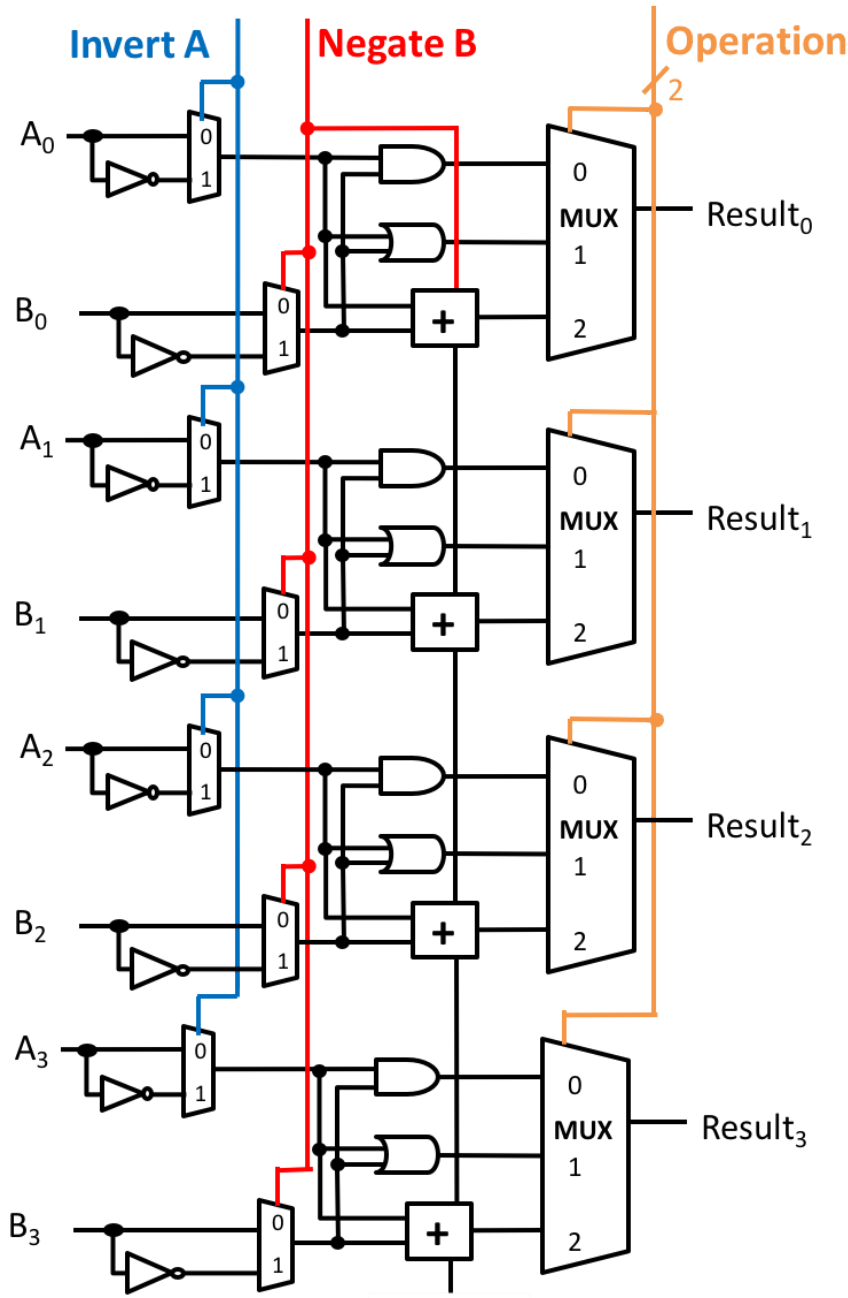2.1(a) Condition Flag circuits; 2.1(b) explanation why Overflow Flag circuit is correct; 2.3(d) Less-Than Flag circuit; 2.4(a) Equals Flag circuit. Label all outputs clearly.




2.1(b) Explain why the Overflow Flag circuit is correct

**Q3. Flop-Flip-Flopping [10 points]**

Time spent on Q3: \_\_\_\_\_

 **3.1 Waveform diagrams (Timing diagrams)**



3.2. Cycles Completed	$Q_2$	$Q_1$	$Q_0$
0 (initial)	0	0	0
1			
2			
3			
4			
5			
6			
7			
8			
9			
10			

**3.3. Explanation**

**Q4 Some Loopy Programs [22 points]**

Time spent on Q4: \_\_\_\_\_

**4.1 [8 points] Execution Table for program P1**

PC	Instruction	State Changes

<b>4.2 [3 points] Final contents</b>	<b>R2:</b>	<b>R3:</b>	<b>R4:</b>
--------------------------------------	------------	------------	------------

**4.3 [4 points] C statements equivalent to P1:**

```
// Alice starts with these C statements for program P1
int R0 = 0;
int R1 = 1;
int R2 = R0+R1;
// Below, fill in the remaining C statements to complete program P1:
```

**4.4 (a)** Execute this program **P2**, assuming **R2** holds 5 and **R3** holds 4. Below, indicate the final register values when the code reaches **HALT**. (Do *not* show the step-by-step execution)

```
0x0: AND R2, R2, R4
0x2: AND R3, R3, R5
0x4: BEQ R5, R0, 3
0x6: SUB R5, R1, R5
0x8: ADD R4, R4, R4
0xA: JMP 2
0xC: HALT # Stops execution.
```

Final register contents after  
executing P2 [3 points]

R2:

R3:

R4:

R5: )

**4.4(b) [2 points] C line for P2**

Single line of C code equivalent to the HW ISA code for **P2**, assuming variables R2 and R3 can hold any integer values. Use only basic C operations (no conditionals, loops, or function calls).

R4 =

**4.3(b) [2 points] Explanation why C line in 4.4(b) calculates the same result as program P2**

**Q5 Taking Control [9 points]**

Time spent on Q5: \_\_\_\_\_

**Control Unit Truth Table**

Instruction Name	Opcode <sub>[3:0]</sub> (4 bits)	Reg Write (1 bit)	ALU Op <sub>[3:0]</sub> (4 bits)	Mem Store (1 bit)	Mem Load (1 bit)	Branch (1 bit)	Jump (1 bit) 7.2 [1]
LW	0000	1	0010	0	1	0	
SW							
ADD							
SUB							
AND							
OR							
BEQ							
NAND 6.2(b) [3]							
JMP 7.3 [3]							

**Q6 Instruction Not Missing [12 points]**

Time spent on Q6: \_\_\_\_\_

**6.1 [4 points]**

**6.1(a) [1 point]** Give a definition of  $\sim X$  in terms of  $X$  and signed two's complement arithmetic:

$\sim X =$

**6.1(b) [3 points]** Based on the previous subpart, the instruction **NOT**  $R_s, R_d$  can be emulated by running the following instructions instead:


----- 16-bit encoding -----

Assembly	Meaning	Opcode [15:12]	Rs [11:8]	Rt [7:4]	Rd [3:0]
<b>6.2(a) [3 points]</b> NAND $R_s, R_t, R_d$	$R[d] \leftarrow \sim(R_s \& R_t)$				
<b>6.3 [2 points]</b> NOT $R_s, R_d$	$R[d] \leftarrow \sim R_s$				

**Q7 Jumping into the Unknown [12 points]**

Time spent on Q7: \_\_\_\_\_

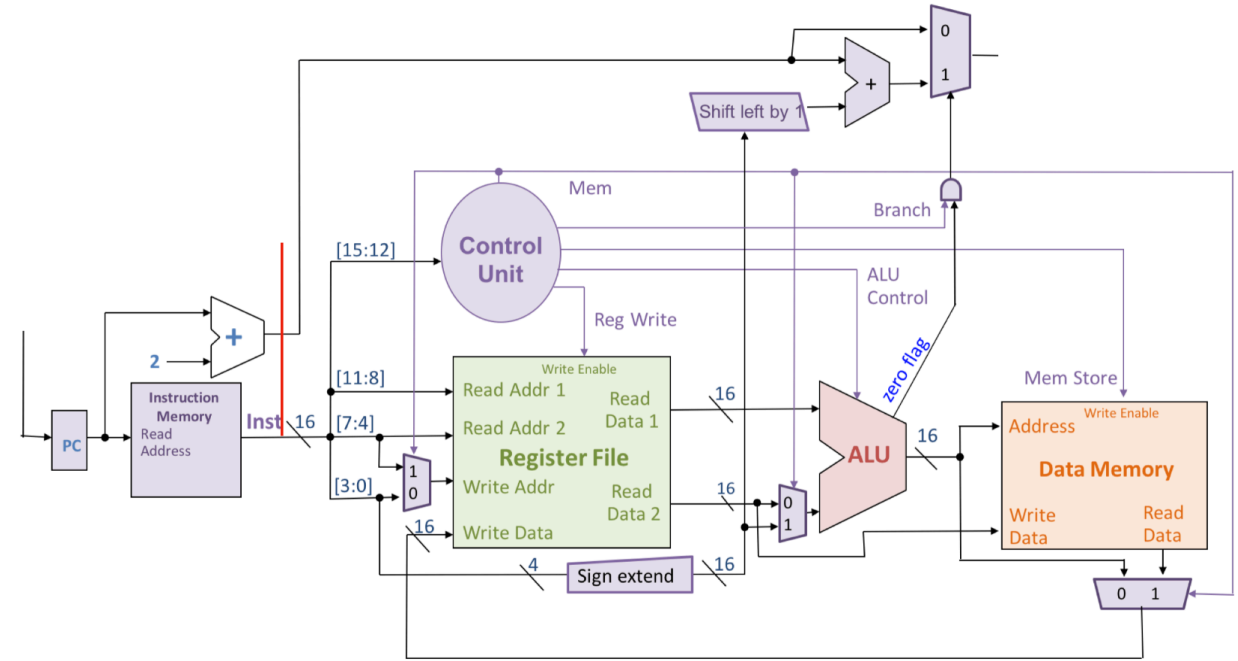**7.1(a) [8 points].** Below, add a Jump output wire from the Control Unit and modify logic to use it to implement JMP instruction. Note: if you use the new red write split off from Inst, be sure to label which range ([?, ?]) of bits you use.



**7.2 [1 point]** For this part, fill out the Jump column in the Control Unit Truth Table in Q5.

**7.3 [3 points]** For this part, fill out the JMP row in the Control Unit Truth Table in Q5. **When the bits in a cell don't matter (they can be anything), you must explicitly write this!**