



# Digital Logic

Gateway to computer science

transistors, gates, circuits, Boolean algebra

Software

Program, Application

Programming Language

Compiler/Interpreter

Operating System

Instruction Set Architecture

Microarchitecture

Digital Logic

Devices (transistors, etc.)

Solid-State Physics

Hardware




## Digital data/computation = Boolean

Boolean value (*bit*): 0 or 1

Boolean functions (AND, OR, NOT, ...)

Electronically:

bit = high voltage vs. low voltage

 


Boolean functions = logic gates, built from transistors

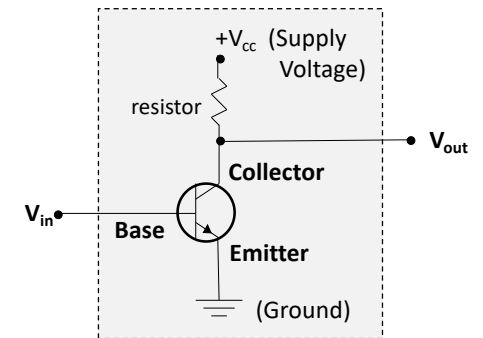
## Transistors (more in lab)

If **Base voltage is high:**  
Current may flow freely from *Collector* to *Emitter*.

If **Base voltage is low:**  
Current may not flow from *Collector* to *Emitter*.



Truth table							
$V_{in}$	$V_{out}$	=	in	out	=	in	out
low	high	=	0	1	=	F	T
high	low		1	0		T	F

 


# Digital Logic Gates

**Abstraction!**


ex

Tiny electronic devices that compute basic Boolean functions.


**NOT**

 

$V_{in}$	$V_{out}$
0	1
1	0

 


$V_1$	$V_2$
0	0
0	1
1	0
1	1

 


Digital Logic 5

# Integrated Circuits (1950s - )


Early (first?) transistor

 


Chip

 

Wafer

 


Small integrated circuit

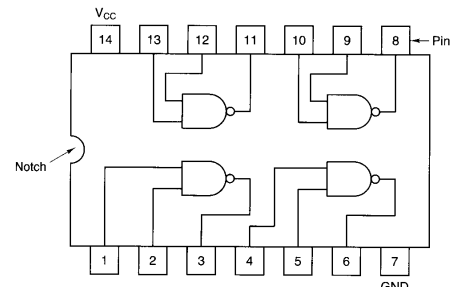


Digital Logic 6

# Five basic gates: define with truth tables


ex

 


<b>NOT</b>	
0	1
1	0

 


<b>NAND</b>	0	1
0	1	1
1	1	0

 

<b>NOR</b>	0	1
0		
1		

 

<b>AND</b>	0	1
0		
1		

 

<b>OR</b>	0	1
0		
1		

Digital Logic 7


# Simple Boolean Expressions

for combinational logic


- inputs* = *variables*
- wires* = *expressions*
- gates* = *operators/functions*
- circuits* = *functions*




wire: identity

 

NOT: inverse or complement

 

OR = Boolean sum

 

AND = Boolean product

Orange forms are most convenient in text editors.

A **boolean literal** is a variable or its complement.

E.g.,  $A, A', B, B'$  are literal boolean expressions, but  $A + B, AB,$  and  $(AB)'$  are not.

Digital Logic 8

## General Boolean Expressions

Boolean expressions are generated by this context free grammar:

$BE ::= \text{variable} \mid 0 \mid 1 \mid BE' \mid BE + BE \mid BE * BE \mid (BE)$

**Precedence:** (...) > NOT > AND > OR


E.g.,  $A'B + CD'$  means  $((A')*B) + (C*(D'))$
 
## Circuits & Boolean Expressions



Given input variables, **circuits** specify outputs as functions of inputs using wires & gates.

- Crossed wires touch *only if* there is an explicit dot.
- T intersections copy the value on a wire and don't need a dot.
- It doesn't make sense to wire together two inputs or two outputs; instead, combine two independent wires with a gate!



What is the truth table for Q in the example circuit?

A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Each output can be translated to a boolean expression in terms of the input variables.

What is a boolean expression for Q in the above circuit?

## Translation Exercise



Connect gates to implement these functions. Check with truth tables. Use a direct translation -- it is straightforward and bidirectional.


$$F = (A\bar{B} + C)D$$

$$Z = \bar{W} + (X + \bar{W}Y)$$
 
## Larger gates

Using 2-input AND gates, it's easy to build an AND gate with more than 2 inputs.

E.g., How can we build a 4-input AND gate from three 2-input AND gates?




Multi-input OR gates with can be created analogously.

Multi-input NAND and NOR gates can be created by inverting the outputs of multi-input AND and OR gates.

 
## Circuit derivation: *code detectors*

ex

A multi-input AND gate preceded by some inverters = **code detector** that recognizes **exactly one** input code (a specific combination of inputs).



 E.g., here's a 4-input code detector that outputs 1 if ABCD = 0101, and 0 otherwise:



Design a 4-input code detector to accept two codes (ABCD=1001, ABCD=1101) and reject all others (accept = 1, reject = 0). Use as many gates as you need.

Digital Logic 13

## Sum-of-products (SoP) Form

ex

A **sum-of-product (SoP)** form is a boolean expression for a circuit output that is expressed as a sum of **minterms**, one for each row whose output is 1.

A **minterm** for a row is a product of literals (variables or their negations) whose value is 1 for that row. Think of it as being a **code detector** for that row!

What is the sum-of-products expression for the truth table below?

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

How would you draw the circuit for this expression?

How is it related to **code detectors** from the previous slide?

Digital Logic 14

## Voting machines

ex

A majority circuit outputs 1 if and only if a majority of its inputs equal 1. Design a majority circuit for three inputs. Use a sum of products.

A	B	C	Majority
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

### Triply redundant computers in spacecraft

- Space program also hastened Integrated Circuits.

Digital Logic 15

## Product-of-sums (PoS) Form

ex

A **product-of-sums (PoS)** form is a boolean expression for a circuit output that is expressed as a product of **maxterms**, one for each row whose output is 0.

A **maxterm** for a row is a sum of literals (variable or their negations) whose value is 0 for that row.

What is the product-of-sums expression for this truth table?

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

How would you draw the circuit for this expression?

How can you relate it to the notion of **code detectors**?

Digital Logic 16

# Boolean Algebra: Simple laws

Boolean algebra laws can be proven by truth tables and used to show equivalences between boolean expressions.

For all laws in one place, see the [Boolean Laws Reference Sheet](#)

Name of Law / Theorem	Form	Equivalent/Dual form (interchange AND and OR, and 0 and 1)
<b>Involution</b> (or double negation)	$\overline{\overline{A}} = A$	none
<b>Identity</b>	$0+A = A$	$1*A = A$
<b>Inverse</b> (or Complements)	$A\overline{A} = 0$	$A+\overline{A} = 1$
<b>Commutativity</b>	$A+B = B+A$	$AB = BA$
<b>Associativity</b>	$(AB)C = A(BC)$	$(A+B)+C = A+(B+C)$
<b>Idempotent</b>	$A+A = A$	$AA = A$
<b>Null</b> (or Null Element)	$0*A = 0$ (the Zero Law)	$1+A = 1$ (the One Law)

# Boolean Algebra: More Complex Laws

<b>Distributive</b>	$A+BC = (A+B)(A+C)$	$A(B+C) = AB+AC$
<b>DeMorgan's</b>	$\overline{A+B+C+\dots} = \overline{A}\overline{B}\overline{C}\dots$	$\overline{\overline{A+B+C+\dots}} = \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}}\dots$
<b>Absorption 1 (Covering)</b>	$A+AB = A$	$A(A+B) = A$
<b>Absorption 2</b>	$A+\overline{A}B = A+B$	$A(\overline{A}+B) = AB$
<b>Combining</b>	$AB+A\overline{B} = A$	$(A+B)(A+\overline{B}) = A$
<b>Consensus</b>	$AB+\overline{A}C+BC = AB+\overline{A}C$	$(A+B)(\overline{A}+C)(B+C) = (A+B)(\overline{A}+C)$

You can use truth tables (or other Boolean laws) to convince yourself that these laws hold. (See the exercises on the following slides).

## Boolean Algebra: Proving Laws by Truth Tables ex

<b>DeMorgan's</b>	$\overline{A+B+C+\dots} = \overline{A}\overline{B}\overline{C}\dots$	$\overline{\overline{A+B+C+\dots}} = \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}}\dots$
-------------------	--	--

Complete the truth tables below to show that both DeMorgan's laws hold for two variables.

A	B	(A')+(B')	(AB)'
0	0		
0	1		
1	0		
1	1		

A	B	(A+B)'	(A')(B')
0	0		
0	1		
1	0		
1	1		

## Boolean Algebra: Proving Laws by Truth Tables ex

<b>Distributive</b>	$A+BC = (A+B)(A+C)$	$A(B+C) = AB+AC$
---------------------	---------------------	------------------

Complete the truth tables below to show that both distributive laws hold.

A	B	C	A+BC
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

A	B	C	(A+B)(A+C)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

A	B	C	A(B+C)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

A	B	C	AB+AC
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

### Notes:

- The law in the right column (distributing multiplication over addition) should be familiar from algebra of numbers.
- The law in the left column (distributing addition over multiplication) is **not** true in the algebra of numbers but **is** true for Boolean algebra!

# Boolean Algebra: Proving Laws by Algebra

<b>Absorption 1 (Covering)</b>	$A + AB = A$	$A(A + B) = A$
--------------------------------	--------------	----------------

Each step has a **redex** = the subexpression to which the law is applied.

Here, both the redex and the applied law are highlighted in the same color.

But redexes can also be highlighted by boxing, underlining, etc.

The explicit \*s highlight the duality between \* and +, but can be replaced by juxtaposition.

*Step-by-step derivation*

*explicit*

**Commutativity**

$$\begin{aligned}
 &A + A*B \\
 &= \mathbf{1*A + A*B} \quad [\text{Identity (*)}] \\
 &= \mathbf{A*1 + A*B} \quad [\text{Commutativity (*)}] \\
 &= \mathbf{A*(1 + B)} \quad [\text{Distributivity (*/+)}] \\
 &= \mathbf{A*1} \quad [\text{One law}] \\
 &= \mathbf{1*A} \quad [\text{Commutativity (*)}] \\
 &= A \quad [\text{Identity}]
 \end{aligned}$$

*implicit*

**Commutativity**

$$\begin{aligned}
 &A + A*B \\
 &= \mathbf{A*1 + A*B} \quad [\text{Identity}] \\
 &= \mathbf{A*(1 + B)} \quad [\text{Distributivity}] \\
 &= \mathbf{A*1} \quad [\text{One law}] \\
 &= A \quad [\text{Identity}]
 \end{aligned}$$

*Dual step-by-step derivation*  
(Swap \*  $\leftrightarrow$  +, 0  $\leftrightarrow$  1)

$$\begin{aligned}
 &A*(A + B) \\
 &= \mathbf{(0 + A)*(A + B)} \quad [\text{Identity (+)}] \\
 &= \mathbf{(A + 0)*(A + B)} \quad [\text{Commutativity (+)}] \\
 &= \mathbf{A + 0*B} \quad [\text{Distributivity (+/*)}] \\
 &= \mathbf{A + 0} \quad [\text{Zero law}] \\
 &= \mathbf{0 + A} \quad [\text{Commutativity (+)}] \\
 &= A \quad [\text{Identity}]
 \end{aligned}$$

$$\begin{aligned}
 &A*(A + B) \\
 &= \mathbf{(A + 0)*(A + B)} \quad [\text{Identity (+)}] \\
 &= \mathbf{A + 0*B} \quad [\text{Distributivity (+/*)}] \\
 &= \mathbf{A + 0} \quad [\text{Zero law}] \\
 &= A \quad [\text{Identity}]
 \end{aligned}$$

# Boolean Algebra: Proving Laws by Algebra ex

<b>Combining</b>	$AB + \overline{A}B = A$	$(A + B)(A + \overline{B}) = A$
------------------	--------------------------	---------------------------------


# Boolean Algebra: Proving Laws by Algebra ex

<b>Absorption 2</b>	$A + \overline{A}B = A + B$	$A(\overline{A} + B) = AB$
---------------------	-----------------------------	----------------------------

Why simplify?
 
# Circuit simplification ex

Is there a simpler circuit that performs the same function?




Start with an equivalent Boolean expression, then simplify with algebra, and convert the simplified expression back to a circuit.

$$F(A, B, C) =$$

Check the answer with a truth table.

## XOR: Exclusive OR

 

ex

Output = 1 if exactly one input = 1.


Truth table: Build from earlier gates  
(start with SoP or PoS):

XOR	0	1
0		
1		

Often used as a one-bit comparator.

Digital Logic 25

## NAND is *universal*

 

ex

All Boolean functions can be implemented using only NANDs.  
Build NOT, AND, OR, NOR, using only NAND gates.

In Gates assignment, you will show that XOR can be built from NAND gates

Digital Logic 26

## NOR is also *universal*



ex

All Boolean functions can also be implemented using only NORs.  
Build NAND using only NOR gates; then since NAND is universal,  
NOR must be too! (Why?)

In Gates assignment, you will show that XOR can be built from NOR gates

Digital Logic 27

## Early pioneers in reliable computing

A-0: first compiler, by Grace Hopper

Early 1950s  
Maybe closer to  
assembler/linker/loader

Later: B-0 → FLOW-MATIC  
→ COBOL, late 50s




Jean Sammet also involved

- headed first sci comp group at Sperry in the '50s
- Later first female president of ACM
- Mount Holyoke alum, class of 1948

Plan 28

# Early pioneers in reliable computing

Apollo 11 code print-out

 

## Katherine Johnson

- Calculated first US human space flight trajectories
- Mercury, Apollo 11, Space Shuttle, ...
- Reputation for accuracy in manual calculations, verified early code
- Called to verify results of code for launch calculations for first US human in orbit
- Backup calculations helped save Apollo 13
- Presidential Medal of Freedom 2015

## Margaret Hamilton

- Led software team for Apollo 11 Guidance Computer, averted mission abort on first moon landing.
- Coined “software engineering”, developed techniques for correctness and reliability.
- Presidential Medal of Freedom 2016



# Computers



- Manual calculations
- powered all early US space missions.
- Facilitated transition to digital computers.

## Katherine Johnson


- Supported Mercury, Apollo, Space Shuttle, ...

## Mary Jackson


- NASA's first black female engineer
- Studied air around airplane via wind tunnel experiments.
 
## Dorothy Vaughan

- First black supervisor within NACA
- Early self-taught FORTRAN programmer for NASA move to digital computers.


 
# Wellesley Connection: Mary Allen Wilkes '59



Created LAP operating system at MIT Lincoln Labs for Wesley A. Clark's LINC computer, widely regarded as the first personal computer (designed for interactive use in bio labs). Work done 1961—1965.



Created first interactive keyboard-based text editor on 256 character display. LINC had only 2K 12-bit words; (parts of) editor code fit in 1K section; document in other 1K.

In 1965, she developed LAP6 with LINC in Baltimore living room. First home PC user!



Early versions of LAP developed using LINC simulator on MIT TX2 compute, famous for GUI/PL work done by Ivan and Bert Sutherland at MIT.



Later earned Harvard law degree and headed Economic Crime and Consumer Protection Division in Middlesex (MA) County District Attorney's office.